

THE CRITICALLY DAMPED VOLTAGE RESPONSE

$$s_1 = s_2 = -\alpha = \frac{-1}{2RC}$$


The response is:

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

I.C.'s:

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = D_1 - \alpha D_2$$

EX: For the circuit given below:

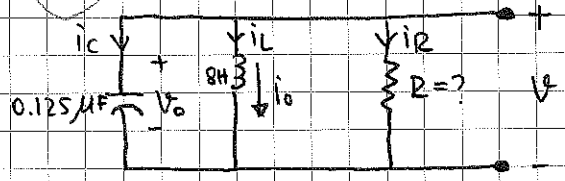

- $v_0 = 0, I_0 = -12.25 \text{ mA}$
- Find the value for R such that the response is critically damped
 - Find $v(t)$.

ANS: a) $\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\frac{10^6}{8(0.125)}} = 10^3 \text{ rad/s}$

In critically damped response $\alpha^2 = \omega_0^2, \alpha = \omega_0$

$$\alpha = 10^3 \text{ rad/s}$$

Thus, $\alpha = 10^3 = \frac{1}{2RC} \Rightarrow R = \frac{10^6}{(2000)(0.125)} = \boxed{4 \text{ k}\Omega}$


b) $v(0^+) = 0$

$D_1 = \frac{i_c(0^+)}{C} \rightarrow -(-12.25 \text{ mA})$
 Since $i_o(D^+) = 0$

$$\frac{dv(0^+)}{dt} = 98.000 \text{ V/s} \Rightarrow D_2 = 0, D_1 = 98.000 \text{ V/s}$$


$v_c(0^+) = 0$
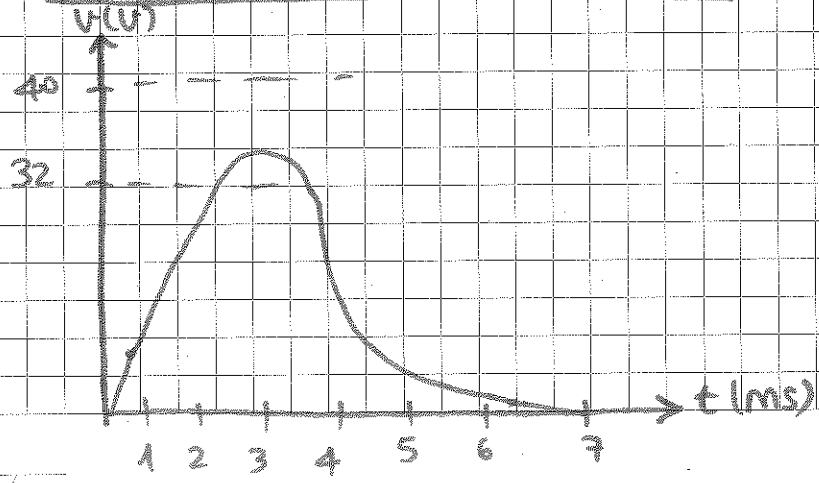
$$v(t) = 98000 t e^{-1000t} \text{ (V)}, t \geq 0$$



STEP RESPONSE OF A PARALLEL RLC-CIRCUIT

→ Consider the following circuit:

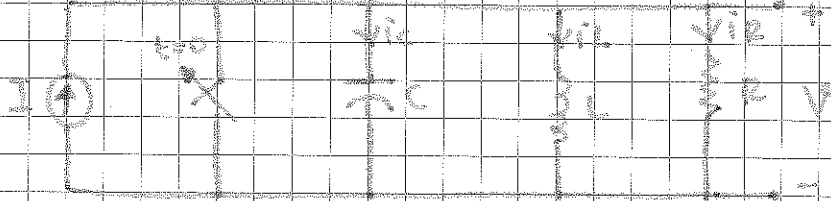

→ After applying the KCL and KVL ... (pg. 302)

The governing equation for the circuit is:

$$\boxed{\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}}$$

→ Thus, we need to solve this differential equation.

The solution can be obtained by expressing i_L as a function of v .

→ Then, we have from $v = L \frac{di_L}{dt}$ differentiate both sides,

$$\frac{dv}{dt} = L \cdot \frac{d^2 i_L}{dt^2}$$

→ Thus the circuit equation is:

$$\frac{1}{L} \frac{dv}{dt} + \frac{1}{RC} \frac{v}{L} + \frac{1}{L^2 C} \int_0^t v dt = \frac{I}{LC}$$

→ multiply both sides by LC

$$\frac{1}{L} \int_0^t v dt + \frac{v}{R} + C \cdot \frac{dv}{dt} = I$$

→ Differentiate both sides with respect to t

$$\boxed{\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \cdot \frac{d^2 v}{dt^2} = 0} \quad \underline{\underline{\text{OR}}} \quad \boxed{\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0}$$

whose solution is: $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$\underline{\underline{\text{OR}}} \quad v = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\underline{\underline{\text{OR}}} \quad v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

depending on the roots s_1 and s_2 .

→ The solution for i_L is:

$$i_L = I + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

OR

$$i_L = I + B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

OR


$$i_L = I + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

(Ex: 8.6) p. 304

Depending on the roots which are s_1 and s_2

THE NATURAL and STEP RESPONSE OF A SERIES RLC CIRCUIT

Consider the circuit:

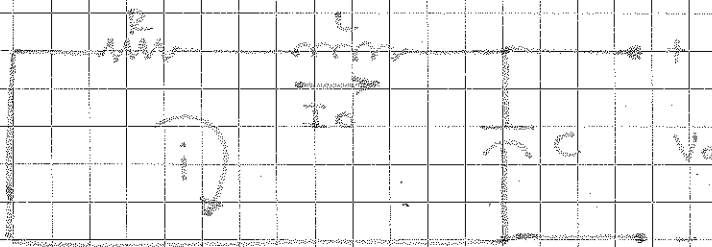

→ The governing equation is: $Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0$

→ Differentiate both sides:

$$R \cdot \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

→ Rearranging: $\left[\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \right]$

→ The characteristic equation: $\left[s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \right]$

where, $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ where $\alpha = \frac{R}{2L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$


and the solution of the natural response:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{overdamped})$$

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad (\text{underdamped})$$

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \quad (\text{critically damped})$$

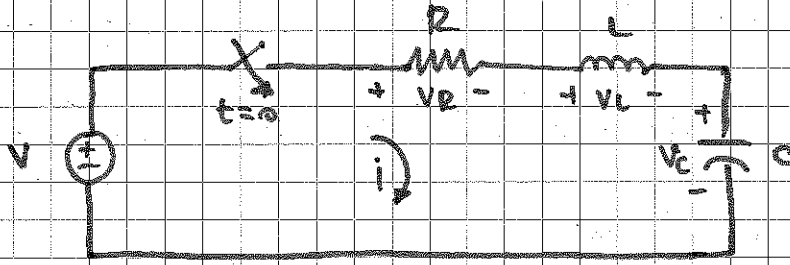→ In order to find the step response we consider the following circuit



→ After KVL applications we have:

$$\boxed{\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC} = \frac{V}{LC}}$$


→ The solution is:

$$V_C = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{overdamped})$$

$$V_C = V_f + B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad (\text{underdamped})$$

$$V_C = V_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \quad (\text{critically damped})$$

EX: For the given circuit:

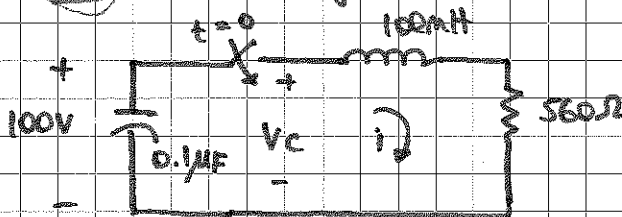

a) Find $i(t)$ for $t \geq 0$

b) Find $V_C(t)$ for $t \geq 0$

Ans a) $\omega_0 = \frac{1}{LC} = 10^8 \text{ rad/s}$, $\alpha = \frac{R}{2L} = 2800 \text{ rad/s}$

Thus, $\omega_0^2 > \alpha^2 \Rightarrow$ underdamped

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad \text{where } \alpha = 2800 \text{ rad/s}$$

$\omega_d = 96.000 \text{ rad/s}$

→ B_1 & B_2 are obtained from the initial conditions:

$$\boxed{i(0) = 0 = B_1}$$

For B_2 , we need $\frac{di(0^+)}{dt}$ so, $L \frac{di(0^+)}{dt} = V_0$ or $\frac{di(0^+)}{dt} = \frac{V_0}{L}$

so, $\frac{100}{100} \times 10^3 \rightarrow \frac{di(0^+)}{dt} = 1000 \text{ A/s}$

since $B_1 = 0$, $\frac{di}{dt} = 400 B_2 e^{-2800t} (24 \cos(9600t) - 7 \sin(9600t))$

Thus; $\frac{di(0^+)}{dt} = 9600 B_2 \rightarrow B_2 = \frac{1000}{9600} \approx 0.1042 \text{ A}$

Thus, $\boxed{i(t) = 0.1042 e^{-2800t} \sin 9600t, t \geq 0}$

b) $\boxed{V_C(t) = (100 \cos(9600t) + 29.17 \sin(9600t)) \cdot e^{-2800t} \text{ (V)}, t \geq 0}$

since $B_1 = 0$

CHAPTER - 9

SINUSOIDAL STEADY STATE ANALYSIS

The Sinusoidal Source :

Consider the following voltage source :

$$v = V_m \cos(\omega t + \phi)$$



- where t = time variable (s)
- v = voltage (v)
- ω = radian frequency (rad/s)
- V_m = max. amplitude (v)
- ϕ = phase angle (rad)

sinusoidal voltage source wave form

$$\omega = 2\pi f, \quad f = \text{frequency (Hz)},$$



$$T = \frac{1}{f} = \text{period (s)}$$

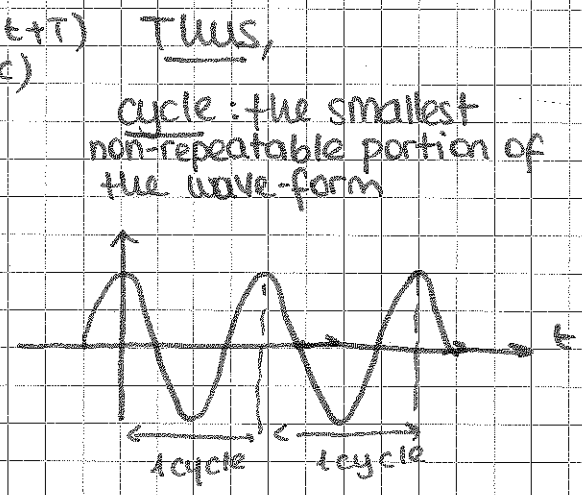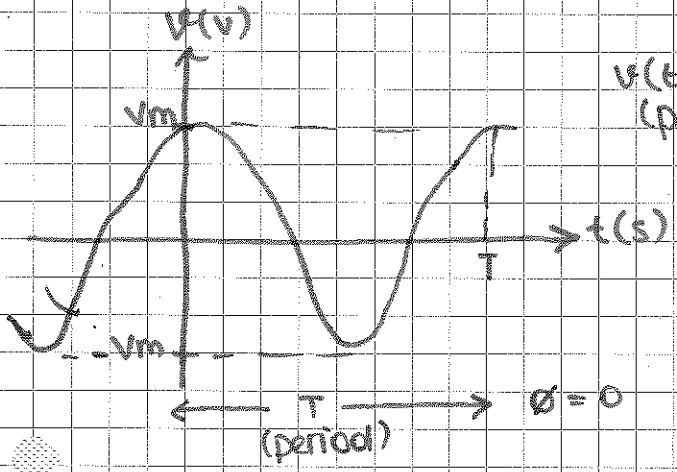→ If we plot the sinusoidal source wave form w.r.t time



Frequency : Number of cycles in 1 sec

Period = T = time takes for 1 cycle

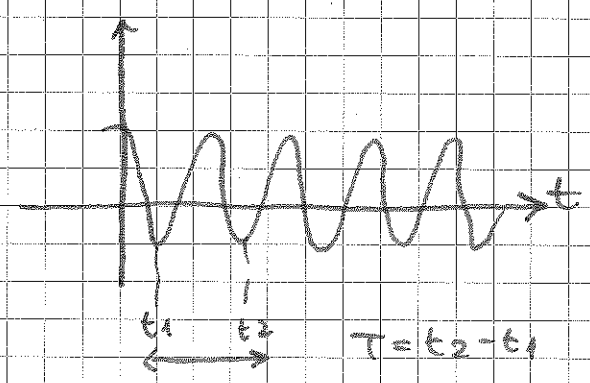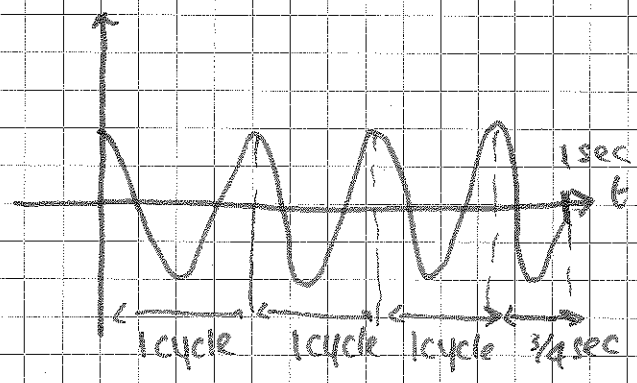

$$f = \frac{15}{4} \text{ Hz}$$

$$T = t_2 - t_1$$

• Another important property of sinusoidal voltage (or current) is the "rms value"


(rms: Root Mean Square)

Thus, if $v = V_m \cos(\omega t + \phi)$

$V_{rms} = \left[\frac{1}{T} \int_{t_0}^{t_0+T} v^2 dt \right]^{1/2}$ OR $V_{rms} = \sqrt{v_{avg}^2}$ Mean value of the squared voltage = v_{avg}

OR $V_{rms} = \frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt$ → $V_{rms} = \frac{V_m}{\sqrt{2}}$ (V) *

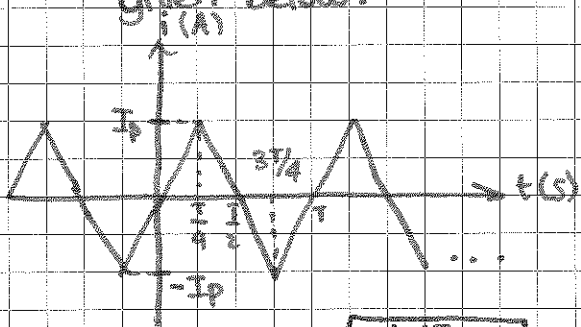× EX: Find the rms value of the periodic triangular function given below:



ANS: $I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2 dt}$

Then, $\int_{t_0}^{t_0+T} i^2 dt = 4 \int_0^{T/4} i^2 dt$

From the graph: $i = \frac{4I_p}{T} t$, $0 < t < T/4$
slope

Substitute the last eqn into the integral,

$4 \int_0^{T/4} \frac{16I_p^2}{T^2} t^2 dt = \frac{I_p^2 T}{3}$

Thus, $i_{mean} = \frac{1}{T} \cdot \frac{I_p^2 T}{3} = \frac{1}{3} I_p^2$

→ $I_{rms} = \sqrt{\frac{I_p^2}{3}}$ → $I_{rms} = \frac{I_p}{\sqrt{3}}$