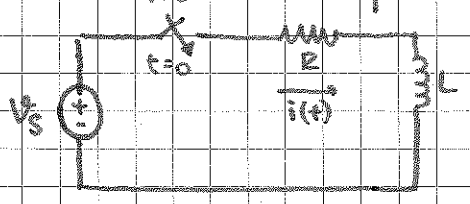


### The Sinusoidal Response

Consider the following circuit:



where  $V_s = V_m \cos(\omega t + \phi)$   
 Assume that  $i(0) = 0$   
 we want to find  $i(t)$ ,  $t \geq 0$ .

→ This is the step response of an RL-circuit as we have seen before. The difference is that we have sinusoidal source,  $V_s$ .

\* The governing equation of the circuit is:

$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$

\* The solution of this equation is:

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi + \theta) e^{-\frac{R}{L}t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

First term  $\rightarrow 0$  as  $t \rightarrow \infty$

where  $\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$

- The first term of this solution is called the "transient response"

- The second term of this solution is called the "steady state response"

- Because for  $t \geq 0$ , the first term decreases rapidly, and the second term starts to dominate

- So, the first term disappears after a while, and the second term will remain.

- We can make the following conclusions for the steady state response:

- 1) It is also sinusoidal
  - \* 2) It has the same frequency as the source (due to linearity!)
  - 3) Amplitude and phase changes.
  - 4) Solutions of the diff. eqn is rather long and complicated.
- The remedy to conclusion 4 is to use "phasors"
- Phasors: are used to make the mathematical solution of the differential eqns for when sinusoidal sources are used

RL  
RC  
RLC } they are all linear circuit

- The phasor is a complex number that carries the amplitude and phase information of a sinusoidal function.

It is based on the Euler's identity:

$$e^{-j\theta} = \cos\theta - j\sin\theta$$

Then,

$$\cos\theta = \text{Re}\{e^{j\theta}\} \text{ and } \sin\theta = \text{Im}\{e^{j\theta}\}$$

Then, we can rewrite the sinusoidal source as:

$$v = V_m \cos(\omega t + \theta) \text{ OR } v = V_m \cdot \text{Re}\{e^{j(\omega t + \theta)}\} \text{ OR } v = V_m \text{Re}\{e^{j\omega t} \cdot e^{j\theta}\}$$

$$v = \text{Re}\{V_m e^{j\omega t} e^{j\theta}\}$$

that carries the amplitude and phase information


- The term inside the bracket is called the "Phasor" of sinusoidal function,  $\bar{v}$ .

$$\bar{v} = V_m e^{j\theta} \text{ Phasor} \text{ SO, } \bar{v} = V_m e^{j\theta} = P \{ V_m \cos(\omega t + \theta) \} \text{ polar form}$$

→ In rectangular form,

$$\bar{v} = V_m \cos\theta + j V_m \sin\theta \text{ rectangular form}$$

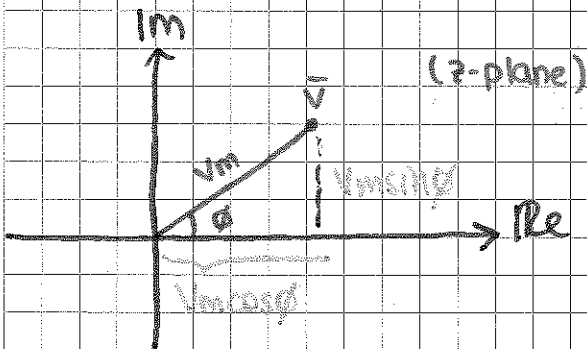• We use the following notation:  $A/\theta = A e^{j\theta}$



11/12/2015

### Inverse Phasor Transform

$p^{-1} \{ V_m e^{j\omega t} \} = \text{Re} \{ V_m e^{j\omega t} e^{j\omega t} \}$  is the formula of the Inverse Phasor Transform

For the current ;

$$i_{ss}(t) = \text{Re} \{ I_m e^{j\omega t} e^{j\omega t} \}$$

EX: If  $y_1 = 20 \cos(\omega t - 30^\circ)$  and  $y_2 = 40 \cos(\omega t + 60^\circ)$

- a) Solve  $y = y_1 + y_2$  by using trigonometric identities
- b) Solve  $y = y_1 + y_2$  by using phasors


Ans: a)  $y_1 = 20 \cos(\omega t) \cos 30^\circ + 20 \sin(\omega t) \sin 30^\circ$

$$y_2 = 40 \cos(\omega t) \cos 60^\circ + 40 \sin(\omega t) \sin 60^\circ$$

$$y_1 + y_2 = (20 \cos 30 + 40 \cos 60) \cos(\omega t) + (20 \sin 30 + 40 \sin 60) \sin(\omega t)$$

$$= 37.32 \cos \omega t - 24.64 \sin \omega t$$

We assume;

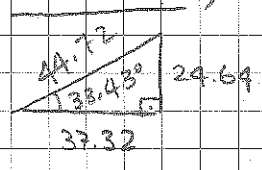

$$y = 44.72 \left( \frac{37.32}{44.72} \cos \omega t - \frac{24.64}{44.72} \sin \omega t \right)$$

$$= 44.72 (\cos(33.43^\circ) \cos \omega t - \sin(33.43^\circ) \sin \omega t)$$

OR From  $\cos A \cos B - \sin A \sin B = \cos(A+B)$

$$y = 44.72 \cos(\omega t + 33.43^\circ)$$

b)  $\bar{Y} = \bar{Y}_1 + \bar{Y}_2 = 20 \angle -30^\circ + 40 \angle 60^\circ$

$$\bar{Y} = (17.32 - j10) + (20 + j34.64)$$

$$= 37.32 + j24.64$$

$$= 44.72 \angle 33.43^\circ$$

and

$$y = \text{Re} \{ \bar{Y} e^{j\omega t} \}$$

$$= \text{Re} \{ 44.72 e^{j33.43^\circ} e^{j\omega t} \}$$

$$y = 44.72 \cos(\omega t + 33.43^\circ)$$

The same, but much faster and simpler!


$$z = a + jb = A e^{j\theta}$$

$$z = \underbrace{A \cos \theta}_a + j \underbrace{A \sin \theta}_b$$

(R, C, L)

Passive Circuit Elements in Frequency Domain:

\* V-I Relation for a Resistor

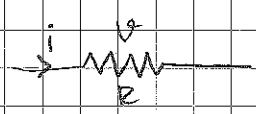

$$v = R [I_m \cos(\omega t + \theta)] = R I_m \cos(\omega t + \theta)$$

$$\boxed{\bar{v} = R I_m e^{j\theta} = R I_m \angle \theta} \quad \text{OR} \quad \boxed{V = R I}$$

\* V-I Relation for Inductor

$$v = L \cdot \frac{di}{dt} = -\omega L I_m \sin(\omega t + \theta)$$

OR

$$v = -\omega L I_m \cos(\omega t + \theta - \frac{\pi}{2})$$

and

$$\bar{v} = -\omega L I_m e^{j(\theta - \pi/2)} = -\omega L I_m e^{j\theta} \cdot \underbrace{e^{-j\pi/2}}_{-j} = j\omega L I_m e^{j\theta}$$

$$\boxed{\bar{v} = j\omega L I}$$

\* V-I Relation for Capacitor

$$i = C \cdot \frac{dv}{dt} \quad \text{where } v = V_m \cos(\omega t + \theta)$$

$$\text{then, } i = -C V_m \omega \sin(\omega t + \theta) \quad ; \text{ (same steps as inductor)}$$

$$\boxed{\bar{I} = j\omega C \bar{V}} \quad \text{OR} \quad \boxed{\bar{V} = \frac{\bar{I}}{j\omega C} = -j \frac{\bar{I}}{\omega C}}$$

\* IMPEDENCE & REACTANCE :

Define,  $\bar{v} = z \bar{I}$  (where z: impedance (frequency dependent resistance))

X = Reactance = Imaginary part of the impedance

R = Resistance = Real part of the impedance

	$\bar{z}$	X
Resistor	R	-
Inductor	j $\omega$ L	$\omega$ L
Capacitor	$\frac{-j}{\omega C}$	$\frac{-1}{\omega C}$

$Y = \frac{1}{z}$  = admittance ( $\Omega^{-1}$  = mho's or S, siemens) ,  $\frac{1}{X}$  = Susceptance (S)

$z$  = resistance depends on frequency

\* KIRCHHOFF'S LAWS IN FREQUENCY DOMAIN

• KVL in Phasors


$$\overline{V}_1 + \overline{V}_2 + \dots + \overline{V}_n = 0$$

• KCL in Phasors

$$\overline{I}_1 + \overline{I}_2 + \dots + \overline{I}_n = 0$$


• Series, Parallel and  $\Delta$ -Y Simplifications

1) Series connections

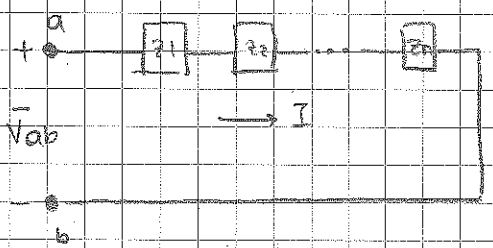

$$z_{ab} = \frac{V_{ab}}{I} = z_1 + z_2 + \dots + z_n$$

2) Parallel connections

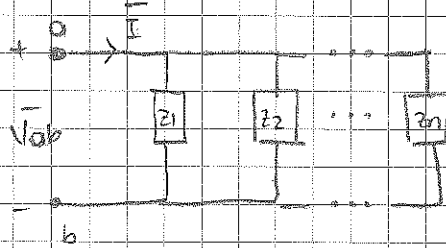

$$\frac{1}{z_{ab}} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}$$


conductance

$$Y_{ab} = \text{Admittance} = G + jB \quad (S)$$

susceptance

$$Y_{ab} = Y_1 + Y_2 + \dots + Y_n$$

3)  $\Delta$ -Y Transformation

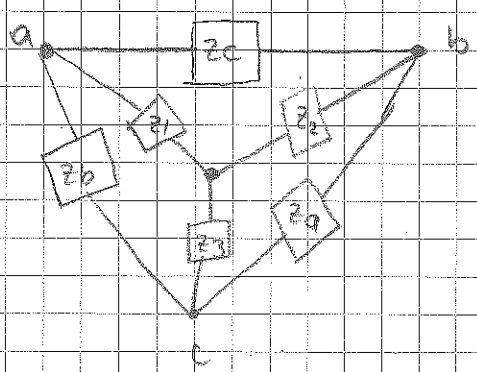

$$z_1 = \frac{z_b z_c}{z_a + z_b + z_c}, \quad z_2 = \frac{z_c z_a}{z_a + z_b + z_c}$$

$$z_3 = \frac{z_a z_b}{z_a + z_b + z_c}$$


$$z_a = \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_2}$$

$$z_b = \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_2}$$


$$z_c = \frac{z_1 z_2 + z_2 z_3 + z_1 z_3}{z_2}$$

# \* SOURCE TRANSFORMATIONS, THEVENIN & NORTON CIRCUITS

The transformation is as follows:

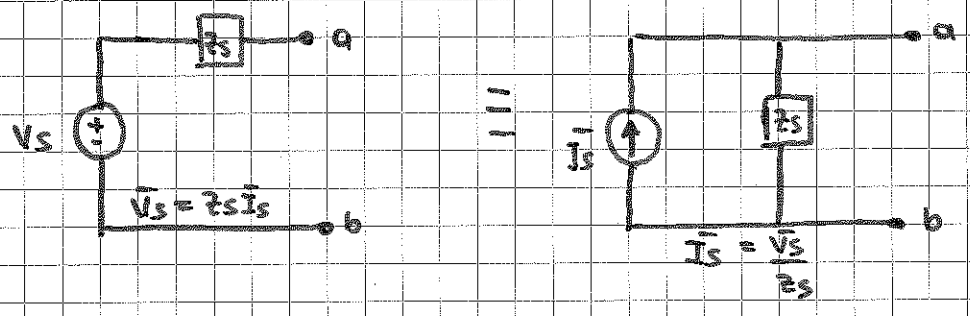


Ex: Find  $V_o$  in the circuit below:

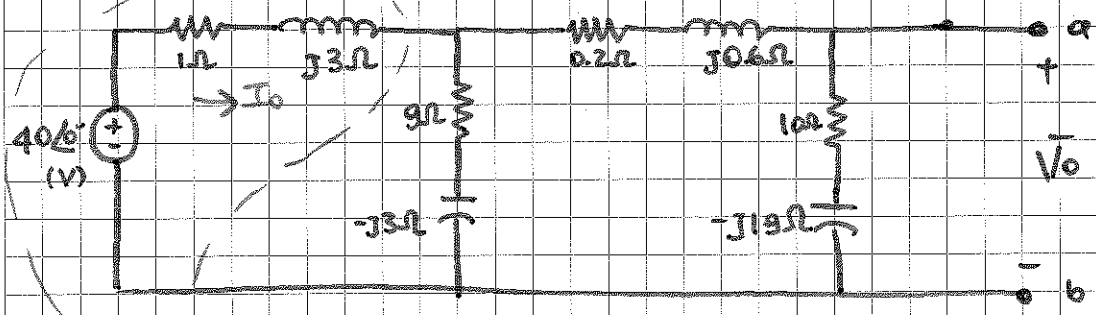

Ans: Replace by Norton-Equivalent

$$I = \frac{40}{1+j3} = \frac{40(1-j3)}{10} = \boxed{4-j12(A)}$$


Thus we have;

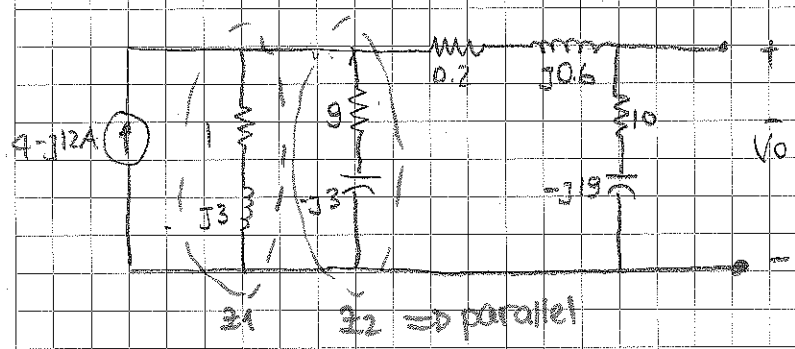

$$\frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\frac{1}{Z_t} = \frac{(1-j3)(9-j3)}{10} = 1.8 + j2.4 \Omega$$

Now we have;

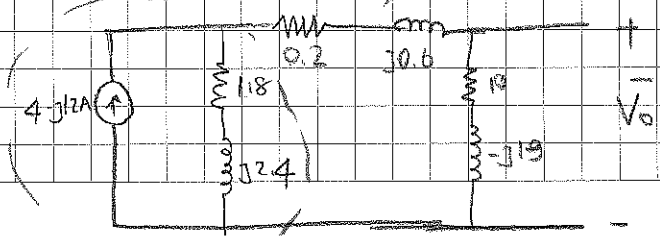

$$V = (4-j12)(1.8 + j2.4)$$

$$\boxed{V = 36 - j12V}$$

Transform to Thevenin Equivalent