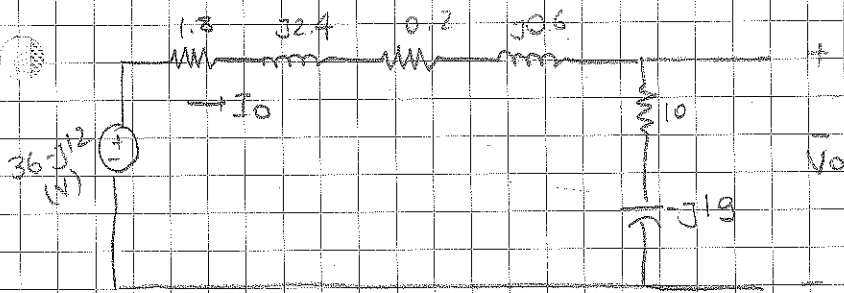


THUS,



$$I_0 = \frac{36 - j12}{1.8 + j32.4} = \frac{12(3 - j1)}{4(3 - j4)} = \frac{39 + j27}{25} = \underline{1.56 + j1.08 \text{ A}}$$


and  $V_0 = (1.56 + j1.08)(10 - j19)$

$$\underline{V_0 = 36.12 + j18.84 \text{ V}}$$

16/11/2015

The same concepts apply when we use the node-voltage method and the mesh current method to analyze the frequency domain circuits.

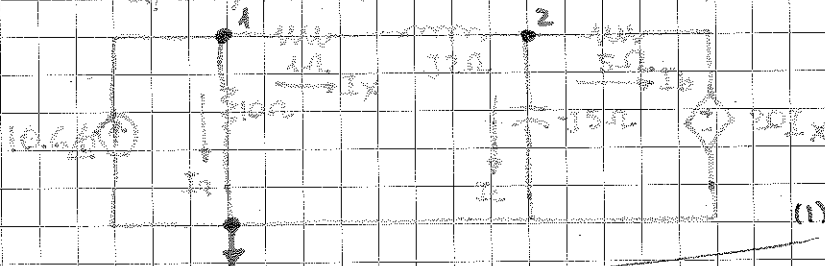EX: Use the node-voltage method to find the branch currents  $I_a, I_b, I_c$  in the circuit below.



Ans: KCL at node-1

$$-10.6 + \frac{V_1}{10} + \frac{V_1 - V_2}{1 + j2} = 0$$

$$(1) \quad V_1(1 + j0.2) - V_2 = 10.6 + j \cdot 21.2$$

From (1) and (4)

$$V_1 = 68.4 - j16.8 \text{ V}$$

$$V_2 = 68 - j26 \text{ V}$$

The controlling current  $I_x$  is:

$$(3) \quad I_x = \frac{V_1 - V_2}{1 + j2}$$

Substitute (3) in (2) and multiply by  $(1 + j2)$  given

$$(4) \quad -5V_1 + (4.8 + j0.6)V_2 = 0$$

Thus the branch currents are


$$I_a = \frac{V_1}{10} = 6.84 - j1.68 \text{ A}$$

$$I_x = \frac{V_1 - V_2}{1 + j2} = 3.76 + j1.68 \text{ A}$$

$$I_b = \frac{V_2 - 20I_x}{5} = -1.44 - j11.92 \text{ A}$$

$$I_c = \frac{V_2}{-j5} = 5.2 + j12.6 \text{ A}$$

# TRANSFORMERS

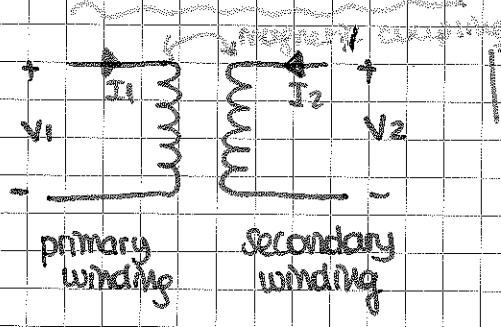


$$V_1, I_1 \propto V_2, I_2 \text{ (coupling)}$$

→ Transformers are used in electronics, communication and power circuits for different purposes.

## - The Analysis of a Linear Transformer Circuit -

Consider the circuit below:

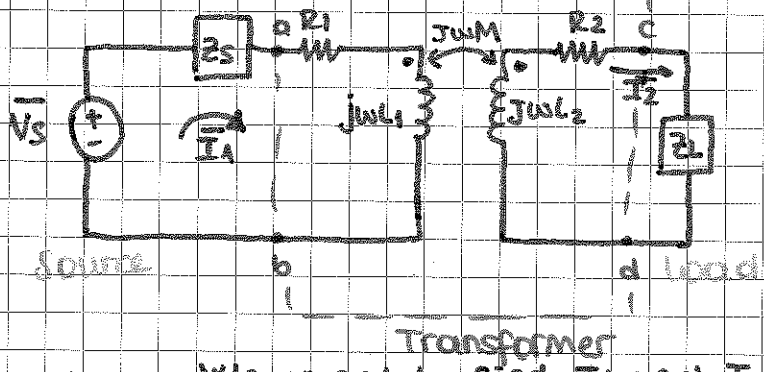

where ;

- R1: Resistance of the primary winding
- R2: Resistance of the secondary winding
- L1: Self inductance of the 1<sup>o</sup> winding
- L2: Self inductance of the 2<sup>o</sup> winding
- M: Mutual inductance

→ We want to find I1 and I2 as a function of the above parameters

The mesh current equations are:

$$V_s = (Z_s + R_1 + j\omega L_1) \bar{I}_1 - j\omega M \bar{I}_2$$

$$0 = -j\omega M \bar{I}_1 + (R_2 + j\omega L_2 + Z_L) \bar{I}_2$$

Let us define :  $Z_{11} = Z_s + R_1 + j\omega L_1$  and  $Z_{22} = R_2 + j\omega L_2 + Z_L$

Then,  $\bar{I}_1 = \frac{Z_{22}}{Z_{11} Z_{22} + \omega^2 M^2} V_s$ ,  $\bar{I}_2 = \frac{j\omega M}{Z_{11} Z_{22} + \omega^2 M^2} V_s = \frac{j\omega M}{Z_{22}} \bar{I}_1$

Also,  $\frac{V_s}{\bar{I}_1} = Z_{int} = \frac{Z_{11} Z_{22} + \omega^2 M^2}{Z_{22}} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$  and

$$Z_{ab} = Z_{int} - Z_s = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s$$

$$= R_1 + j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_2 + R_2 + Z_L}$$

$Z_r$ : Reflected impedance

\*  $Z_r$  depends on the coupling M, Thus, it is called reflected impedance from the 2<sup>nd</sup> circuit)

\*The load impedance is :  $Z_L = R_L + jX_L$  then, the reflected impedance expression becomes :

$$Z_r = \frac{\omega^2 m^2}{R_2 + R_L + j(\omega L_2 + X_L)} = \frac{\omega^2 m^2 [(R_2 + R_L) - j(\omega L_2 + X_L)]}{(R_2 + R_L)^2 + (\omega L_2 + X_L)^2}$$

$$= \frac{\omega^2 m^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)] \quad \text{where ; } Z_{22} = R_2 + R_L + j(\omega L_2 + X_L)$$




EX: The parameters of a linear transformer are

$R_1 = 200 \Omega, R_2 = 100 \Omega, L_1 = 9 \text{ mH}, L_2 = 4 \text{ mH}$  and  $k = 0.5$

The transformer couples an impedance consisting of  $800 \Omega$  in series with  $1 \mu\text{F}$  capacitor.  $300 \text{ V rms}$  source has an internal impedance of  $500 + j100 \Omega$  and frequency of  $400 \text{ rad/sec}$

- a) Freq. domain circuit = ?
- b) Self impedance of primary circuit = ?
- c) Self imp of 2° circuit = ?
- d) Impedance reflected into the 1° winding = ?
- e) Scaling factor for reflected imp = ?
- f) Imp. seen looking into the 1° terminals of the transformer = ?
- g) Thevenin equivalent wrt terminals c, d = ?

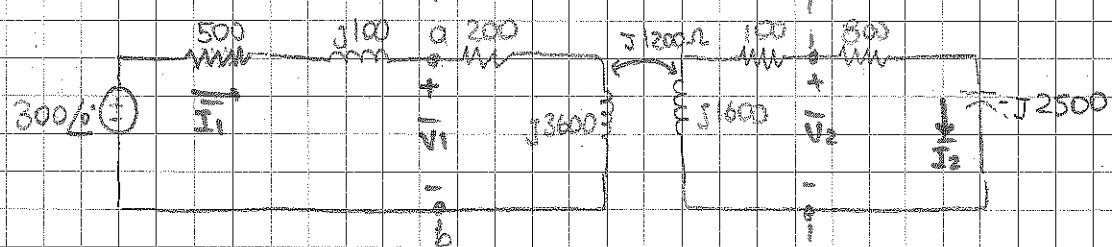a)  $j\omega L_1 = j(400)(9) = j3600 \Omega$        $m = 0.5 \sqrt{(9)(4)} = 3 \text{ H}$   
 $j\omega L_2 = j(400)(4) = j1600 \Omega$        $j\omega R_0 = j(400)(3) = j1200 \Omega$   
 $\frac{1}{j\omega C} = \frac{10^6}{j400} = -j2500 \Omega$  (c)



b) Self impedance of primary circuit =  $Z_{11} = 500 + j100 + 200 + j3600 = 700 + j3700 \Omega$


c)  $Z_{22} = j1600 + 100 + 800 - j2500 = 900 - j900 \Omega$

d)  $Z_r = \left( \frac{1200}{900 - j900} \right)^2 (900 + j900) = \frac{8}{9} (900 + j900) = 800 + j800 \Omega$

e) The scaling factor :  $\frac{Z_r}{Z_{22}} = \frac{8}{9}$

f)  $Z_{ab} = 200 + j3600 + 800 + j800 = 1000 + j4400 \Omega$

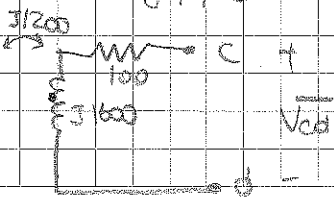
g)  $V_{cd} = (j/200) I_1$  (open circuit)



$I_1 = \frac{300 \angle 0^\circ}{700 + j3700} = 77.67 \angle -79.23^\circ \text{ mA}$

$V_{th} = (j/200) (77.67 \angle -79.23^\circ) = 95.60 \angle 10.71^\circ$

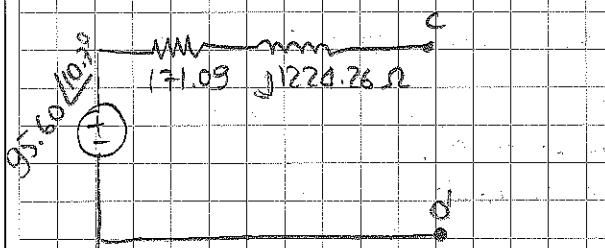$Z_{th} = 100 + j1600 + \left( \frac{1200}{700 + j3700} \right)^2 (700 - j900) = 171.09 + j124.26 \Omega$   
 Impedance of the 2° winding       $Z_r$  from 1° winding



→ Thevenin equivalent wrt cd terminals


18/12/2015

### IDEAL TRANSFORMER

It has the following properties:

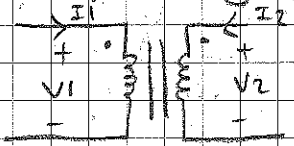- 1) The coefficient of coupling  $k = 1$
- 2) Self inductance  $L_1 = L_2 = \infty$
- 3) coil losses are negligible

The following symbol is used for an ideal transformer:



where we have the following relations:

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \text{and} \quad \boxed{I_1 N_1 = I_2 N_2}$$
 where  $N_1$  and  $N_2$  are number of turns for the 1<sup>o</sup> and the 2<sup>o</sup> windings respectively

### -Determining the Polarity of the Voltage & Current Ratios

→ If the coil voltages  $V_1$  and  $V_2$  are both (+) or (-) at the dot terminal use a (+) sign in equation:

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \text{otherwise, use a (-) sign}$$

→ If the coil currents  $I_1$  and  $I_2$  are both directed into or out of the dot terminal, use a (-) sign in the eqn  $|I_1 N_1| = |I_2 N_2|$ . Otherwise, use the (+) sign

Thus, we have the following cases:

$\frac{V_1}{N_1} = \frac{V_2}{N_2}$	$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$	$\frac{V_1}{N_1} = \frac{V_2}{N_2}$	$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$
$N_1 I_1 = -N_2 I_2$	$N_1 I_1 = N_2 I_2$	$N_1 I_1 = N_2 I_2$	$N_1 I_1 = -N_2 I_2$


→ There are three ways to show turn ratios:



We use "a" to denote the ratio:

$$a = \frac{N_2}{N_1}$$

Ex: For the given circuit:

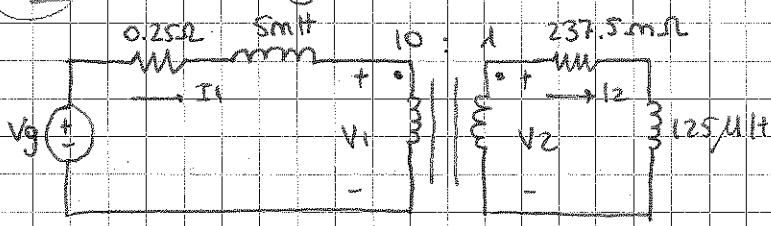

$$V_g = 2500 \cos(400t)$$

Find the steady-state expressions for

- a)  $i_1 = ?$  b)  $V_1 = ?$  c)  $i_2 = ?$  d)  $V_2 = ?$

Ans:  $V_g = 2500 \angle 0^\circ$

$P \{ 5mH \} = j2 \Omega$

$P \{ 125uH \} = j0.05 \Omega$

a) KVL in primary circuit given:

$$2500 \angle 0^\circ = (0.25 + j2) \bar{I}_1 + \bar{V}_1$$

$$\bar{V}_1 = 10 \bar{V}_2 = 10 [(0.2375 + j0.05) \bar{I}_2]$$

Because  $\bar{I}_2 = 10 \bar{I}_1$  we have  $\bar{V}_1 = 10 [(0.2375 + j0.05) 10 \bar{I}_1]$

$$\bar{V}_1 = (23.75 + j0.05) \bar{I}_1$$

then,  $2500 \angle 0^\circ = (25 + j2) \bar{I}_1$  or  $|\bar{I}_1| = 100 \angle -16.26^\circ \text{ A}$

Thus  $|\bar{I}_1| = 100 \cos(400t - 16.26^\circ) \text{ A}$

b)  $V_1 = 2500 \angle 0^\circ - [(100 \angle -16.26^\circ) (0.25 + j2)] = 2500 - 80 - j185$

$V_1 = 2420 - j185 = 2427.06 \angle -4.37^\circ \text{ V}$

Hence,  $|\bar{V}_1| = 2427.06 \cos(400t - 4.37^\circ) \text{ V}$

c)  $\bar{I}_2 = 10 \bar{I}_1 = 1000 \angle -16.26^\circ \text{ A}$

then  $|\bar{I}_2| = 1000 \cos(400t - 16.26^\circ) \text{ A}$

d)  $V_2 = 10 V_1 = 242.71 \angle -4.37^\circ \text{ V}$


then  $|\bar{V}_2| = 242.71 \cos(400t - 4.37^\circ) \text{ V}$



lag = gerisinde kalmak  
lead = ilerisinde kalmak

## THE USE OF AN IDEAL TRANSFORMER FOR IMPEDANCE MATCHING

Consider the following circuit

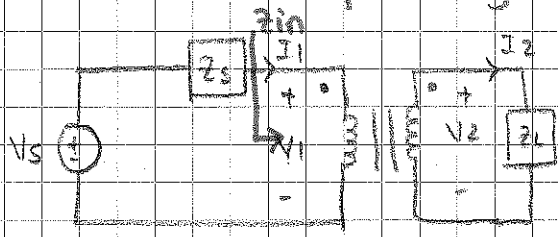

$$V_1 = \frac{V_2}{a} \quad \text{and} \quad I_1 = a \cdot I_2$$

Thus the impedance seen by the source is:

$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{a^2} \frac{V_2}{I_2}$$

Since,  $\frac{V_2}{I_2} = Z_L$ ,  $Z_{in} = \frac{1}{a^2} Z_L$


Thus, the secondary coil reflects the load impedance back to primary coil by  $1/a^2$ .

We use ideal transformer to match  $Z_s$  and  $Z_L$ , but this is the subject of the next chapter

### Phasor Diagrams

Steady state sinusoidal circuit analysis can be shown in the complex phasor diagram or graph

\* EX: For the following circuit:

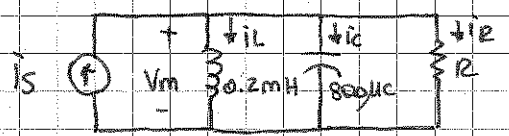



Use the phasor diagram to find the value of R that will cause  $I_2$  to lag the source current is by  $45^\circ$  when  $\omega = 5k \text{ rad/sec}$

Ans:  $I_L = \frac{V_m \angle 0^\circ}{j(5000)(0.2 \times 10^{-3})} = V_m \angle -90^\circ$

$I_0 = \frac{V_m \angle 0^\circ}{j/(5000)(800 \times 10^{-6})} = 4 V_m \angle 90^\circ$

$I_R = \frac{V_m \angle 0^\circ}{R} = \frac{V_m}{R} \angle 0^\circ$

The complex plane:

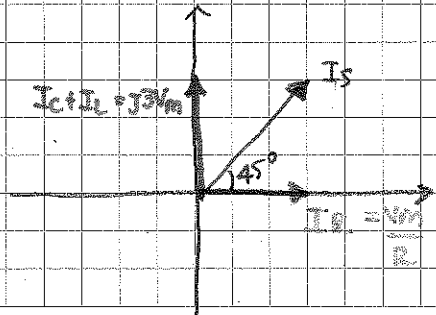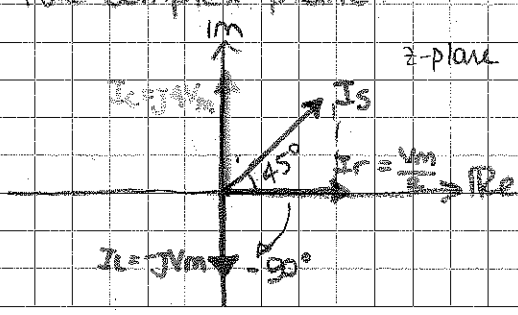

$\frac{V_m}{R} = |I_c + I_L| = 3 V_m$

$R = \frac{1}{3} \Omega$