

EE205 Lecture Notes:

P1

26 Eylül 2020 Cumartesi 17:16

Electric potential (voltage): Work done by charges $= \frac{E}{q}$

E = Electric potential energy. (Joules) = Work capacity

q = charge. (Coulombs)

\downarrow
 $F \cdot d$

$$\text{Current} = \frac{q}{t} \text{ (A)} = I$$

q = charge.


t = time. (sec.)

$$\text{Power} = \frac{E}{t} \text{ (Watts)} = \underbrace{\frac{E}{q}}_V \cdot \underbrace{\frac{q}{t}}_I = V \cdot I \text{ (W)}$$


I deal Basic Circuit Elements:

It is an electrical component with the following Properties:

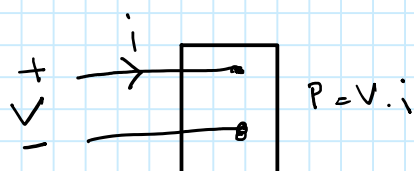- 1-) Two terminals.
- 2-) Can be described as voltage or current.
- 3-) Can not be subdivided into other elements.



Symbol for
ideal circuit element.

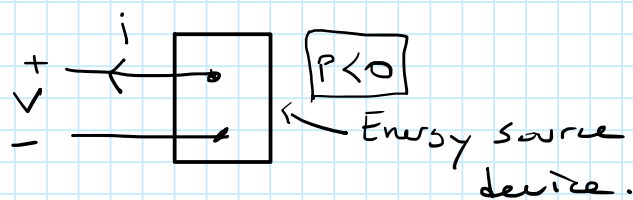

If the current is going out of the circuit element, this refers to the existence of an energy source (generator).

If the power consumption by the element is positive, ($P > 0$), the power is being delivered to the circuit inside the box.

If the power is negative, $P < 0$, the power is being extracted from the circuit inside the box.

Chapter 2 : Circuit Elements :

There are two circuit elements, voltage and current sources.

- Ideal voltage source: Provides a constant voltage across its terminals regardless of the current.
- Ideal current source: Similar to the voltage source. It provides current across its terminals regardless of the voltage.

If circuit elements do not depend on any other parameter, they are called "independent sources".


Circuit symbols:




Ideal Independent voltage source.



Ideal indep. current source.

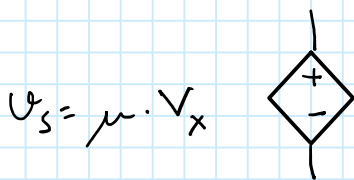


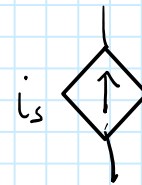Ideal dependent voltage controlled voltage source.




Ideal dependent voltage controlled current source.

$$\bar{i}_s = \alpha \cdot V_x$$

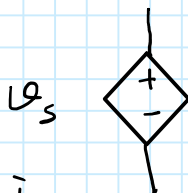

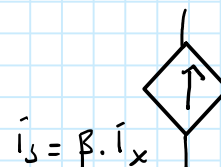Ideal dependent current controlled voltage source.



Ideal dependent current controlled current source.



$$V_s = g \cdot \bar{i}_x$$

P2a



16 Ekim 2020 Cuma 09:22

Constraints for the Connection of Circuit Elements:

- Two independent voltage sources:

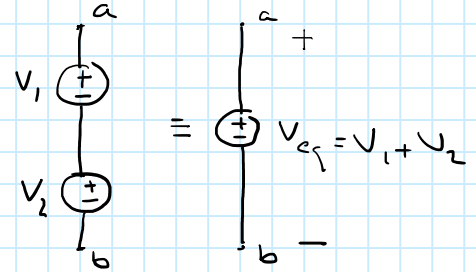
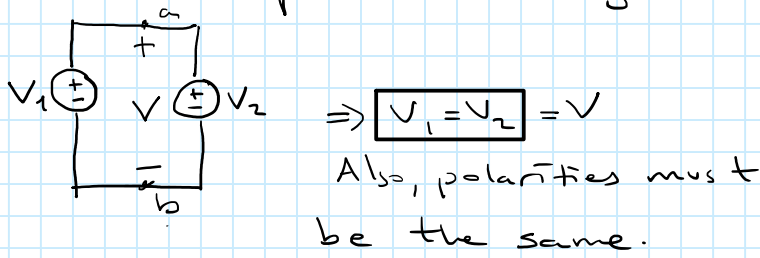


- Two independent current sources:

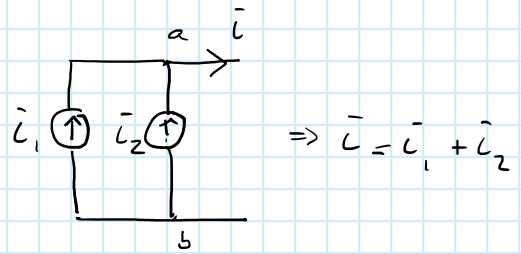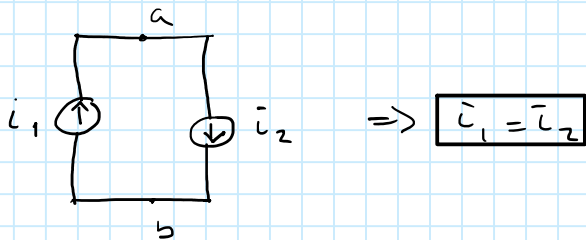


Ex:


Determine which connections are valid.

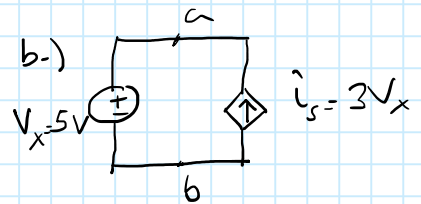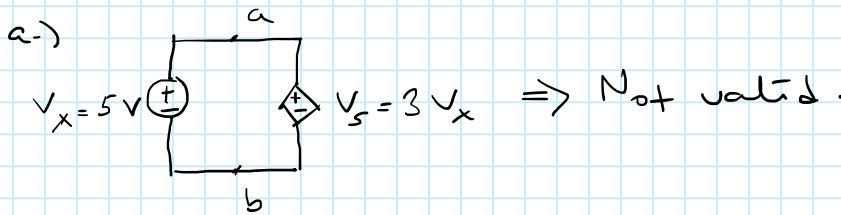

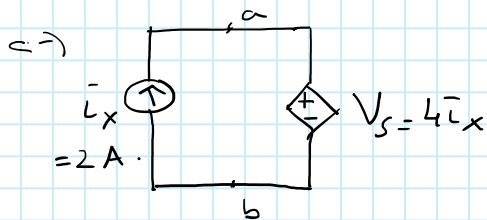\Rightarrow Ideal voltage source supplies the same voltage regardless of the current, and vice versa. Thus, this is valid.



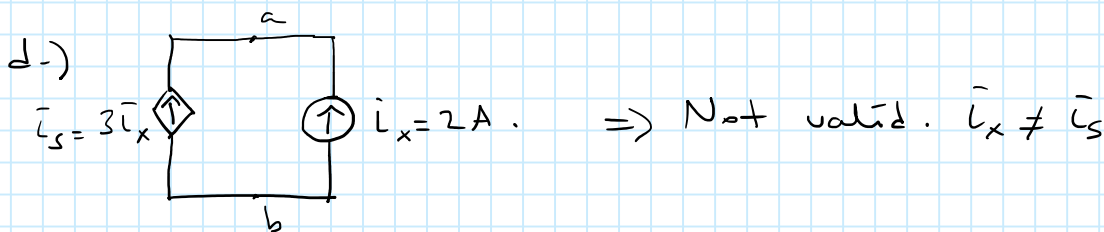\Rightarrow Valid. Because of the same reason in part b.



Two important concepts:

- Active element: A device capable of generating electrical energy. ($P < 0$)
- Passive element: A device that can not generate electrical energy. ($P > 0$). Examples: Resistors, inductors, capacitors. (lumped elements).



Resistance: ("R")

is the capacity of materials to resist the current flow. (impede, oppose)

Ohm's law: $V = I \cdot R$

Reciprocal of resistance is called "conductance" with a symbol "G".

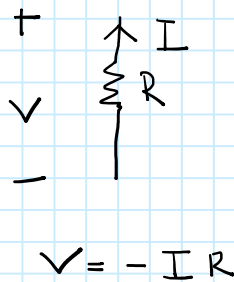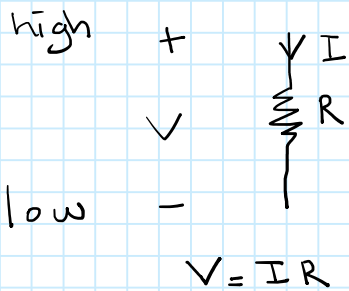$\Rightarrow G = \frac{1}{R}$ (Siemens or S) \rightarrow "mho" $R (\Omega = \text{ohm})$



$G = \frac{1}{R} \cdot (S)$





$P = VI = I^2 R (W)$

Also, $P = \frac{V^2}{R} (W)$

$I = VG$

Ex:

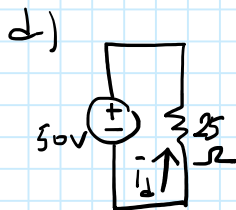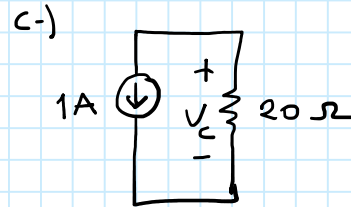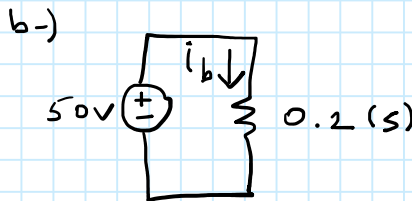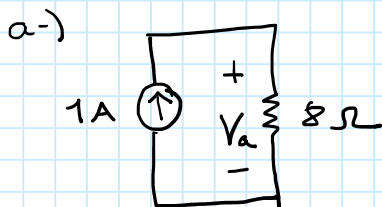Calculate the values of v and i , and determine the power dissipated in each resistor.




Ans:

a-) $V_a = I \cdot R = (1A)(8\Omega) = 8V$, $P_{8\Omega} = \frac{V^2}{R} = \frac{8^2}{8} = 8 \text{ Watts}$.

b-) $i_b = \frac{V}{R} = V \cdot G = (50V)(0.2S) = 10A$, $P_{0.2S} = V^2 G = 500W$.

Delta to Wye Equivalent Circuits:



Consider the following circuit:

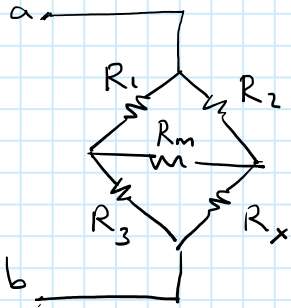

⇒ The resistors R_1, R_2, R_m or R_3, R_m, R_x are called "Delta (Δ)" connection.

⇒ The resistors R_1, R_m, R_3 or R_2, R_m, R_x are called "Wye (γ)" connection.

Δ to γ Transformation:

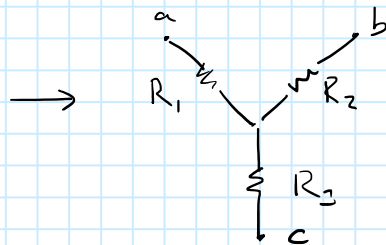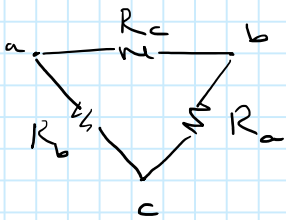

where

$$R_1 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$


Also,

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}, \quad R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

Ex:

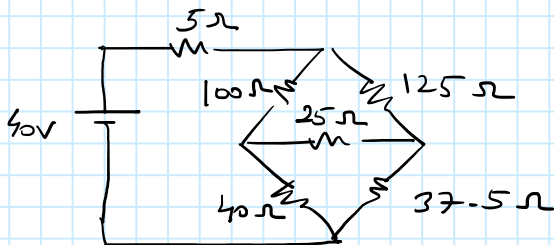Find the current and power supplied by the 40V source.




Ans:

First, replace the upper delta circuit ($100\Omega, 125\Omega, 25\Omega$) by its γ -equivalent.

$$\Rightarrow R_1 = \frac{100 \cdot 125}{250} = 50\Omega, \quad R_2 = \frac{125 \cdot 25}{250} = 12.5\Omega, \quad R_3 = \frac{100 \cdot 25}{250} = 10\Omega$$

$$\Rightarrow R_{eq} = 5 + 50 + (10 + 40) \parallel (12.5 + 37.5)$$
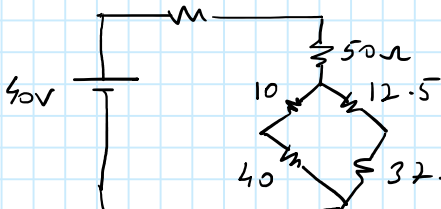
$$= 55 + (50 \parallel 50) = 80\Omega \quad \text{in parallel.}$$



$$\Rightarrow P = V \cdot i = -40 \cdot 0.5 = -20W \quad \Rightarrow I = V/R = \frac{40}{80} = 0.5A$$




$$c-) V_c = i \cdot R = \underbrace{- (1A)}_i (20 \Omega) = \underbrace{-20V}_V; \quad P_{20\Omega} = \frac{V^2}{R} = \frac{(-20)^2}{20} = 20W.$$

$$d-) i_d = \frac{V}{R} = \frac{-50V}{25\Omega} = -2A. \quad P = \frac{V^2}{R} = \frac{(-50)^2}{25} = 100W.$$

↑ "−" sign indicates that the original selection of the current direction is really the opposite.

Kirchoff's Laws:

Suppose we have the following circuit,

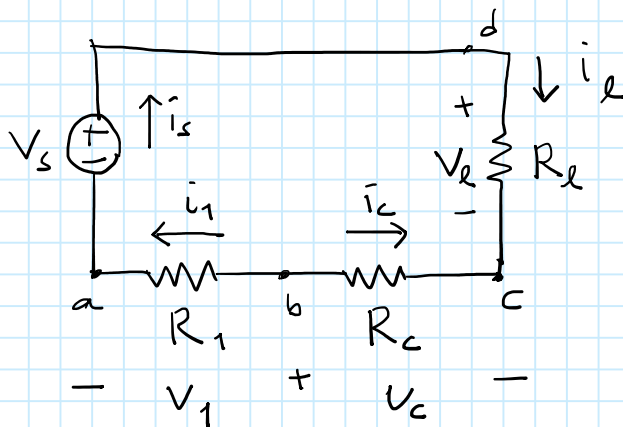

$$V_1 = i_1 R_1$$

$$V_c = i_c R_c$$

$$V_d = i_d R_d$$

We consider leaving currents positive, and entering currents negative.

Kirchoff's Current Law (KCL):

The algebraic sum of the currents at any point in a circuit is zero.

At point a:

$$\bar{i}_s - \bar{i}_1 = 0$$

At point b:

$$\bar{i}_1 + \bar{i}_c = 0$$

At point c:

$$-\bar{i}_c - \bar{i}_d = 0$$

At point d:

$$\bar{i}_d - \bar{i}_s = 0$$

Note that initial assumption of currents and voltages are not important. At the end of the solution, we get results which are + or −, indicating the real directions.

Kirchoff's Voltage Law (KVL):

The algebraic sum of all the voltages around any closed path in a circuit is zero.

Closed path: dcbad (we follow clockwise direction.)

$$V_L - V_C + V_1 - V_S = 0 \quad (\text{KVL equation.})$$


(+ \rightarrow - is always positive.)

Closed path: dabcd (ccw)

$$V_S - V_1 + V_C - V_L = 0 \quad (\text{The same equation as before.})$$

Ex:

Given the circuit below:

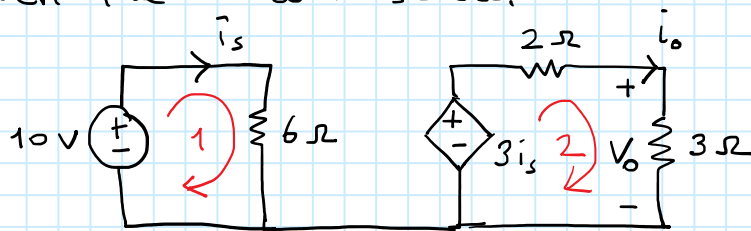

a-) Find V_o from KVL and Ohm's law.

b-) Show that $P_{\text{total}} \Big|_{\text{dissipated}} = P_{\text{total}} \Big|_{\text{developed}}$ (Conservation of energy.)

Ans:

a-) KVL in loop 1:

$$-10V + 6i_s = 0$$

$$\Rightarrow i_s = \frac{10}{6} = \frac{5}{3} \text{ A}$$

Also, KVL for loop 2:

$$-3i_s + 2i_o + V_o = 0$$

$$-5 + 2i_o + V_o = 0$$

Ohm's law:

$$V_o = 3i_o$$

Thus,

$$-5 + 2i_o + 3i_o = 0$$

$$5i_o = 5$$

$$\Rightarrow i_o = 1 \text{ A}$$

$$\text{Then, } V_o = 3i_o = 3 \text{ V}$$

b-) Power for indep. voltage source:

$$P = Vi = (10V) \cdot i_s = 10 \cdot \left(\frac{5}{3}\right) = -16.7 \text{ W}$$

Also,

$$P_{6\Omega} = vi = (10V) i_s = 16.7 \text{ W}$$

$$P_{2\Omega} = i^2 R = i_o^2 (2) = (1)^2 (2) = 2 \text{ W}$$

$$P_{3\Omega} = i^2 R = i_o^2 (3) = (1)^2 (3) = 3 \text{ W}$$


Power delivered by the dependent source:

$$P = v \cdot i = (-3 \hat{i}_y) (\hat{i}_x) = -3 \cdot \frac{5}{3} \cdot (1A) = -5 \text{ W.}$$

Electric Shock:

Electric current flow through the human body. In many cases, the current flows from head towards feet passing through heart. This causes heart to stop beating (fibrillation).

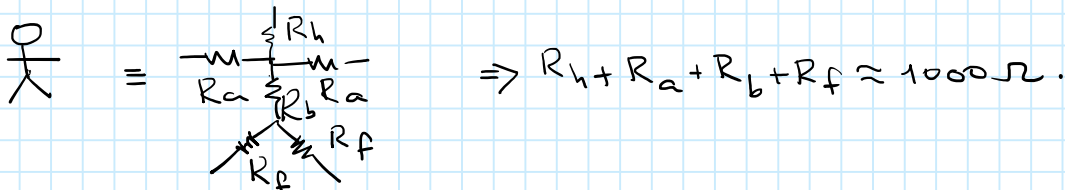Majority of 220V contacts, electric shocks result in fibrillation. This also depends on the time of exposure and the body resistance.



Dangerous limits of currents:

For AC current: 3-5 mA amplitude \rightarrow barely acceptable.

Amplitude > 30 mA is the limit. and always risk of life.

For DC current: $I > 300-500$ mA


is the limit for danger of life.

Ex:

A person with a dry body gets electric shock with 220V. Find the current passing through his body?

Ans:

$$I = \frac{V}{R} = \frac{220}{1000} = 0.22 \text{ A} = 220 \text{ mA} > 30 \text{ mA (dangerous)}$$

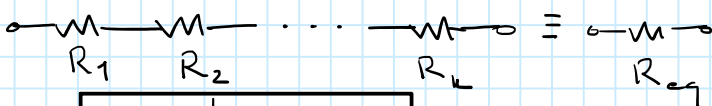Resistive Circuits:Resistors in Series:


$$R_{eq} = \sum_{i=1}^k R_i \text{ (}\Omega\text{)}$$

Resistors in Parallel:

$$R_{eq} = \frac{1}{\sum_{i=1}^k \left(\frac{1}{R_i} \right)} \text{ (}\Omega\text{)}$$

Voltage Divider:

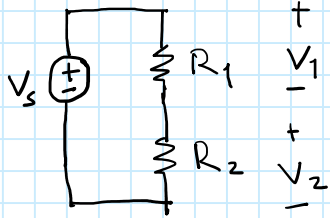
- Short method to find voltages when several resistors are connected in series.



$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$

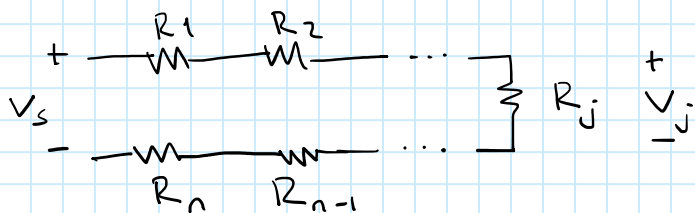In case of n resistors connected in series:




$$V_j = V_s \cdot \frac{R_j}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Current Divider:

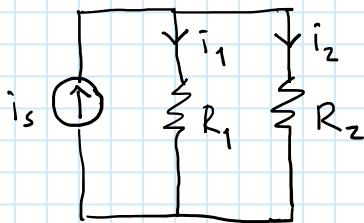
It is a rule for finding the current passing through the resistors which are connected in parallel.



$$i_1 = i_s \cdot \frac{R_2}{R_1 + R_2}$$

$$i_2 = i_s \cdot \frac{R_1}{R_1 + R_2}$$

For general current division, we have:

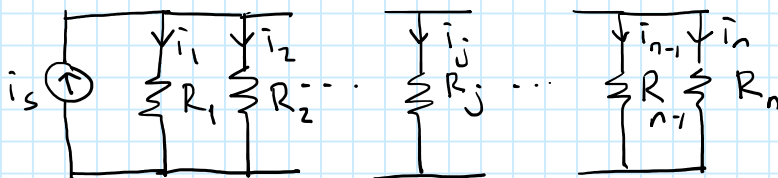


$$i_j = i_s \cdot \frac{R_{eq}}{R_j}$$


where

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Ex:

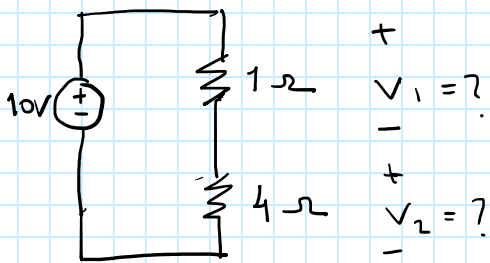

Ans:

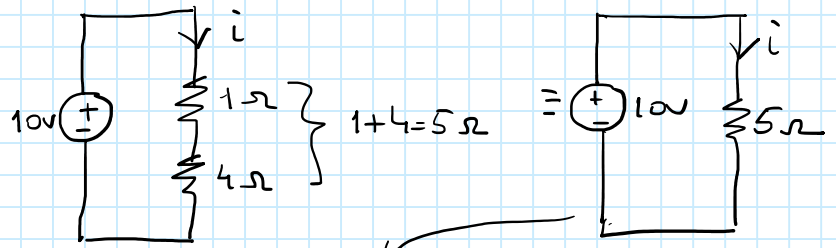

$$i = \frac{V}{R} = \frac{10}{5} = 2 \text{ A.}$$

$$V_1 = i \cdot R_1 = (2)(1) = 2 \text{ V.}$$


$$V_2 = i \cdot R_2 = (2)(4) = 8 \text{ V}$$

By using the voltage division rule:

$$V_1 = 10 \cdot \frac{1}{1+4} = \frac{10}{5} = 2 \text{ V.}$$

$$V_2 = 10 \cdot \frac{4}{1+4} = 10 \cdot \frac{4}{5} = 8 \text{ V.}$$

Ex:

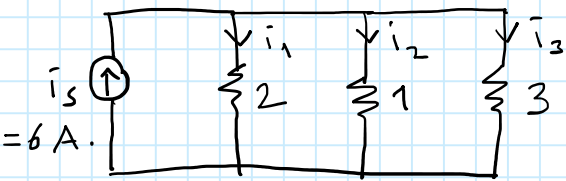

Find i_1 , i_2 and i_3 ?

Ans:


$$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{1} + \frac{1}{3}} = \frac{1}{\frac{3+6+2}{6}} = \frac{6}{11} \Omega.$$

$$i_1 = i_s \cdot \frac{R_{eq}}{R_j} = 6 \cdot \frac{\frac{6}{11}}{2} = \frac{18}{11} = 1.636 \text{ A.}$$

$$i_2 = 6 \cdot \frac{6}{11} \cdot \frac{1}{1} = \frac{36}{11} = 3.273$$

$$i_3 = 6 \cdot \frac{6}{11} \cdot \frac{1}{3} = \frac{12}{11} = 1.1$$

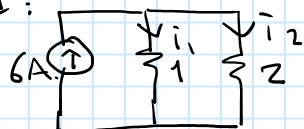IF we had: $i_1 + i_2 + i_3 = 1.636 + 3.273 + 1.1 = 6 \text{ A} = i_s. \text{ (KCL) } \checkmark$



$$\Rightarrow i_1 = i_s \cdot \frac{2}{1+2} = 6 \cdot \frac{2}{3} = 4 \text{ A.}$$


$$i_2 = 6 \cdot \frac{1}{3} = 2 \text{ A.}$$

Cp. 4. Techniques of Circuit Analysis:

In a given circuit with some node and closed loops, we use the KCL, KVL and Ohm's law to derive algebraic equations. Then, we solve these equations simultaneously to find the unknown voltages and/or currents.

1-) Node-Voltage Method:


Suppose we have the following circuit:

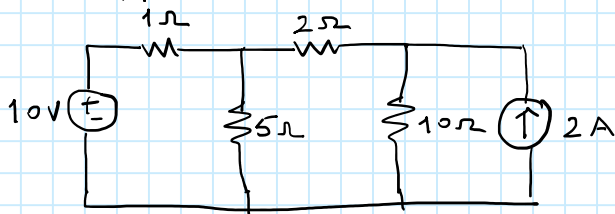

Step 1: Simplify the circuit such that no branches cross over and we can mark the essential nodes. (3 nodes in this case.)


Step 2:

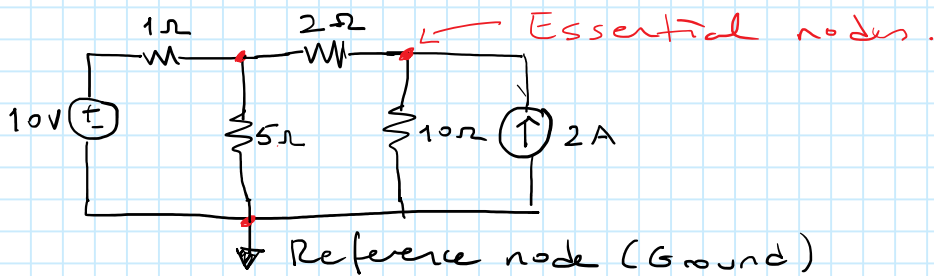Select one of the nodes as a reference node. The node with most branches is usually taken as the reference node. (In this case, it is the lower node.)




Step 3:

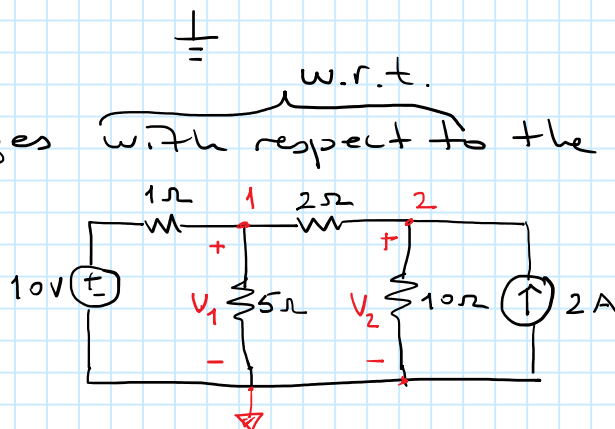Define node voltages with respect to the reference node. Thus, we have



Step 4:

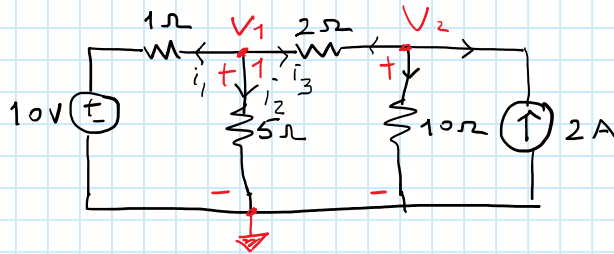Generate node-voltage equations by:
Writing the node equations for each node employing the leaving current convention.



KCL at node 1 gives:

$$i_1 + i_2 + i_3 = 0$$

$$\downarrow \qquad \downarrow$$

$$\frac{V_1 - 10}{1\Omega} + \frac{V_1}{5\Omega} + \frac{V_1 - V_2}{2\Omega} = 0 \quad (1)$$

KCL at node 2 gives:

$$\frac{V_2 - V_1}{2\Omega} + \frac{V_2}{10\Omega} - 2 = 0 \quad (2)$$

Equations (1) and (2) can be solved simultaneously to find

$$V_1 = 9.09\text{V}, \quad V_2 = 10.91\text{V}.$$

The currents can be found by Ohm's law.

$$\text{For example } i_3 = \frac{V_1 - V_2}{2} = \frac{9.09 - 10.91}{2} = -0.51$$


- The minus sign indicates that the real direction of the current is opposite of our initial selection.
- Voltage polarities and direction of currents can be arbitrarily selected in the beginning. The important point is that we must be consistent with our initial selections throughout the solution.

P11

9 Ekim 2020 Cuma 11:34


Ex:

Given the following circuit

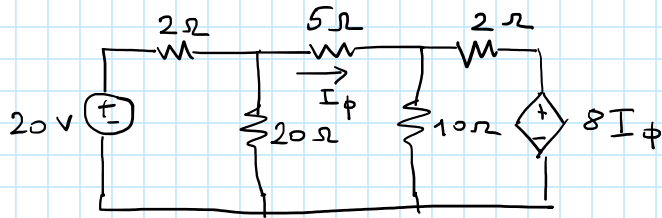

Find $P_{5\Omega} = ?$

Ans:

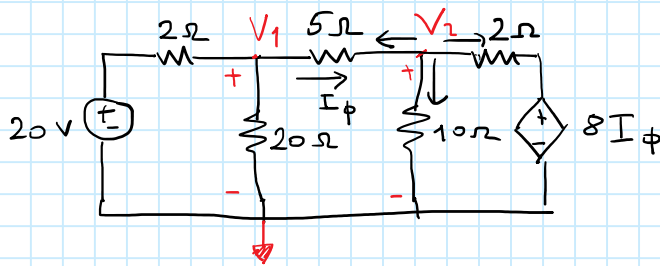

$$I_{\phi} = \frac{V_1 - V_2}{5} \text{ from the Ohm's law.} \quad \text{--- (1)}$$

Use the node-voltage method:

KCL at node 1:

$$\frac{V_1 - 20}{2} + \frac{V_1}{20} + I_{\phi} = 0 \quad \text{--- (2)}$$

KCL at node 2:

$$-I_{\phi} + \frac{V_2}{10} + \frac{V_2 - 8I_{\phi}}{2} = 0 \quad \text{--- (3)}$$

Thus, we have 3 equations with 3 unknowns which can be solved simultaneously.

$$\Rightarrow V_1 = 16V, \quad V_2 = 10V, \quad I_{\phi} = 1.2A.$$

$$P_{5\Omega} = I_{\phi}^2 \cdot R = (1.2)^2 (5) = 7.2W //$$


2-) Mesh-Current Method:

Mesh \rightarrow loop with no other loops inside.

For example, consider the following circuit:

P12

9 Ekim 2020 Cuma 11:47

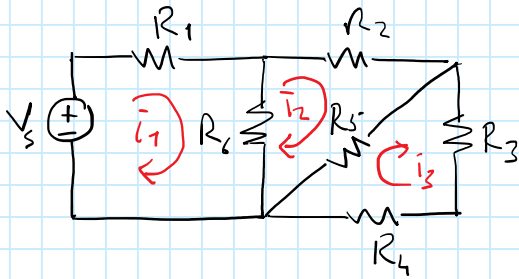


How many meshes are there in this circuit?

Ans: There are 3 meshes with currents \bar{i}_1 , \bar{i}_2 and \bar{i}_3 .


For mesh-current analysis, we write the KVL equations for each mesh, and solve the equations simultaneously.

Ex:

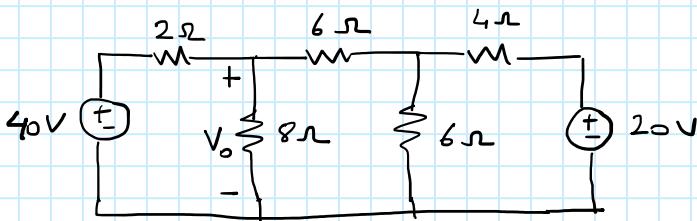Use the mesh-current method to determine the power associated with each voltage source. Also find V_o .



Ans:

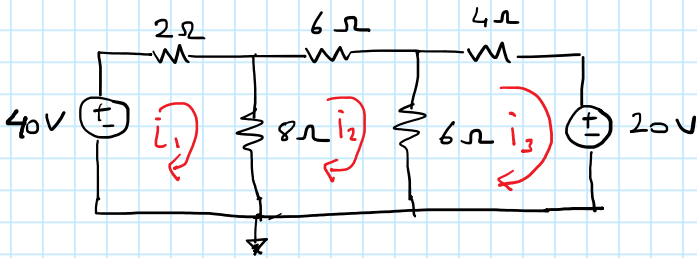

KVL for mesh 1:

$$-40V + 2i_1 + 8(i_1 - i_2) = 0 \quad \text{--- (1)}$$

KVL for mesh 2:

$$8(i_2 - i_1) + 6i_2 + 6(i_2 - i_3) = 0 \quad \text{--- (2)}$$

KVL for mesh 3:

$$6(i_3 - i_2) + 4i_3 + 20 = 0 \quad \text{--- (3)}$$

Again, we have 3 equations with 3 unknowns (i_1, i_2, i_3).

Re-arranging the equations:

$$\begin{aligned} 10i_1 - 8i_2 &= 40 \\ -8i_1 + 20i_2 - 6i_3 &= 0 \\ -6i_2 + 10i_3 &= -20 \end{aligned}$$

P13

9 Ekim 2020 Cuma 12:05

$$\begin{aligned} 10\bar{i}_1 - 8\bar{i}_2 &= 40 \\ 8\bar{i}_1 + 20\bar{i}_2 - 6\bar{i}_3 &= 0 \\ -6\bar{i}_2 + 10\bar{i}_3 &= -20 \end{aligned}$$

$$\begin{bmatrix} 10 & -8 & 0 \\ -8 & 20 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} \bar{i}_1 \\ \bar{i}_2 \\ \bar{i}_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ -20 \end{bmatrix}$$

$\Rightarrow A \cdot \mathbf{I} = \mathbf{b}$ (matrix equation)

$$A \cdot \mathbf{I} = \mathbf{b}$$

The solution is:

$$\mathbf{I} = A^{-1} \cdot \mathbf{b}$$

$$\bar{i}_1 = 5.6 \text{ A}, \quad \bar{i}_2 = 2 \text{ A}, \quad \bar{i}_3 = -0.8 \text{ A}.$$


$$\left. \begin{aligned} P_{40\text{V}} &= -40 \cdot \bar{i}_1 = -224 \text{ W} \\ P_{20\text{V}} &= -20 \cdot \bar{i}_3 = -16 \text{ W} \end{aligned} \right\} \text{Power delivered.}$$

$$V_o = 8(\bar{i}_1 - \bar{i}_2) = 8(3.6) \Rightarrow V_o = 28.8 \text{ V} //$$

Special Case of Mesh-Current Method:

When there is a current source in the circuit, the number of unknown currents is reduced by one.

Ex:

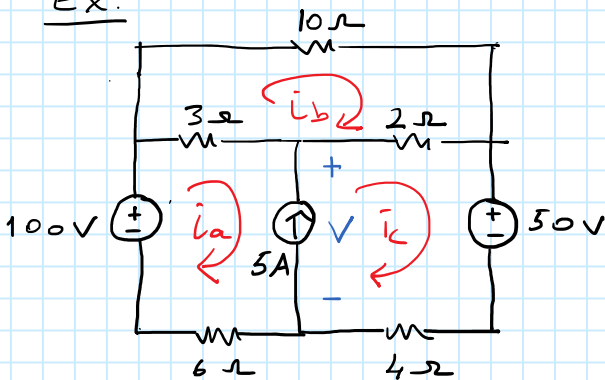

Find the loop currents \bar{i}_a , \bar{i}_b and \bar{i}_c in this circuit.

Ans:

For mesh a: (KVL)

$$-100 + 3(\bar{i}_a - \bar{i}_b) + V + 6\bar{i}_a = 0 \quad (1)$$

For mesh c:

$$50 + 4\bar{i}_c - V + 2(\bar{i}_c - \bar{i}_b) = 0 \quad (2)$$

Re-write eqn's (1) and (2) as

$$100 = 3(\bar{i}_a - \bar{i}_b) + V + 6\bar{i}_a \quad \text{--- (1)}$$

$$-50 = 4\bar{i}_c - V + 2(\bar{i}_c - \bar{i}_b) \quad \text{--- (2)}$$

Add (1) and (2)

$$50 = 9\bar{i}_a - 5\bar{i}_b + 6\bar{i}_c \quad \text{--- (3)}$$

KVL for mesh b:

$$0 = 3(\bar{i}_b - \bar{i}_a) + 10\bar{i}_b + 2(\bar{i}_b - \bar{i}_c) \quad \text{--- (4)}$$

We also have

$$\bar{i}_c - \bar{i}_a = 5A. \quad \text{--- (5)}$$

Eqn's (3), (4) and (5) can be solved for \bar{i}_a , \bar{i}_b and \bar{i}_c .

$$\begin{bmatrix} 9 & -5 & 6 \\ -3 & 15 & -2 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \bar{i}_a \\ \bar{i}_b \\ \bar{i}_c \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}$$

$\underbrace{\hspace{10em}}_A \cdot \underbrace{\begin{bmatrix} \bar{i}_a \\ \bar{i}_b \\ \bar{i}_c \end{bmatrix}}_{\bar{i}} = \underbrace{\begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}}_b$

$$9\bar{i}_a - 5\bar{i}_b + 6\bar{i}_c = 50 \quad \text{--- (3)}$$

$$-3\bar{i}_a + 15\bar{i}_b - 2\bar{i}_c = 0$$

$$-\bar{i}_a + \bar{i}_c = 5$$


$$\Rightarrow \bar{i} = A^{-1} \cdot b$$

$$\Rightarrow \bar{i}_a = 1.75A, \bar{i}_b = 1.25A, \bar{i}_c = 6.75A.$$


Chapter 5:

Thévenin and Norton Equivalents:

We want to replace

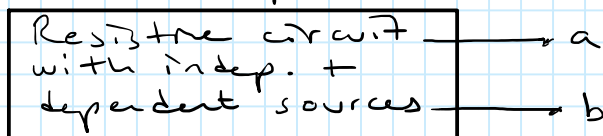

with the following circuit:

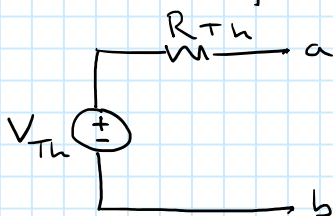


where V_{Th} = Thévenin voltage.

R_{Th} = Thévenin resistance.

P15

16 Ekim 2020 Cuma 10:44

Consider the following circuit:

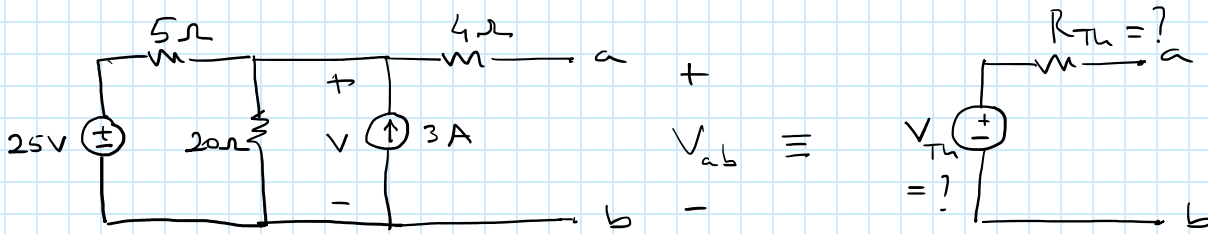


- If we connect another circuit to the given circuit at points a and b, this other circuit sees no difference if it is connected to Thévenin equivalent circuit.

V_{Th} = Open circuit voltage btw the terminals a and b, and we short circuit a and b, and find the current btw a and b (I_{sc}).

Thus, $I_{sc} = \frac{V_{Th}}{R_{Th}} \Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}}$

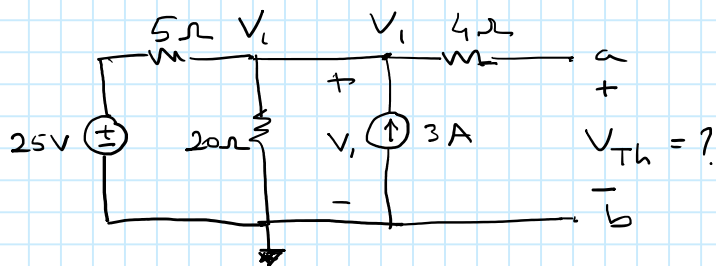For the given circuit; using the node-voltage method:



The current passing through the 4Ω resistor is zero.

$$V = i \cdot R = 0$$

$$\downarrow$$

$$0 \quad \text{---} \quad 4\Omega \quad \text{---}$$

$$+ \quad 0 \quad -$$

$$V_1 \quad \quad V_2$$

$$V_1 - V_2 = 0$$

$$\boxed{V_1 = V_2}$$

$$\Rightarrow \boxed{V_1 = V_{Th}}$$

KCL at node 1:


$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0$$

$$\Rightarrow V_1 = 32V.$$

$$V_{Th} = 32V.$$

- In order to find R_{Th} , we short circuit points a and b, and

find I_{sc} .

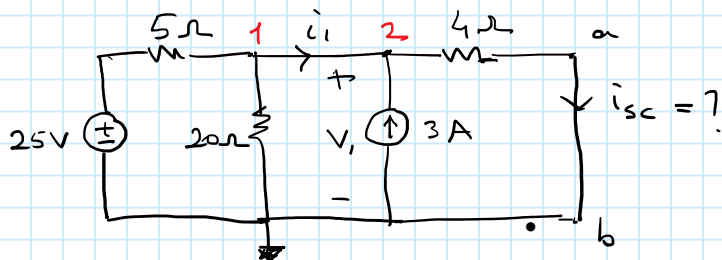


KCL at node 1:

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + i_1 = 0 \quad (1)$$

where $i_1 = -3 + I_{sc}$

P16

16 Ekim 2020 Cuma 11:08

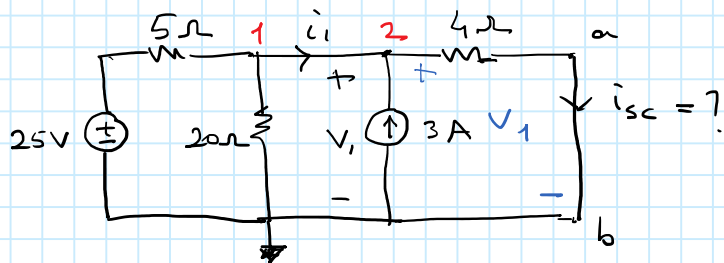

KCL at node 2:

$$-i_1 - 3A + i_{sc} = 0$$

or

$$i_{sc} - i_1 = 3A \quad \text{where } i_{sc} = \frac{V_1}{4} \Rightarrow \frac{V_1}{4} - i_1 = 3 \quad (2)$$

Earlier, we had

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + i_1 = 0 \quad (1)$$


Thus, (1) and (2) can be solved

$$\Rightarrow V_1 = 16V.$$

$$\Rightarrow i_{sc} = \frac{V_1}{4} = \frac{16}{4} = 4A.$$

$$\Rightarrow R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32V}{4A} = 8\Omega.$$

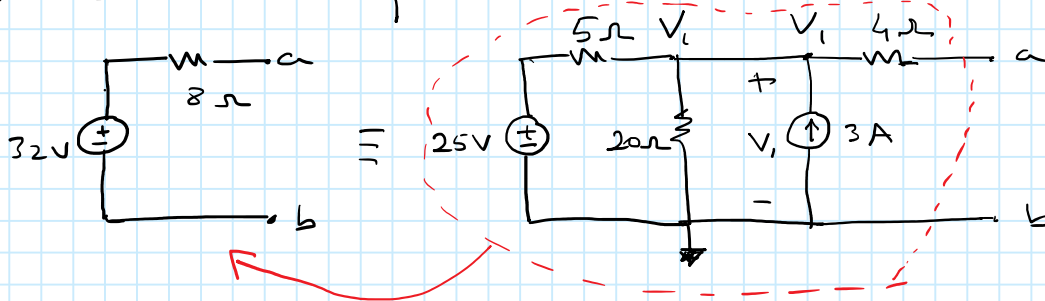
Thus, the Thevenin equivalent circuit is:



In order to obtain the "Norton Equivalent Circuit", we can make "source transformation", where $R_{Th} |_{\text{Thevenin}} = R_{Th} |_{\text{Norton}}$

The current source of Norton circuit is the short circuit current, that is i_{sc} .

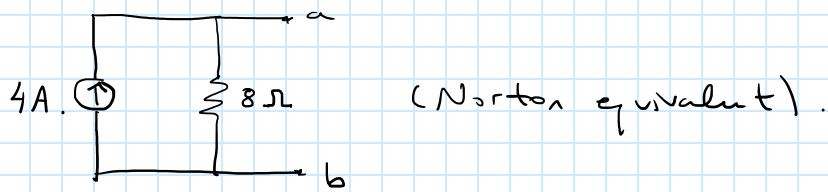Then, for this example, the Norton equivalent circuit is




Alternative technique to find Thévenin equivalent resistance:

If there are only independent sources, to find the Thévenin equivalent circuit:


- Short circuit voltage sources and
- Open circuit current sources.
- Then, evaluate the resistance R_{Th} .

Ex:

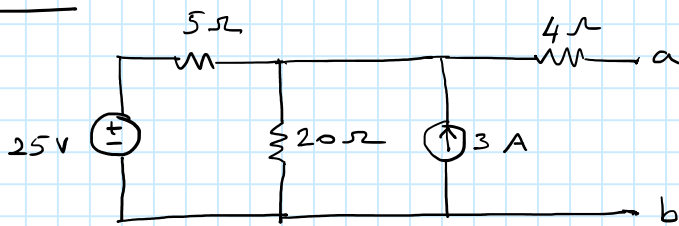

Find $R_{Th} = ?$ w.r.t points a and b.

Ans:

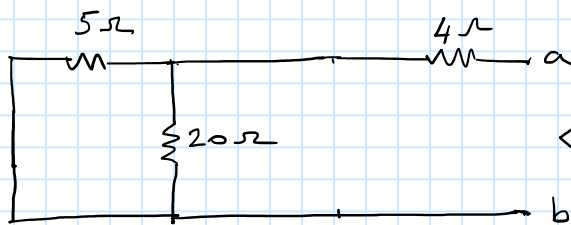

$$\begin{aligned} \Rightarrow R_{Th} &= 4 + (5 \parallel 20) \\ &= 4 + \frac{20 \cdot 5}{20 + 5} = 4 + \frac{20 \cdot 5}{25} \\ &= 4 + 4 = 8 \Omega. \end{aligned}$$


Another alternative technique to find Thévenin resistance:

If the circuit contains dependent sources:

- First, deactivate all indep. sources
(s.c. voltage sources + o.c. current sources)
- Apply a test voltage " V_T " btw terminals a and b.
- $R_{Th} = \frac{V_T}{i_T}$, where i_T is the current passing through V_T .


Ex:

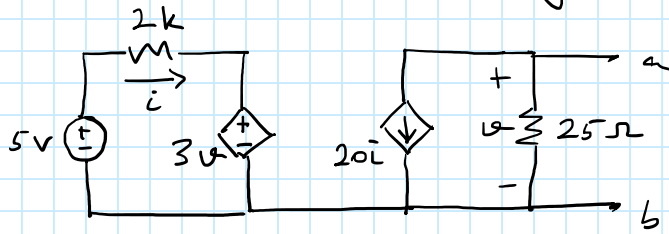Find the Thevenin resistance R_{Th} for the circuit below using the method that was just described.




Ans:

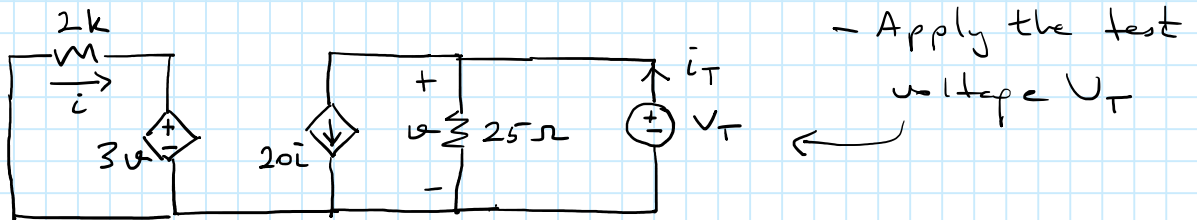— First, we de-activate all indep. sources:



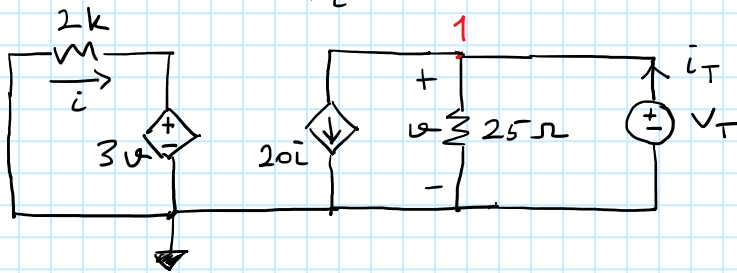— We need to find $\frac{V_T}{i_T} = R_{Th}$. Let us use the node-voltage method:



KCL at node 1:

$$20\bar{i} + \frac{v}{25} = \bar{i}_T \quad (1)$$

where $\bar{i} = \frac{-3v}{2k} = \frac{-3V_T}{2000}$ (since $v = V_T$)

Then,

$$20 \cdot \left(\frac{-3V_T}{2000} \right) + \frac{V_T}{25} = \bar{i}_T \quad (2)$$


Solve equation (2) for $\frac{V_T}{\bar{i}_T}$.

$$\frac{\bar{i}_T}{V_T} = \frac{1}{100} \Rightarrow R_{Th} = \frac{V_T}{\bar{i}_T} = 100\Omega //$$

P19

Friday, October 30, 2020 9:25 AM

- If V_T is asked to be found, then

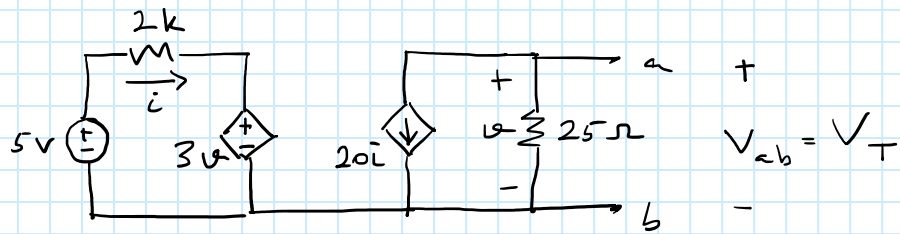

$$\Rightarrow V_{Th} = V_{ab} = (-20i)(25) = -500i \text{ and}$$


from the 1st circuit loop,

$$i = \frac{5 - 3V}{2000} = \frac{5 - 3V_{ab}}{2000} = \frac{5 - 3(-500i)}{2000}$$

$$\Rightarrow 2000i = 5 + 1500i \Rightarrow 500i = 5 \Rightarrow i = 0.01 \text{ A} = 10 \text{ mA}$$


$$\Rightarrow V_{Th} = -500(10 \text{ mA}) = -500(0.01) = -5 \text{ V}$$

Thus, the Thevenin Eq. circuit is:

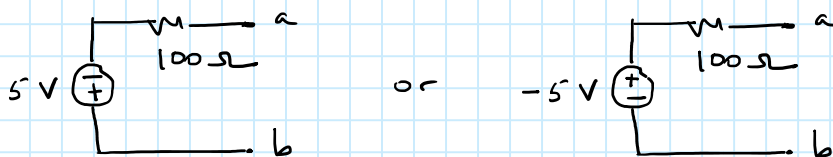

Maximum Power Transfer:

Consider the following circuit:

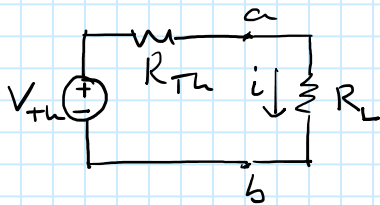

- The power consumed by the resistor R_L is:

$$P_{R_L} = i^2 \cdot R_L \text{ (W)}$$

- We want to find a value for R_L such that P_{R_L} is maximum. This is called "maximum power transfer".

- The power consumed by R_L , P_{R_L} is a function of R_L .

$$\Rightarrow P_{R_L} = P_{R_L}(R_L) = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

$$P_{R_L} = P_{R_L}(R_L) = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

To find the max. $P_{R_L}(R_L)$

$$\frac{dP_{R_L}(R_L)}{dR_L} = 0.$$

$$\Rightarrow 2 \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \left[\frac{-V_{Th}}{(R_{Th} + R_L)^2} \right] R_L + \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 = 0$$

Re-arrange the equation,


$$2 \left(\frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \frac{1}{(R_{Th} + R_L)} \cdot R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2$$

$$2R_L = R_{Th} + R_L$$

$$\Rightarrow \boxed{R_L = R_{Th}} \quad (\text{Condition for max. power transfer}).$$

Ex:


For the given circuit below:

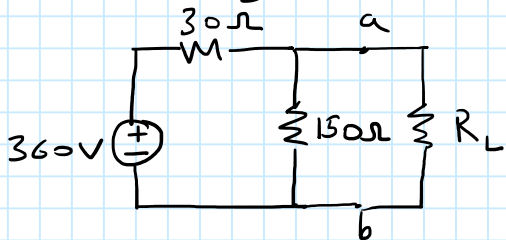


- i) Find R_L for max. power transfer
- ii) Find $P_{R_L} |_{\max}$.

Ans:

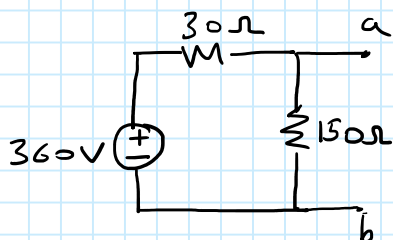- First, we find the Thévenin equivalent circuit for the left side of the terminals a and b.



\equiv Thévenin equivalent = ?

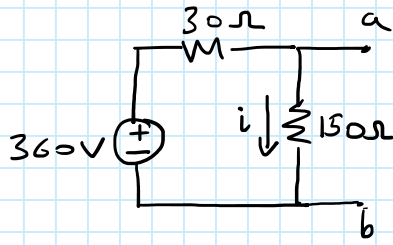

$$i) V_{TH} = 360 \cdot \frac{150}{150+30} = 360 \cdot \frac{150}{180} = 300 \text{ V.}$$

$$R_{TH} = 30\Omega \parallel 150\Omega = \frac{150 \cdot 30}{150+30} = \frac{150 \cdot 30}{180} = 25\Omega.$$


$$R_L = R_{TH} \text{ for max. power transfer} \Rightarrow R_L = 25\Omega.$$

$$ii) P_{R_L} = i^2 \cdot R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L = \left(\frac{300}{25+25} \right)^2 \cdot 25 \Rightarrow P_{R_L} = 900 \text{ W.}$$

Superposition:

Superposition is the concept of "linearity". It means that when a system is fed by more than one independent sources. The total response is sum of individual responses.


Ex:

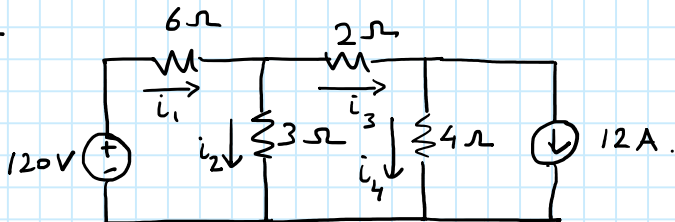

Find \bar{i}_1 , \bar{i}_2 , \bar{i}_3 and \bar{i}_4 by using the superposition.


Ans:

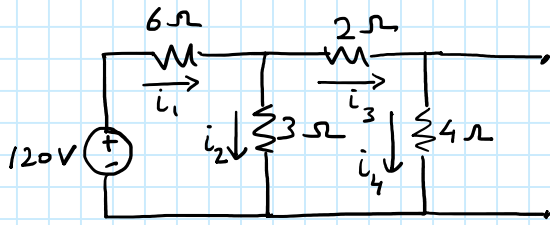- This circuit has 2 indep. sources.
- De-activate one of the sources, and solve the circuit. Then de-activate the other source, and solve the circuit.
- Sum the two solutions from the previous step. Because the resistive circuits with indep. sources are linear.
- Thus, let us first de-activate the 12A source, and find the unknown currents \bar{i}_1 , \bar{i}_2 , \bar{i}_3 and \bar{i}_4 :



$$\begin{aligned} \bar{i}_1' &= 5\text{ A} \\ \bar{i}_2' &= 10\text{ A} \\ \dots \\ \bar{i}_3' &= 5\text{ A} \\ \bar{i}_4' &= 5\text{ A} \end{aligned}$$

Now, de-activate the 1st indep. source:

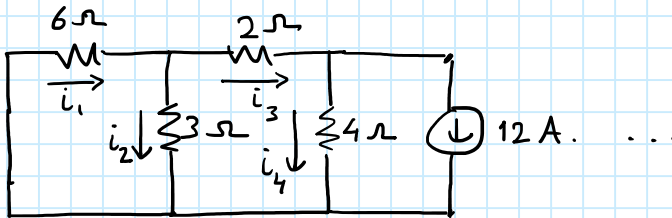

$$\begin{aligned} \bar{i}_1'' &= 2\text{ A} \\ \bar{i}_2'' &= -4\text{ A} \\ \bar{i}_3'' &= 6\text{ A} \\ \bar{i}_4'' &= -6\text{ A} \end{aligned}$$

Therefore, the unknown currents are

$$\bar{i}_1 = \bar{i}_1' + \bar{i}_1'' \Rightarrow \bar{i}_1 = 7\text{ A}$$


$$\bar{i}_2 = \bar{i}_2' + \bar{i}_2'' \Rightarrow \bar{i}_2 = 6\text{ A}$$

$$\bar{i}_3 = \bar{i}_3' + \bar{i}_3'' \Rightarrow \bar{i}_3 = 11\text{ A}$$

$$\bar{i}_4 = \bar{i}_4' + \bar{i}_4'' \Rightarrow \bar{i}_4 = -1\text{ A}$$

Chapter 6: Inductance and Capacitance:

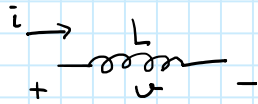- Inductor: It is an electrical element that can be a part of a wire having circular turns.



- The relation among v , i and L is:

$$v = L \cdot \frac{di}{dt}, \quad v = v(t), \quad i = i(t), \quad L$$


$L = \text{Inductance} =$
constant (Henry)

- Conversely

$$i(t) = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0)$$

Ex:

For the given circuit:

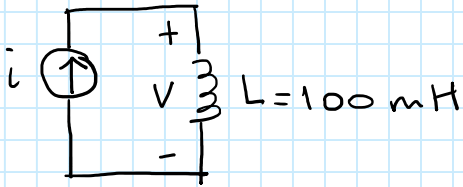

Given that

$$\bar{i} = 0, t < 0$$

and

$$\bar{i}(t) = 10t e^{-5t} \text{ (A)}, t \geq 0$$

Find $V = ?$

Ans:

$$V = L \frac{di}{dt} = (0.1) \cdot \frac{d}{dt} i(t) = (0.1) \frac{d}{dt} [10t e^{-5t}]$$

or

$$V = (0.1) \cdot [10 e^{-5t} + 10t \cdot (-5 e^{-5t})]$$


$$V = (0.1) (10 e^{-5t}) (1 - 5t) = e^{-5t} (1 - 5t) \text{ V}, t \geq 0.$$

and

$$V = 0, t < 0$$

Ex:

For the given circuit:

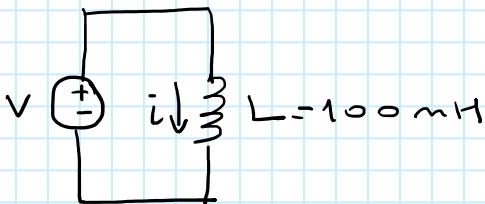

Given:

$$v = 20t e^{-10t} \text{ (V)}, t > 0$$

$$\bar{i} = 0, t \leq 0.$$

Find $i(t), t > 0$.


$$\tau = \text{tau.}$$

$$\tau = \text{tau.}$$

Ans:

$$i(t) = \frac{1}{L} \int_{t_0}^t v \, d\tau + i(t_0) = \frac{1}{0.1} \cdot \int_0^t 20\tau e^{-10\tau} \, d\tau + 0.$$
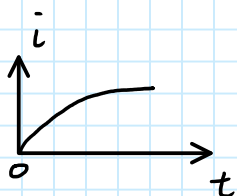
$$\Rightarrow i(t) = 2 (1 - 10t e^{-10t} - e^{-10t}) \text{ (A)}, t > 0.$$



Power and Energy in an Inductor:

- For $p = i \cdot v$, substitute, i and v for an inductor:

$$p = i \cdot L \cdot \frac{di}{dt} = L i \frac{di}{dt} \quad (\text{W})$$

- The energy is


$$p = \frac{dE}{dt} \quad \text{or} \quad \frac{dE}{dt} = L i \frac{di}{dt} \quad \Rightarrow \quad \underbrace{dE}_{\text{differential energy}} = L i \underbrace{di}_{\text{differential current}}$$

Take the integral of both sides:

$$\int_0^E dE = L \int_0^i i di \quad \Rightarrow \quad \int_0^E dE = L \int_0^i i di$$


$$\Rightarrow E = L \cdot \frac{i^2}{2} \quad \Rightarrow \quad \boxed{E = \frac{1}{2} L i^2} \quad (\text{Stored energy inside an inductor.})$$

Capacitor:

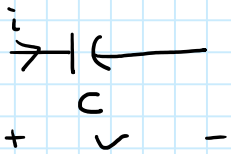

- Capacitor is an electrical element that is made of two conductors separated by an insulator (dielectric).

$C = \text{constant} =$
capacitance

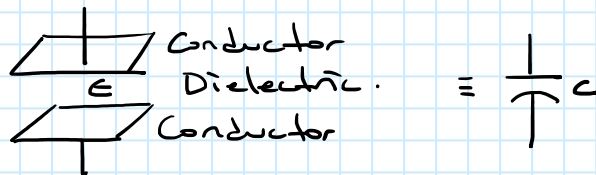

- We have the following circuit relation for a capacitor:

$$\boxed{i = C \cdot \frac{dV}{dt}}$$

Conversely, we have

$$\boxed{V(t) = \frac{1}{C} \int_{t_0}^t i d\tau + V(t_0)}$$

Power and Energy in a Capacitor:

$$p = v \cdot i = C \cdot v \cdot \frac{dv}{dt} \text{ (W)}$$

$$E = \frac{1}{2} C V^2 \text{ (J)}$$

→ $\phi = \Phi = \text{and.}$

Series and Parallel Connection of Inductors & Capacitors:

Series:

For inductors, $L_{eq} = L_1 + L_2 + \dots + L_n$ (n inductors in series)

For capacitors, $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$ (n capacitors in series)


Parallel:

For inductors, $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$

For capacitors, $C_{eq} = C_1 + C_2 + \dots + C_n$

Mutual Inductance:

Consider the following circuit

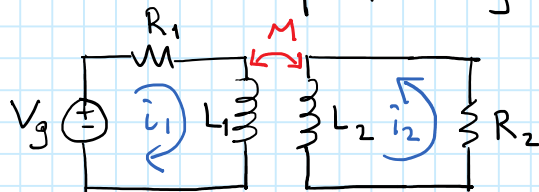


M: Mutual inductance.

Dot Conversion:


When the reference direction for a current enters the dotted terminal, the reference polarity of the voltage that is induced in the other coil is positive at its dotted terminal.

Ex:

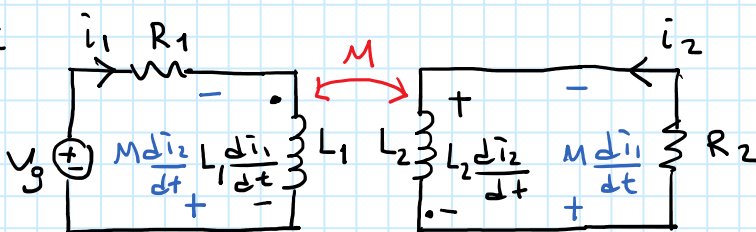

- $M \frac{di_1}{dt}$ and $M \frac{di_2}{dt}$ are mutual induced voltage.

Ex:

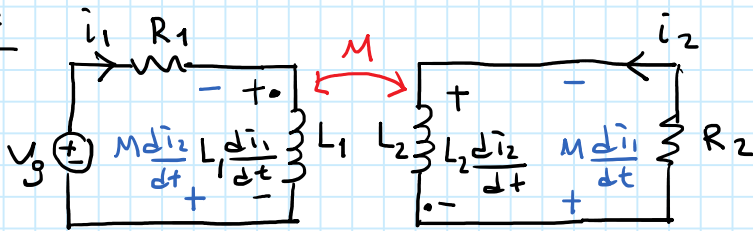

Write KVL equations.

- $M \frac{di_1}{dt}$ and $M \frac{di_2}{dt}$ are

the mutual induced voltage.

- $L_1 \frac{di_1}{dt}$ and $L_2 \frac{di_2}{dt}$ are

the self inductance voltages.

Ans:

In the 1st loop:


$$-V_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0 \quad (1)$$

In the 2nd loop:

$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0 \quad (2)$$

Determining Dot Markings:

Consider the following inductor (toroid):

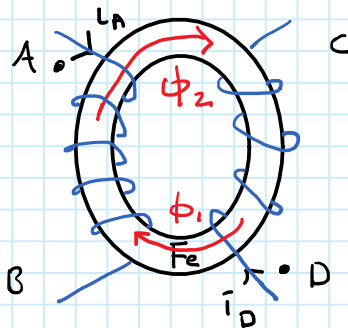Steps:


1-) Arbitrarily select one terminal, and mark it with a dot. (Let's say D)

2-) Assign a current into the dotted terminal (i_D).3-) Determine the magnetic flux by i_D using the "Right hand rule" (ϕ_1).4-) Pick one terminal on the 2nd coil (Let's say A), and assign a current into this terminal (i_A).5-) Find ϕ_2 by i_A .6-) If ϕ_1 and ϕ_2 are in the same direction, then put a dot on the selected terminal (in this case, terminal A).

If not, put a dot on the opposite terminal (terminal B).


Ex:

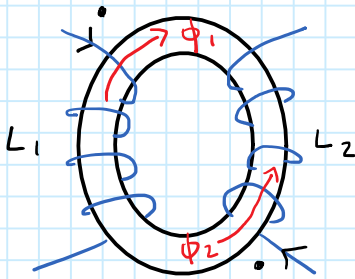For the given toroidal inductor find the dot convention.



Ex:

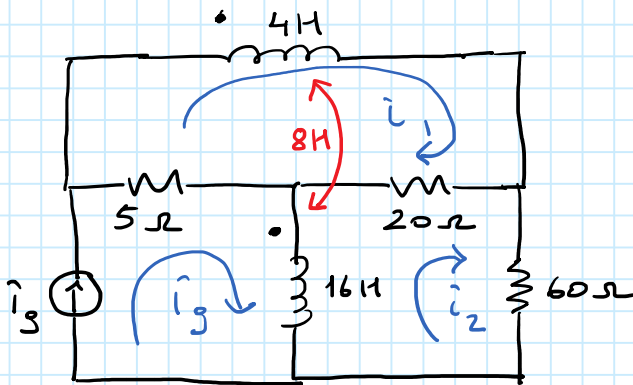For the given circuit, write the equations for the mesh currents i_1 and i_2 .



Ans:

For mesh 1:

$$4 \frac{di_1}{dt} + 8 \frac{d(i_1 - i_2)}{dt} + 20(i_1 - i_2) + 5(i_1 - i_3) = 0 \quad \text{--- (1)}$$


For mesh 2:

$$20(i_2 - i_1) + 60i_2 + 16 \frac{d(i_2 - i_3)}{dt} - 8 \frac{di_1}{dt} = 0 \quad \text{--- (2)}$$

mutual induced voltage.
self induced voltage

Sample Questions:

1-)

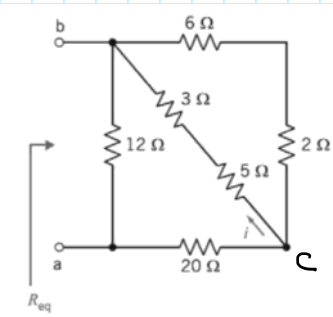


Find i and R_{eq} if $V_{ab} = 40V$

Ans:

$$R_{eq} = 12 \parallel \left\{ 20 + \left[\underbrace{(5+3)}_8 \parallel \underbrace{(6+2)}_8 \right] \right\}$$


$$\underbrace{\hspace{10em}}_4$$

$$\underbrace{\hspace{15em}}_{24}$$

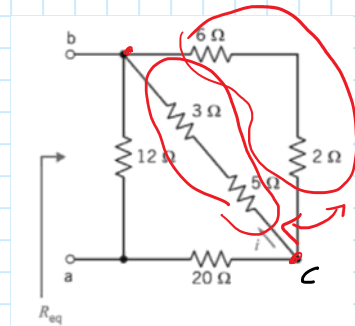

$$\Rightarrow R_{eq} = 12 \parallel 24 = \frac{12 \cdot 24}{12 + 24} = \frac{12 \cdot 24}{36} = 8 \Omega$$

To find i ,

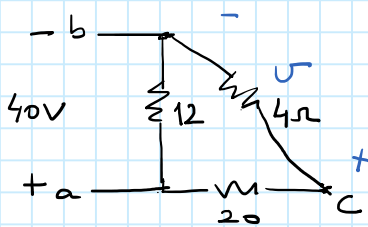

$$V_{ab} = V_a - V_b$$

$$V_{cb} = 40 \cdot \frac{4}{20+4}$$

$$\Rightarrow V_{cb} = 40 \cdot \frac{4}{6 \cdot \frac{4}{4}} = \frac{40}{6}$$

Then,

$$i = \frac{V_{cb}}{R} = \frac{40/6}{8} = \frac{40}{6} \cdot \frac{1}{8} = \frac{5}{6} A$$

2-)

For the circuit in Fig.2, if the power delivered by the source is 20 mW, find R and V_s .

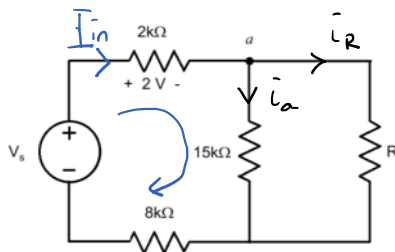


Figure 2: Circuit for question 2.

$$I_{in} = \frac{2V}{2k} = 1 mA$$

$$P_{Vs} = 20mW = I_{in} \cdot V_s$$

$$\Rightarrow V_s = \frac{20mW}{1mA} = 20V$$

KVL in the left loop: $-20 + 2 + i_a \cdot (15k) + i_{in} (8k) = 0$

P29

Saturday, October 31, 2020 9:50 AM

KVL in the left loop: $-20 + 2 + \bar{i}_a \cdot (15k) + \bar{i}_a (8k) = 0$

or $\bar{i}_a (15k) + (1mA)(8k) = 18$

$$\bar{i}_a = \frac{10}{15k} = \frac{10}{15} mA = \frac{2}{3} mA.$$

KCL at node a:

$$-I_{in} + \bar{i}_a + \bar{i}_R = 0$$

$$1 mA + \frac{2}{3} mA + \bar{i}_R = 0$$

$$\Rightarrow \bar{i}_R = (1 - \frac{2}{3}) mA = \frac{1}{3} mA.$$

Also, $V_a = \bar{i}_a \cdot (15k)$

$$\Rightarrow R = \frac{V_a}{\bar{i}_R} = \frac{\frac{2}{3} mA (15k)}{\frac{1}{3} mA} = \frac{10}{1} k = 10k.$$

3-)

Find the voltage v_a in Fig.3 by

- a-) Node-voltage analysis
- b-) Source transformation.

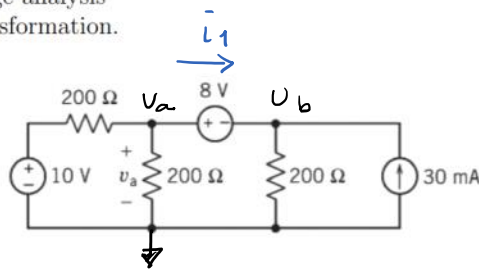


Figure 3: Circuit for question 3.

a-) KCL at node a:

$$\frac{V_a - 10}{200} + \frac{V_a}{200} + i_1 = 0 \quad (1)$$

KCL at node b:

$$-i_1 + \frac{V_b}{200} - 30mA = 0 \quad (2)$$

$$V_a - V_b = 8 \quad (3)$$

Add (1) and (2):

$$\frac{V_a - 10}{200} + \frac{V_a}{200} + \frac{V_b}{200} = 30mA.$$

$$V_a - 10 + V_a + V_b = (2/200)(30mA) = 6$$

$$2V_a + V_b = 16 \quad (4)$$







Add (3) and (4):


$$V_a - V_b = 8$$

$$+ 2V_a + V_b = 16$$

$$3V_a = 24 \Rightarrow \boxed{V_a = 8V}$$

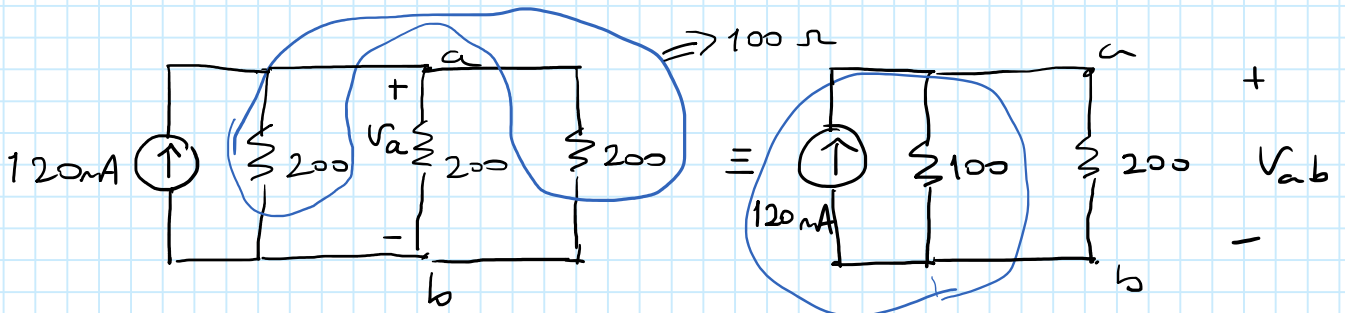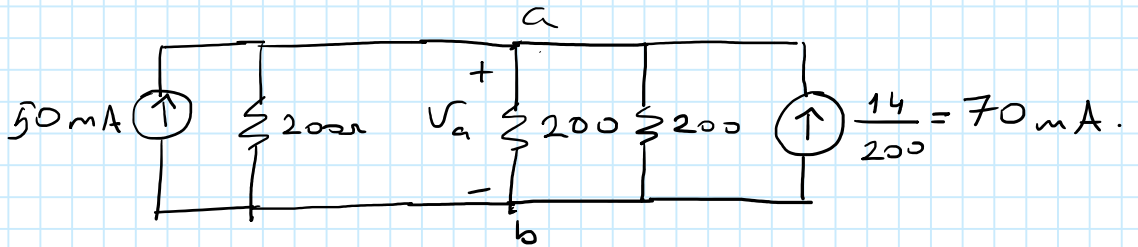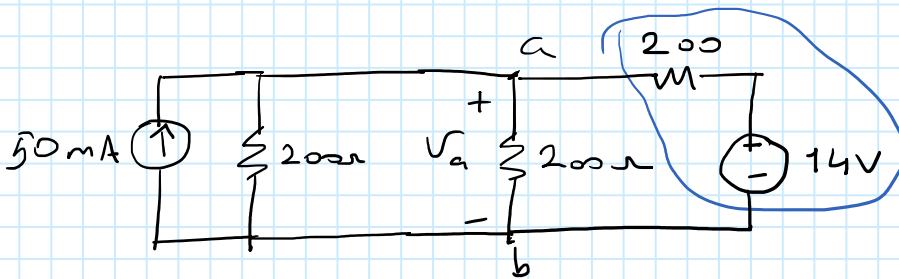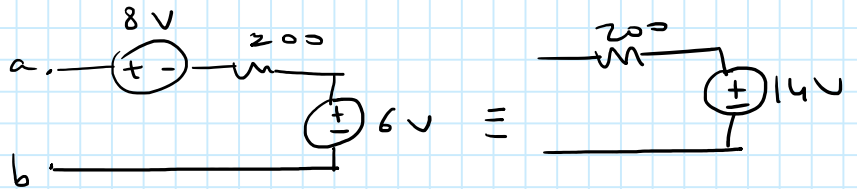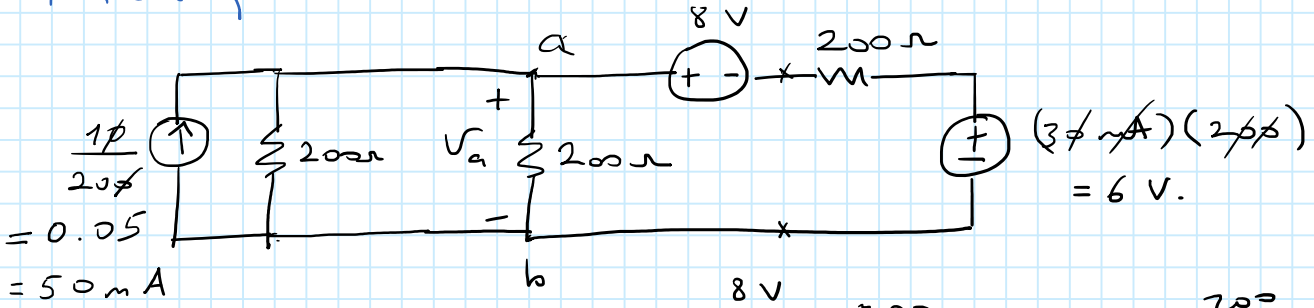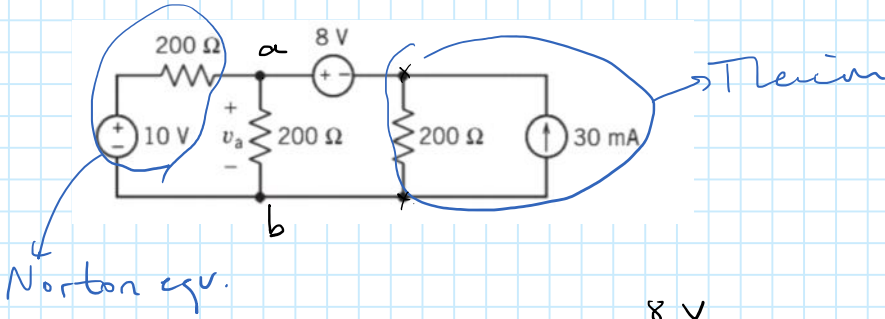b-) Source transformation = Thévenin \rightarrow Norton \rightarrow Thévenin ...



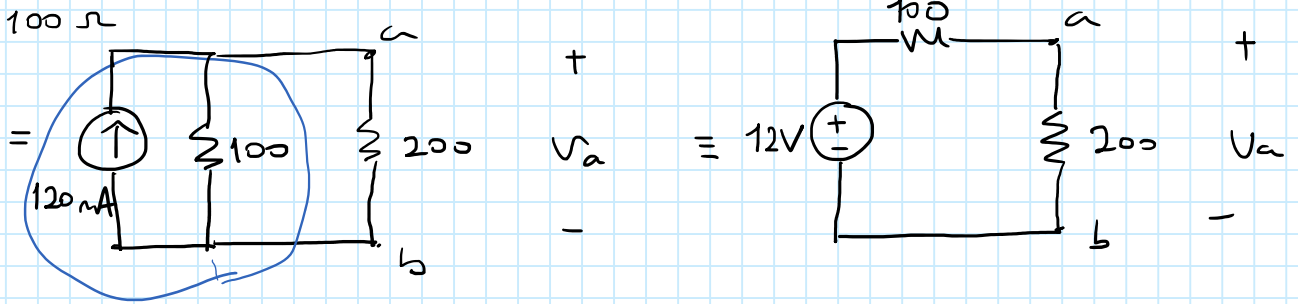

$$V_a = 12 \cdot \frac{200}{200+100} = 12 \cdot \frac{2}{3} = 8V.$$

4-)

- a-) Calculate the value of R for maximum power.
- b-) Determine the maximum power absorbed by R.


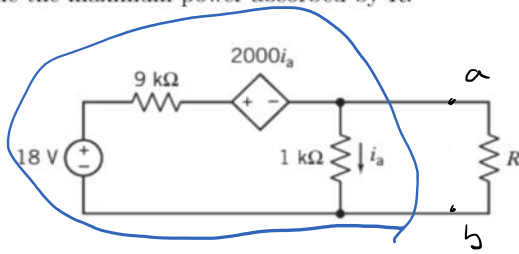
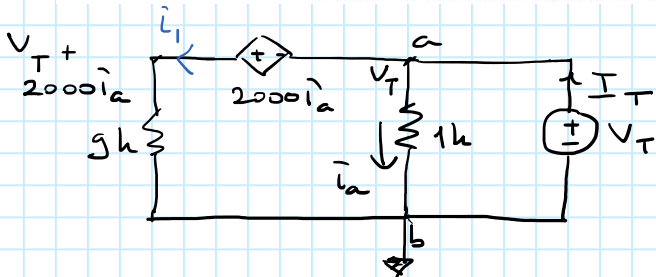


Figure 4: Circuit for question 4.

- Thevenin btw. a and b :

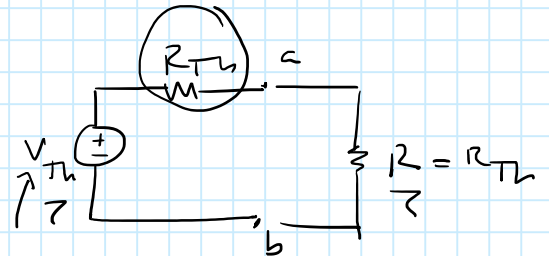

$$R_{Th} = \frac{V_T}{I_T}$$

KCL at node a:

$$i_1 + i_a - I_T = 0 \quad (1)$$

$$i_a = \frac{V_T}{1k} \quad (2)$$

Substitute (2) in (1)

$$i_1 + \frac{V_T}{1k} - I_T = 0 \quad (3)$$

$$\frac{V_T + 2000i_a}{9k} + \frac{V_T}{1k} = I_T$$

$$\frac{V_T + 2000 \cdot \left(\frac{V_T}{1k}\right)}{9k} + \frac{V_T}{1k} = I_T$$

$$\frac{3V_T}{9k} + \frac{V_T}{1k} = I_T$$


$$\frac{3V_T + 9V_T}{9k} = I_T$$

$$\frac{12V_T}{9k} = I_T$$

$$\Rightarrow \frac{V_T}{I_T} = \frac{9000}{12} = 750\Omega = R_{Th}$$

$$R = R_{Th} = 750\Omega$$

To find V_{Th} :

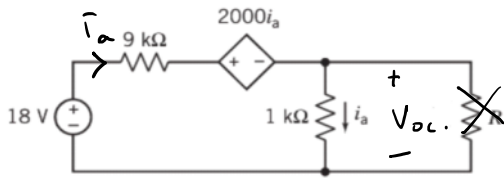

$$V_{Th} = V_{oc}$$

KVL for the mesh:


$$-18 + i_a(9k) + 2000i_a + i_a(1k) = 0$$

$$12000i_a = 18$$

$$i_a = \frac{18}{12000} \text{ A}$$

$$\Rightarrow V_{Th} = V_{oc} = i_a \cdot 1k = \frac{18}{12000} (1k) = \frac{18}{12} \text{ V} = \frac{3}{2} \text{ V}$$

b.)

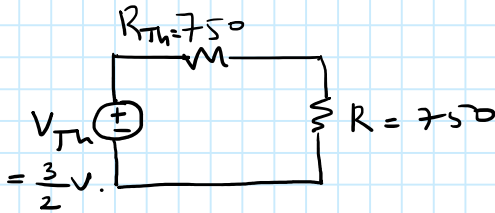

$$P_R |_{\max} \quad (R = 750\Omega)$$

$$P_R |_{\max} = i^2 \cdot R = \left(\frac{V_{Th}}{2R_{Th}} \right)^2 R_{Th}$$


$$= \frac{V_{Th}^2}{4R_{Th}} \cdot R_{Th}$$

$$\Rightarrow \boxed{P_R |_{\max} = \frac{V_{Th}^2}{4R_{Th}}}$$

$$\Rightarrow P_R |_{\max} = \frac{(3/2)^2}{4 \cdot 750} = \frac{9/4}{4 \cdot 750} = \frac{9}{4} \cdot \frac{1}{4 \cdot 750} = \frac{9}{12000} = \frac{3}{4000} \text{ mW} = 0.75 \text{ mW} = 750 \mu\text{W}$$

5-)

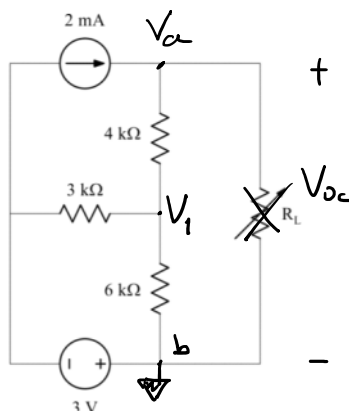- a-) Calculate the value of R_L for maximum power.
- b-) Determine the maximum power absorbed by R_L .



To find V_{oc} :

Node-voltage method:

KCL at node a:


$$-2\text{mA} + \frac{U_a - U_1}{4k} = 0$$

$$\Rightarrow \frac{U_a - U_1}{4k} = 2\text{mA}$$

or

$$U_a - U_1 = 8 \quad (1)$$

Figure 5: Circuit for question 5.

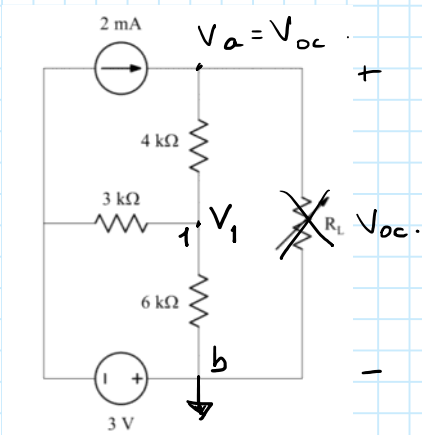

$$U_a - U_1 = 8 \quad (1)$$

KCL at node 1:

$$\frac{U_1 - U_a}{4k} + \frac{U_1 - (-3V)}{3k} + \frac{U_1}{6k} = 0$$

(3) (4) (2)

$$3U_1 - 3U_a + 4U_1 + 12 + 2U_1 = 0$$

$$9U_1 - 3U_a = -12$$

or

$$3U_a - 9U_1 = 12$$

$$U_a - 3U_1 = 4 \quad (2)$$

Solve (1) and (2):


$$U_a - U_1 = 8$$

$$-U_a + 3U_1 = -4$$

$$2U_1 = 4 \Rightarrow U_1 = 2, U_a = 10V.$$

$$\Rightarrow U_{Th} = 10V.$$

R_{Th} :

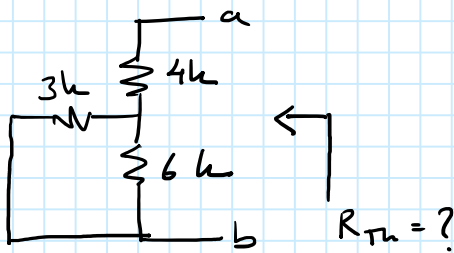

$$\Rightarrow R_{Th} = 4k + (3k \parallel 6k) = 6k \Omega$$

b-)

$$P_R \Big|_{max} = \frac{U_{Th}^2}{4R_{Th}}$$

$$\Rightarrow P_R = \frac{(10)^2}{4 \cdot 6000} = \frac{100}{2400} = \frac{1}{24} W \approx 4.2 mW.$$

b-)

Find V_0 , P_{40V} and $P_{5\Omega}$ for the circuit in Fig.1.

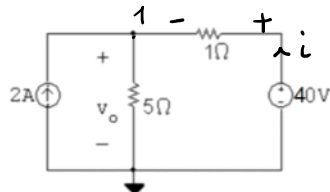


Figure 1: Circuit for question 1.

KCL at node 1:

$$-2 + \frac{V_0}{5} + \frac{V_0 - 40}{1} = 0$$

$$\frac{V_0}{5} + V_0 = 42$$

$$\frac{6V_0}{5} = 42 \Rightarrow V_0 = \frac{42 \cdot 5}{6} = 35V$$

$$P_{40V} = -i \cdot V = -i(40) \Rightarrow i = \frac{40 - V_0}{1} = 40 - 35 = 5A.$$

$$\Rightarrow P_{40V} = -(5A)(40V) = -200W, \quad P_{5\Omega} = \frac{V_0^2}{R} = \frac{35^2}{5} = \frac{7}{8} \cdot 35 = 245W.$$

P34

Saturday, October 31, 2020 11:52 AM

7-)

Find v_1 and v_2 for the circuit in Fig.2.

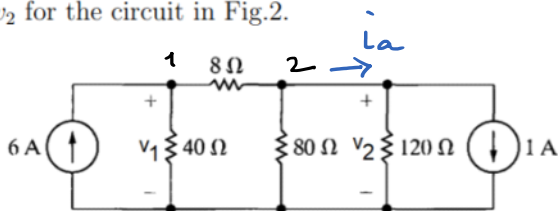


Figure 2: Circuit for question 2.

KCL at node 1:

$$-6 + \frac{v_1}{40} + \frac{v_1 - v_2}{8} = 0 \quad (1)$$

KCL at node 2:

$$\frac{v_2 - v_1}{8} + \frac{v_2}{80} + i_a = 0 \quad (2)$$

$$\text{Also, } i_a = \frac{v_2}{120} + 1 \quad (3)$$

Substitute (3) in (2):

$$\frac{v_2 - v_1}{8} + \frac{v_2}{80} + \frac{v_2}{120} + 1 = 0 \quad (4)$$

Solve (1) and (4) simultaneously:

$$\frac{v_1}{40} + \frac{v_1 - v_2}{8} = 6 \quad (1)$$

$$v_1 + 5v_1 - 5v_2 = 6 \cdot 40 = 240 \quad (1) \quad *$$

$$\frac{v_2 - v_1}{8} + \frac{v_2}{80} + \frac{v_2}{120} = -1 \quad (4)$$

$$30v_2 - 30v_1 + 3v_2 + 2v_2 = -240 \quad (4)$$

$$35v_2 - 30v_1 = -240$$

$$7v_2 - 6v_1 = -48 \quad (4) \quad *$$

$$+ 6v_1 - 5v_2 = 240 \quad (1)$$


$$7v_2 - 5v_2 = 240 - 48$$

$$2v_2 = 192 \Rightarrow v_2 = 96 \text{ V.}$$

$$6v_1 = 240 + 5(96) \Rightarrow v_1 = \frac{240 + 5(96)}{6} = 120 \text{ V.}$$


Ex:

For the circuit below,

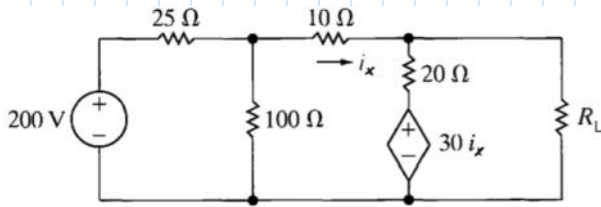

Find R_L for maximum power transfer. Find P_{R_L} at max. power.




Ans:

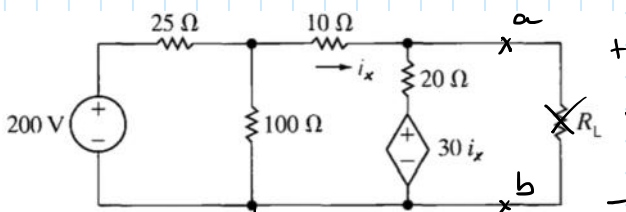

We find the Thevenin circuit wrt. a and b.

$V_{o.c} = ?$

Source Transformation

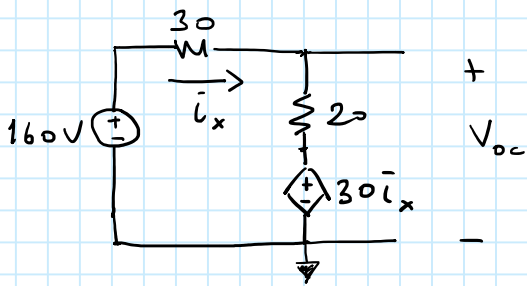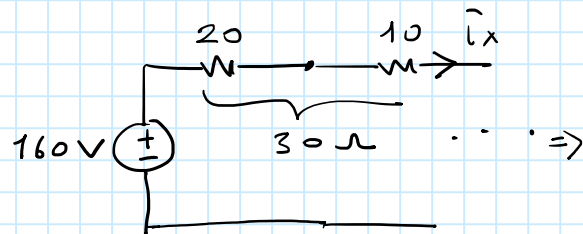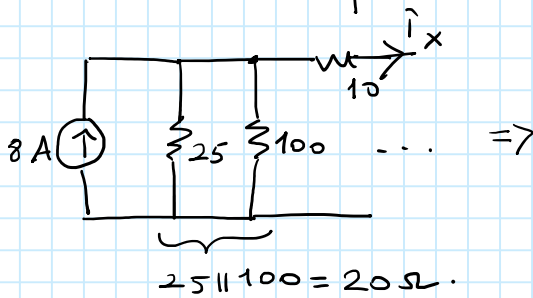

Mesh Equation (KVL) for mesh 1:

$$-160 + 30\hat{i}_x + V_{oc} = 0 \quad (1)$$

Ohm's law across 20Ω resistor:

$$V_{oc} - 30\hat{i}_x = 20\hat{i}_x \quad (2)$$

$$\hookrightarrow \hat{i}_x = \frac{V_{oc}}{50}$$

Substitute \hat{i}_x into (1),


$$30\left(\frac{V_{oc}}{50}\right) + V_{oc} = 160 \Rightarrow \frac{3V_{oc}}{5} + V_{oc} = 160 \Rightarrow \frac{8V_{oc}}{5} = 160$$

$$\Rightarrow V_{oc} = \frac{5 \cdot 160}{8} = 100 = V_{Th}$$

→ To find R_{Th} , we can use the test voltage, V_T , method:

P36

Friday, November 6, 2020 9:16 AM

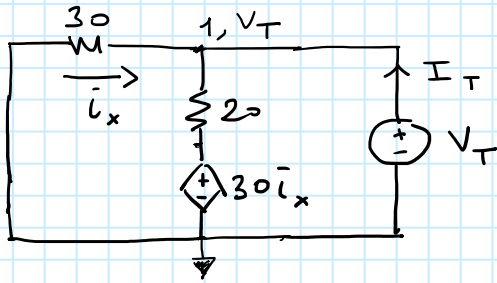

KCL at node 1:

$$-i_x + \frac{V_T - 30i_x}{20} - I_T = 0 \quad (1)$$

Ohm's law across 30 ohm resistor:

$$30i_x = -V_T \quad (2)$$

$$\Rightarrow i_x = \frac{-V_T}{30}$$

Substitute i_x in (1):

$$\frac{V_T}{30} + \frac{V_T - 30\left(\frac{-V_T}{30}\right)}{20} = I_T \Rightarrow \frac{V_T}{30} + \frac{V_T}{10} = I_T \Rightarrow$$


$$\frac{4V_T}{30} = I_T \Rightarrow R_{Th} = \frac{V_T}{I_T} = \frac{30}{4} = 7.5 \Omega.$$

To find P_{RL} :

$$P_{RL} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(100)^2}{4(7.5)} \approx 333 \text{ W.}$$


Ex:

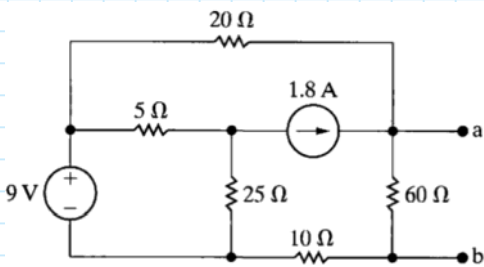For the circuit below, find the Thevenin circuit wrt. a-b.



Ans:

To find V_{Th} :

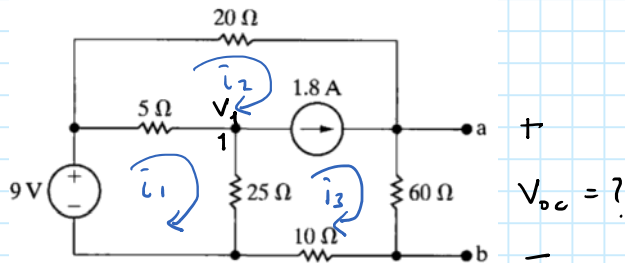

KVL for mesh 1:

$$-9 + 5(i_1 - i_2) + 25(i_1 - i_3) = 0 \quad (1)$$


KVL for mesh 2:

$$20i_2 + (V_{oc} - V_1) + 5(i_2 - i_1) = 0$$

\Rightarrow 5 unknown already \Rightarrow Let us not use "Mesh-current" method.

P37

Friday, November 6, 2020 10:02 AM

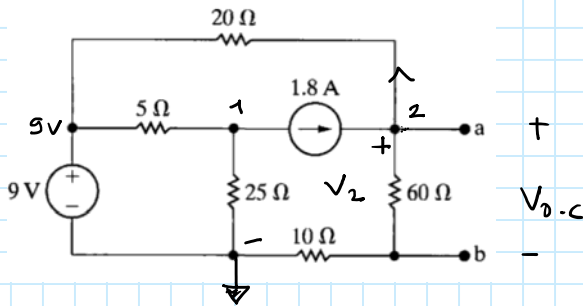

KCL at node 2:

$$\frac{V_2 - 9}{20} - 1.8 + \frac{V_2}{70} = 0$$


$$\frac{V_2 - 9}{20} + \frac{V_2}{70} = 1.8$$

$$\vdots$$

$$\Rightarrow V_2 = 35V.$$

$$\Rightarrow V_{Th} = V_{oc} = 35 \cdot \frac{60}{60 + 10} \text{ (Voltage division)} = 30V.$$

To find R_{Th} :

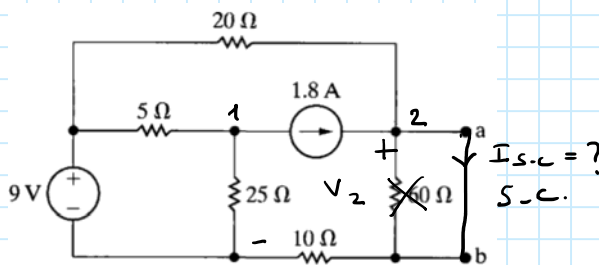

KCL at node 2:

$$\frac{V_2 - 9}{20} - 1.8 + \frac{V_2}{10} = 0$$



$$\Rightarrow V_2 = 15V.$$

Using Ohm's law across 10Ω:

$$\Rightarrow I_{sc} = \frac{V_2}{10} = 1.5A.$$

$$\Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{30}{1.5} = \frac{30}{\frac{3}{2}} = 20\Omega.$$

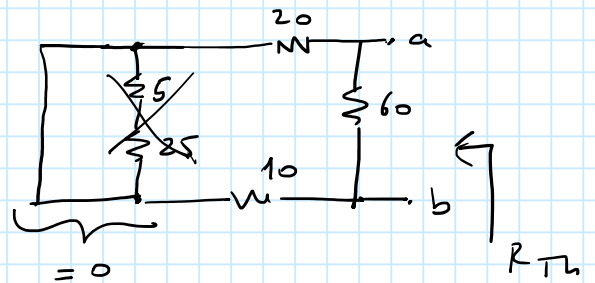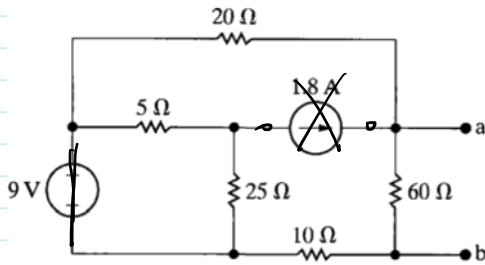Alternatively, we could use the de-activation technique:




$$\Rightarrow R_{Th} = (20 + 10) \parallel 60 = 30 \parallel 60$$


$$= \frac{30 \cdot 60}{90} = 20\Omega //$$

Ex:

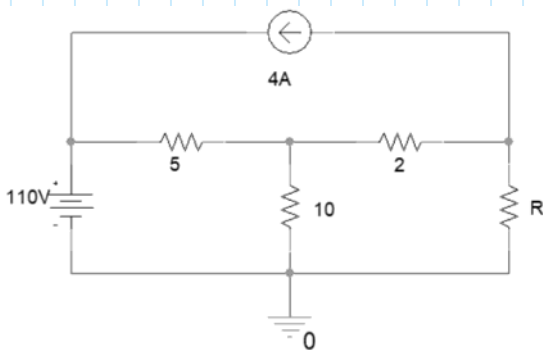For the circuit given below, find R for max. power transfer and $P_{RL} = ?$




Ans:

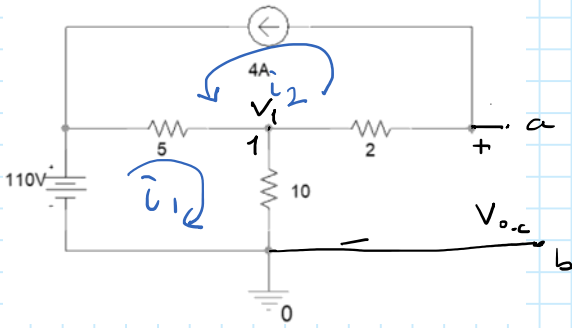

$$\Rightarrow V_{o.c} = 60 - 8 = 52V.$$

$$\Rightarrow V_{Th} = 52V.$$

To find R_{Th} :

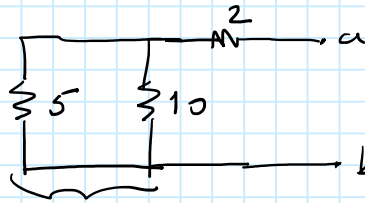

KVL in mesh 1:

$$-110 + 5(\hat{i}_1 + 4) + 10\hat{i}_1 = 0 \quad \text{--- (1)}$$

$$15\hat{i}_1 = 110 - 20 = 90$$

$$\Rightarrow \hat{i}_1 = 6A.$$

Ohm's law across 10Ω resistor:

$$V_1 = \hat{i}_1 \cdot 10 = 6 \cdot 10 = 60V$$

Ohm's law across 2Ω resistor:

$$V_1 - V_{o.c} = 2(4) = 8V.$$


$$\downarrow$$

$$60$$

$$R_{Th} = 2 + (5 \parallel 10) \approx 5.3 \Omega.$$

Ex:

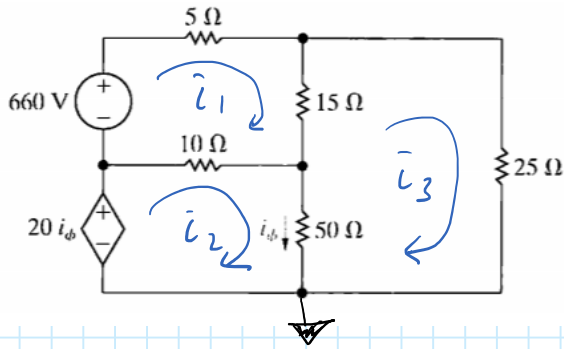Given the circuit below, find the power delivered by the dependent source:



Ans:

KVL in mesh 1:

$$-660 + 5\hat{i}_1 + 15(\hat{i}_1 - \hat{i}_3) + 10(\hat{i}_1 - \hat{i}_2) = 0$$

$$\Rightarrow 30\hat{i}_1 - 10\hat{i}_2 - 15\hat{i}_3 = 660 \quad \text{--- (1)}$$

KVL in mesh 2:

$$-20\hat{i}_\phi + 10(\hat{i}_2 - \hat{i}_1) + 50(\hat{i}_2 - \hat{i}_3) = 0$$

$$\text{Also, } \hat{i}_\phi = \hat{i}_2 - \hat{i}_3$$

$$\text{or } -10\hat{i}_1 + 60\hat{i}_2 - 50\hat{i}_3 = 20\hat{i}_\phi = 20\hat{i}_2 - 20\hat{i}_3$$

$$\text{or } -10\hat{i}_1 + 40\hat{i}_2 - 30\hat{i}_3 = 0 \quad \text{--- (2)}$$

KVL in mesh 3:

$$50(\hat{i}_3 - \hat{i}_2) + 15(\hat{i}_3 - \hat{i}_1) + 25\hat{i}_3 = 0$$

$$-15\hat{i}_1 - 50\hat{i}_2 + 50\hat{i}_3 = 0 \quad \text{--- (3)}$$

Let us solve (1), (2) and (3) simultaneously,

P39

Friday, November 6, 2020 10:58 AM

$$30\hat{i}_1 - 10\hat{i}_2 - 15\hat{i}_3 = 660$$

or

$$6\hat{i}_1 - 2\hat{i}_2 - 3\hat{i}_3 = 132 \quad \text{--- (1)}$$

Similarly, eqn (2) also simplifies

$$-10\hat{i}_1 + 40\hat{i}_2 - 30\hat{i}_3 = 0$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\hat{i}_3 = 0 \quad \text{--- (2)}$$

Also, eqn (3) can be re-written as

$$-15\hat{i}_1 - 50\hat{i}_2 + 50\hat{i}_3 = 0$$

$$3\hat{i}_1 + 10\hat{i}_2 - 18\hat{i}_3 = 0 \quad \text{--- (3)}$$

$$6\hat{i}_1 - 2\hat{i}_2 - 3\hat{i}_3 = 132 \quad \text{--- (1)}$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\hat{i}_3 = 0 \quad \text{--- (2)}$$

$$3\hat{i}_1 + 10\hat{i}_2 - 18\hat{i}_3 = 0 \quad \text{--- (3)}$$

$$\left. \begin{array}{l} (1) \\ (2) \\ (3) \end{array} \right\} \begin{bmatrix} 6 & -2 & -3 \\ 1 & -4 & 3 \\ 3 & 10 & -18 \end{bmatrix} \begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \\ \hat{i}_3 \end{bmatrix} = \begin{bmatrix} 132 \\ 0 \\ 0 \end{bmatrix}$$

$$A \cdot \hat{i} = b$$

$$\hat{i} = A^{-1} \cdot b$$

Solve \hat{i}_1 from (2)

$$\hat{i}_1 = 4\hat{i}_2 - 3\hat{i}_3 \quad \text{--- (4)}$$

Substitute (4) into (3):

$$3(4\hat{i}_2 - 3\hat{i}_3) + 10\hat{i}_2 - 18\hat{i}_3 = 0$$

or

$$12\hat{i}_2 - 9\hat{i}_3 + 10\hat{i}_2 - 18\hat{i}_3 = 0$$

or

$$22\hat{i}_2 = 27\hat{i}_3 \Rightarrow \hat{i}_3 = \frac{22}{27}\hat{i}_2 \quad \text{--- (5)}$$

Substitute (5) in (1) and (2)

$$6\hat{i}_1 - 2\hat{i}_2 - 3\left(\frac{22}{27}\hat{i}_2\right) = 132 \quad \text{--- (1)} \Rightarrow 6\hat{i}_1 - 2\hat{i}_2 - \frac{22}{9}\hat{i}_2 = 132 \quad \text{--- (1)}$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\left(\frac{22}{27}\hat{i}_2\right) = 0 \quad \text{--- (2)} \Rightarrow \left(\hat{i}_1 - 4\hat{i}_2 + \frac{22}{9}\hat{i}_2\right) = (0) \cdot (-6) \quad \text{--- (2)}$$

Add (6) and (7)

$$22\hat{i}_2 - \frac{22}{9}\hat{i}_2 - \frac{6 \cdot 22}{9}\hat{i}_2 = 132$$

$$22\hat{i}_2 \left(1 - \frac{1}{9} - \frac{6}{9} \right) = 132$$

(3) (1) (3)

$$= -6\hat{i}_1 + 24\hat{i}_2 - \frac{6 \cdot 22}{9}\hat{i}_2 = 0 \quad \text{--- (7)}$$

$$\Rightarrow 22\hat{i}_2 \left(\frac{9-1-6}{9} \right) = 132 \Rightarrow \hat{i}_2 = \frac{132 \cdot 9}{22 \cdot 2} = 27 \text{ A} \Rightarrow \hat{i}_1 = 42 \text{ A}, \hat{i}_3 = 22 \text{ A}$$

$$\Rightarrow \hat{i}_\phi = 5 \text{ A} \Rightarrow 20\hat{i}_\phi = 100 \text{ V}$$


$$P_{20\hat{i}_\phi} = -\hat{i} \cdot V = -100 \hat{i}_2 = -100 \cdot 27 = -2.7 \text{ kW}$$

or

$$P_{20\hat{i}_\phi} = 2.7 \text{ kW delivered power}$$

↓
(- power)

Ex:

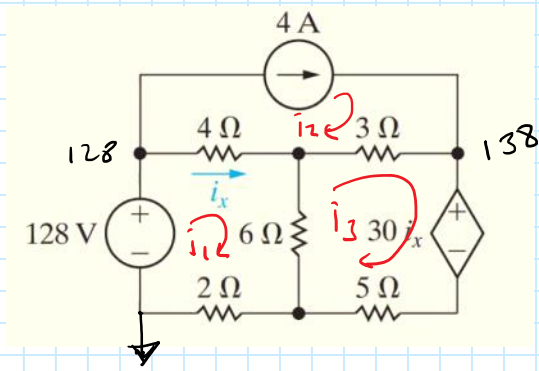

KVL for mesh 1:

$$-128 + 4i_x + 6(i_1 - i_3) + 2i_1 = 0 \quad (1)$$

KVL for mesh 2:

$$(128 - V_1) + 3(i_2 - i_3) + 4(i_2 - i_1) = 0 \quad (2)$$

KVL for mesh 3:

$$6(i_3 - i_1) + 3(i_3 - i_2) + 30i_x + 5i_3 = 0$$

$$i_2 = 4$$

$$i_x = i_1 - 4$$

$$4(i_1 - 4) + 6i_1 - 6i_3 + 2i_1 = 128$$

$$12i_1 - 6i_3 = 144 \quad (1)$$

$$128 - V_1 + 12 - 3i_3 + 16 - 4i_1 = 0$$

$$-4i_1 - 3i_3 - V_1 = -156 \quad (2)$$


$$6i_3 - 6i_1 + 3i_3 - 12 + 30(i_1 - 4) + 5i_3 = 0$$

$$24i_1 + 14i_3 = 132 \quad (3)$$

$$\begin{bmatrix} 12 & -6 & 0 \\ +4 & +3 & +1 \\ 24 & 14 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \\ V_1 \end{bmatrix} = \begin{bmatrix} 144 \\ 156 \\ 132 \end{bmatrix}$$

$$i_1 = 9, i_2 = -6, V_1 = 138$$

Ex!

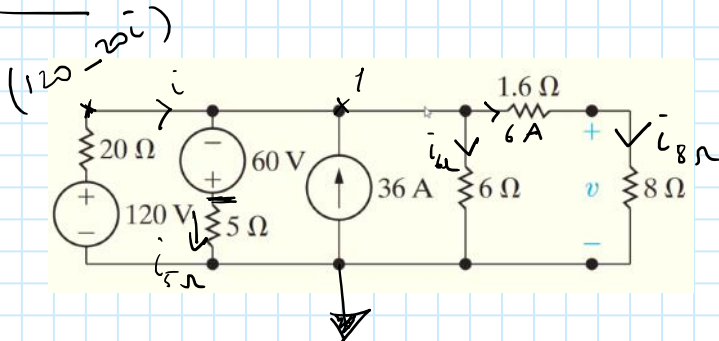

$$V = 48V$$


$$P_{120} = 374.4W$$

$$i_{8\Omega} = \frac{V}{R} = \frac{48}{8} = 6A \quad \checkmark$$

$$i_{6A} = \frac{120 - 20i}{6} = 20 - \frac{10}{3}i \quad \checkmark$$

$$i_{5\Omega} = \frac{180 - 20i}{5} = 36 - 4i$$

KCL at node 1:

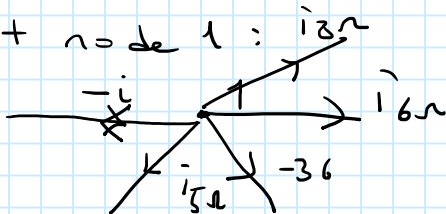

$$-i + i_{5\Omega} + i_{6A} + i_{8\Omega} - 36 = 0$$

$$-i + 36 - 4i + 20 - \frac{10}{3}i + 6 - 36 = 0$$

$$-5i - \frac{10}{3}i = -26$$

$$i(5 + \frac{10}{3}) = 26$$

$$i = \frac{26}{\frac{25}{3}} = \frac{26 \cdot 3}{25} A$$

$$P_{120V} = 120 \cdot \frac{26 \cdot 3}{25} = 374.4W$$


- RL & RC Circuits -

P41

Tuesday, November 10, 2020 4:35 PM

Natural Response of an RL-Circuit: (Discharging the current of the inductor)

Consider the following circuit:

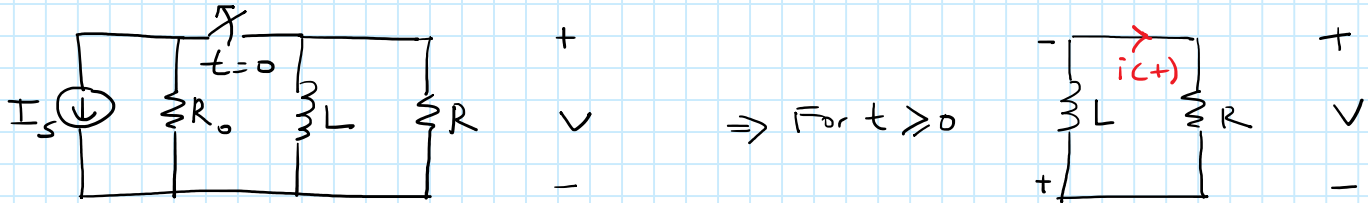

Norton circuit is used to charge L for $t < 0$

Assume that $L \frac{di}{dt} = 0$, $t < 0$ (the inductor is a short circuit before the release of the switch.)

\Rightarrow For $t < 0$, currents in R_0 and $R = 0$.
 All current flows through the L .
 For $t = 0$, the inductor begins to release its energy.
 For $t \geq 0$, the KVL equation for $i(t)$ is:


$$\boxed{L \frac{di(t)}{dt} + Ri(t) = 0} \quad (1^{st} \text{ order ODE}) \quad \hookrightarrow \text{Ordinary D.Y. Eqn.}$$

$i(0^-) = i(0^+) = I_0$
 \hookrightarrow just before 0, just after 0.

$\Rightarrow i(0) = I_0 = I_s$

\Rightarrow The solution is: $\boxed{i(t) = I_0 \cdot e^{-\left(\frac{R}{L}\right)t}} \quad (A), \text{ and}$

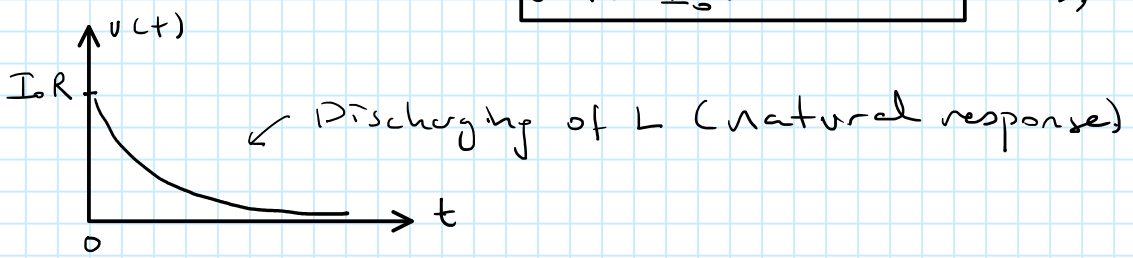$v(t) = i(t)R$ gives $\boxed{v(t) = I_0 R e^{-\left(\frac{R}{L}\right)t}} \quad (V), t \geq 0.$



The power dissipation: $p = v \cdot i = i^2 R = \frac{v^2}{R}$. Thus,

$$p = i(t)^2 \cdot R = I_0^2 R e^{-2(R/L)t}, \quad t \geq 0.$$

The energy delivered to the resistor at any time t :

$$W = \int_0^t p \cdot dx = \int_0^t I_0^2 R \cdot e^{-2(R/L)x} dx = \frac{1}{2} L I_0^2 [1 - e^{-2(R/L)t}], \quad t \geq 0$$

Now,

$$\lim_{t \rightarrow \infty} W = \lim_{t \rightarrow \infty} \left\{ \frac{1}{2} L I_0^2 [1 - e^{-2(R/L)t}] \right\} = \frac{1}{2} L I_0^2 \text{ (J) is the initial energy stored in the inductor.}$$

Here, the constant $(\frac{L}{R})$ is called the "time constant":

$$\text{Time constant} = \tau = \frac{L}{R}$$


At one τ after $t=0$,

$$i(\tau) = I_0 \cdot e^{-\left(\frac{R}{L}\right)\left(\frac{L}{R}\right)} = I_0 e^{-1} \Rightarrow \text{The current is reduced to } 0.37 \text{ } 37\% \text{ of its value at } t=0.$$

At 2τ , $i(2\tau) = 0.13 I_0 \Rightarrow$ Reduced to 13%.


At 5τ , it is conventional to assume that $i(t)$ is reduced to zero, and all inductor energy is released.

Remark: Consider the overall response.

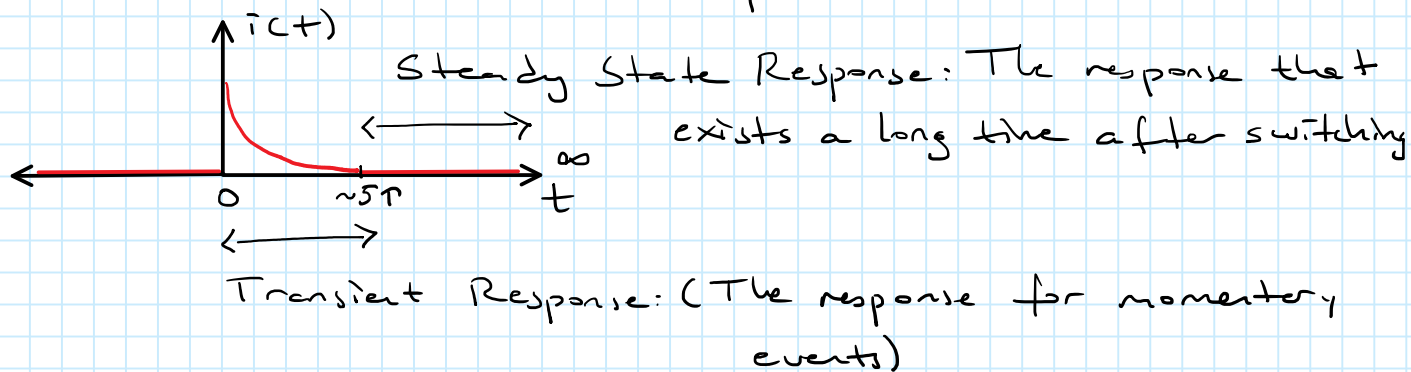


Natural Response of an RC-Circuit:

Consider the following circuit:

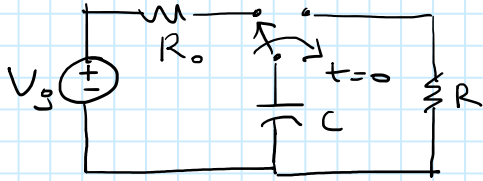

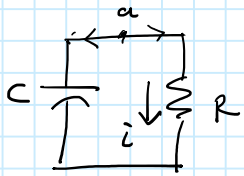For $t \geq 0$, the response is the "natural response":



KCL equation is:

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

$$V(0) = V_0 \text{ (initial capacitor voltage)}$$

The solution is:

$$V(t) = V_0 e^{-t/\tau}, \quad t \geq 0 \text{ where } \tau = RC \text{ (time constant)}$$

and

$$i(t) = \frac{V(t)}{R} = \frac{V_0}{R} e^{-t/\tau}, \quad t \geq 0.$$


$$P = \frac{V_0^2}{R} e^{-2t/\tau}, \quad t \geq 0.$$

$$W(t) = \frac{1}{2} C [V_0^2 (1 - e^{-2t/\tau})], \quad t \geq 0$$

$$\lim_{t \rightarrow \infty} W(t) = \frac{1}{2} C V_0^2 \text{ (initial energy stored in the capacitor)}$$

Step Response of an RL-Circuit: (Charging the inductor)

Consider the following circuit:

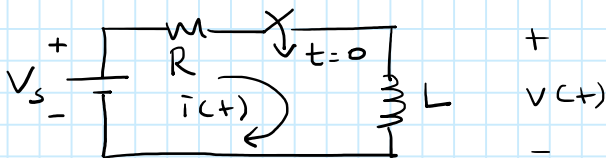

After the switch is closed, the KVL eqn is:

$$V_s = R i(t) + L \frac{di(t)}{dt}$$

$$\text{or } \frac{di(t)}{dt} = \frac{1}{L} [V_s - R i(t)]$$

$$\frac{d\bar{i}(t)}{dt} = \frac{1}{L} [V_s - R\bar{i}(t)]$$

or $\frac{d\bar{i}(t)}{dt} + \frac{R}{L}\bar{i}(t) = \frac{V_s}{L}$ (1st order ODE, linear non-homogeneous)

The initial condition is $\bar{i}(0) = I_0 = 0$


The solution is:

$$\bar{i}(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R}) e^{-\left(\frac{R}{L}\right)t}, \quad t \geq 0$$

For $I_0 = 0$:

(Step response of 1st order RL circuit)

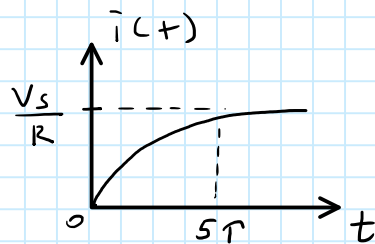
$$\bar{i}(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\left(\frac{R}{L}\right)t}$$



The voltage can be obtained from:


$$v = L \frac{d\bar{i}(t)}{dt} = L \left(-\frac{R}{L}\right) \left(\underbrace{I_0}_0 - \frac{V_s}{R}\right) e^{-\left(\frac{R}{L}\right)t}$$
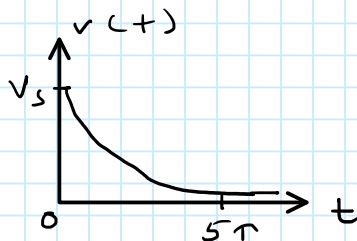
$$v(t) = V_s e^{-\left(\frac{R}{L}\right)t} \quad (v), \quad t \geq 0.$$



Ex:

For the following circuit

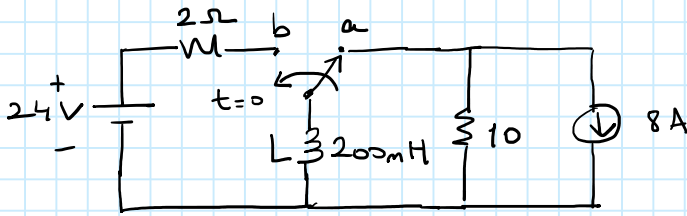


For $t < 0$, the circuit is already settled.

a-) Find $i(t)$, $t \geq 0$

b-) What is the initial voltage across the inductor just

after the switch is moved to position b.

Ans:

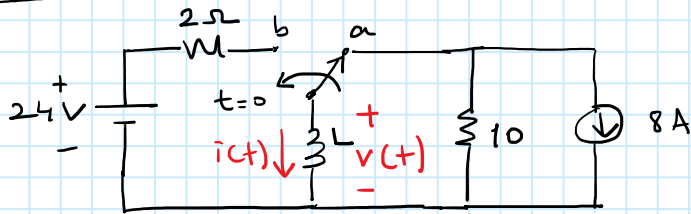

For $t < 0$, $i(0) = I_0 = -8A$.

$$i(\infty) = I_{final} = \frac{24V}{2\Omega} = 12A.$$

$$\text{and } \tau = \frac{L}{R} = \frac{200mH}{2} = 100ms.$$

a-) Using the step response for RL circuit:

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}}, \quad V_s = 24, R = 2\Omega.$$

$\underbrace{\hspace{1.5cm}}_{I_{final}} \quad \underbrace{\hspace{1.5cm}}_{-8A.} \quad \underbrace{\hspace{1.5cm}}_{I_{final}}$


$$\Rightarrow i(t) = 12 - 20e^{-10t} \text{ A.}$$

$$b-) v = L \cdot \frac{di(t)}{dt} = 0.2 (200 e^{-10t}) = 40 e^{-10t} \text{ (V)}, t \geq 0.$$

$$\Rightarrow v(0^+) = 40 \text{ V.} //$$

Step Response of an RC-Circuit:

Consider the following circuit:

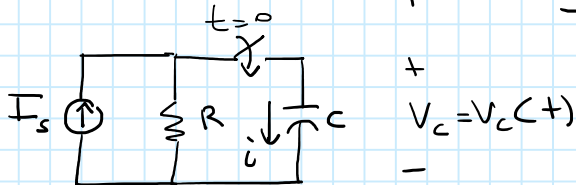

The KCL eqn is:

$$C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R} = I_s$$

or

$$\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = \frac{I_s}{C} \quad (1^{st} \text{ order ODE})$$

The solution is:

$$V_c(t) = I_s R + \left[U_0 - I_s R \right] e^{-t/RC}, \quad t \geq 0.$$

and

$$i(t) = \left[I_s - \frac{U_0}{R} \right] e^{-t/RC}, \quad t \geq 0.$$

General Response for Step & Natural Responses:

of 1st order diff. equations.

The general response is given as:

$$x(t) = X_f + [X(t_0) - X_f] e^{-(t-t_0)/\tau}$$

In another interpretation;

The Unknown variable = The final value + of the variable

$$\left[\begin{array}{l} \text{The initial value} \\ \text{of the variable} \end{array} - \begin{array}{l} \text{The final} \\ \text{value of} \\ \text{the variable} \end{array} \right] e^{\frac{-(t-t_0)}{\tau}}$$

When computing the step and/or natural responses of an RL or RC circuits using this general formulation, the following steps are used:

1-) Identify the variable of interest:

For an RL circuit \rightarrow Inductor current.

For an RC circuit \rightarrow Capacitor voltage.

2-) Determine the initial value of the variable, which is its value at t_0 . If chosen as capacitor voltage or inductor current as the variable of interest, then

$$V_C(t_0^-) = V_C(t_0^+) \text{ and } I_L(t_0^-) = I_L(t_0^+)$$

Otherwise, we must use the t_0^+ value of the variable as initial value.


3-) Calculate the final value of the variable at $t \rightarrow \infty$.

4-) Calculate the time constant.

5-) Substitute all variables into the general formulation.

Ex:

For the following circuit

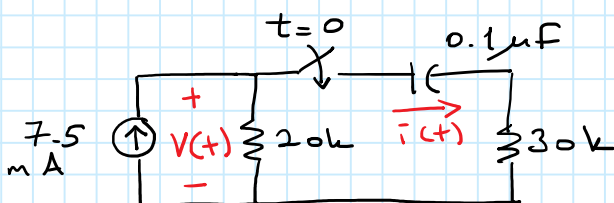


For $t < 0$, the circuit is already settled. Initial charge of the capacitor is 0.

Find, a-) $i(t)$ for $t \geq 0$
b-) $v(t)$, $t \geq 0$.

P47

Saturday, November 21, 2020 11:27 AM

Ans:

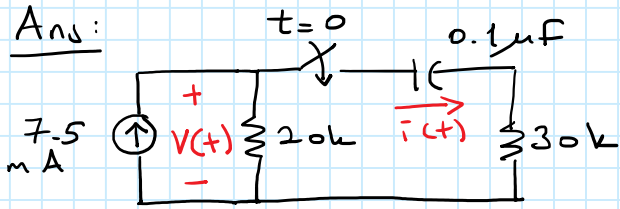


- a)
- 1) Variable of interest is $i(t)$.
 - 2) Variable of interest is the cap. current.

$$t_0 = 0$$

$$i(0^+) = ?$$

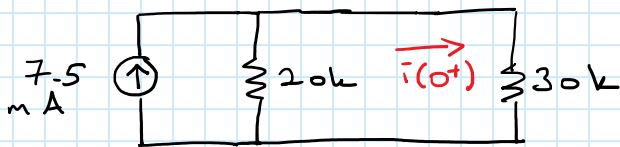At $t = 0^+$ → At this instant, the rate of change in current is max. \nearrow max.



For the capacitor, $i(t) = C \frac{dy_c(t)}{dt}$ \nearrow max.


When is $i(t)$ max? \Rightarrow short circuit.

$$i(0^+) = (7.5 \text{ mA}) \cdot \frac{20k}{50k} = 3 \text{ mA} \quad (\text{from current division})$$

Note that $i(0^-) = 0$
 $i(0^+) = 3 \text{ mA}$ } $i(0^-) \neq i(0^+)$

3-) $i(t = \infty) = i_{\text{final}} = 0$ and

4-) $\tau = RC = ?$

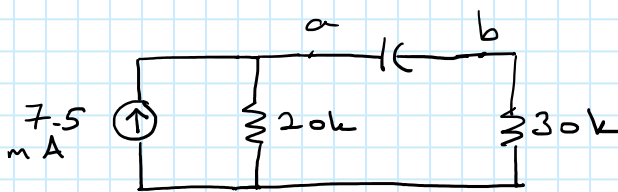

$R = R_{Th}$ wrt. point a-b.

To find R_{Th} : Deactivate the indep. sources:

$$\Rightarrow R_{Th} = 20k + 30k = 50k \Omega$$


$$\Rightarrow \tau = RC = (50k)(0.1 \mu F) = 5 \text{ ms}$$

$$5-) i(t) = 0 + (3 - 0)e^{-t/5 \times 10^{-3}} \text{ (mA)}, t \geq 0.$$

or $i(t) = 3e^{-200t}$, (mA), $t \geq 0$.

b-) Choose the unknown variable as the cap. voltage:
 Then find $V(t)$.

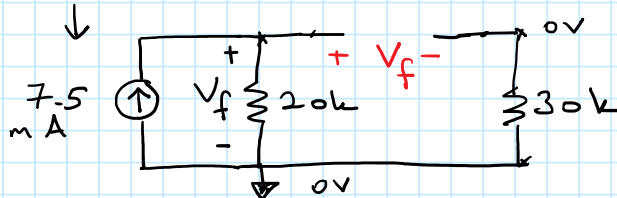
$$\Rightarrow V_c(0^+) = 0V, V_f = (7.5)(20) = 150V, \tau = 5 \text{ ms}$$



P48

Saturday, November 21, 2020 11:47 AM
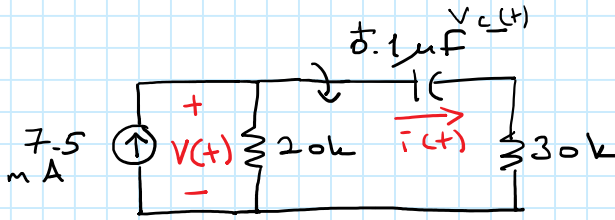
$$\Rightarrow v_C(t) = 150 - 150 e^{-200t}, \quad t \geq 0$$



$$\Rightarrow v(t) = v_C(t) + v_R(t), \quad t \geq 0$$


\downarrow \downarrow
 v_R $i_C(t) \cdot R$

$$\Rightarrow v(t) = 150 - 150 e^{-200t} + (30)(3) e^{-200t}$$

$$\Rightarrow v(t) = 150 - 60 e^{-200t} \text{ (V)}, \quad t \geq 0. \quad //$$

Ex:

For the circuit

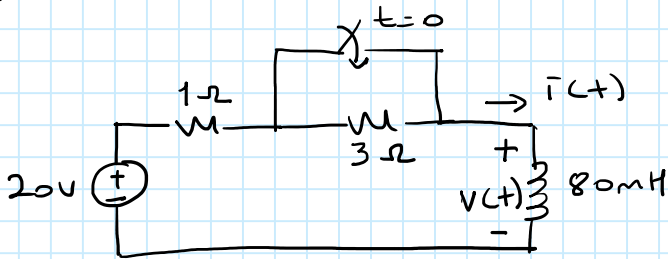

Find $v(t)$ and $i(t)$ for $t \geq 0$.

Ans:

Variable of interest \rightarrow inductor current $i(t)$.

$$I_0 = \frac{20V}{4\Omega} = 5A, \quad I_f = \frac{20V}{1\Omega} = 20A.$$


$$\tau = \frac{L}{R} = \frac{80mH}{1\Omega} = \frac{80mH}{1\Omega} = 80ms.$$

$$\Rightarrow i(t) = 20 + (5 - 20) e^{-t/80ms} = 20 - 15 e^{-12.5t} \text{ (A)}, \quad t \geq 0.$$

$$\Rightarrow v(t) = L \frac{di(t)}{dt} = 15 e^{-12.5t} \text{ (V)}, \quad t \geq 0.$$

HW:


Given the circuit below:

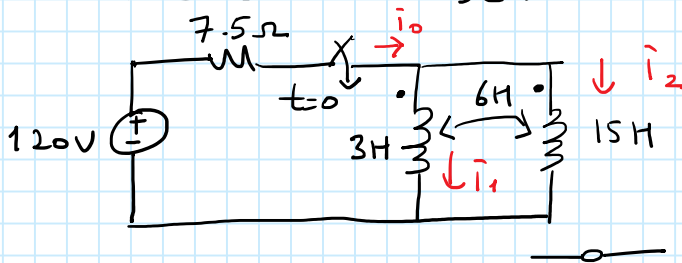

Find i_0 , i_1 , and i_2 for $t \geq 0$.


Ex:

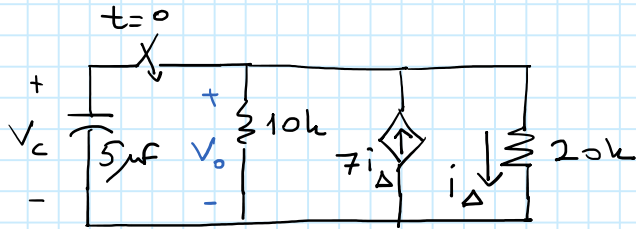For the given circuit, find V_o . ($V_c = 10V$ for $t < 0$)




Ans:

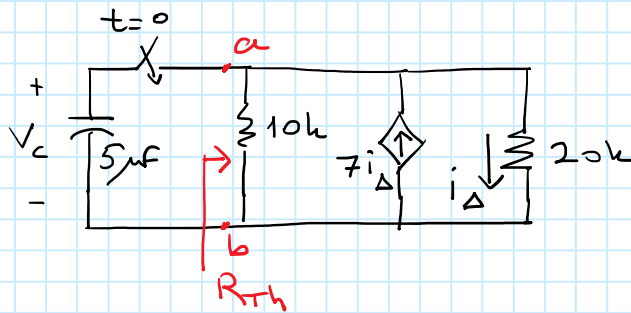- Variable of interest is the cap. voltage ($V_c = V_o, t \geq 0$)
- To determine $V_o(0)$, we can first replace the capacitor terminals by its Thevenin resistance.



To find R_{Th} :

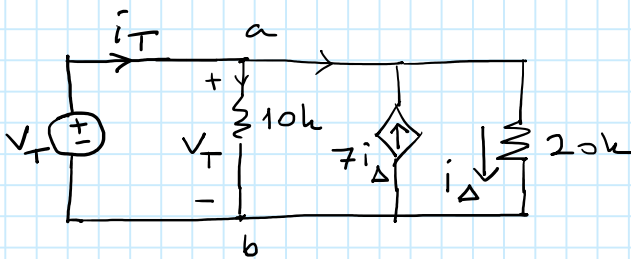

KCL at node a:


$$\Rightarrow \bar{i}_T = \left[\frac{V_T}{10k} - 7i_\Delta + i_\Delta \right]$$

where $i_\Delta = \frac{V_T}{20k}$ (Ohm's law across 20kΩ)

$$\Rightarrow \bar{i}_T = \left[\frac{V_T}{10k} - 7 \frac{V_T}{20k} + \frac{V_T}{20k} \right]$$

$$\Rightarrow R_{Th} = \frac{V_T}{\bar{i}_T} = -5k\Omega.$$

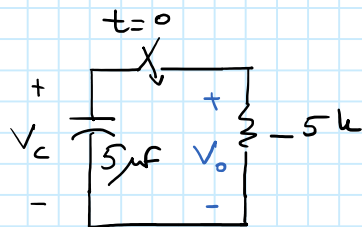Negative resistance indicates that signal grows.



$$- V_c(0^-) = V_c(0^+) = 10V.$$

$$- V_c(\infty) = V_o(\infty) = 0V.$$

$$- \tau = RC = (5\mu F)(-5k) = -25ms.$$

$$- V(t) = V_f + [V(0) - V_f] e^{-[t/(-25ms)]}$$

\downarrow \downarrow \downarrow
 V_o 10V 0


$$\Rightarrow V(t) = 10e^{40t}, t \geq 0 \text{ (Unbounded response) (not realistic!)}$$

RLC Circuits (Chapter 8)

Natural & Step Response:

1-) Natural Response of Parallel RLC Circuit:

The RLC circuit is given as: (parallel)

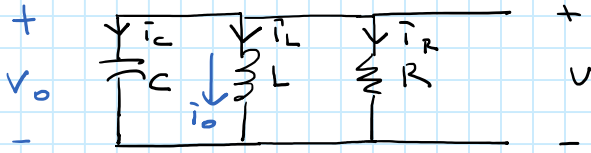

KCL at the top node:

$$\underbrace{\frac{v}{R}}_{i_R} + \underbrace{\frac{1}{L} \int v dt + I_0}_{i_L} + \underbrace{C \frac{dv}{dt}}_{i_C} = 0$$

Differentiate both sides wrt. t :

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2 v}{dt^2} = 0$$

Re-arranging this equation,

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \quad (2^{\text{nd}} \text{ order differential equation})$$

The classical approach to solve this equation is to assume a solution in the form which is exponential.

Let $v = Ae^{st}$ be the solution. Then, substitute this solution into the equation:

$$As^2 e^{st} + \frac{1}{RC} Ase^{st} + \frac{Ae^{st}}{LC} = 0$$

or

$$Ae^{st} \left(s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$$

$A=0$ is a trivial solution, it cannot be accepted.

$$\Rightarrow s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad \text{This equation is called the "characteristic equation".}$$

There are 2 roots:

$$s_{1,2} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Thus, $v = A_1 e^{s_1 t}$ and $v = A_2 e^{s_2 t}$ are the 2 solutions.

Also, $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ is a solution.

Consider the roots of the characteristic equation in another notation:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$\alpha = \frac{1}{2RC}$ is called the "Neper frequency".

and

$\omega_0 = \frac{1}{\sqrt{LC}}$ is called the "Resonant radian frequency".

There are 3 possible outcomes:

- 1-) If $\omega_0^2 < \alpha^2$ → Both roots are real. The response is called "overdamped".
- 2-) If $\omega_0^2 > \alpha^2$ → Both roots are complex, and conjugate of each other. That is; $s_1 = a + jb_1$, then $s_2 = a - jb_1$ or vice versa. The response is called "underdamped".
- 3-) If $\omega_0^2 = \alpha^2$ → $s_{1,2}$ are real and equal. The response is called "critically damped".

Ex:

For an RLC circuit, with $R = 200 \Omega$, $L = 50 \text{ mH}$, $C = 0.2 \mu\text{F}$

- a) Find the roots of the characteristic equation.
- b) Determine the type of response?
- c) Repeat part a and b for $R = 312.5 \Omega$.
- d) What values of R causes the response to be critically damped?

Ans:

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(200)(0.2)} = 1.25 \times 10^4 \text{ rad/s}, \alpha^2 = 1.5625 \times 10^8$$

$$\omega_0^2 = \frac{1}{LC} = \frac{10^3 \cdot 10^6}{(50)(0.2)} = 10^8 \text{ rad}^2/\text{s}^2$$

$$a-) s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1.25 \times 10^4 \pm \sqrt{1.5625 \times 10^8 - 10^8}$$

$$\Rightarrow s_1 = -5000 \text{ rad/s}, s_2 = -20000 \text{ rad/s}.$$

b-) Since $\omega_0^2 < \alpha^2$, it is overdamped.

c-) For $R = 312.5 \Omega$, $\alpha = 8000 \frac{\text{rad}}{\text{s}}$, $\alpha^2 = 0.64 \times 10^8 \text{ rad}^2/\text{s}^2$
and $\omega_0^2 = 10^8 (\text{rad}/\text{s})^2$

$$s_1 = -8000 + j6000 \text{ (rad/s)}, \quad s_2 = -8000 - j6000 \text{ (rad/s)}$$

The response is underdamped since $\omega_0^2 > \alpha^2$.

d-) For critically damped response, $\alpha^2 = \omega_0^2$

$$\Rightarrow \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = 10^8 \Rightarrow \frac{1}{2RC} = 10^4 \Rightarrow \boxed{R = 250 \Omega}$$

\downarrow
0.2 μF .

The Overdamped Voltage Response:

The solution is in the form:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{where } s_1 \text{ and } s_2 \text{ are the}$$

roots of the characteristic equation. A_1 and A_2 are the constants to be determined by the initial conditions

\Rightarrow Initial conditions: $v(0^+)$ or $\frac{dv(0^+)}{dt}$

Then, $v(0^+) = A_1 + A_2$ and $\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2$.

- The $v(0^+)$ is the initial voltage on the capacitor.

- The value of $\frac{dv(0^+)}{dt}$ can be obtained by finding the current through the capacitor

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

Also,

$$i_c(0^+) = \frac{-V_0}{R} - I_0.$$

Summary for Finding the "Overdamped" Response:

1-) Find s_1 and s_2

2-) Find $v(0^+)$ and $\frac{dv(0^+)}{dt}$


3-) Find A_1 and A_2 from $v(0^+) = A_1 + A_2$,
 $\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2$.

4-) Substitute the values into the solution

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Ex:

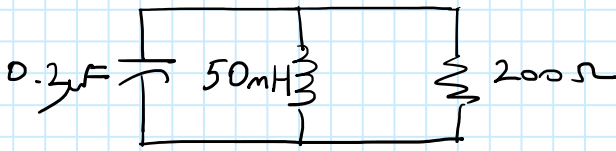For the circuit below, given that $v(0^+) = 12V$, $i_L(0^+) = 30mA$




a-) Find the initial current in each branch of the circuit.

b-) Find the initial value of $\frac{dv}{dt}$.

c-) Find the response for $v(t)$.

Ans:

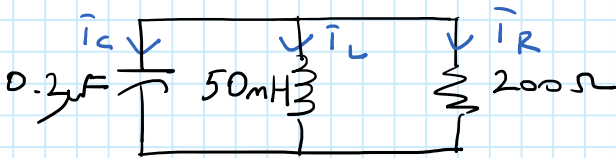

a-) $i_L(0^+) = i_L(0^-) = i_L(0) = 30mA$.

$$i_R(0^+) = \frac{12V}{200} = 60mA$$

Then, from the KCL at the top node:

top node:

$$i_c(0^+) = -i_L(0^+) - i_R(0^+) = -90mA \quad (\text{the real direction is opposite to our assumption.})$$

b-) $\frac{dv(0^+)}{dt} = ?$, $i_c(0^+) = C \frac{dv(0^+)}{dt}$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{1}{C} i_c(0^+) = \frac{-90 \times 10^{-3}}{0.2 \times 10^{-6}} = -450 \frac{kV}{s}$$

c-) The roots of the characteristic equation are

$$s_1 = -1.25 \times 10^4 + \sqrt{1.5625 \times 10^8 - 10^8} = -5000 \text{ rad/s}$$


$$s_2 = -1.25 \times 10^4 - \sqrt{1.5625 \times 10^8 - 10^8} = -20000 \text{ rad/s}$$

To find the coefficients A_1 and A_2 :


$$12 = A_1 + A_2 \quad , \quad -450 \times 10^3 = -5000 A_1 - 20000 A_2$$

$$\Rightarrow A_1 = -14V, \quad A_2 = 26V$$
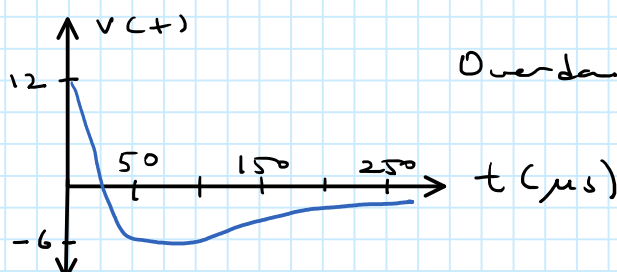
$$\Rightarrow v(t) = (-14e^{-5000t} + 26e^{-20000t}) (V), \quad t \geq 0$$



Overdamped!

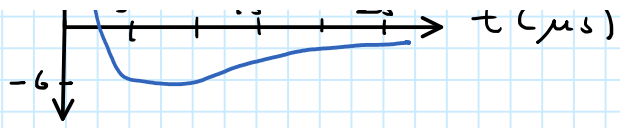

Underdamped Voltage Response:

When $\omega_0^2 > \alpha^2$, the roots are

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \quad , \quad j = i = \sqrt{-1}$$

$$s_1 = -\alpha + j\omega_d \quad , \quad s_2 = -\alpha - j\omega_d$$

where

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ is called the "damped radian frequency".

The response is:

$$v(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$


where the coefficients B_1 and B_2 can be obtained from:

$$v(0^+) = V_0 = B_1 \quad , \quad \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

(α : damping factor)

Ex:

For the given circuit

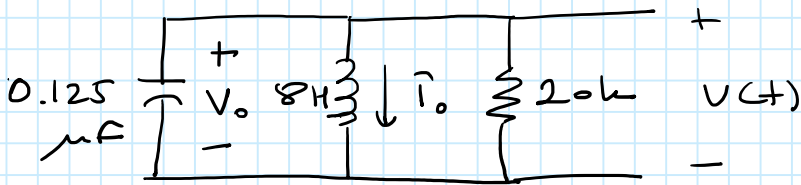

Given:

$$V_0 = 0V \quad , \quad i_0 = -12.25mA$$

a-) $s_1, s_2 = ?$

b-) $v|_{t=0} = v(0) \quad , \quad \frac{dv}{dt}|_{t=0} = ?$

c-) $v(t) = ? \quad , \quad t \geq 0$

Ans:

$$\alpha = \frac{1}{2RC} = 200 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^3 \text{ rad/s}$$

$$\Rightarrow \omega_0^2 > \alpha^2 \Rightarrow \text{Underdamped!}$$

Now,

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 100\sqrt{96} = 979.80 \text{ rad/s}$$

$$s_1 = -\alpha + j\omega_d = -200 + j979.8 \text{ rad/s}$$

$$s_2 = -\alpha - j\omega_d = -200 - j979.8 \text{ rad/s}$$

$$b-) v(0^+) = ? , \frac{dv(0^+)}{dt} = ?$$

$$v(0) = v(0^+) = V_0 = 0V.$$

To find $\frac{dv(0^+)}{dt}$, we need $i_C(0^+)$.

$$\Rightarrow i_R(0^+) = 0 \text{ (since } V_0 = 0)$$

$$\Rightarrow i_C(0^+) = -i_L(0^+) - i_R(0^+) = -(-12.25 \text{ mA}) = 12.25 \text{ mA}.$$


Then,

$$\frac{dv(0^+)}{dt} = \frac{1}{C} i_C(0^+) = \frac{(12.25)(10^{-3})}{(0.125)(10^{-6})} = 98000 \frac{V}{s}.$$

c-) To find B_1 and B_2 :

$$v(0^+) = V_0 = B_1 = 0, \quad \frac{dv(0^+)}{dt} = 98000 = -\alpha B_1 + \omega_d B_2$$
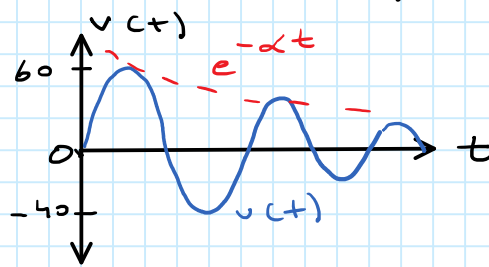
$$\Rightarrow v(t) = 100 e^{-200t} \sin(979.8t) \Rightarrow B_2 = 100.$$



α : damping factor

$$\alpha = \frac{1}{2RC}$$

If R is \uparrow

α is small

it takes longer to

damp.

- The oscillation frequency is ω_d .

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}, \text{ for a large } R \uparrow, \alpha \text{ is small } \downarrow$$

$$\Rightarrow \omega_d \approx \omega_0 \text{ (resonant radian frequency.)}$$

- Note that oscillators or sine wave generators are based on RLC circuit underdamped response.

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L, C \text{ determines the freq. of oscillation}$$

Critically Damped Voltage Response:


$$s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

The response is $v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

I.C.'s: $v(0^+) = D_2, \quad \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$

Ex:

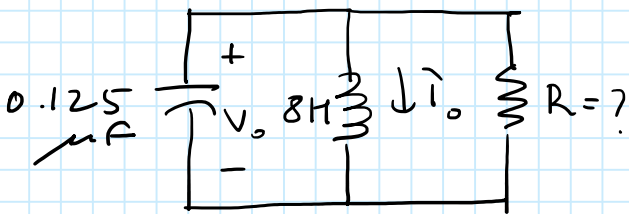For the circuit given below, $V_0 = 0$, $I_0 = -12.25 \text{ mA}$



- + a-) Find the value for
 V R such that the response
 is critically damped.
 - b-) Find $v(t)$.

Ans:

$$a-) \omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\frac{10^6}{8(0.125)}} = 10^3 \text{ rad/s.}$$


In critically damped response, $\alpha^2 = \omega_0^2$, $\alpha = \omega$

$$\alpha = 10^3 = \frac{1}{2RC} \Rightarrow R = \frac{10^6}{(2000)(0.125)} = 4 \text{ k}\Omega.$$

$$b-) v(0^+) = 0 = D_2$$


$$\frac{dv(0^+)}{dt} = 98000 \frac{\text{V}}{\text{s}} \Rightarrow D_1 = 98000 \frac{\text{V}}{\text{s}}.$$
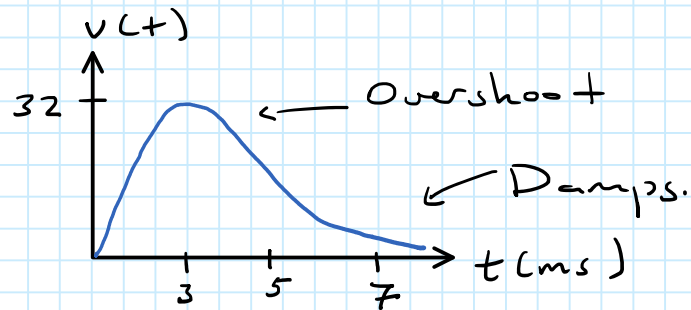
$$\Rightarrow v(t) = 98000 t e^{-1000t} \text{ (V)}, t \geq 0$$



Step Response of Parallel RLC-Circuit: (Charging)

→ Consider the following circuit:

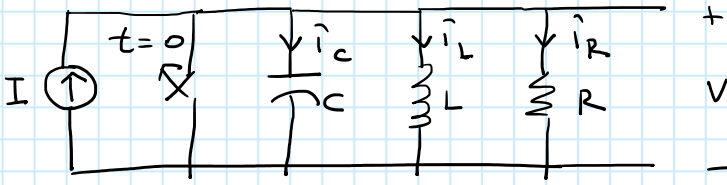

The governing equation for this circuit is:

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

- The solution can be expressed as i_L as a function of t .
Then, we have from $v = L \frac{di_L}{dt}$, differentiating both sides,

$$\frac{dv}{dt} = L \cdot \frac{d^2 i_L}{dt^2}$$

- Thus, the circuit equation is:

$$\frac{1}{L} \frac{dv}{dt} + \frac{1}{RC} \frac{v}{L} + \frac{1}{L^2 C} \int_0^t v d\tau = \frac{I}{LC}$$

- Multiply both sides by LC ,

$$\frac{1}{L} \int_0^t v d\tau + \frac{v}{R} + C \frac{dv}{dt} = I,$$

- Differentiate both sides wrt. t :

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2 v}{dt^2} = 0$$

or

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \quad (\text{Circuit eqn. in terms of } v)$$

→ The solution is:

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$\text{or } v = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad (\text{Underdamped})$$

$$\text{or } v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad \text{depending on the roots } s_1 \text{ and } s_2 \text{ of the characteristic equation.}$$

→ The solution for i_L is:

$$i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t} \quad (\text{Over damped})$$

$$\text{or } i_L = I + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t) \quad (\text{Under damped})$$

$$\text{or } i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t} \quad (\text{Critically damped})$$

Ex:

The initial energy stored in the circuit is zero. At $t=0$ a DC current source of 24 mA is applied to the circuit.


The value of the resistor is 400Ω .

a-) What is the initial value of i_L ?

b-) " " " " " " $\frac{di_L}{dt}$?

c-) Find s_1, s_2 .

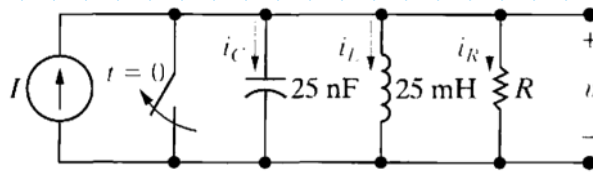d-) Find the expression for $i_L(t)$ for $t \geq 0$.



Ans:

$$a-) i_L(0) = 0 \Rightarrow i_L(0^+) = 0$$

$$b-) v = L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = \frac{v}{L} \quad \text{and } v(0) = v(0^+) = 0 \text{ from the cap. voltage.}$$

$$\Rightarrow \frac{di_L(0^+)}{dt} = 0.$$

$$c-) \omega_0^2 = \frac{1}{LC} = \frac{10^{12}}{(25)(25)} = 16 \times 10^8$$

and

$$\alpha = \frac{1}{2RC} = \frac{10^9}{2(400)25} = 5 \times 10^4 \text{ rad/s.}$$

$$\text{or } \alpha^2 = 25 \times 10^8$$

Because, $\omega_0^2 < \alpha^2$, the roots of the characteristic equation are real and distinct. Thus,

$$s_1 = -5 \times 10^4 + 3 \times 10^4 = -20000 \text{ rad/s.}$$

$$s_2 = -5 \times 10^4 - 3 \times 10^4 = -80000 \text{ rad/s.}$$

d-) The inductor current response is overdamped. Thus,

$$i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

To find A_1' and A_2' :

$$i_L(0) = I + A_1' + A_2' = 0$$


and

$$\frac{d i_L(0)}{dt} = s_1 A_1' + s_2 A_2' = 0$$

Solving these equations yields $A_1' = -32 \text{ mA}$, $A_2' = 8 \text{ mA}$.

→ Thus, the solution for $i_L(t)$ is:

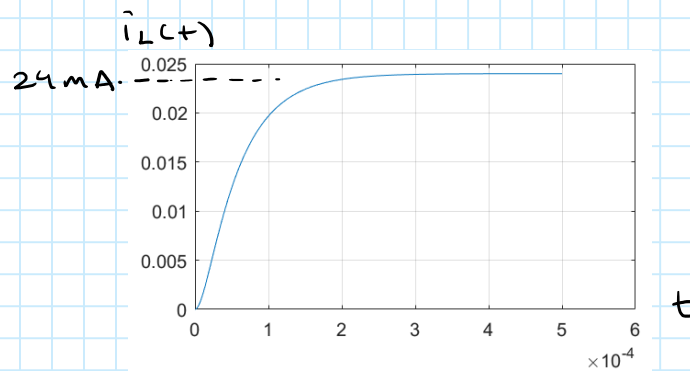
$$i_L(t) = (24 - 32 e^{-20000t} + 8 e^{-80000t}) \text{ mA}, t \geq 0.$$



— 0 —

If R was 625Ω , then

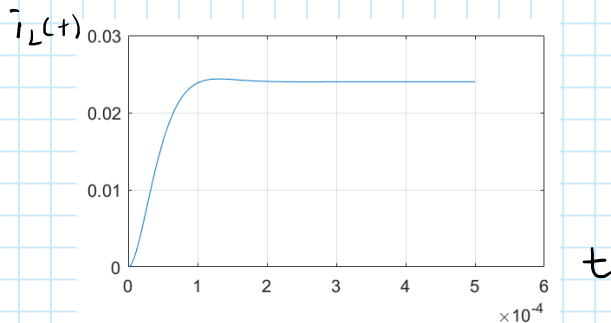
$$i_L(t) = \left[24 - 24 e^{-32000t} \cos(24000t) - 32 e^{-32000t} \sin(24000t) \right] \text{ mA}.$$



— 0 —

Natural and Step Response of Series RLC-Circuit:

Consider the circuit,

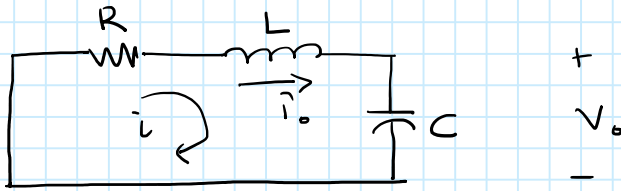

- The governing equation is: $Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0$
- Differentiate both sides:

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

- Re-arranging,

$$\boxed{\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = 0}$$

→ The characteristic eqn is: $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

where

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{where} \quad \boxed{\alpha = \frac{R}{2L}}, \quad \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$


and the solution of the natural response is:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad \text{overdamped.}$$

$$\text{or } i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t), \quad \text{underdamped.}$$

$$\text{or } i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad \text{critically damped responses.}$$

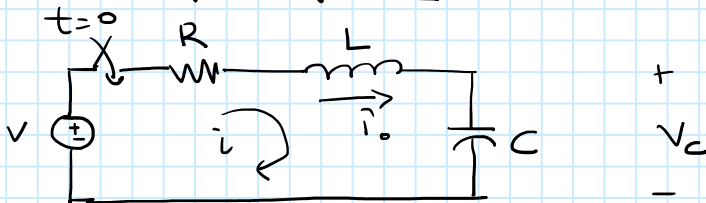To find the step response, we consider the following circuit:



- The governing eqn is: $\frac{d^2V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{V_c}{LC} = \frac{V}{LC}$

- The solution is:


$$V_c = V_f + A_1' e^{s_1 t} + A_2' e^{s_2 t} \quad (\text{overdamped})$$

$$\text{or } V_c = V_f + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t) \quad (\text{under-damped})$$

$$\text{or } V_c = V_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t} \quad (\text{critically damped})$$

Ex:

For the given circuit,

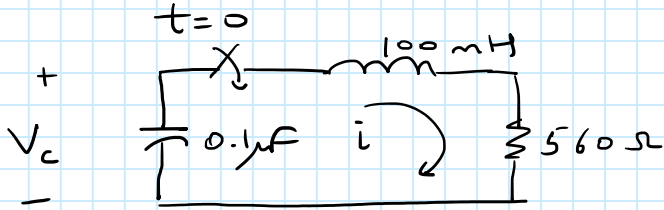

a-) Find $i(t)$, $t \geq 0$

b-) Find $V_c(t)$, $t \geq 0$.

$V_c(0) = 100V$.

Ans:

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(0.1)(0.1) \times 10^{-6}} = 10^8 \text{ rad/s}.$$

and

$$\alpha = \frac{R}{2L} = \frac{560}{2(0.1)} = 2800 \text{ rad/s}.$$

$$\Rightarrow \omega_0^2 > \alpha^2 \Rightarrow \text{Underdamped!}$$

 \Rightarrow The solution is:

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2} = [10^8 - (2800)^2]^{1/2} = 9600 \text{ rad/s}.$$

and B_1 and B_2 can be obtained from:

$$i(0) = 0 = B_1.$$

$$\text{For } B_2, \text{ we need } \frac{di(0^+)}{dt}, \text{ so } L \frac{di(0^+)}{dt} = V_0.$$

$$\text{or } \frac{di(0^+)}{dt} = \frac{V_0}{L} = \frac{100}{0.1} = 1000 \frac{A}{s}.$$

$$\Rightarrow \frac{di(t)}{dt} = B_2 (-\alpha) e^{-\alpha t} \sin(\omega_d t) + B_2 e^{-\alpha t} \omega_d \cos(\omega_d t)$$


(with $B_1 = 0$)

Now,

$$\frac{di(0^+)}{dt} = 1000 = B_2 \omega_d \Rightarrow B_2 = \frac{1000}{\omega_d} = \frac{1000}{9600} \approx 0.1042 \text{ A}$$

Thus,
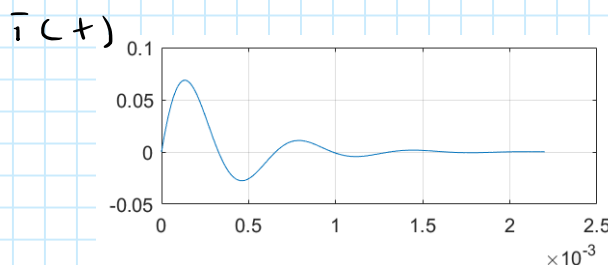
$$i(t) = 0.1042 e^{-2800t} \sin(9600t), \quad t \geq 0.$$



(Underdamped)

To find $V_c(t)$, we use the KVL in the circuit:

$$\text{Then, } V_c = iR + L \frac{di}{dt} \quad \text{or} \quad V_c = -\frac{1}{C} \int_0^t i(\tau) d\tau + 100$$

$$\begin{aligned} V_c(t) &= R i(t) + L \frac{di(t)}{dt} \\ &= 560 \left[0.1042 e^{-2800t} \sin(5600t) \right] \\ &\quad + 0.1 \left[(0.1042)(-2800) e^{-2800t} \sin(5600t) + \right. \\ &\quad \left. (0.1042) e^{-2800t} (5600) \cos(5600t) \right] \end{aligned}$$

Re-arranging this expression gives us:

$$V_c(t) = \left[100 \cos(5600t) + 25.17 \sin(5600t) \right] e^{-2800t}, \quad t \geq 0.$$

- Sinusoidal Steady State Analysis - (Cp.5)

- Sinusoidal Source:

Consider the following voltage source:

$$v = V_m \cos(\omega t + \phi)$$

where

t = time variable (s)

v = Voltage (V)

ω = Radian frequency (rad/s)

V_m = Maximum amplitude (V)

ϕ = Phase angle (rad)


and

$$\omega = 2\pi f, \quad f = \text{frequency (Hz)}$$

and

$$T = \frac{1}{f} = \text{Period (s)}$$

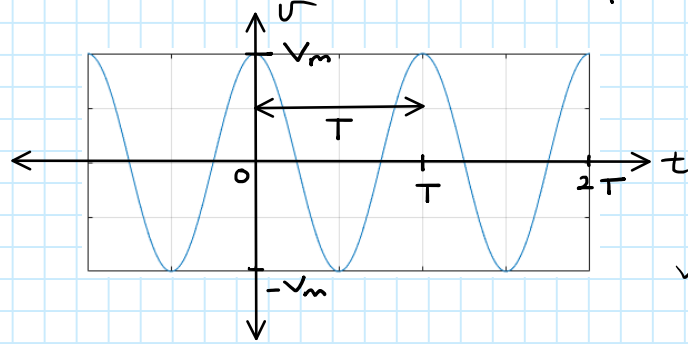If we plot a sinusoidal source wave form wrt. time:




$$v(t) = v(t + T)$$


(Periodic)

Thus,

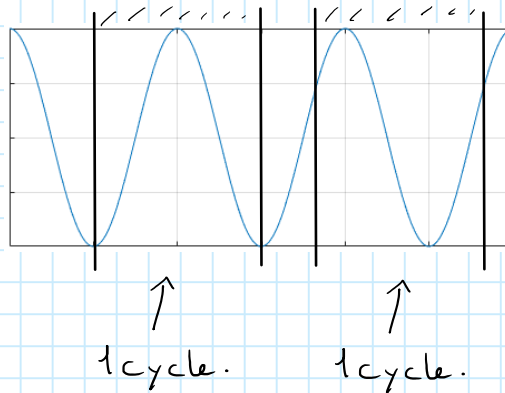Cycle: The smallest non-repeatable portion of the periodic waveform.




Frequency: # of cycles in 1 sec.

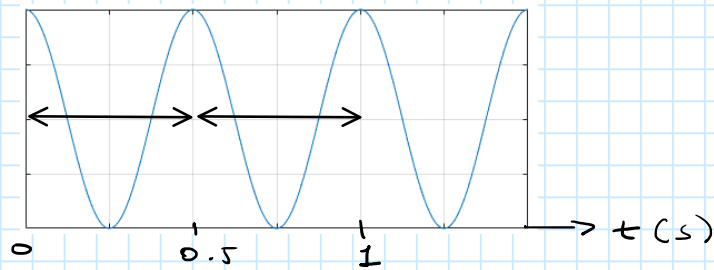


There are 2 cycles $\Rightarrow f = 2 \text{ Hz}$.

or

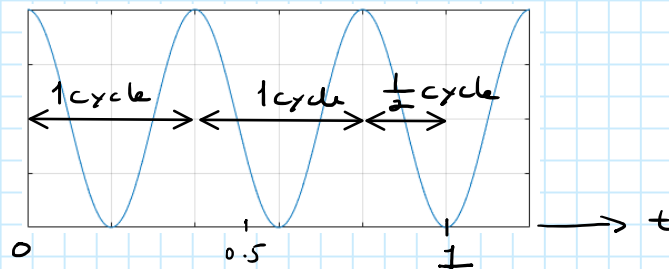

$$f = 1 + 1 + \frac{1}{2} = 2 + \frac{1}{2} = \frac{5}{2} \text{ Hz} = 2.5 \text{ Hz}$$


Period $= T =$ Time for 1 cycle.

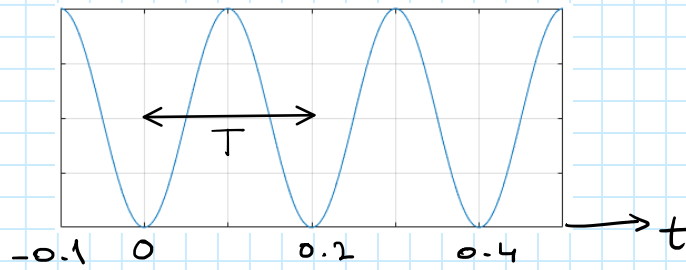

$$\Rightarrow T = 0.2 \text{ sec.} \Rightarrow f = \frac{1}{T} = \frac{1}{0.2} = 5 \text{ Hz.}$$

Phase Angle $= \phi$

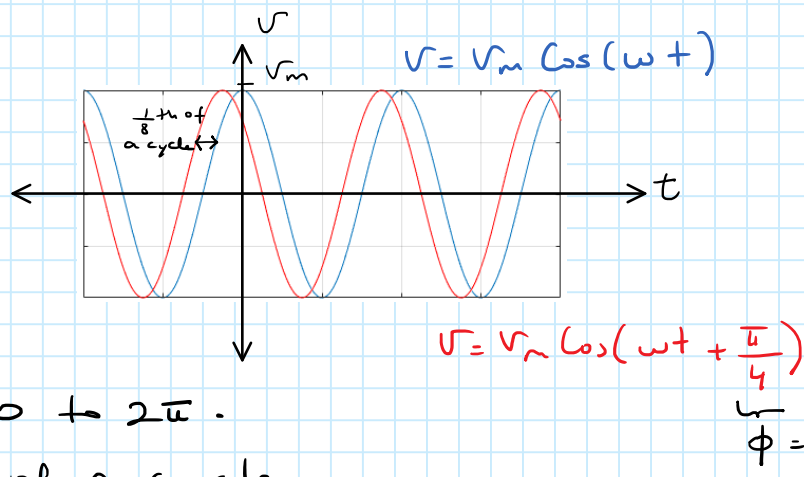It shifts the graph left or right for $+$ or $- \phi$ respectively.



- 1 cycle is from 0 to 2π .

$\Rightarrow \frac{\pi}{4}$ is $\frac{1}{8}$ th of a cycle.

That's why we shift the graph of $v = V_m \cos(\omega t)$ by a $\frac{1}{8}$ th of a cycle to the left.

Another important property of a sinusoidal voltage (or current) is the "rms value".

rms: Root Mean Square.

Thus, if $v = V_m \cos(\omega t + \phi)$

$$V_{rms} = \left[\frac{1}{T} \int_{t_0}^{t_0+T} v^2 dt \right]^{\frac{1}{2}} = \text{Root of the mean value (average) of the squared voltage.}$$


$$\Rightarrow V_{rms} = \left[\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt \right]^{\frac{1}{2}} =$$

Using the identity $\cos^2 x = \frac{1}{2} (1 + \cos 2x)$

$$V_{rms} = \left[\frac{1}{T} V_m^2 \int_{t_0}^{t_0+T} \frac{1}{2} [1 + \cos(2\omega t + 2\phi)] dt \right]^{\frac{1}{2}}$$

$$= \left[\frac{1}{T} V_m^2 \left(\int_{t_0}^{t_0+T} \frac{1}{2} dt + \int_{t_0}^{t_0+T} \cos(2\omega t + 2\phi) dt \right) \right]^{\frac{1}{2}}$$
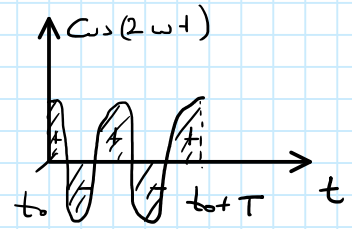
$$= \left[\frac{1}{T} V_m^2 \left(\frac{T}{2} + 0 \right) \right]^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} (V)$$




$$V_{rms} = \left[\frac{1}{T} V_m^2 \frac{T}{2} \right]^{\frac{1}{2}} = \left(\frac{V_m^2}{2} \right)^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} (V)$$

or

$V_{rms} = \frac{V_m}{\sqrt{2}} (V)$

Ex:

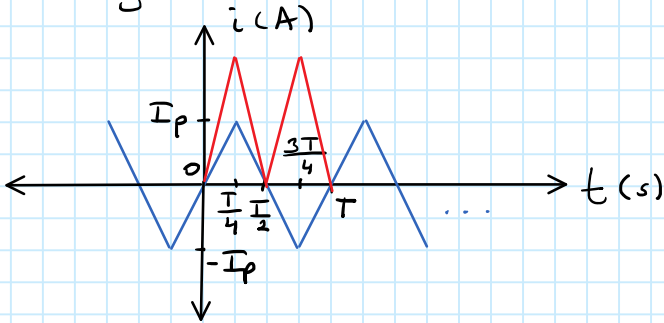Find the rms value of the period T triangular function given below.



Ans:

$$i_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2 dt}$$

Then,

$$\int_{t_0}^{t_0+T} i^2 dt = 4 \int_0^{T/4} i^2 dt$$

\downarrow
 $i(t)$

From the graph:

$$i(t) = \frac{4I_p}{T} t, \quad 0 < t < T/4$$

$$\Rightarrow 4 \int_0^{T/4} i^2(t) dt = 4 \int_0^{T/4} \frac{16 I_p^2}{T^2} t^2 dt = \frac{I_p^2 T}{3} \Rightarrow i_{rms} = \sqrt{\frac{1}{T} \cdot \frac{I_p^2 T}{3}} = \frac{I_p}{\sqrt{3}}$$

The use of rms value for sinusoidal voltage and/or current:

$$U = U_m \cos(\omega t + \phi) \quad P_R = ? \quad P_R = U \cdot i = \frac{U^2}{R} = i^2 \cdot R \quad (\text{W})$$


$$\Rightarrow P_R = \frac{U_m^2}{R} \cos^2(\omega t + \phi) \quad (\text{W})$$

Using the identity $\cos^2 x = \frac{1}{2} (1 + \cos 2x)$

$$P_R = \frac{U_m^2}{R} \frac{1}{2} [1 + \cos(2\omega t + 2\phi)] = \frac{U_m^2}{2R} + \frac{U_m^2}{2R} \cos(2\omega t + 2\phi)$$

Let's say $\phi = 0$ for simplicity.
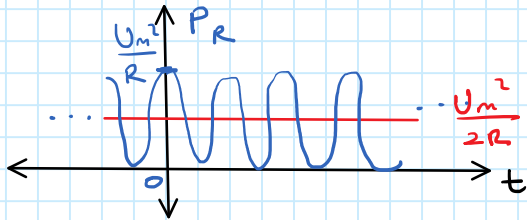
$$P_R = \frac{U_m^2}{2R} + \frac{U_m^2}{2R} \cos(2\omega t)$$



- This power keeps changing.

Thus, it is not useful.

- Thus, we use the average of this power.

$$P_{\text{avg}} = \frac{1}{T} \int_0^T P_R dt = \frac{1}{T} \left[\int_0^T \frac{U_m^2}{2R} dt + \underbrace{\int_0^T \frac{U_m^2}{2R} \cos(2\omega t + 2\phi) dt}_{=0} \right]$$

$$\Rightarrow P_{\text{avg}} = \frac{1}{T} \frac{U_m^2}{2R} T = \frac{U_m^2}{2R} \quad (\text{W})$$

Ex:

A light bulb is connected to $v = 311 \cos(\omega t)$ (V) where $\omega = 2\pi f = 2\pi(50) = 100\pi$. Find the power consumed by $R = 100 \Omega$ when connected to this voltage source.

Ans:

The power consumed means the average power P_{avg} .

$$\Rightarrow P_{\text{avg}} = \frac{V_m^2}{2R} = \frac{(311)^2}{2(100)} = 484 \text{ W.}$$

- We could also use the relation $V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$. Thus,

$$P_{\text{avg}} = \frac{(\sqrt{2} V_{\text{rms}})^2}{2R} = \frac{2 V_{\text{rms}}^2}{2R} = \frac{V_{\text{rms}}^2}{R} \quad (\text{W})$$

Thus, the same problem could be solved by finding the rms voltage first,

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{311}{\sqrt{2}} = 220 \text{ V.}$$


Then, for finding the average power, we

$$P_{avg} = \frac{V_{rms}^2}{R} = \frac{220^2}{100} = 484 \text{ W.}$$

Ex:

Find the resistance of a 60 W light bulb?

Ans:

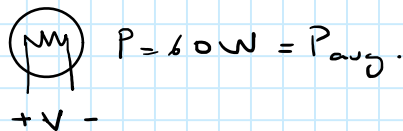


$$P_{avg} = \frac{V_m^2}{2R}$$

or


$$P_{avg} = \frac{V_{rms}^2}{R} \checkmark$$

$$\Rightarrow 60 = \frac{(220)^2}{R} \Rightarrow R = 806 \Omega.$$

Ex:

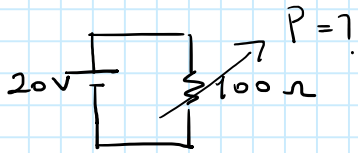
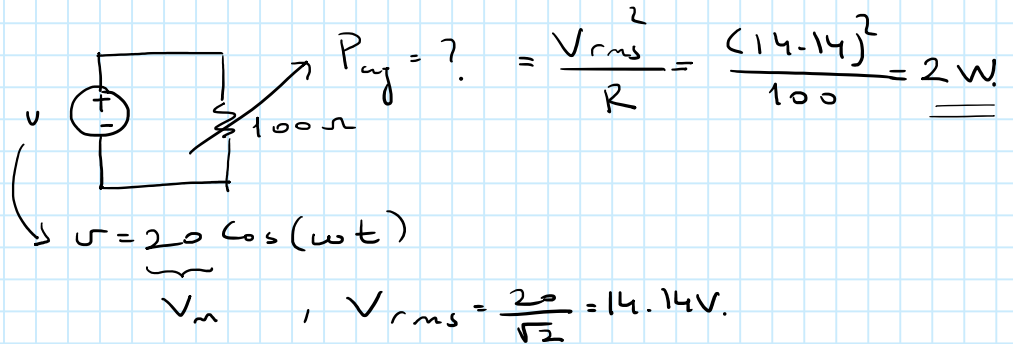
$$P = \frac{20^2}{100} = \frac{20 \cdot 20}{100} = 4 \text{ W.}$$




$$v = 20 \cos(\omega t)$$

$$V_m, \quad V_{rms} = \frac{20}{\sqrt{2}} = 14.14 \text{ V.}$$

Sinusoidal Response: (sin autu you!) ↓

Consider the following circuit:

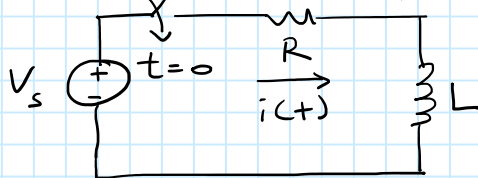

where $V_s = V_m \cos(\omega t + \phi)$

$i(0) = 0$

$i(t) = ? , t \geq 0.$

→ This is the step response of an RL-circuit as we've known before. The difference is that we have a sinusoidal source, V_s .

Writing the mesh equation (KVL):

$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$

The solution is:

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi + \theta) e^{-\left(\frac{R}{L}t\right)} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

where $\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$.

- The first term of this solution is called the "transient response".
 - The 2nd term of this solution is called the "Steady State Response".
 - Because for $t \geq 0$, the 1st term decreases rapidly, and the 2nd term starts to dominate.
 - So, the 1st term disappears after a while, and the 2nd term remains.
 - We can make the following conclusions for the steady state response:
 - 1) It is also sinusoidal.
 - 2) It has the same frequency as the source.
 - 3) Amplitude and phase change.
 - 4) The solution of the differential equation is rather long and complicated.
 - The remedy for conclusion 4 is to use "Phasors".
- Phasor = Complex number representation of the sinusoidal expressions to make mathematized computations easier.

- The phasor is a complex number that carries the amplitude and phase information of a sinusoidal function.

- It is based on the Euler's identity


$$e^{j\theta} = \cos\theta + j\sin\theta.$$

- Before moving further, let us study complex numbers:


Complex Numbers:

We show real numbers on the horizontal axis:

by addition, translate on real axis.

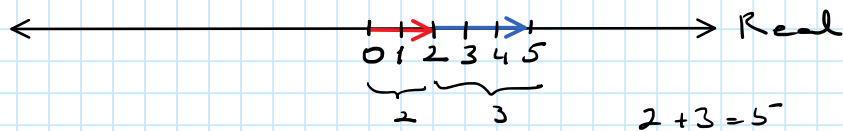


⇒ Subtraction is also

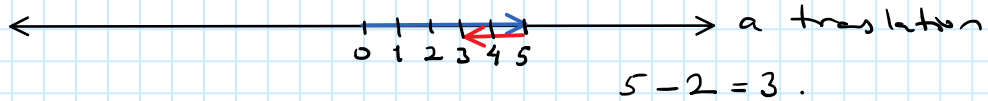


on the opposite direction.

Multiplication = scaling the number.

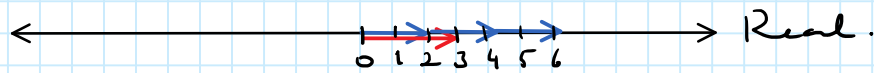

↑ is scaled by 3.

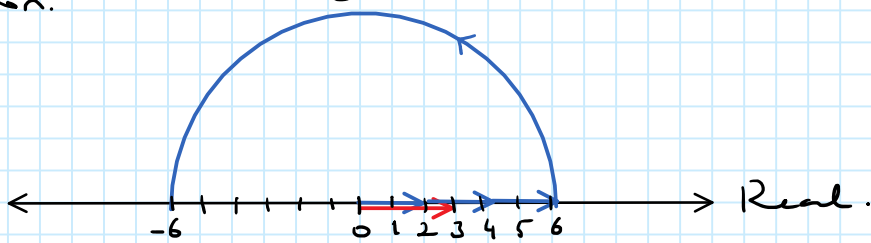
Multiplication by a "-" number: yields scaling + rotation.



$2 \times (-3) = -6$ (scaling + rotation)

Similarly, $(-6) \times (-1)$ means scaling + rotation.


$$(-6) \times (-1) = 6$$

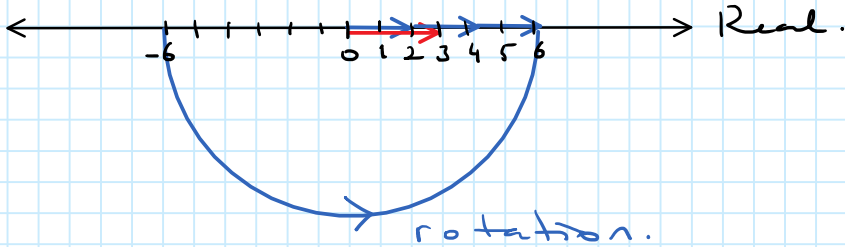


Division = Multyp:

$$6 \div (-3) = -2$$

\Rightarrow Scaling + rotation.

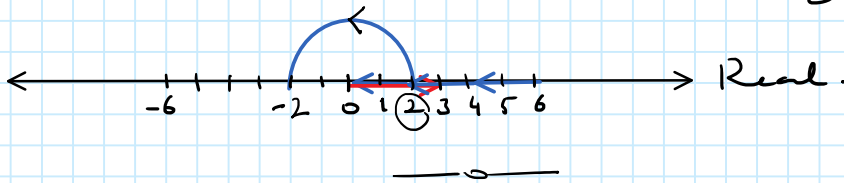

Let us consider the following case:

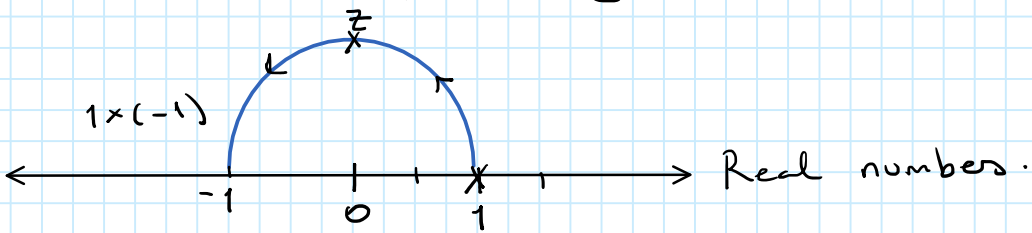

$$1 \times z \times z = -1$$


, z = the number that makes a quarter turn.

$$z^2 = -1$$


$$z = \sqrt{-1} = i$$


$$= j$$

For example,

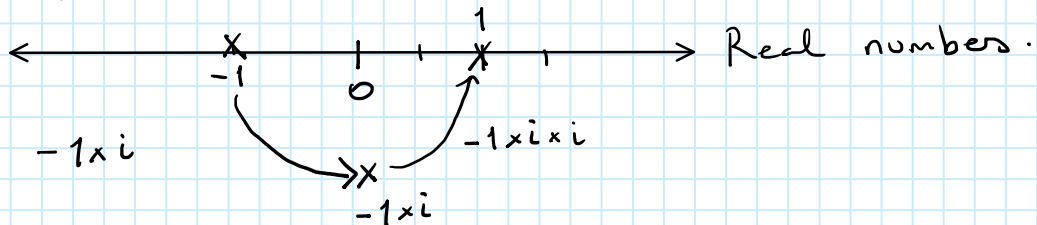


Now,

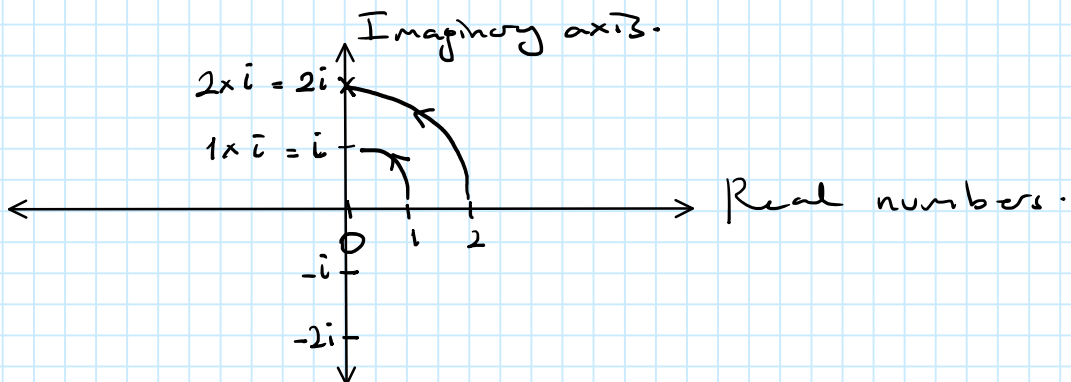

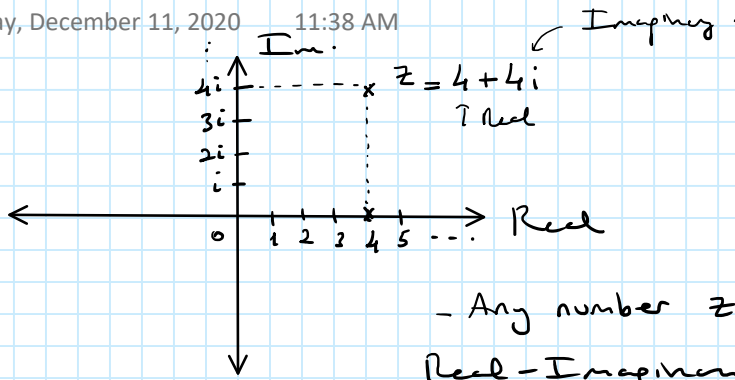


- Any number z on this
Reel-Imaginary plane is called
"complex numbers".

For example,

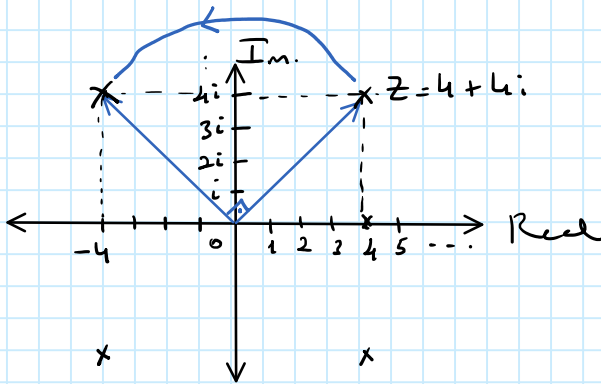

$$\begin{aligned} z \cdot \bar{z} &= i(4 + 4i) \\ &= 4i + 4(-1) \\ &= 4i - 4 \\ &= -4 + 4i \end{aligned}$$

Consider a case:

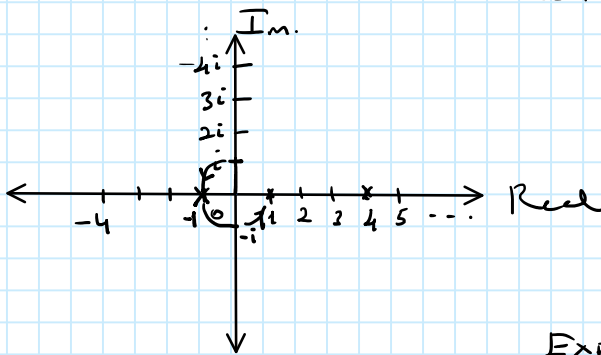


Let us take

$$\begin{aligned} z &= i \\ z \cdot z &= i \cdot i = -1 \\ z \cdot z \cdot z &= -1 \cdot z \\ &= -1 \cdot i = -i \\ z^4 &= -i \cdot (i) = 1 \end{aligned}$$

Exponentiating (powers)


or taking powers of a complex number rotates
ccw by the number.

For example:

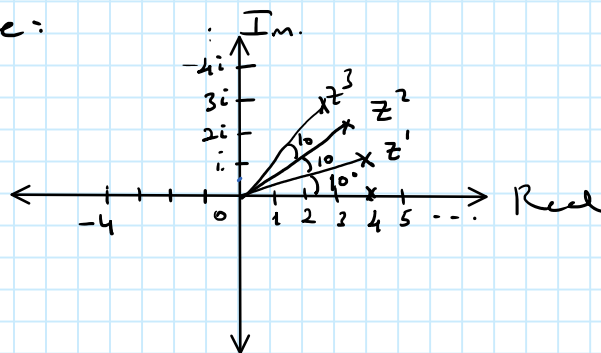

-Exam Review-

1-)

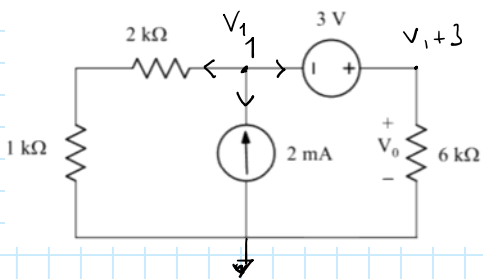

$V_0 = ?$

Node-voltage analysis:

KCL at node 1:

$$\frac{V_1}{3k} - 2mA + \frac{V_1+3}{6k} = 0$$

$$3V_1 + 3 = 12 \Rightarrow V_0 = V_1 + 3 = 6V.$$

$$3V_1 = 9$$

$$V_1 = 3V$$



or

$$\frac{V_1}{3k} + \frac{V_1+3}{6k} = 2mA$$

(2) (1)

$$\frac{2V_1 + V_1 + 3}{6k} = 2mA$$



2. Method: Source Transformation:

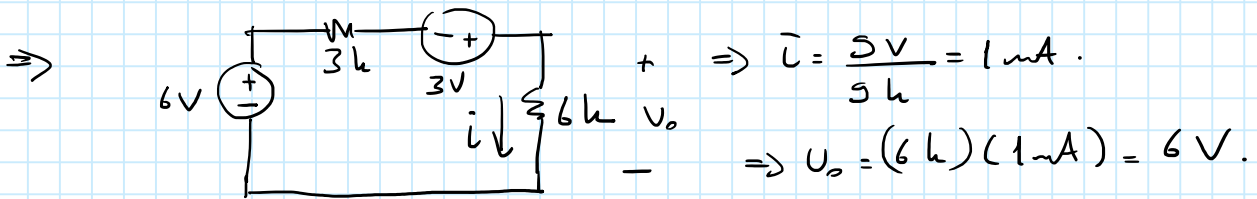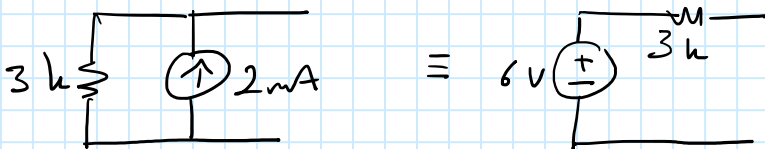

$$\Rightarrow \bar{i} = \frac{3V}{3k} = 1mA.$$

$$\Rightarrow V_0 = (6k)(1mA) = 6V.$$

2-)

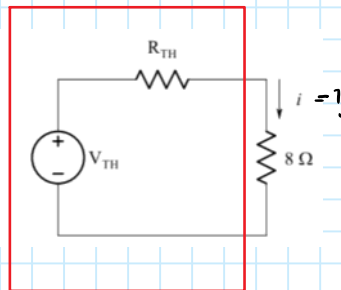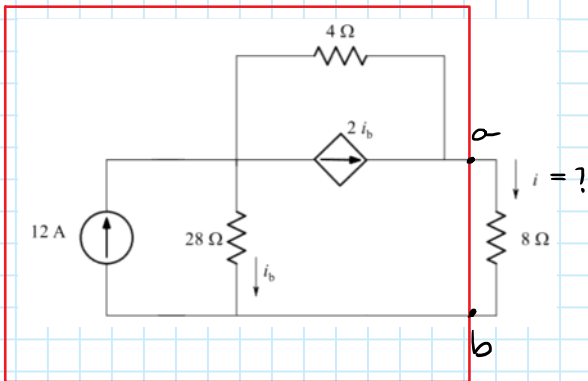

$$\Rightarrow \bar{i} = \frac{V_{TH}}{R_{TH} + 8}$$

$$V_{TH} = V_{oc}.$$

Using the node-voltage method:

KCL at node 1:

$$-12 + \bar{i}_b + 2\bar{i}_b - 2\bar{i}_b = 0$$

$$\Rightarrow \bar{i}_b = 12A.$$

$$\text{Also, } \frac{V_1}{28} = \bar{i}_b \Rightarrow V_1 = 28\bar{i}_b = 336V.$$


Ohm's law across 4Ω resistor:

$$V_{oc} - V_1 = 4(2i_b)$$

$$V_{oc} - 336 = 8(12)$$

$$\Rightarrow V_{oc} = U_{Th} = 336 + 96 = 432 \text{ V.}$$

To find R_{Th} :

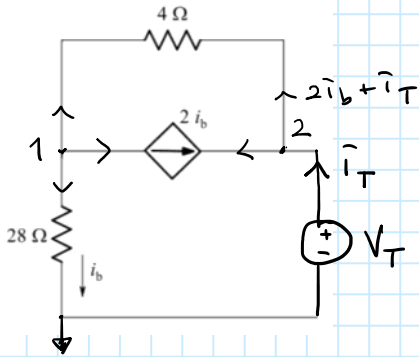

KCL at node 1:

$$i_b + 2i_b - (2i_b + i_T) = 0$$

$$3i_b - 2i_b - i_T = 0$$

$$\Rightarrow \boxed{i_T = i_b}$$

Ohm's law for 4Ω :

$$V_T - V_1 = 4(2i_b + i_T)$$


$$V_T - (28i_b) = 12i_b$$

$$\Rightarrow V_T = 40i_b$$

$$\Rightarrow \frac{V_T}{i_b} = R_{Th} = 40\Omega.$$

$$\Rightarrow i = \frac{V_{Th}}{R_{Th} + 8} = \frac{432}{40 + 8} = \frac{432}{48} = 9 \text{ A.}$$

3-)

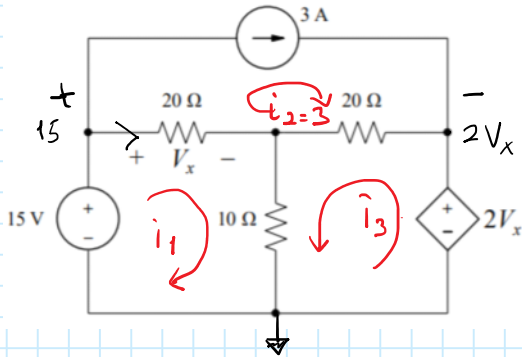

$V_x = ?$

KVL in mesh 1:

$$-15 + V_x + 10(i_1 + i_3) = 0 \quad (1)$$

Also,

$$V_x = 20(i_1 - 3) \quad (2)$$

KVL in mesh 3:

$$-2V_x + 20(i_3 + 3) + 10(i_3 + i_1) = 0 \quad (3)$$

KVL mesh 2:

$$20(3 + i_3) + 20(3 - i_1) + 15 - 2V_x = 0 \quad (4)$$

Using (1), (2) and (3):

$$V_x + 10i_1 + 10i_3 = 15 \quad (1)$$

$$V_x - 20i_1 = -60 \quad (2)$$


$$-2V_x + 10i_1 + 30i_3 = -60 \quad (3)$$

$$A \cdot \bar{x} = \bar{b} \Rightarrow \boxed{\bar{x} = A^{-1} \cdot \bar{b}}$$

$$\begin{bmatrix} 1 & 10 & 10 \\ 1 & -20 & 0 \\ -2 & 10 & 30 \end{bmatrix} \begin{bmatrix} V_x \\ i_1 \\ i_3 \end{bmatrix} = \begin{bmatrix} 15 \\ -60 \\ -60 \end{bmatrix}$$

$$\Rightarrow \boxed{V_x = 7.5 \text{ V}}, \quad i_1 = 3.375 \text{ A}, \quad i_3 = -2.625 \text{ A.}$$

2nd Method: KCL at node 1:

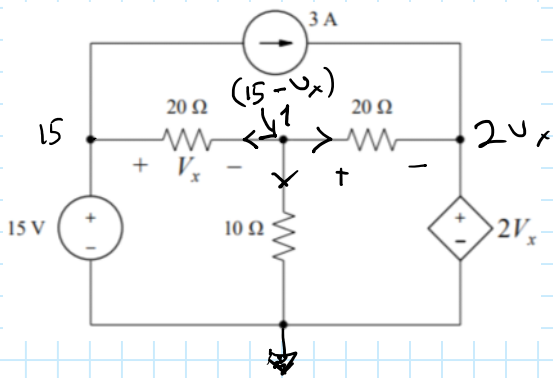

$$\frac{-V_x}{20} + \frac{(15-V_x)}{10} + \frac{(15-V_x) - 2V_x}{20} = 0$$

$$\frac{-V_x}{20} + \frac{15-V_x}{10} + \frac{15-3V_x}{20} = 0$$


(1) (2) (1)

$$-V_x + 30 - 2V_x + 15 - 3V_x = 0$$

$$45 = 6V_x$$

$$\Rightarrow V_x = 7.5V.$$

4-)

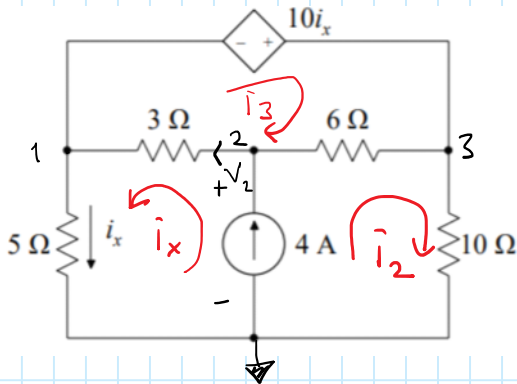

a-) $\bar{i}_x = ?$

Mesh current: (KVL)

Mesh \bar{i}_x :

$$-V_2 + 3(\bar{i}_x + \bar{i}_3) + 5\bar{i}_x = 0 \quad (1)$$

Mesh for \bar{i}_2 :

$$-V_2 + 6(\bar{i}_2 - \bar{i}_3) + 10\bar{i}_2 = 0 \quad (2)$$

KVL for mesh \bar{i}_3 :

$$-10\bar{i}_x + 6(\bar{i}_3 - \bar{i}_2) + 3(\bar{i}_3 + \bar{i}_x) = 0 \quad (3)$$

Also, $4 = \bar{i}_x + \bar{i}_2 \quad (4)$

Solving equations:

$$-V_2 + 8\bar{i}_x + 3\bar{i}_3 = 0 \quad (1)$$

$$-V_2 + 16\bar{i}_2 - 6\bar{i}_3 = 0 \quad (2)$$

$$-7\bar{i}_x - 6\bar{i}_2 + 5\bar{i}_3 = 0 \quad (3)$$


$$\bar{i}_x + \bar{i}_2 = 4 \quad (4)$$

$$\begin{bmatrix} -1 & 8 & 0 & 3 \\ -1 & 0 & 16 & -6 \\ 0 & -7 & -6 & 9 \\ 0 & 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_2 \\ \bar{i}_x \\ \bar{i}_2 \\ \bar{i}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 4 \end{bmatrix}$$

$$\bar{i}_x = 1.6A.$$

b-) $P = V_2 \cdot (4A) = (21.3) \cdot (4) = 85.3 \text{ W. delivered power}$
 $\quad \quad \quad = -85.3 \text{ W power.}$

5-)

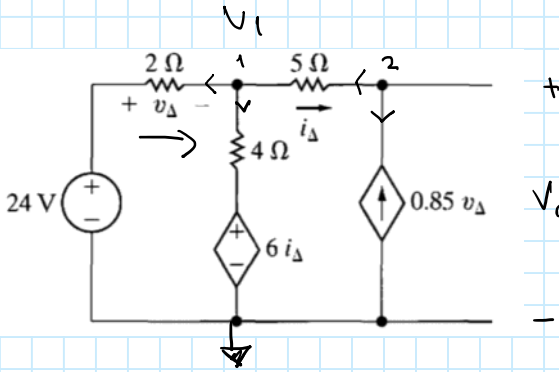

Using the nodal analysis:

KCL at node 1:

$$-\frac{V_\Delta}{2} + \frac{V_1 - 6i_\Delta}{4} + i_\Delta = 0 \quad (1)$$

Also,

$$24 - V_1 = V_\Delta \quad (2)$$

$$V_\Delta + V_1 = 24$$

KCL at node 2:

$$-i_\Delta - 0.85V_\Delta = 0 \quad \text{or} \quad i_\Delta = -0.85V_\Delta \quad (3)$$

Re-writing the equations:

$$-\frac{V_\Delta}{2} + \frac{V_1 - 6i_\Delta}{4} + i_\Delta = 0 \Rightarrow -2V_\Delta + V_1 - 6i_\Delta + 4i_\Delta = 0$$

$$-2V_\Delta + V_1 - 2i_\Delta = 0 \quad (1)$$

$$V_\Delta + V_1 = 24 \quad (2)$$

$$0.85V_\Delta + i_\Delta = 0 \quad (3)$$

$$V_\Delta = x, \quad V_1 = y, \quad i_\Delta = z$$


$$V_\Delta = \frac{240}{13}, \quad V_1 = \frac{72}{13}, \quad i_\Delta = \frac{-264}{13}$$

$$\Rightarrow V_\Delta = 18.46V, \quad V_1 = 5.54V, \quad i_\Delta = -15.7$$

$$\Rightarrow V_1 - V_{Th} = 5i_\Delta$$

$$\text{or} \quad V_{Th} = V_1 - 5i_\Delta = 5.54 - 5(-15.7) = 84V.$$

R_{Th}:

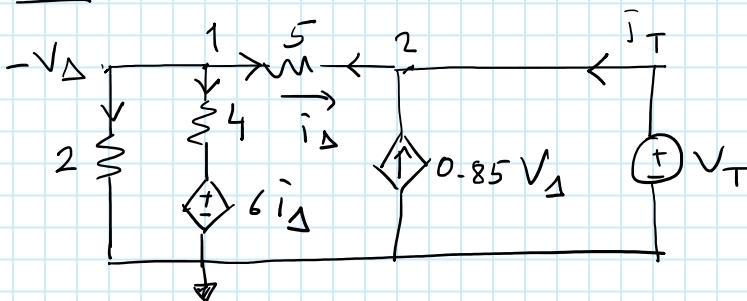

KCL at node 1:

$$-\frac{V_\Delta}{2} + \frac{-V_\Delta - 6i_\Delta}{4} + i_\Delta = 0 \quad (1)$$

KCL at node 2:

$$-i_\Delta - 0.85V_\Delta - i_T = 0 \quad (1)$$

Also,

$$-V_\Delta - V_T = 5i_\Delta \quad (\text{ohm's law for } 5\Omega)$$

Re-writing the equations:

$$-3V_{\Delta} - 2\hat{i}_{\Delta} = 0 \quad \text{--- (1)} \rightarrow \hat{i}_{\Delta} = \left(-\frac{3}{2} \cdot V_{\Delta}\right)$$

$$2 / 0.85V_{\Delta} + \hat{i}_{\Delta} + \hat{i}_T = 0 \quad \text{--- (2)} \rightarrow 1.7V_{\Delta} + 2\hat{i}_{\Delta} + 2\hat{i}_T = 0$$

$$V_{\Delta} + 5\hat{i}_{\Delta} + V_T = 0 \quad \text{--- (3)}$$

(1) + (2) gives:

$$-1.3V_{\Delta} + 2\hat{i}_T = 0 \quad \text{--- (4)}$$

$$\left| V_{\Delta} = \frac{2}{1.3} \hat{i}_T \right|$$

Substitute in (3)


$$\frac{2}{1.3} \hat{i}_T + 5 \left(-\frac{3}{2} \cdot \frac{2}{1.3} \hat{i}_T \right) + V_T = 0$$

$$\Rightarrow \frac{V_T}{\hat{i}_T} = 10 \Omega = R_{Th}$$

$$b-) P = \frac{V_{Th}^2}{4R_{Th}} = \frac{84^2}{4 \cdot 10} = 176.4 \text{ W}$$

- Final Exam Preparation -

Ex:

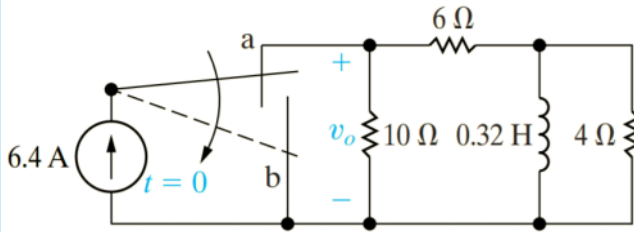

For $t < 0$:

$$i_0(0) = 6.4 \cdot \frac{10}{(10+6)} = 6.4 \cdot \frac{10}{16} = 4.$$

For $t > 0$:

$$R_{th} = (10+6) \parallel 4 = 16 \parallel 4 = \frac{16 \cdot 4}{20} = 3.2 \text{ ohm}.$$

Also,

$$i_f = 0.$$

Also,

$$\tau = L/R = 0.32/3.2 = 0.1 \text{ s}.$$

Using the general solution expression:

$$i(t) = i_f + (i(0) - i_f) \cdot \exp(-t/\tau)$$

Or

$$i(t) = 0 + (4 - 0) \cdot \exp(-t/0.1) = 4 \cdot \exp(-10t) \text{ A}.$$

To find v_0 :

Using current division:

$$i_1(t) = i(t) \cdot \frac{4}{(10+6+4)} = i(t) \cdot \frac{1}{5} = \frac{4}{5} \cdot \exp(-10t) \text{ A}, t > 0.$$

From the Ohm's law,

$$v_0(t) = -10 \cdot i_1(t) = -8 \exp(-10t) \text{ V}, t > 0.$$

b) $P(t) = i^2(t) \cdot R$

$$E = \int_0^\infty P(t) dt = \left(\frac{1}{2}\right) L \cdot i(0)^2 = 0.5 \cdot 0.32 \cdot 4^2 = 2.56 \text{ J}.$$

$$E = \int_0^\infty i_1^2(t) \cdot R dt = 0.512 \text{ J}$$

$$E_{ohm} = 2.56 - 0.512 = 2.048 \cdot 100 / 2.56 = 80\%.$$

5 Questions

3 questions

for circuit analysis

- 1-) Node-voltage
- 2-) Mesh-current
- 3-) Thevenin, Norton
- 4-) Max. power transfer.

2 questions

1-) RL-RC circuits


natural & step response. (switching)

2-) RLC circuit:

Parallel or Series:

3-) RMS → square, triangular, etc...

Ex:

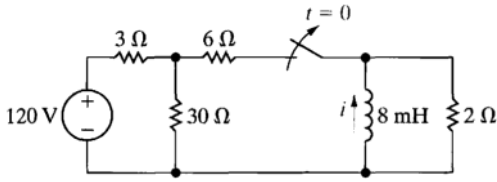

Find $i(t)$, $t \geq 0$.

Natural (discharge) or ~~step~~ (charge)

Ans:


$$x(t) = x_f + [x(t_0) - x_f] e^{-(t-t_0)/\tau}$$

$$i(t) = i_f + (i_0 - i_f) e^{-(t-0)/\tau} \quad , \tau = \frac{L}{R} \text{ (sec.)}$$

i_f = Final value of i

i_0 = Initial " " " = $i(0^-) = i(0^+)$

For $t < 0$:

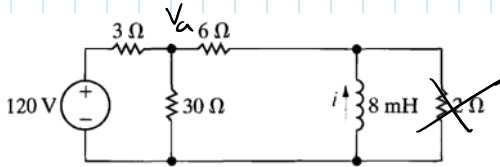

$$R = 6 || 30 = \frac{6 \cdot 30}{3+6} = 5 \Omega$$

$$V_a = 120 \cdot \frac{5}{3+5} = \frac{120 \cdot 5}{8} = 75 \text{ V}$$


$$i_0 = -\frac{V_a}{6} = -\frac{75}{6} = -12.5 \text{ V}$$

Also,


$$i_f = 0$$

To find $\tau = \frac{8 \text{ mH}}{2 \Omega} = 4 \text{ ms}$.
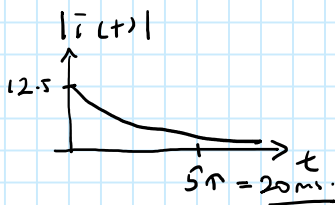
$$\Rightarrow i(t) = -12.5 e^{-\frac{t}{4 \text{ ms}}} = -12.5 e^{-0.25 \times 1000 t} = -12.5 e^{-250 t} \text{ A}, t \geq 0$$



Ex:

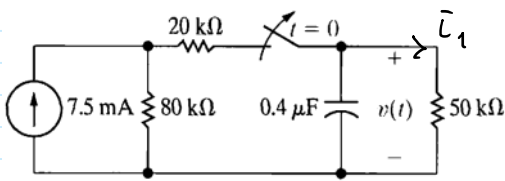

Find $v(t)$ for $t \geq 0$?

Ans:

$V_0 = ?$

From the current division:

$$i_1 = (7.5 \times 10^{-3}) \times \frac{80 \text{ k}\Omega}{80 \text{ k}\Omega + 50 \text{ k}\Omega} = \frac{8}{13} \cdot \frac{8}{15} \text{ mA} = 4 \text{ mA}$$


$$V_0 = (50 \text{ k}\Omega)(i_1) = (50 \text{ V})(4 \text{ mA}) = 200 \text{ V}$$

$V_f = 0$

$\tau = RC = (50 \text{ k}\Omega)(0.4 \mu\text{F}) = 20 \text{ ms}$

$\Rightarrow v(t) = 200 e^{-\frac{t}{20 \text{ ms}}} = 200 e^{-50 t} \text{ V}$

Ex:

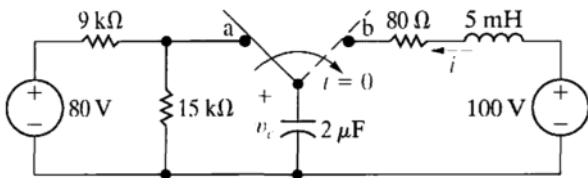

Find $v_c(t)$, $t \geq 0$.

Ans:

Series RLC circuit, step response.

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{where } \alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \alpha = \frac{80}{2 \times 8 \times 10^{-3}} = \frac{8}{10^{-3}} = 8000 \Rightarrow \alpha^2 = 64 \times 10^6$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(5 \times 10^{-3})(2 \times 10^{-6})} = \frac{1}{10 \times 10^{-9}} = \frac{10^9}{10} = 10^8$$

$\omega_0^2 > \alpha^2 \Rightarrow$ underdamped!

$$s_{1,2} = -8000 \pm \sqrt{64 \times 10^6 - 10^8} = -8000 \pm j6000$$

The response is for $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^8 - 64 \times 10^6} = 6000 \text{ rad/s}$.

$$v_c = V_f + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t)$$

P80

Friday, December 25, 2020 11:31 AM

To find B_1' and B_2' :

$$V_C(0) = V_C(0^-) = 80 \cdot \frac{15}{15+5} = 80 \cdot \frac{15}{20} = 50 \text{ V.} = 100 + B_1'$$

$$B_1' = -50 \text{ V.}$$



$$\frac{dV_C(0^+)}{dt} = \frac{1}{C} i(0^+) = 0 = 6000 B_2' - 2 B_1'$$

$$6000 B_2' = 8000(-50)$$

$$B_2' = \frac{8}{6}(-50) = -\frac{400}{6} = -66.67.$$

$$\Rightarrow V_C(t) = 100 - 50 e^{-8000t} \cos(6000t) - 66.67 e^{-8000t} \sin(6000t) \text{ V.}$$

Ex:

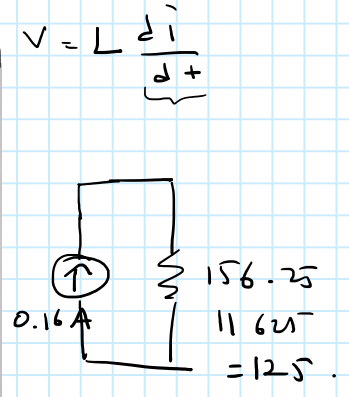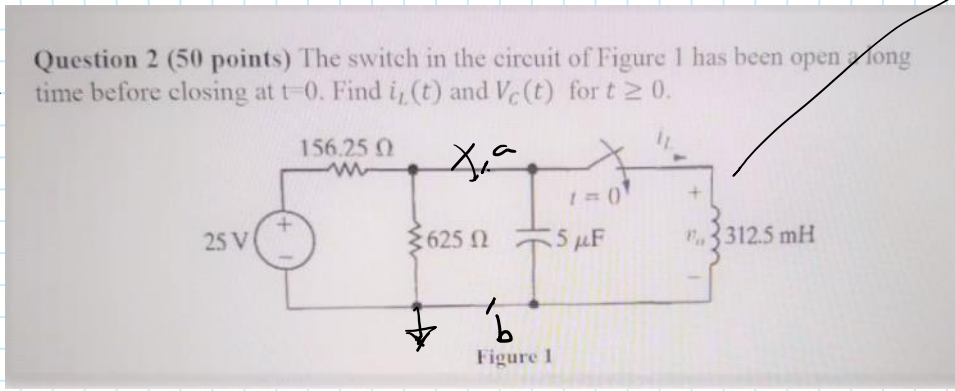

Step Response of Parallel RLC Circuit:

1-) $i_L(0) = 0 \Rightarrow i_L(0^+) = 0$, $i_C(0^+) =$ $i_C = C \frac{dV_C}{dt}$

$V_C(0) = 25 \cdot \frac{625}{625 + 156.25} = 20 \text{ V} \Rightarrow V_C(0^+) = 20 \text{ V}$

$V = L \frac{di_L}{dt} \Rightarrow V(0^+) = L \frac{di_L(0^+)}{dt} \Rightarrow \frac{di_L(0^+)}{dt} = \frac{20000}{312.5} = 64$

2-) $\omega_0^2 = \frac{1}{LC} = \frac{1}{(312.5 \times 10^{-3})(5 \times 10^{-6})} = 640000 \text{ rad}^2/\text{s}^2$

$\alpha = \frac{1}{2RC} = \frac{1}{2(125)(5 \times 10^{-6})} = 800 \text{ rad/sec}$

or $\alpha^2 = 640000$

$\Rightarrow \omega_0^2 = \alpha^2 \Rightarrow$ Critically damped!

3-) $S_{1,2} = -\alpha = -800$

$i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$, $t \geq 0$

$i_L(0^+) = 0.16 + D_2' = 0 \Rightarrow D_2' = -0.16$

$\frac{di_L(0^+)}{dt} = D_1' e^{-\alpha t} + D_1' t (-\alpha) e^{-\alpha t} + D_2' (-\alpha) e^{-\alpha t} = 64$

$D_1' + D_2' (-\alpha) = 64$
 $D_1' = 64 - (0.16)(800) = -64$

$\Rightarrow i_L(t) = 0.16 - 64t e^{-800t} - 0.16 e^{-800t} \text{ A} , t \geq 0$

$V = L \frac{di_L(t)}{dt} = (312.5 \times 10^{-3}) \left[-64 e^{-800t} - 64t(-800) e^{-800t} + 0.16(800) e^{-800t} \right]$
 $= e^{-800t} \left[(0.16(800) - 64) \cdot (312.5 \times 10^{-3}) \right] + 64(800)t e^{-800t} \cdot (312.5 \times 10^{-3}) \text{ V}$
 $= 2000 e^{-800t} \cdot 11.625 + 0.16 e^{-800t} \text{ V}$

$$= 20e^{-800t} + 16000te^{-800t} \text{ V.}$$