

# EE205 Lecture Notes:

P1

26 Eylül 2020 Cumartesi 17:16

Electric potential (voltage): Work done by charges  $= \frac{E}{q}$   
 $E$  = Electric potential energy. (Joules) = Work capacity  
 $q$  = charge. (Coulombs)  $\downarrow$   
F.d.

$$\text{Current} = \frac{q}{t} \text{ (A)} = I$$

$q$  = charge.


$t$  = time. (sec.)

$$\text{Power} = \frac{E}{t} \text{ (Watts)} = \underbrace{\frac{E}{q}}_V \cdot \underbrace{\frac{q}{t}}_I = V \cdot I \text{ (W)}.$$

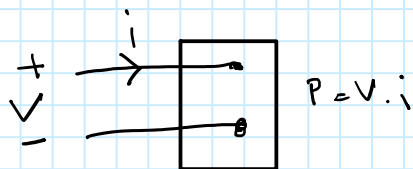
## I deal Basic Circuit Elements:

It is an electrical component with the following Properties:

- 1-) Two terminals.
- 2-) Can be described as voltage or current.
- 3-) Can not be subdivided into other elements.



Symbol for  
ideal circuit element.

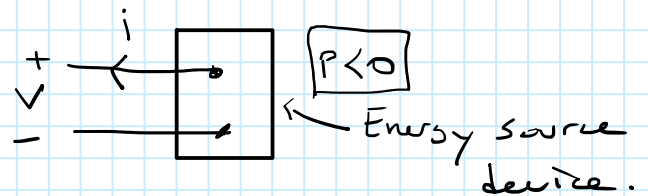

If the current is going out of the circuit element, this refers to the existence of an energy source (generator).

If the power consumption by the element is positive, ( $P > 0$ ), the power is being delivered to the circuit inside the box.

If the power is negative,  $P < 0$ , the power is being extracted from the circuit inside the box.







## Chapter 2 : Circuit Elements :

There are two circuit elements, voltage and current sources.

- Ideal voltage source: Provides a constant voltage across its terminals regardless of the current.
- Ideal current source: Similar to the voltage source. It provides current across its terminals regardless of the voltage.

If circuit elements do not depend on any other parameter, they are called "independent sources".

Circuit symbols:

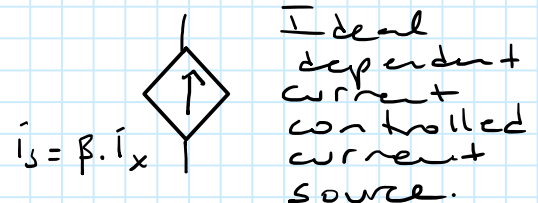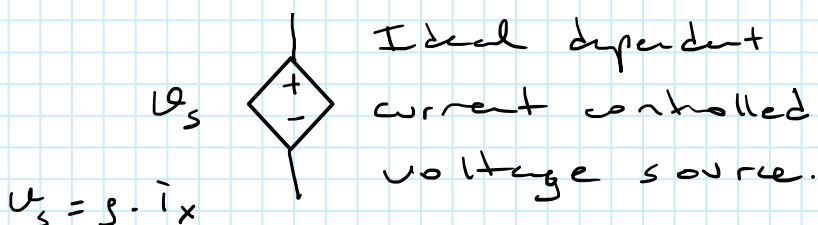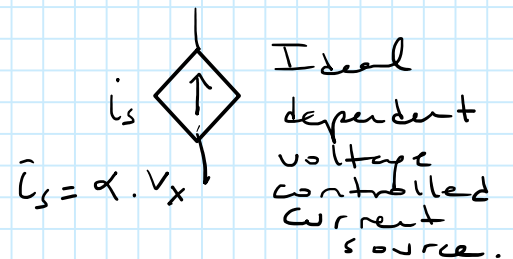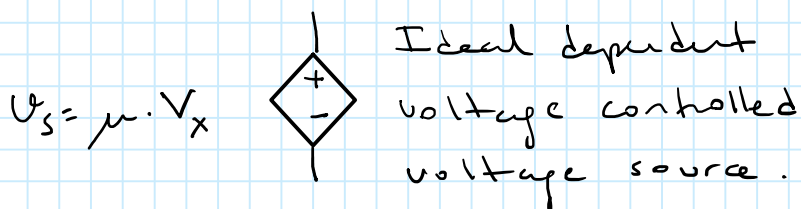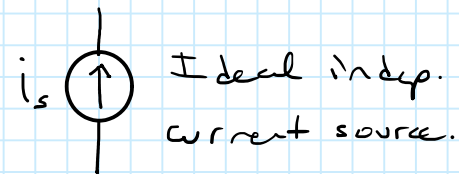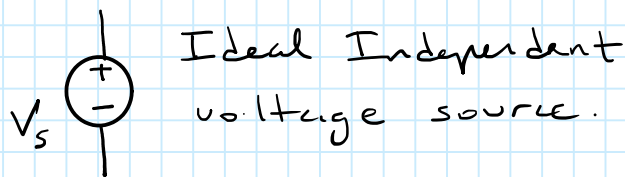


# P2a

16 Ekim 2020 Cuma 09:22


## Constraints for the Connection of Circuit Elements:

- Two voltage sources:

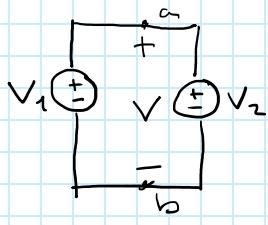


$$\Rightarrow \boxed{V_1 = V_2} = V$$


Also, the polarities must be the same.

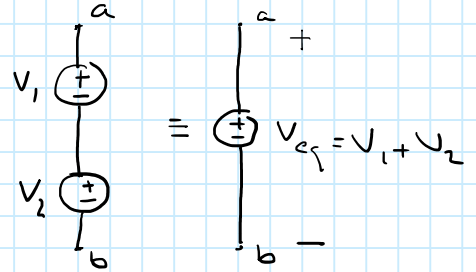

- Two current sources:


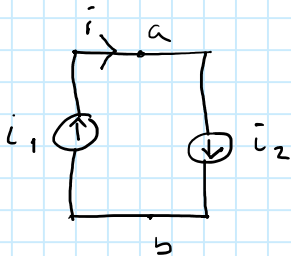

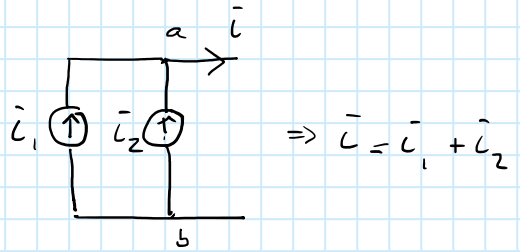
$$\Rightarrow \boxed{\bar{i}_1 = \bar{i}_2} = i$$




Ex:


Determine which connections are valid.

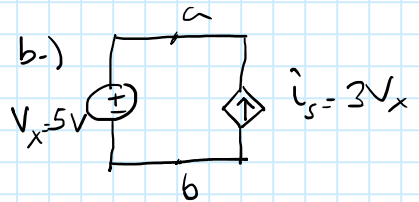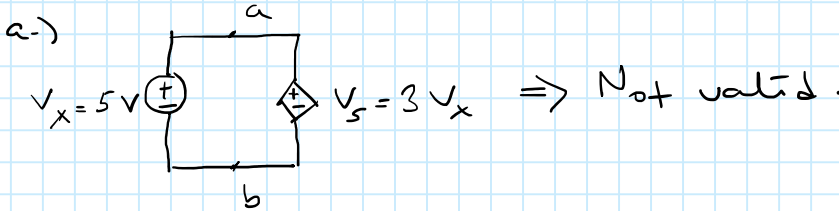

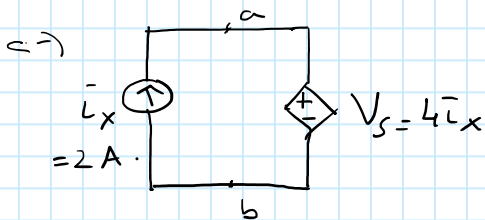$\Rightarrow$  Ideal voltage source supplies the same voltage regardless of the current, and vice versa. Thus, this is valid.



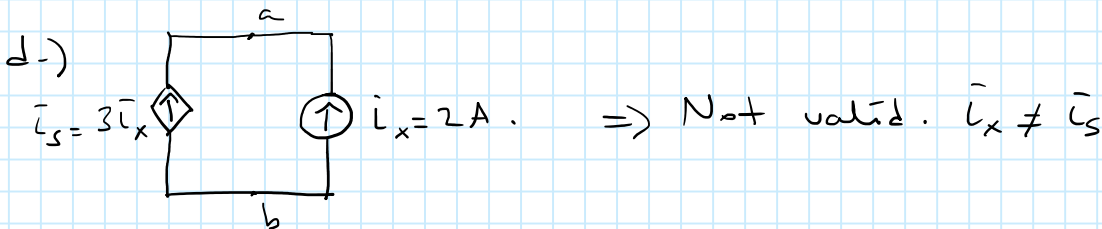$\Rightarrow$  Valid. Because of the same reason in part b.



Two important concepts:

- Active element: A device capable of generating electrical energy. ( $P < 0$ )
- Passive element: A device that can not generate electrical energy. ( $P > 0$ ). Examples: Resistors, inductors, capacitors. (lumped elements).


Resistance: ("R")

is the capacity of materials to resist the current flow. (impede, oppose)


Ohm's law:  $V = I \cdot R$

Reciprocal of resistance is called "conductance" with a symbol "G".
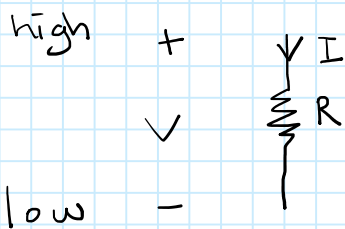
$$\Rightarrow G = \frac{1}{R} \text{ (Siemens or } \Omega^{-1} \text{)} \quad R \text{ (}\Omega = \text{ohm)} \\ \text{("mho")}$$



$$V = IR$$

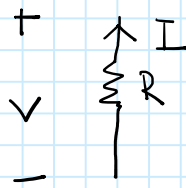

$$V = -IR$$

$$G = \frac{1}{R} \cdot (S)$$





$$P = VI = I^2 R \text{ (W)}$$

Also,  $P = \frac{V^2}{R} \text{ (W)}$

$$I = VG$$

Ex:

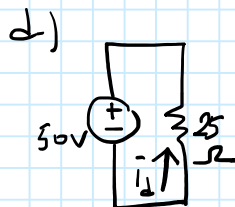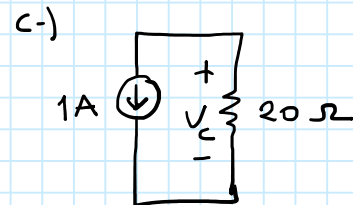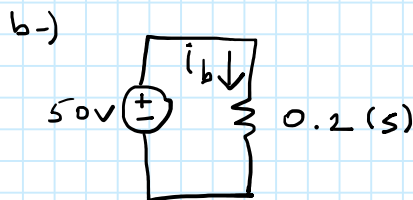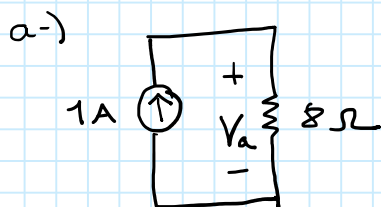Calculate the values of  $v$  and  $i$ , and determine the power dissipated in each resistor.



Ans:


a-)  $V_a = i \cdot R = (1A)(8\Omega) = 8V$ ,  $P_{8\Omega} = \frac{V^2}{R} = \frac{8^2}{8} = 8 \text{ Watts}$ .

b-)  $i_b = \frac{V}{R} = V \cdot G = (50V)(0.2S) = 10A$ ,  $P_{0.2S} = V^2 G = 500W$ .



**Delta to Wye Equivalent Circuits:**



Consider the following circuit:

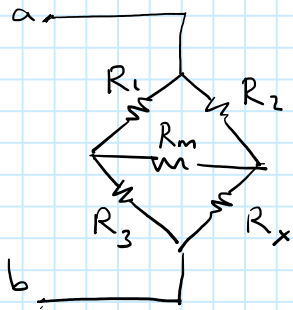

⇒ The resistors  $R_1, R_2, R_m$  or  $R_3, R_m, R_x$  are called "Delta ( $\Delta$ )" connection.

⇒ The resistors  $R_1, R_m, R_3$  or  $R_2, R_m, R_x$  are called "Wye ( $\gamma$ )" connection.

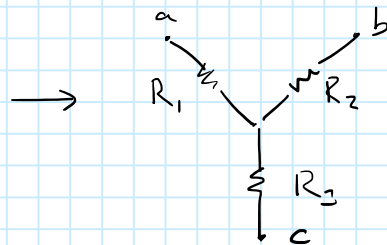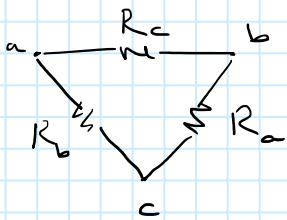**$\Delta$  to  $\gamma$  Transformation:**



where

$$R_1 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$


Also,

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}, \quad R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

Ex:

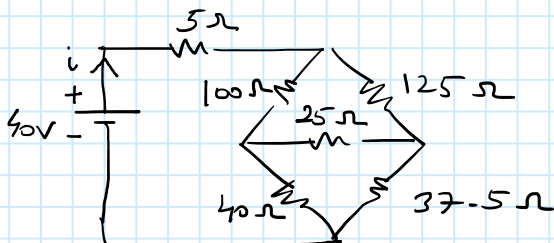Find the current and power supplied by the 40V source.



$$R_{eq} = \frac{1}{\frac{1}{50} + \frac{1}{56}} = \frac{1}{\frac{100}{2500}} = \frac{2500}{100} = 25\Omega$$


Ans:

First, replace the upper delta circuit ( $100\Omega, 125\Omega, 25\Omega$ ) by its  $\gamma$ -equivalent.

$$\Rightarrow R_1 = \frac{100 \cdot 125}{250} = 50\Omega, \quad R_2 = \frac{125 \cdot 25}{250} = 12.5\Omega, \quad R_3 = \frac{100 \cdot 25}{250} = 10\Omega$$

$$\Rightarrow R_{eq} = 5 + 50 + (10 + 40) \parallel (12.5 + 37.5)$$
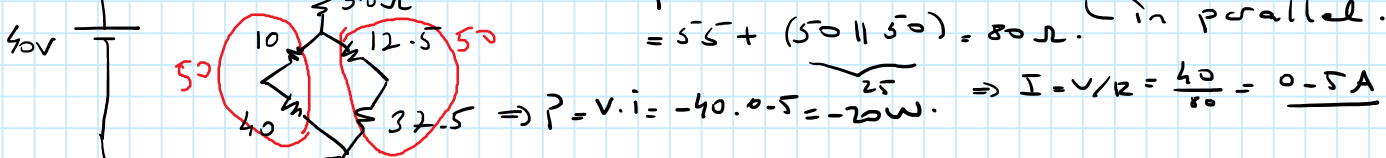
$$= 55 + (50 \parallel 50) = 80\Omega \quad \text{in parallel.}$$



$5V$   
 $40$   
 $37.5$   $\Rightarrow P = V \cdot i = -40 \cdot 0.5 = -20W$ .  $\Rightarrow I = V/R = \frac{40}{80} = \underline{0.5A}$

$$c-) V_c = i \cdot R = \underbrace{- (1A)}_i (20 \Omega) = \underbrace{-20V}_V, \quad P_{20\Omega} = \frac{V^2}{R} = \frac{(-20)^2}{20} = 20W.$$

$$d-) i_d = \frac{V}{R} = \frac{-50V}{25\Omega} = -2A. \quad P = \frac{V^2}{R} = \frac{(-50)^2}{25} = 100W.$$


"-" sign indicates that the original selection of the current direction is really the opposite.

$$V = -i_d(25)$$

$$\text{or } 50 = -i_d(25) \Rightarrow i_d = -2A$$

### Kirchoff's Laws:

Suppose we have the following circuit,

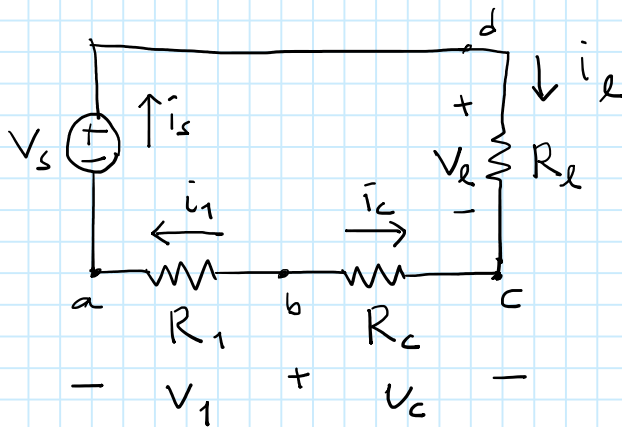

$$V_1 = i_1 R_1$$

$$V_c = i_c R_c$$

$$V_d = i_d R_d$$

We consider leaving currents positive, and entering currents negative.

### Kirchoff's Current Law (KCL):

The algebraic sum of the currents at any point in a circuit is zero.

At point a:

$$i_s - i_1 = 0$$

At point b:

$$i_1 + i_c = 0$$

At point c:

$$-i_c - i_d = 0$$

At point d:

$$i_d - i_s = 0$$

Note that initial assumption of currents and voltages are not important. At the end of the solution, we get results which are + or -, indicating the real directions.

## Kirchoff's Voltage Law (KVL):

The algebraic sum of all the voltages around any closed path in a circuit is zero.

Closed path: dcbad (we follow clockwise direction.)

$$V_L - V_C + V_1 - V_S = 0 \quad (\text{KVL equation.})$$


(+  $\rightarrow$  - is always positive.)

Closed path: dabcd (ccw)

$$V_S - V_1 + V_C - V_L = 0 \quad (\text{The same equation as before.})$$

Ex:

Given the circuit below:

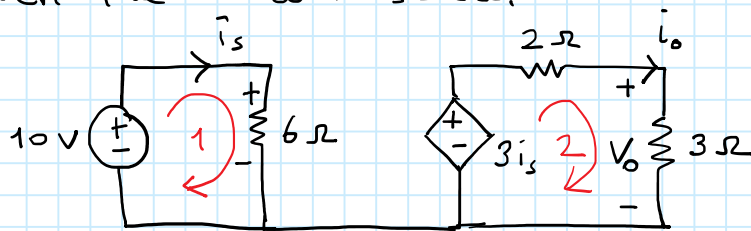

a-) Find  $V_o$  from KVL and Ohm's law.

b-) Show that  $P_{\text{total}} \Big|_{\text{dissipated}} = P_{\text{total}} \Big|_{\text{developed}}$  (Conservation of energy.)

Ans:

a-) KVL in loop 1:

$$-10V + 6i_s = 0$$

$$\Rightarrow i_s = \frac{10}{6} = \frac{5}{3} \text{ A.}$$

Also, KVL for loop 2:

$$-3i_s + 2i_o + V_o = 0$$

$$-5 + 2i_o + V_o = 0$$

Ohm's law:

$$V_o = 3i_o$$

Thus,

$$-5 + 2i_o + 3i_o = 0$$

$$5i_o = 5$$

$$\Rightarrow i_o = 1 \text{ A.}$$

$$\text{Then, } V_o = 3i_o = 3 \text{ V.}$$

b-) Power for indep. voltage source:

$$P = Vi = (10V) \cdot i_s = 10 \cdot \left(\frac{5}{3}\right) = -16.7 \text{ W}$$

Also,

$$P_{6\Omega} = vi = (10V) i_s = 16.7 \text{ W.}$$

$$P_{2\Omega} = i^2 R = i_o^2 (2) = (1)^2 (2) = 2 \text{ W.}$$

$$P_{3\Omega} = i^2 R = i_o^2 (3) = (1)^2 (3) = 3 \text{ W.}$$


Power delivered by the dependent source:

$$P = v \cdot i = (-3 \hat{i}_z) (1 \hat{i}_0) = -3 \cdot \frac{5}{3} \cdot (1A) = -5 \text{ W.}$$

Electric Shock:

Electric current flow through the human body. In many cases, the current flows from head towards feet passing through heart. This causes heart to stop beating (fibrillation).

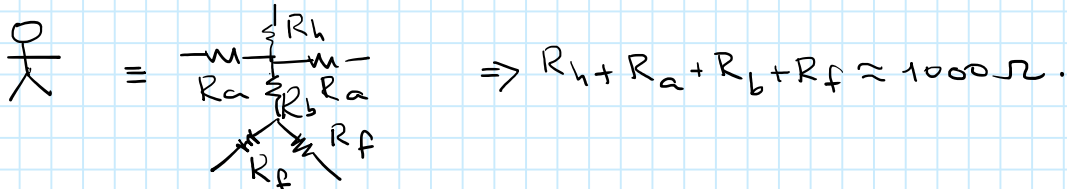Majority of 220V contacts, electric shocks result in fibrillation. This also depends on the time of exposure and the body resistance.



Dangerous limits of currents:

For AC current: 3-5 mA amplitude  $\rightarrow$  barely acceptable.

Amplitude  $> 30$  mA is the limit. and always risk of life.

For DC current:  $I > 300-500$  mA


is the limit for danger of life.

Ex:

A person with a dry body gets electric shock with 220V. Find the current passing through his body?

Ans:

$$I = \frac{V}{R} = \frac{220}{1000} = 0.22 \text{ A} = 220 \text{ mA} > 30 \text{ mA (dangerous)}$$

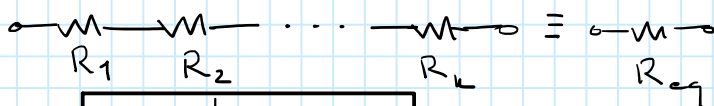Resistive Circuits:Resistors in Series:


$$R_{eq} = \sum_{i=1}^k R_i \text{ (}\Omega\text{)}$$

Resistors in Parallel:

$$R_{eq} = \frac{1}{\sum_{i=1}^k \left(\frac{1}{R_i}\right)} \text{ (}\Omega\text{)}$$
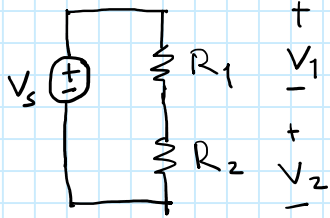
## Voltage Divider:


- Short method to find voltages when several resistors are connected in series.



$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_s \cdot \frac{R_2}{R_1 + R_2}$$

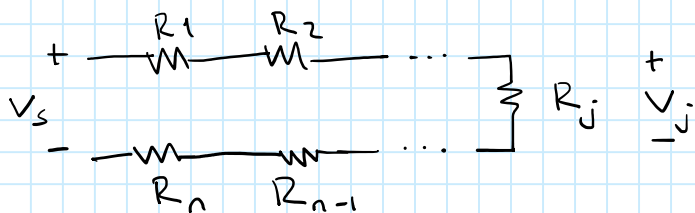In case of  $n$  resistors connected in series:




$$V_j = V_s \cdot \frac{R_j}{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + \dots + R_n$$
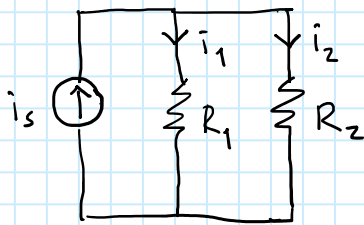
## Current Divider:


It is a rule for finding the current passing through the resistors which are connected in parallel.



$$i_1 = i_s \cdot \frac{R_2}{R_1 + R_2}$$

$$i_2 = i_s \cdot \frac{R_1}{R_1 + R_2}$$

For general current division, we have:

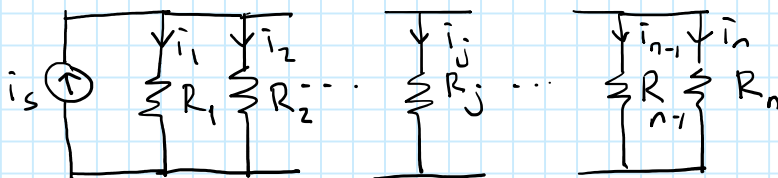


$$i_j = i_s \cdot \frac{R_{eq}}{R_j}$$


where

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

Ex:

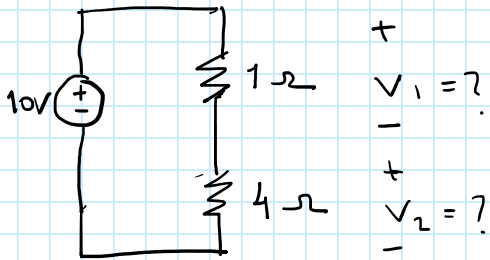

Ans:

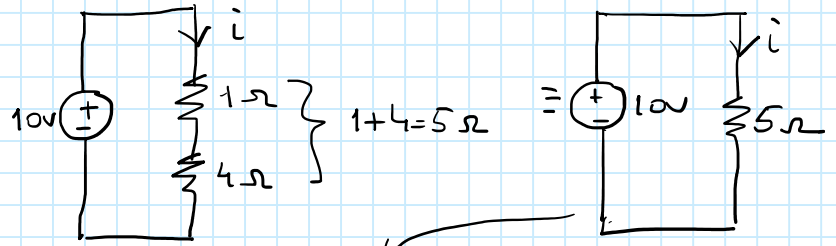

$$i = \frac{V}{R} = \frac{10}{5} = 2 \text{ A.}$$

$$V_1 = i \cdot R_1 = (2)(1) = 2 \text{ V.}$$


$$V_2 = i \cdot R_2 = (2)(4) = 8 \text{ V}$$

By using the voltage division rule:

$$V_1 = 10 \cdot \frac{1}{1+4} = \frac{10}{5} = 2 \text{ V.}$$

$$V_2 = 10 \cdot \frac{4}{1+4} = 10 \cdot \frac{4}{5} = 8 \text{ V.}$$

Ex:

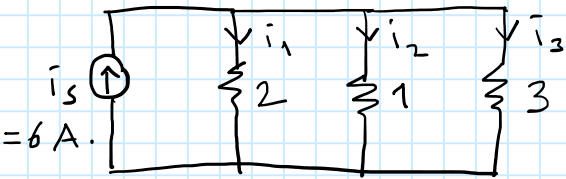

Find  $i_1$ ,  $i_2$  and  $i_3$  ?

Ans:


$$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{1} + \frac{1}{3}} = \frac{1}{\frac{3+6+2}{6}} = \frac{6}{11} \Omega.$$

$$i_1 = i_s \cdot \frac{R_{eq}}{R_j} = 6 \cdot \frac{6}{11} \cdot \frac{1}{2} = \frac{18}{11} = 1.636 \text{ A.}$$

$$i_2 = 6 \cdot \frac{6}{11} \cdot \frac{1}{1} = \frac{36}{11} = 3.273$$

$$i_3 = 6 \cdot \frac{6}{11} \cdot \frac{1}{3} = \frac{12}{11} = 1.1$$

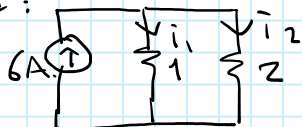IF we had:  $i_1 + i_2 + i_3 = 1.636 + 3.273 + 1.1 = 6 \text{ A} = i_s. \text{ (KCL) } \checkmark$



$$\Rightarrow i_1 = i_s \cdot \frac{2}{1+2} = 6 \cdot \frac{2}{3} = 4 \text{ A.}$$

$$i_2 = 6 \cdot \frac{1}{3} = 2 \text{ A.}$$




Cp. 4. Techniques of Circuit Analysis:

In a given circuit with some nodes and closed loops, we use the KCL, KVL and Ohm's law to derive algebraic equations. Then, we solve these equations simultaneously to find the unknown voltages and/or currents.

1-) Node-Voltage Method:


Suppose we have the following circuit:

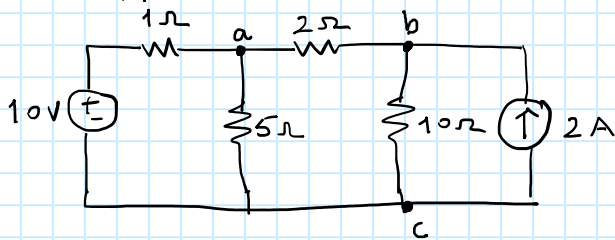

Step 1: Simplify the circuit such that no branches cross over and we can mark the essential nodes. (3 nodes in this case.)


Step 2:

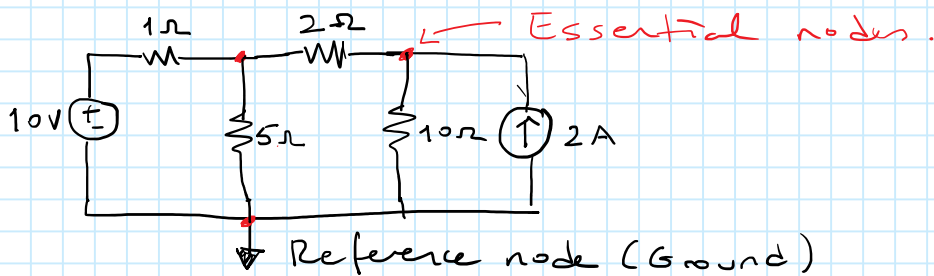Select one of the nodes as a reference node. The node with most branches is usually taken as the reference node. (In this case, it is the lower node.)




Step 3:

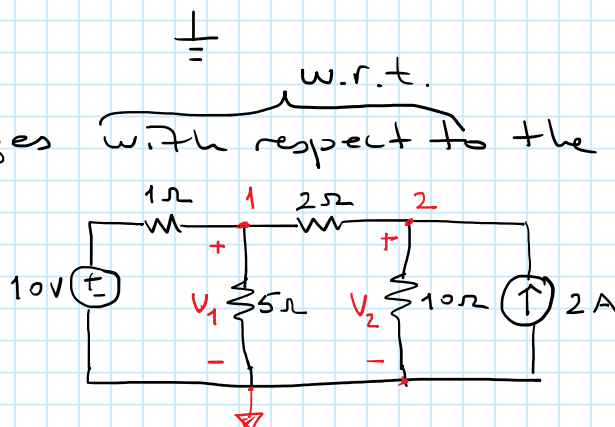Define node voltages with respect to the reference node. Thus, we have



Step 4:

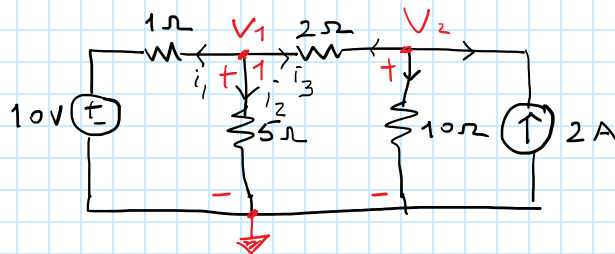Generate node-voltage equations by:  
Writing the node equations for each node employing the leaving current convention.



KCL at node 1 gives:

$$i_1 + i_2 + i_3 = 0$$

$$\downarrow \qquad \qquad \downarrow$$

$$\frac{V_1 - 10}{1\Omega} + \frac{V_1}{5\Omega} + \frac{V_1 - V_2}{2\Omega} = 0 \quad \text{--- (1)}$$

KCL at node 2 gives:

$$\frac{V_2 - V_1}{2\Omega} + \frac{V_2}{10\Omega} - 2 = 0 \quad \text{--- (2)}$$

Equations (1) and (2) can be solved simultaneously to find

$$V_1 = 9.09\text{V}, \quad V_2 = 10.91\text{V}.$$



The currents can be found by Ohm's law.

$$\text{For example } i_3 = \frac{V_1 - V_2}{2} = \frac{9.09 - 10.91}{2} = -0.91$$

- The minus sign indicates that the real direction of the current is opposite of our initial selection.
- Voltage polarities and direction of currents can be arbitrarily selected in the beginning. The important point is that we must be consistent with our initial selections throughout the solution.

Ex:

Given the following circuit

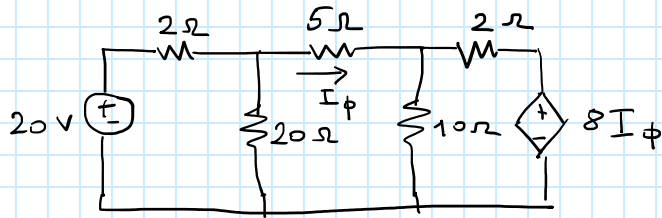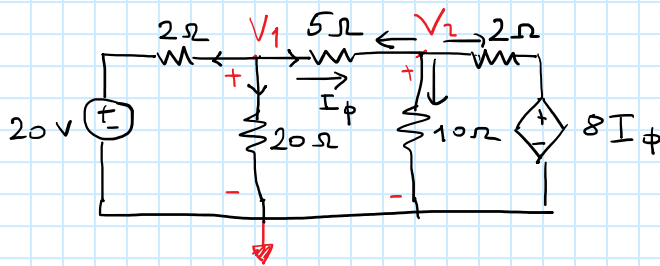Find  $P_{5\Omega} = ?$ Ans:

$$I_{\phi} = \frac{V_1 - V_2}{5} \text{ from the Ohm's law.} \quad \text{--- (1)}$$

Use the node-voltage method:

KCL at node 1:

$$\frac{V_1 - 20}{2} + \frac{V_1}{20} + I_{\phi} = 0 \quad \text{--- (2)}$$

KCL at node 2:

$$-I_{\phi} + \frac{V_2}{10} + \frac{V_2 - 8I_{\phi}}{2} = 0 \quad \text{--- (3)}$$

Thus, we have 3 equations with 3 unknowns which can be solved simultaneously.

$$\Rightarrow V_1 = 16V, \quad V_2 = 10V, \quad I_{\phi} = 1.2A.$$


$$P_{5\Omega} = I_{\phi}^2 \cdot R = (1.2)^2 (5) = 7.2W //$$

2-) Mesh-Current Method:Mesh  $\rightarrow$  loop with no other loops inside.

For example, consider the following circuit:

# P12

9 Ekim 2020 Cuma 11:47

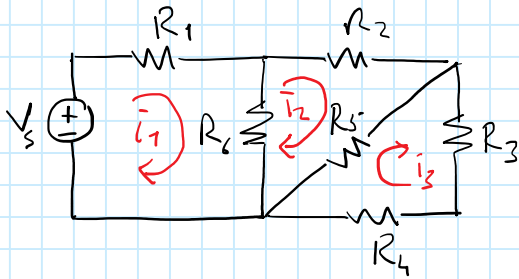


How many meshes are there in this circuit?

Ans: There are 3 meshes with currents  $\bar{i}_1$ ,  $\bar{i}_2$  and  $\bar{i}_3$ .


For mesh-current analysis, we write the KVL equations for each mesh, and solve the equations simultaneously.

Ex:

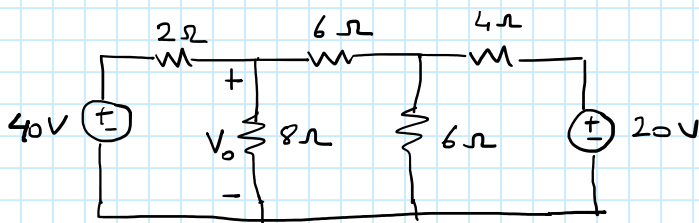Use the mesh-current method to determine the power associated with each voltage source. Also find  $V_o$ .



Ans:

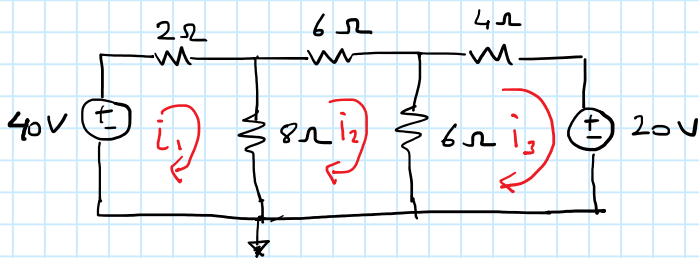

KVL for mesh 1:

$$-40V + 2i_1 + 8(i_1 - i_2) = 0 \quad \text{--- (1)}$$

KVL for mesh 2:

$$8(i_2 - i_1) + 6i_2 + 6(i_2 - i_3) = 0 \quad \text{--- (2)}$$

KVL for mesh 3:

$$6(i_3 - i_2) + 4i_3 + 20 = 0 \quad \text{--- (3)}$$

Again, we have 3 equations with 3 unknowns ( $i_1, i_2, i_3$ ).

Re-arranging the equations:

$$\begin{aligned} 10i_1 - 8i_2 &= 40 \\ -8i_1 + 20i_2 - 6i_3 &= 0 \\ -6i_2 + 10i_3 &= -20 \end{aligned}$$

# P13

9 Ekim 2020 Cuma 12:05

$$\begin{aligned} 10\bar{i}_1 - 8\bar{i}_2 &= 40 \\ -8\bar{i}_1 + 20\bar{i}_2 - 6\bar{i}_3 &= 0 \\ -6\bar{i}_2 + 10\bar{i}_3 &= -20 \end{aligned}$$

$$\begin{bmatrix} 10 & -8 & 0 \\ -8 & 20 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} \bar{i}_1 \\ \bar{i}_2 \\ \bar{i}_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ -20 \end{bmatrix}$$

$\Rightarrow A \cdot \mathbf{I} = \mathbf{b}$  (matrix equation)

$$\underbrace{\quad}_{A} \cdot \underbrace{\quad}_{\mathbf{I}} = \underbrace{\quad}_{\mathbf{b}}$$

The solution is:

$$\boxed{\mathbf{I} = A^{-1} \cdot \mathbf{b}}$$

$$\bar{i}_1 = 5.6 \text{ A}, \quad \bar{i}_2 = 2 \text{ A}, \quad \bar{i}_3 = -0.8 \text{ A}.$$


$$\left. \begin{aligned} P_{40\text{V}} &= -40 \cdot \bar{i}_1 = -224 \text{ W} \\ P_{20\text{V}} &= -20 \cdot \bar{i}_3 = -16 \text{ W} \end{aligned} \right\} \text{Power delivered.}$$

$$V_o = 8(\bar{i}_1 - \bar{i}_2) = 8(3.6) \Rightarrow V_o = 28.8 \text{ V} //$$

## Special Case of Mesh-Current Method:

When there is a current source in the circuit, the number of unknown currents is reduced by one.

Ex:

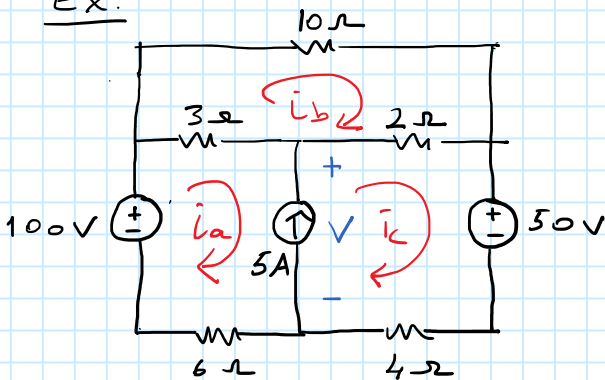

Find the loop currents  $\bar{i}_a$ ,  $\bar{i}_b$  and  $\bar{i}_c$  in this circuit.

Ans:

For mesh a: (KVL)

$$-100 + 3(\bar{i}_a - \bar{i}_b) + V + 6\bar{i}_a = 0 \quad (1)$$

For mesh c:

$$50 + 4\bar{i}_c - V + 2(\bar{i}_c - \bar{i}_b) = 0 \quad (2)$$

Re-write eqn's (1) and (2) as

$$100 = 3(\bar{i}_a - \bar{i}_b) + V + 6\bar{i}_a \quad \text{--- (1)}$$

$$-50 = 4\bar{i}_c - V + 2(\bar{i}_c - \bar{i}_b) \quad \text{--- (2)}$$

Add (1) and (2)

$$50 = 9\bar{i}_a - 5\bar{i}_b + 6\bar{i}_c \quad \text{--- (3)}$$

KVL for mesh b:

$$0 = 3(\bar{i}_b - \bar{i}_a) + 10\bar{i}_b + 2(\bar{i}_b - \bar{i}_c) \quad \text{--- (4)}$$

We also have

$$\bar{i}_c - \bar{i}_a = 5A. \quad \text{--- (5)}$$

Eqn's (3), (4) and (5) can be solved for  $\bar{i}_a$ ,  $\bar{i}_b$  and  $\bar{i}_c$ .

$$\begin{bmatrix} 9 & -5 & 6 \\ -3 & 15 & -2 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} \bar{i}_a \\ \bar{i}_b \\ \bar{i}_c \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}$$

$\underbrace{\hspace{10em}}_A \cdot \underbrace{\begin{bmatrix} \bar{i}_a \\ \bar{i}_b \\ \bar{i}_c \end{bmatrix}}_{\bar{i}} = \underbrace{\begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}}_b$

$$9\bar{i}_a - 5\bar{i}_b + 6\bar{i}_c = 50 \quad \text{--- (3)}$$

$$-3\bar{i}_a + 15\bar{i}_b - 2\bar{i}_c = 0$$

$$-\bar{i}_a + \bar{i}_c = 5$$


$$\Rightarrow \bar{i} = A^{-1} \cdot b$$

$$\Rightarrow \bar{i}_a = 1.75A, \bar{i}_b = 1.25A, \bar{i}_c = 6.75A.$$


## Chapter 5:

### Thévenin and Norton Equivalents:

We want to replace

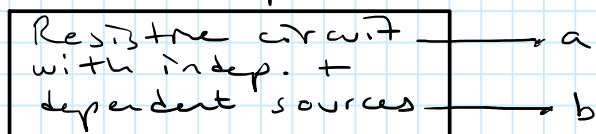


with the following circuit:

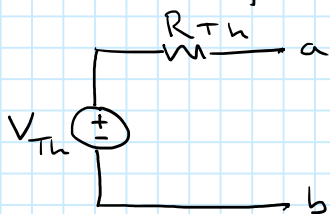

where  $V_{Th}$  = Thévenin voltage.

$R_{Th}$  = Thévenin resistance.

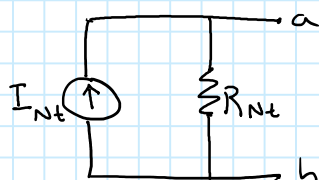


where  $I_{Nt}$  = Norton current

$R_{Nt}$  = Norton resistance

# P15

16 Ekim 2020 Cuma 10:44

Consider the following circuit:

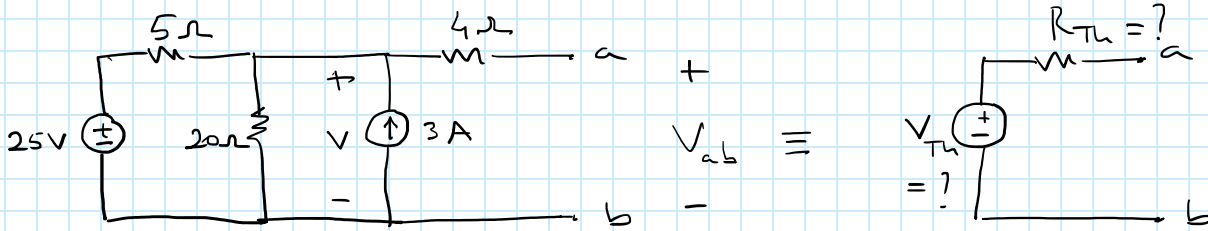


- If we connect another circuit to the given circuit at points a and b, this other circuit sees no difference if it is connected to Thévenin equivalent circuit.

$V_{Th}$  = Open circuit voltage btw the terminals a and b, and we short circuit a and b, and find the current btw a and b ( $I_{sc}$ ).

Thus,  $I_{sc} = \frac{V_{Th}}{R_{Th}} \Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}}$

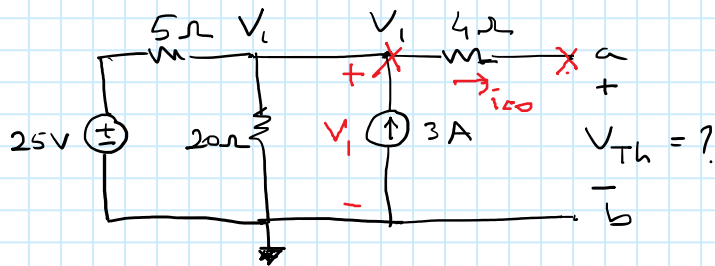For the given circuit; using the node-voltage method:



The current passing through the 4Ω resistor is zero.

$$V = i \cdot R = 0$$

$$\downarrow$$

$$0 \quad \frac{4\Omega}{\quad}$$

$$+ \quad 0 \quad -$$

$$V_1 \quad \quad V_2$$

$$V_1 - V_2 = 0$$

$$\boxed{V_1 = V_2}$$

$$\Rightarrow \boxed{V_1 = V_{Th}}$$

KCL at node 1:


$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0$$

$$\Rightarrow V_1 = 32V.$$

$$V_{Th} = 32V.$$

- In order to find  $R_{Th}$ , we short circuit points a and b, and

find  $I_{sc}$ .

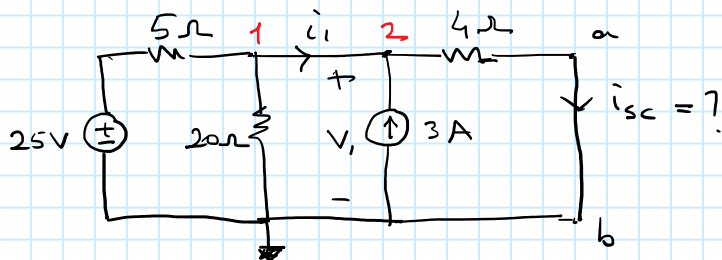


KCL at node 1:

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + i_1 = 0 \quad (1)$$

# P16

16 Ekim 2020 Cuma 11:08

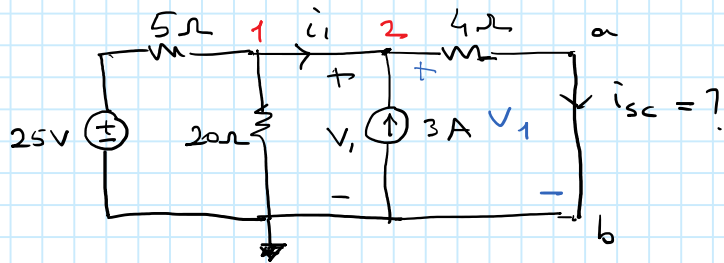

KCL at node 2:

$$-i_i - 3A + i_{sc} = 0$$

or

$$i_{sc} - i_i = 3A \quad \text{where } i_{sc} = \frac{V_1}{4} \Rightarrow \frac{V_1}{4} - i_i = 3 \quad (2)$$

Earlier, we had

$$\frac{V_1 - 25}{5} + \frac{V_1}{20} + i_i = 0 \quad (1)$$


Thus, (1) and (2) can be solved simultaneously and

$$\Rightarrow V_1 = 16V.$$

$$\Rightarrow i_{sc} = \frac{V_1}{4} = \frac{16}{4} = 4A.$$

$$\Rightarrow R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32V}{4A} = 8\Omega.$$

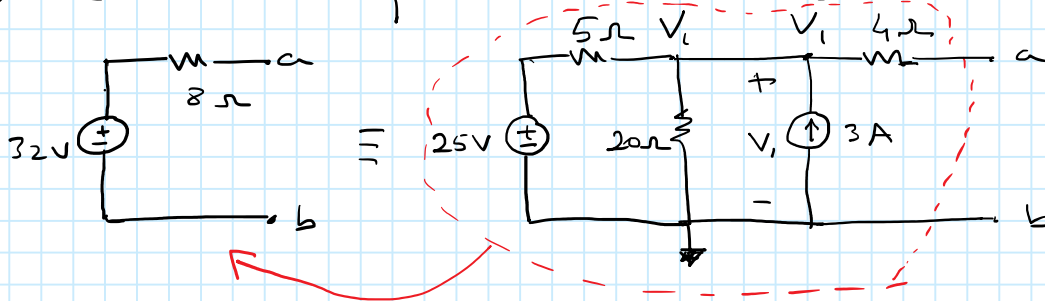Thus, the Thevenin equivalent circuit is:




In order to obtain the "Norton Equivalent Circuit", we can make "source transformation", where  $R_{Th} | = R_{Nt}$

Thevenin      Norton

The current source of Norton circuit is the short circuit current, that is  $i_{sc}$ .



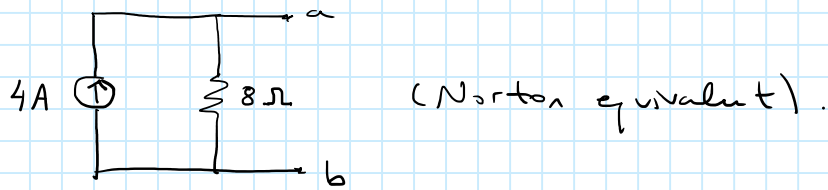Then, for this example, the Norton equivalent circuit is




Alternative technique to find Thévenin equivalent resistance:

If there are only independent sources, to find the Thévenin equivalent resistance:


- Short circuit voltage sources and
- Open circuit current sources. } Deactivating the indep sources
- Then, evaluate the resistance  $R_{Th}$  w.r.t a and b.

Ex:

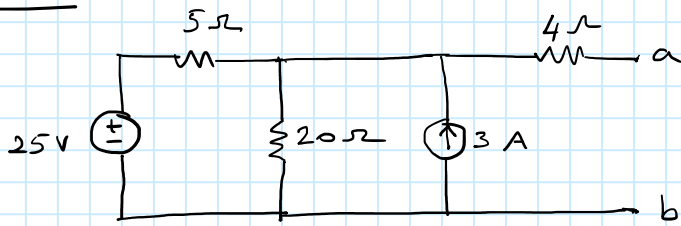

Find  $R_{Th} = ?$  w.r.t points a and b.

Ans:

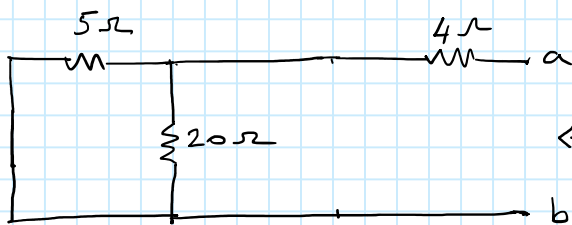

$$\begin{aligned} \Rightarrow R_{Th} &= 4 + (5 \parallel 20) \\ &= 4 + \frac{20 \cdot 5}{20 + 5} = 4 + \frac{20 \cdot 5}{25} \\ &= 4 + 4 = 8 \Omega. \end{aligned}$$


Another alternative technique to find Thévenin resistance:

If the circuit contains dependent sources:

- First, deactivate all indep. sources
- Apply a test voltage " $V_T$ " btw. terminals a and b.
- $R_{Th} = \frac{V_T}{i_T}$ , where  $i_T$  is the current passing through  $V_T$ .


Ex:

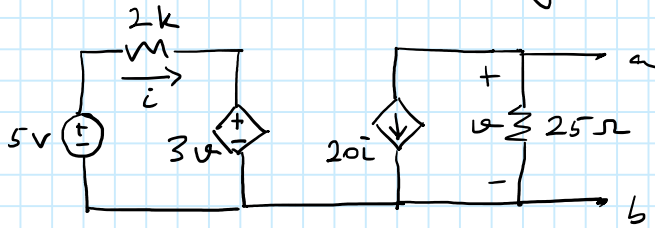Find the Thevenin resistance  $R_{Th}$  for the circuit below using the method that was just described.




Ans:

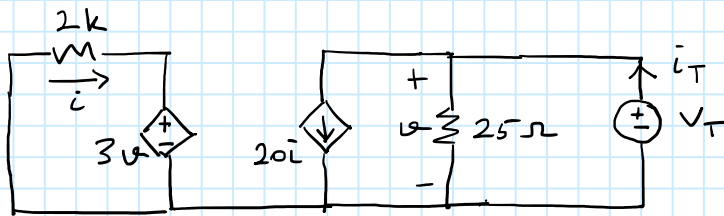First, we de-activate all indep. sources:



Apply the test voltage  $V_T$

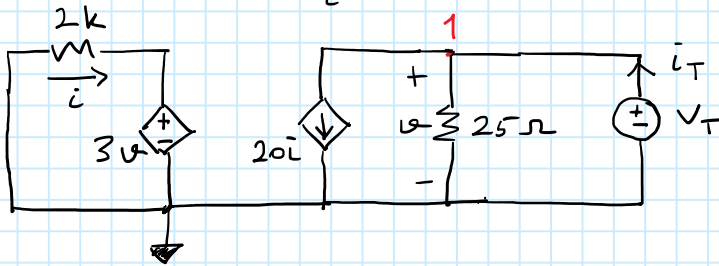We need to find  $\frac{V_T}{i_T} = R_{Th}$ . Let us use the node-voltage method:



KCL at node 1:

$$20\bar{i} + \frac{v}{25} = \bar{i}_T \quad (1)$$

where  $\bar{i} = \frac{-3v}{2k} = \frac{-3V_T}{2000}$  (since  $v = V_T$ )

Then,

$$20 \cdot \left( \frac{-3V_T}{2000} \right) + \frac{V_T}{25} = \bar{i}_T \quad (2)$$

Solve equation (2) for  $\frac{V_T}{\bar{i}_T}$ .

$$\frac{\bar{i}_T}{V_T} = \frac{1}{100} \Rightarrow R_{Th} = \frac{V_T}{\bar{i}_T} = 100\Omega$$


Prefix	Value
T (tera)	$10^{12}$
G (giga)	$10^9$
M (mega)	$10^6$
k (kilo)	$10^3$
c (centi)	$10^{-2}$
m (milli)	$10^{-3}$
$\mu$ (micro)	$10^{-6}$
n (nano)	$10^{-9}$
p (pico)	$10^{-12}$
f (femto)	$10^{-15}$

$$\frac{-3V_T}{100} + \frac{V_T}{25} = \bar{i}_T$$

$$\frac{-3V_T + 4V_T}{100} = \bar{i}_T$$

$$\frac{V_T}{100} = \bar{i}_T$$

- If  $V_T$  is asked to be found, then

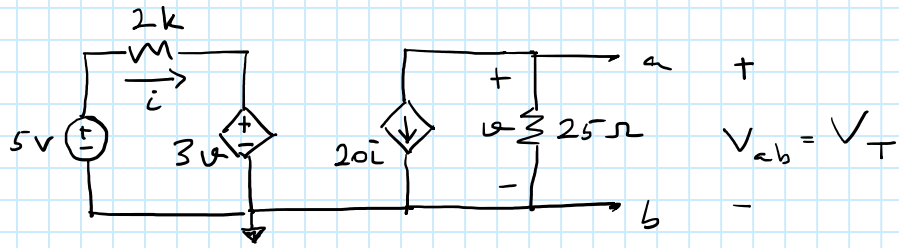

$$\Rightarrow V_{Th} = V_{ab} = (-20i)(25) = -500i \text{ and}$$


from the 1<sup>st</sup> circuit loop,

$$i = \frac{5 - 3V}{2000} = \frac{5 - 3V_{ab}}{2000} = \frac{5 - 3(-500i)}{2000}$$

$$\Rightarrow 2000i = 5 + 1500i \Rightarrow 500i = 5 \Rightarrow i = 0.01 \text{ A} = 10 \text{ mA.}$$


$$\Rightarrow V_{Th} = -500(10 \text{ mA}) = -500(0.01) = -5 \text{ V.}$$

Thus, the Thevenin Eq. circuit is:

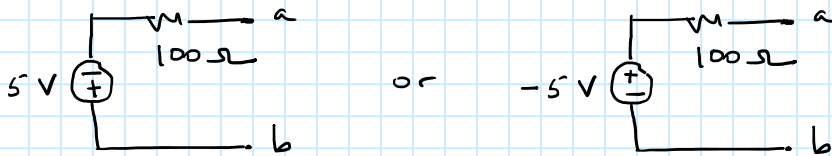

Maximum Power Transfer:

Consider the following circuit:

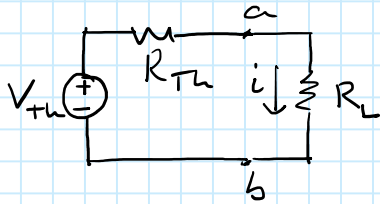

- The power consumed by the resistor  $R_L$  is:

$$P_{R_L} = i^2 \cdot R_L \text{ (W)}$$

- We want to find a value for  $R_L$  such that  $P_{R_L}$  is maximum. This is called "maximum power transfer".

- The power consumed by  $R_L$ ,  $P_{R_L}$ , is a function of  $R_L$ .

$$\Rightarrow P_{R_L} = P_{R_L}(R_L) = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

$$P_{R_L} = P_{R_L}(R_L) = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L$$

To find the max.  $P_{R_L}(R_L)$

$$\frac{dP_{R_L}(R_L)}{dR_L} = 0.$$

$$\Rightarrow 2 \left( \frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \left[ \frac{-V_{Th}}{(R_{Th} + R_L)^2} \right] R_L + \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 = 0$$

Re-arrange the equation,

$$2 \left( \frac{V_{Th}}{R_{Th} + R_L} \right) \cdot \frac{1}{(R_{Th} + R_L)} \cdot R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2$$


$$2R_L = R_{Th} + R_L$$

$\Rightarrow$   $R_L = R_{Th}$  (Condition for max. power transfer).

Ex:

$$P_{R_L} = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 \cdot R_L = \frac{V_{Th}^2}{4R_L^2} \cdot R_L = \frac{V_{Th}^2}{4R_L} \text{ (W)}$$


For the given circuit below:

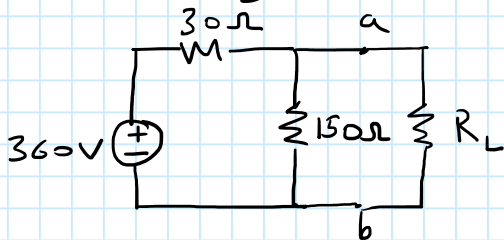


- i) Find  $R_L$  for max. power transfer
- ii) Find  $P_{R_L}|_{\max}$ .

Ans:

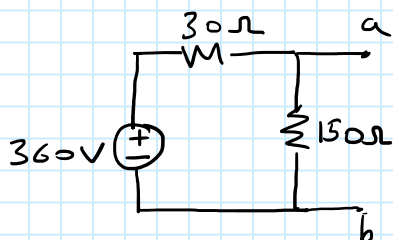- First, we find the Thévenin equivalent circuit for the left side of the terminals a and b.



$\equiv$  Thévenin equivalent = ?

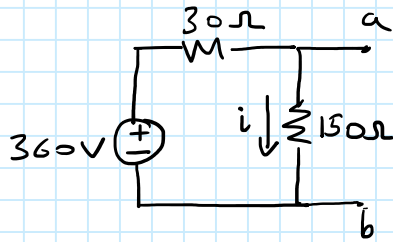

$$i) V_{TH} = 360 \cdot \frac{150}{150+30} = 360 \cdot \frac{150}{180} = 300 \text{ V.}$$

$$R_{TH} = 30\Omega \parallel 150\Omega = \frac{150 \cdot 30}{150+30} = \frac{150 \cdot 30}{180} = 25\Omega.$$

$$R_L = R_{TH} \text{ for max. power transfer} \Rightarrow R_L = 25\Omega.$$


$$ii) P_{R_L} = i^2 \cdot R_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L = \left( \frac{300}{25+25} \right)^2 \cdot 25 \Rightarrow P_{R_L} = 900 \text{ W.}$$

$$\frac{300^2}{4 \cdot 25} = \frac{300 \cdot 300}{100} = 900 \text{ W}$$

### Superposition:

Superposition is the concept of "linearity". It means that when a system is fed by more than one independent sources, the total response is sum of individual responses.


Ex:

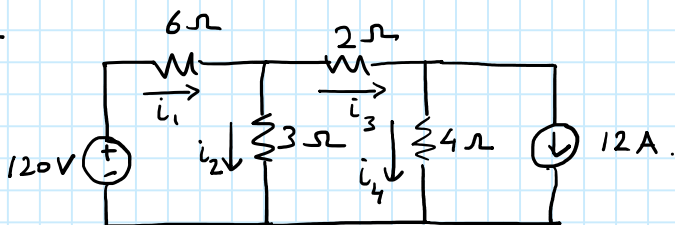

Find  $\bar{i}_1, \bar{i}_2, \bar{i}_3$  and  $\bar{i}_4$  by using the superposition.


Ans:

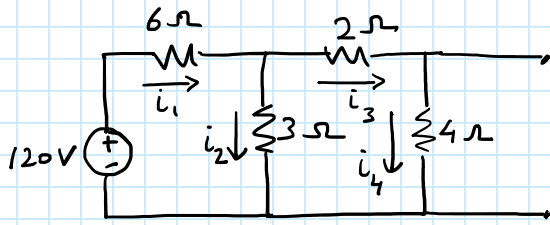- This circuit has 2 indep. sources.
- De-activate one of the sources, and solve the circuit. Then de-activate the other source, and solve the circuit.
- Sum the two solutions from the previous step. Because the resistive circuits with indep. sources are linear.
- Thus, let us first de-activate the 12A source, and find the unknown currents  $\bar{i}_1, \bar{i}_2, \bar{i}_3$  and  $\bar{i}_4$ :



$$\begin{aligned} \bar{i}_1' &= 5\text{ A} \\ \bar{i}_2' &= 10\text{ A} \\ \dots \\ \bar{i}_3' &= 5\text{ A} \\ \bar{i}_4' &= 5\text{ A} \end{aligned}$$

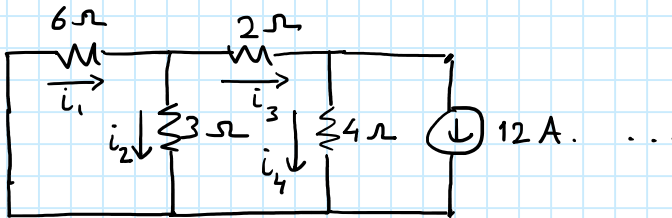Now, de-activate the 1<sup>st</sup> indep. source:



$$\begin{aligned} \bar{i}_1'' &= 2\text{ A} \\ \bar{i}_2'' &= -4\text{ A} \\ \bar{i}_3'' &= 6\text{ A} \\ \bar{i}_4'' &= -6\text{ A} \end{aligned}$$

Therefore, the unknown currents are

$$\bar{i}_1 = \bar{i}_1' + \bar{i}_1'' \Rightarrow \bar{i}_1 = 7\text{ A}$$


$$\bar{i}_2 = \bar{i}_2' + \bar{i}_2'' \Rightarrow \bar{i}_2 = 6\text{ A}$$

$$\bar{i}_3 = \bar{i}_3' + \bar{i}_3'' \Rightarrow \bar{i}_3 = 11\text{ A}$$

$$\bar{i}_4 = \bar{i}_4' + \bar{i}_4'' \Rightarrow \bar{i}_4 = -1\text{ A}$$
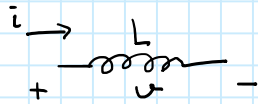
## Chapter 6: Inductance and Capacitance:

- Inductor: It is an electrical element that can be a part of a wire having circular turns.



- The relation among  $v$ ,  $i$  and  $L$  is:

$$v = L \cdot \frac{di}{dt}, \quad v = v(t), \quad i = i(t), \quad L$$

$L = \text{Inductance} =$


constant (Henry)

- Conversely

$$i(t) = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0)$$

Ex:

For the given circuit:

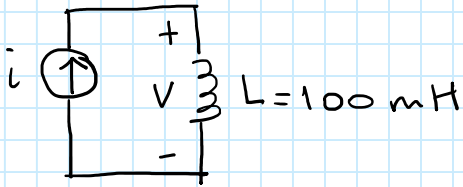

Given that

$$\bar{i} = 0, t < 0$$

and

$$\bar{i}(t) = 10t e^{-5t} \text{ (A)}, t \geq 0$$

Find  $v = ?$  for  $t \geq 0$ .Ans:

$$V = L \frac{di}{dt} = (0.1) \cdot \frac{d}{dt} i(t) = (0.1) \frac{d}{dt} [10t e^{-5t}]$$


or

$$V = (0.1) \cdot [10 e^{-5t} + 10t \cdot (-5 e^{-5t})]$$

$$\therefore V = (0.1) (10 e^{-5t}) (1 - 5t) = e^{-5t} (1 - 5t) \text{ V}, t \geq 0.$$

Ex:

For the given circuit:

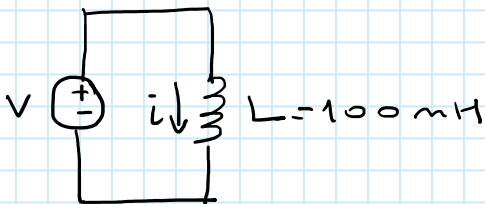

Given:

$$v = 20t e^{-10t} \text{ (V)}, t > 0$$

$$\bar{i} = 0, t \leq 0.$$

Find  $i(t)$ ,  $t > 0$ .


$$\tau = \text{tau.}$$

$$\tau = \text{tau.}$$

Ans:

$$i(t) = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) = \frac{1}{0.1} \cdot \int_0^t 20\tau e^{-10\tau} d\tau + 0.$$
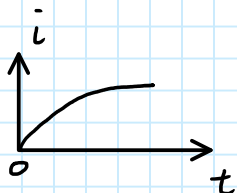
$$\Rightarrow i(t) = 2 (1 - 10t e^{-10t} - e^{-10t}) \text{ (A)}, t > 0.$$



## Power and Energy in an Inductor:

- For  $p = i \cdot v$ , substitute,  $i$  and  $v$  for an inductor:

$$p = i \cdot L \cdot \frac{di}{dt} = L i \frac{di}{dt} \quad (\text{W})$$

- The energy is


$$p = \frac{dE}{dt} \quad \text{or} \quad \frac{dE}{dt} = L i \frac{di}{dt} \quad \Rightarrow \quad \underbrace{dE}_{\text{differential energy}} = L \underbrace{i}_{\text{differential current}} di$$

Take the integral of both sides:

$$\int_0^E dE = L \int_0^i i di \quad \Rightarrow \quad \int_0^E dE = L \int_0^i i di$$


$$\Rightarrow E = L \cdot \frac{i^2}{2} \quad \Rightarrow \quad \boxed{E = \frac{1}{2} L i^2} \quad (\text{Stored energy inside an inductor.})$$

## Capacitor:

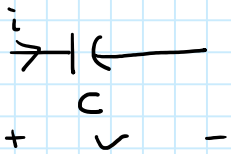

$C = \text{constant} =$   
capacitance

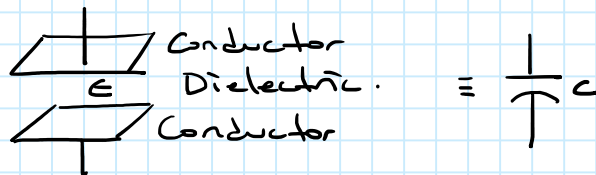- Capacitor is an electrical element that is made of two conductors separated by an insulator (dielectric).



- We have the following circuit relation for a capacitor:

$$\boxed{i = C \cdot \frac{dv}{dt}}$$

Conversely, we have

$$\boxed{v(t) = \frac{1}{C} \int_{t_0}^t i d\tau + v(t_0)}$$



Power and Energy in a Capacitor:

$$p = v \cdot i = c \cdot v \cdot \frac{dv}{dt} \text{ (w)}$$

$$E = \frac{1}{2} c v^2 \text{ (J)}$$

→  $\phi = \oint \mathbf{E} \cdot d\mathbf{l}$   
and

Series and Parallel Connection of Inductors & Capacitors:

Series:

For inductors,  $L_{eq} = L_1 + L_2 + \dots + L_n$  (n inductors in series)

For capacitors,  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$  (n capacitors in series)


Parallel:

For inductors,  $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$

For capacitors,  $C_{eq} = C_1 + C_2 + \dots + C_n$

Mutual Inductance:

Consider the following circuit

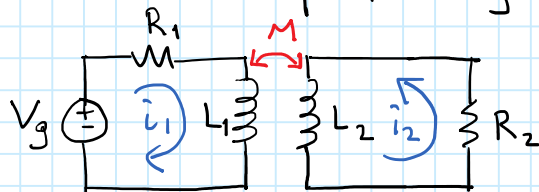


M: Mutual inductance.

Dot Convention:


When the reference direction for a current enters the dotted terminal, the reference polarity of the voltage that is induced in the other coil is positive at its dotted terminal.

Ex:

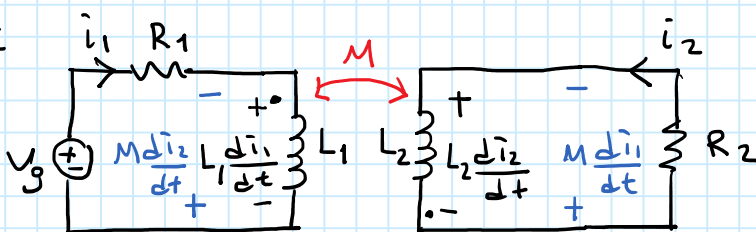

-  $M \frac{di_1}{dt}$  and  $M \frac{di_2}{dt}$  are mutual induced voltage.

Ex:

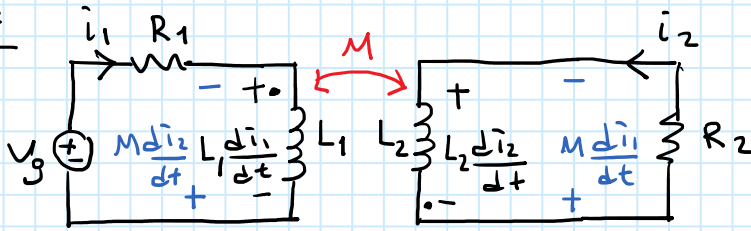

-  $M \frac{di_1}{dt}$  and  $M \frac{di_2}{dt}$  are

the mutual induced voltage.

-  $L_1 \frac{di_1}{dt}$  and  $L_2 \frac{di_2}{dt}$  are

the self inductance voltages.

Write the KVL equations for the above circuit

Ans:

In the 1<sup>st</sup> loop:


$$-V_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0 \quad (1)$$

In the 2<sup>nd</sup> loop:

$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0 \quad (2)$$
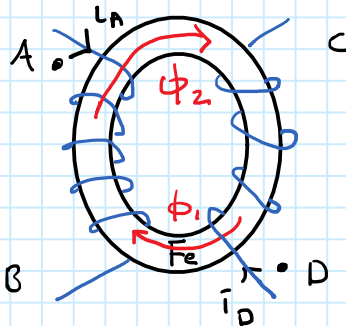
### Determining Dot Markings:

Consider the following inductor (toroid):



Steps:

1-) Arbitrarily select one terminal, and mark it with a dot. (Let's say D)

2-) Assign a current into the dotted terminal ( $i_D$ ).

3-) Determine the magnetic flux by  $i_D$  using the "Right hand rule" ( $\phi_1$ ).

4-) Pick one terminal on the 2<sup>nd</sup> coil (Let's say A), and assign a current into this terminal ( $i_A$ ).


5-) Find  $\phi_2$  by  $i_A$ .

6-) If  $\phi_1$  and  $\phi_2$  are in the same direction, then put a dot on the selected terminal (in this case, terminal A).

If not, put a dot on the opposite terminal (terminal B).


Ex:

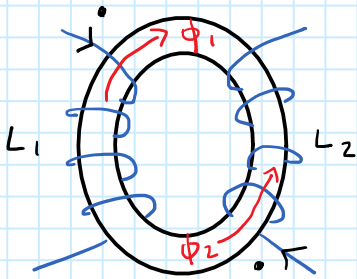For the given toroidal inductors find the dot convention.



Ex:

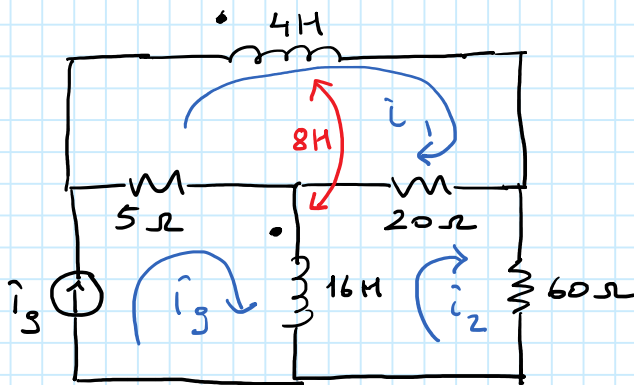For the given circuit, write the equations for the mesh currents  $i_1$  and  $i_2$ .



Ans:

For mesh 1:

$$4 \frac{d\bar{i}_1}{dt} + 8 \frac{d(\bar{i}_1 - \bar{i}_2)}{dt} + 20(\bar{i}_1 - \bar{i}_2) + 5(\bar{i}_1 - \bar{i}_3) = 0 \quad \text{--- (1)}$$


For mesh 2:

$$20(\bar{i}_2 - \bar{i}_1) + 60\bar{i}_2 + 16 \frac{d(\bar{i}_2 - \bar{i}_3)}{dt} - 8 \frac{d\bar{i}_1}{dt} = 0 \quad \text{--- (2)}$$

*mutual induced voltage.*  
*self induced voltage*

Sample Questions:

1-)

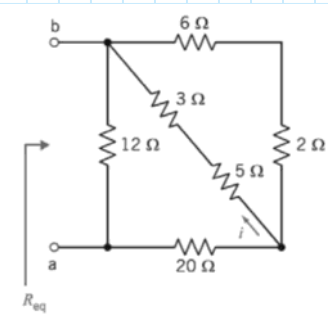


Find  $i$  and  $R_{eq}$  if  $V_{ab} = 40V$

Ans:

$$R_{eq} = 12 \parallel \left\{ 20 + \left[ \underbrace{(5+3)}_8 \parallel \underbrace{(6+2)}_8 \right] \right\}$$


$$\underbrace{\hspace{10em}}_4$$

$$\underbrace{\hspace{15em}}_{24}$$

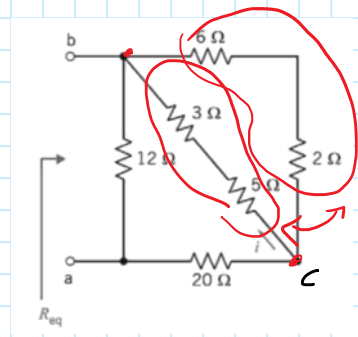

$$\Rightarrow R_{eq} = 12 \parallel 24 = \frac{12 \cdot 24}{12 + 24} = \frac{12 \cdot 24}{36} = 8 \Omega$$


To find  $i$ ,

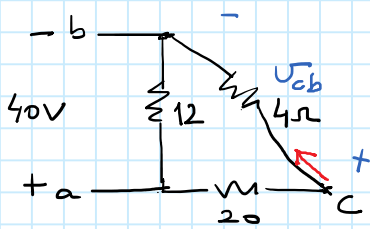

$$V_{ab} = V_a - V_b$$

$$V_{cb} = 40 \cdot \frac{4}{20+4}$$
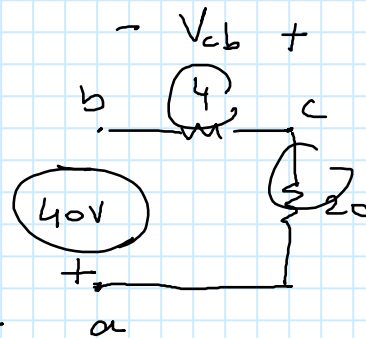
$$\Rightarrow V_{cb} = 40 \cdot \frac{4}{6 \cdot \frac{4}{3}} = \frac{40}{6}$$



Then,

$$i = \frac{V_{cb}}{R} = \frac{40/6}{8} = \frac{40}{6} \cdot \frac{1}{8} = \frac{5}{6} A$$

2-)

For the circuit in Fig.2, if the power delivered by the source is 20 mW, find  $R$  and  $V_s$ .

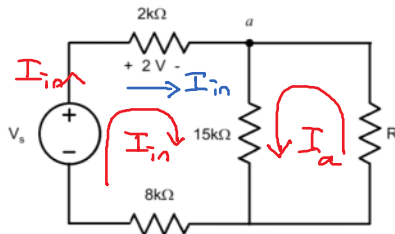


Figure 2: Circuit for question 2.

$$I_{in} = \frac{2V}{2k} = 1 mA$$

$$P_{Vs} = 20mW = I_{in} \cdot V_s$$

$$\Rightarrow V_s = \frac{20mW}{1mA} = 20V$$

KVL in the left loop:  $-20 + 2 + (I_a + I_{in})(15k) + I_{in}(8k) = 0$

# P29

Saturday, October 31, 2020 9:50 AM

$$-20 + 2 + (I_a + I_{in})(15k) + I_{in}(8k) = 0$$

$$15k I_a + 23k \underbrace{I_{in}}_{1mA} = 18$$

$$\Rightarrow I_a = \frac{18 - 23}{15} mA = \frac{-5}{15} mA = -\frac{1}{3} mA$$

$$\begin{aligned} \Rightarrow V_a &= (I_{in} + I_a)(15k) \\ &= \left(1 - \frac{1}{3}\right) mA (15k) \\ &= \frac{2}{3} (15)^5 = 10V. \end{aligned}$$

$$\text{Thus, } R = \frac{V_a}{-I_a} = \frac{10}{-\frac{1}{3} mA} = 30k\Omega.$$

For the circuit in Fig.2, if the power delivered by the source is 20 mW, find R and  $V_a$ .

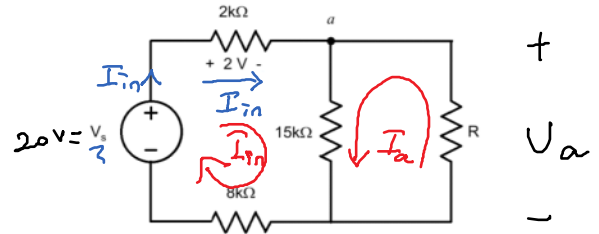


Figure 2: Circuit for question 2.

3-)

Find the voltage  $v_a$  in Fig.3 by

- Node-voltage analysis
- Source transformation.

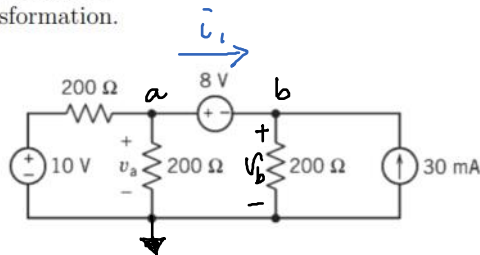


Figure 3: Circuit for question 3.

a-) KCL at node a:

$$\frac{v_a - 10}{200} + \frac{v_a}{200} + i_1 = 0 \quad (1)$$

KCL at node b:

$$-i_1 + \frac{v_b}{200} - 30mA = 0 \quad (2)$$

$$v_a - v_b = 8 \quad (3)$$

Add (1) and (2):

$$\frac{v_a - 10}{200} + \frac{v_a}{200} + \frac{v_b}{200} = 30mA$$

$$v_a - 10 + v_a + v_b = (2/2) (30 mA) = 6$$

$$2v_a + v_b = 16 \quad (4)$$







Add (3) and (4):


$$v_a - v_b = 8$$

$$+ 2v_a + v_b = 16$$

$$3v_a = 24 \Rightarrow \boxed{v_a = 8V}$$

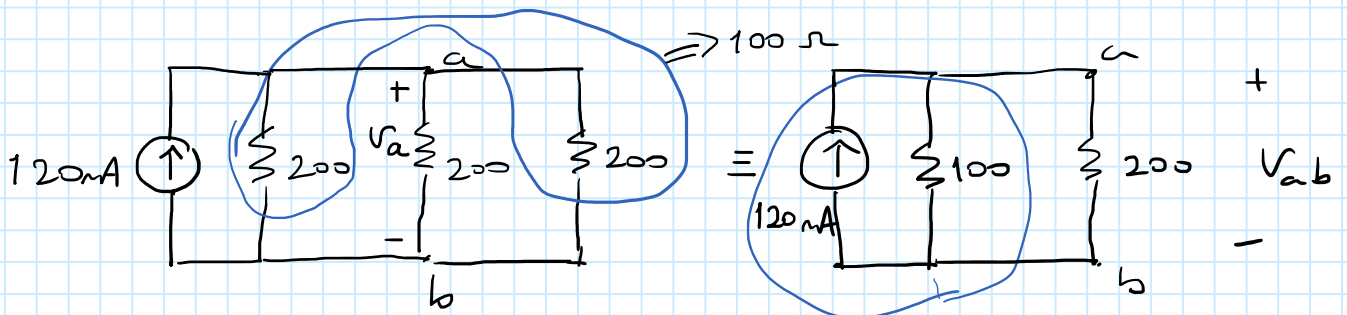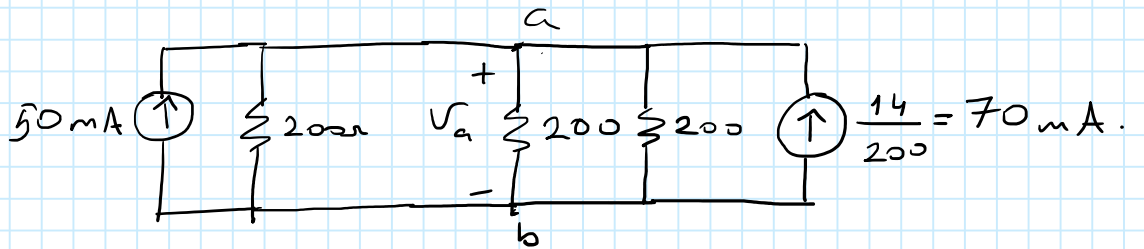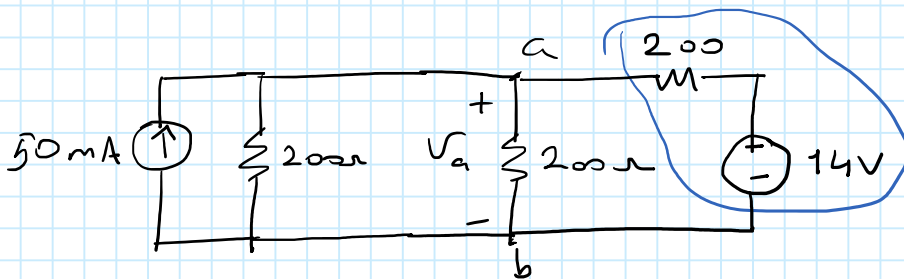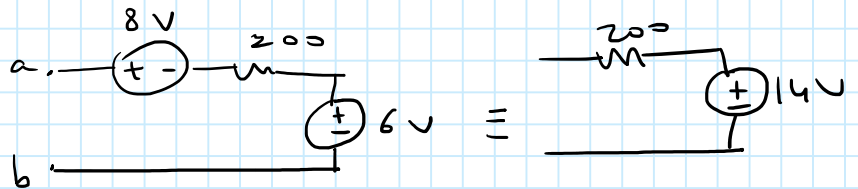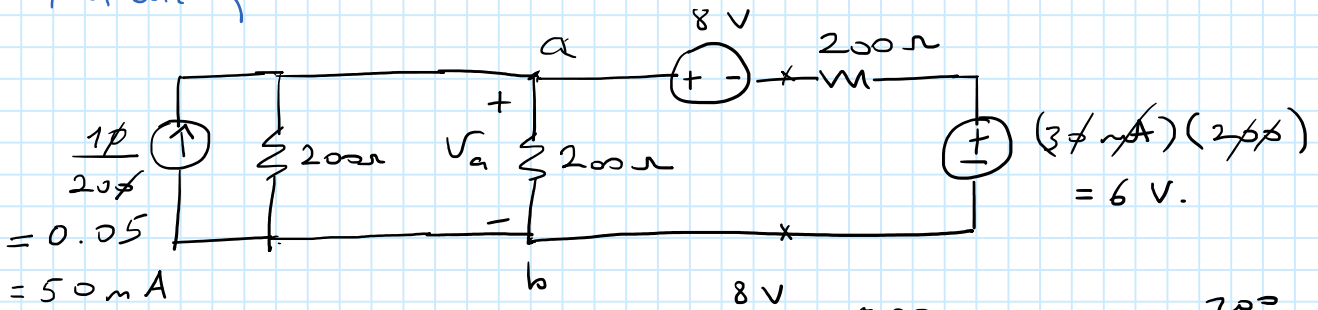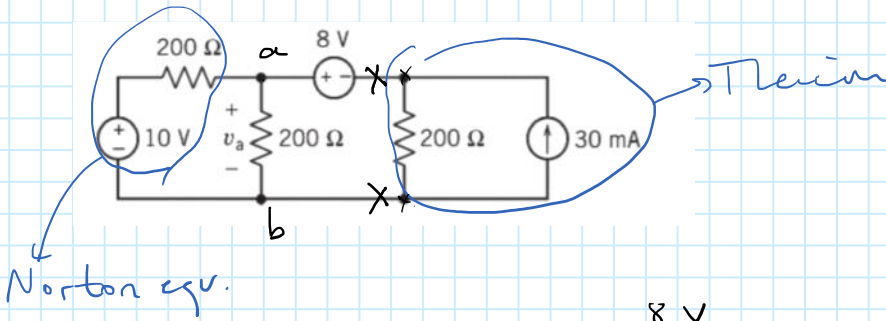b-) Source transformation = Thévenin → Norton → Thévenin...



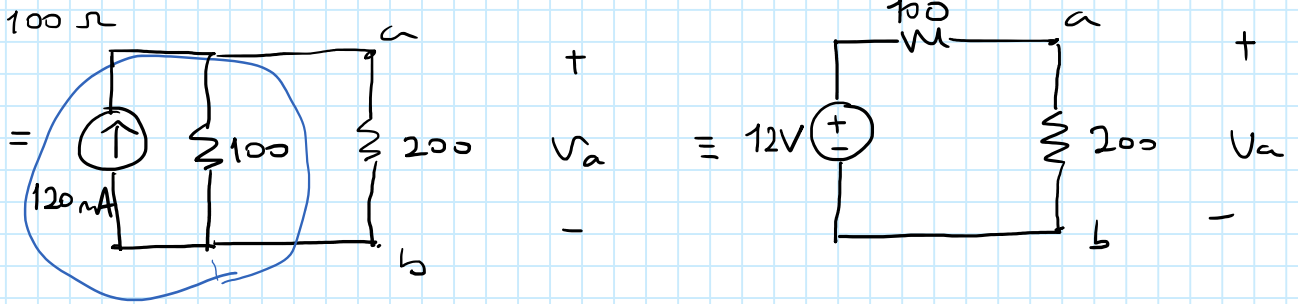

$$V_a = 12 \cdot \frac{200}{200+100} = 12 \cdot \frac{2}{3} = 8V.$$

4-)

- a-) Calculate the value of R for maximum power.
- b-) Determine the maximum power absorbed by R.


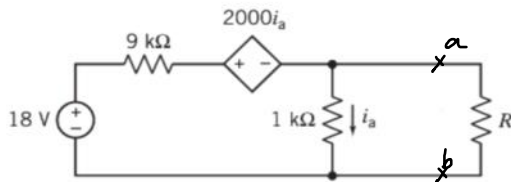
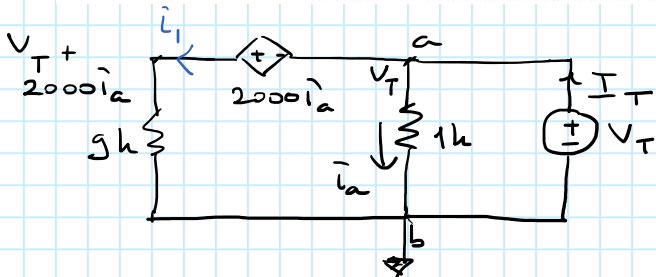


Figure 4: Circuit for question 4.

- Thevenin btw. a and b :

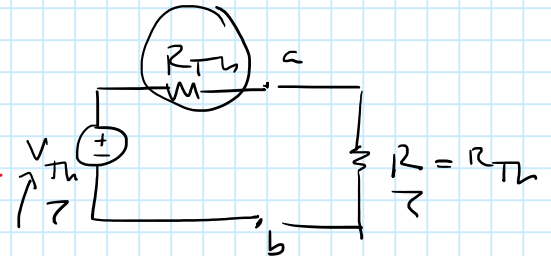

$$R_{Th} = \frac{V_T}{I_T}$$

KCL at node a:

$$i_1 + i_a - I_T = 0 \quad (1)$$

$$i_a = \frac{V_T}{1k} \quad (2)$$

Substitute (2) in (1)

$$i_1 + \frac{V_T}{1k} - I_T = 0 \quad (3)$$

$$\frac{V_T + 2000 i_a}{9k} + \frac{V_T}{1k} = I_T$$

$$\frac{V_T + 2000 \cdot \left(\frac{V_T}{1k}\right)}{9k} + \frac{V_T}{1k} = I_T$$

$$\frac{3V_T}{9k} + \frac{V_T}{1k} = I_T$$


$$\frac{3V_T + 9V_T}{9k} = I_T$$

$$\frac{12V_T}{9k} = I_T$$

$$\Rightarrow \frac{V_T}{I_T} = \frac{9000}{12} = 750 \Omega = R_{Th}$$

$$R = R_{Th} = 750 \Omega$$

To find  $V_{Th}$ :

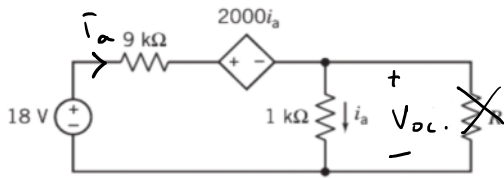

$$V_{Th} = V_{oc}$$

KVL for the mesh:


$$-18 + i_a(9k) + 2000i_a + i_a(1k) = 0$$

$$12000i_a = 18$$

$$i_a = \frac{18}{12000} \text{ A}$$

$$\Rightarrow V_{Th} = V_{oc} = i_a \cdot 1k = \frac{18}{12000} (1k) = \frac{18}{12} \text{ V} = \frac{3}{2} \text{ V}$$

b.)

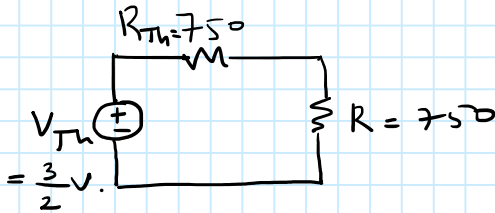

$$P_R |_{\max} = ? \quad (R = 750 \Omega)$$

$$P_R |_{\max} = i^2 \cdot R = \left( \frac{V_{Th}}{2R_{Th}} \right)^2 R_{Th}$$


$$= \frac{V_{Th}^2}{4R_{Th}} \cdot R_{Th}$$

$$\Rightarrow P_R |_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$\Rightarrow P_R |_{\max} = \frac{(3/2)^2}{4 \cdot 750} = \frac{9/4}{4 \cdot 750} = \frac{9}{4} \cdot \frac{1}{4 \cdot 750} = \frac{9}{12000} = \frac{3}{4000} \text{ mW} = 0.75 \text{ mW} = 750 \mu\text{W}$$

5-)

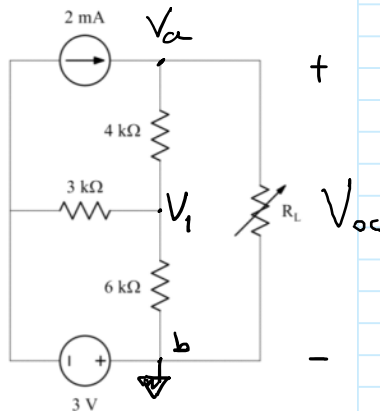- a-) Calculate the value of  $R_L$  for maximum power.
- b-) Determine the maximum power absorbed by  $R_L$ .



To find  $V_{oc}$ :

Node-voltage method:

KCL at node a:

$$-2 \text{ mA} + \frac{V_a - V_1}{4k} = 0$$


$$\Rightarrow \frac{V_a - V_1}{4k} = 2 \text{ mA}$$

or

$$V_a - V_1 = 8 \quad (1)$$

Figure 5: Circuit for question 5.



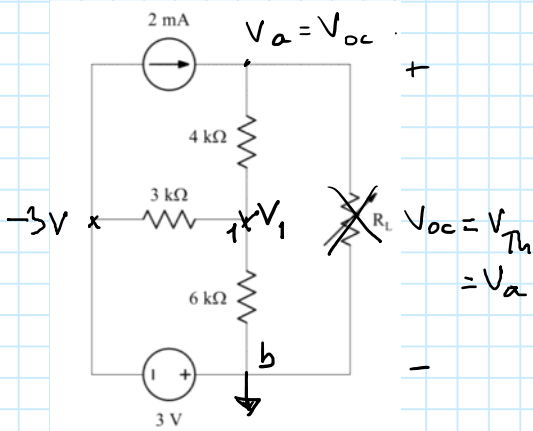

$$U_a - U_i = 8 \quad (1)$$

KCL at node 1:

$$\frac{U_i - U_a}{4k} + \frac{U_i - (-3V)}{3k} + \frac{U_i}{6k} = 0$$

(3)                      (4)                      (2)

$$3U_i - 3U_a + 4U_i + 12 + 2U_i = 0$$

$$9U_i - 3U_a = -12$$

or

$$3U_a - 9U_i = 12$$

$$U_a - 3U_i = 4 \quad (2)$$


Solve (1) and (2):

$$\begin{aligned} U_a - U_i &= 8 \\ + \quad -U_a + 3U_i &= -4 \end{aligned}$$

$$2U_i = 4 \Rightarrow U_i = 2, \quad U_a = 10V.$$

$$\Rightarrow U_{Th} = 10V.$$

$R_{Th}$ :

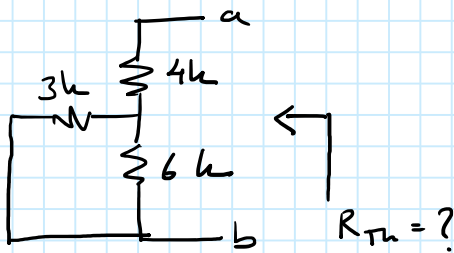

$$\Rightarrow R_{Th} = 4k + (3k \parallel 6k) = 6k \Omega$$

2k

b-)

$$P_R \Big|_{\max} = \frac{U_{Th}^2}{4R_{Th}} \Rightarrow P_R = \frac{(10)^2}{4 \cdot 6000} = \frac{100}{2400} = \frac{1}{24} W \approx 4.2 mW.$$

b-)

Find  $V_o$ ,  $P_{40V}$  and  $P_{5\Omega}$  for the circuit in Fig.1.

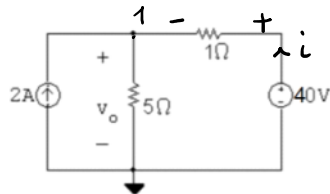


Figure 1: Circuit for question 1.

KCL at node 1:

$$-2 + \frac{V_o}{5} + \frac{V_o - 40}{1} = 0$$

$$\frac{V_o}{5} + V_o = 42$$

$$\frac{6V_o}{5} = 42 \Rightarrow V_o = \frac{42 \cdot 5}{6} = 35V$$

$$P_{40V} = -i \cdot V = -i(40) \Rightarrow i = \frac{40 - V_o}{1} = 40 - 35 = 5A.$$

$$\Rightarrow P_{40V} = -(5A)(40V) = -200W, \quad P_{5\Omega} = \frac{V_o^2}{R} = \frac{35^2}{5} = \frac{1225}{5} = 245W.$$

# P33a

Monday, November 8, 2021 12:34 PM

Alternatively,

- a-) Calculate the value of  $R_L$  for maximum power.
- b-) Determine the maximum power absorbed by  $R_L$ .

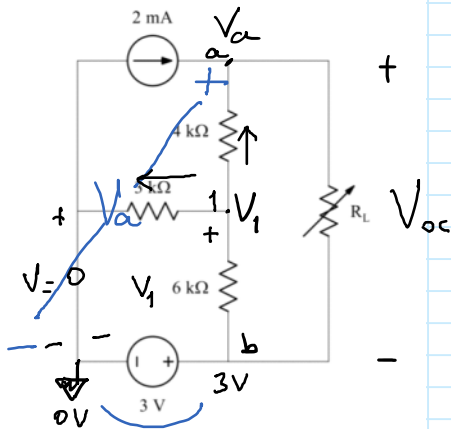


Figure 5: Circuit for question 5.

To find  $V_{Th}$ : Use node-voltage method.

KCL at node a:

$$-2\text{mA} + \frac{V_a - V_1}{4\text{k}} = 0$$

$$V_a - V_1 = 2\text{mA} \cdot 4\text{k}$$

$$V_a - V_1 = 8 \quad \text{--- (1)}$$

KCL at node 1:

$$\frac{V_1 - V_a}{4\text{k}} + \frac{V_1}{3\text{k}} + \frac{V_1 - 3}{6\text{k}} = 0$$

$$(3) \quad (4) \quad (2)$$

$$3V_1 - 3V_a + 4V_1 + 2V_1 - 6 = 0$$

$$9V_1 - 3V_a = 6$$

$$\text{--- (2)}$$

Solve (1) and (2) simultaneously,

$$V_a - V_1 = 8$$

$$+ \frac{3V_1 - V_a}{1} = 2$$

$$2V_1 = 10 \Rightarrow V_1 = 5\text{V} \Rightarrow V_a = 13\text{V}$$

$$V_{Th} = V_{oc} = V_a - 3\text{V} = 13 - 3 = 10\text{V}.$$

# P34

Saturday, October 31, 2020 11:52 AM

7-)

Find  $v_1$  and  $v_2$  for the circuit in Fig.2.

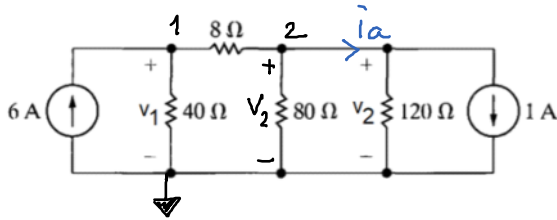


Figure 2: Circuit for question 2.

KCL at node 1:

$$-6 + \frac{U_1}{40} + \frac{U_1 - U_2}{8} = 0 \quad (1)$$

KCL at node 2:

$$\frac{U_2 - U_1}{8} + \frac{U_2}{80} + \bar{i}_a = 0 \quad (2)$$

$$\text{Also, } \bar{i}_a = \frac{U_2}{120} + 1 \quad (3)$$

Substitute (3) in (2):

$$\frac{U_2 - U_1}{8} + \frac{U_2}{80} + \frac{U_2}{120} + 1 = 0 \quad (4)$$

Solve (1) and (4) simultaneously:

$$\frac{U_1}{40} + \frac{U_1 - U_2}{8} = 6 \quad (1)$$

$$U_1 + 5U_1 - 5U_2 = 6 \cdot 40 = 240 \quad (1) \quad *$$

$$\frac{U_2 - U_1}{8} + \frac{U_2}{80} + \frac{U_2}{120} = -1 \quad (4)$$

$$30U_2 - 30U_1 + 3U_2 + 2U_2 = -240 \quad (4)$$

$$35U_2 - 30U_1 = -240$$

$$7U_2 - 6U_1 = -48 \quad (4) \quad *$$

$$+ 6U_1 - 5U_2 = 240 \quad (1)$$


$$7U_2 - 5U_2 = 240 - 48$$

$$2U_2 = 192 \Rightarrow U_2 = 96 \text{ V.}$$

$$6U_1 = 240 + 5(96) \Rightarrow U_1 = \frac{240 + 5(96)}{6} = 120 \text{ V.}$$


Ex:

For the circuit below,

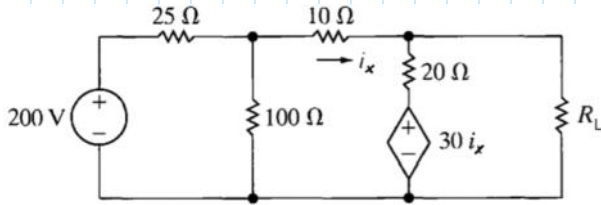

Find  $R_L$  for maximum power transfer. Find  $P_{R_L}$  at max. power.




Ans:

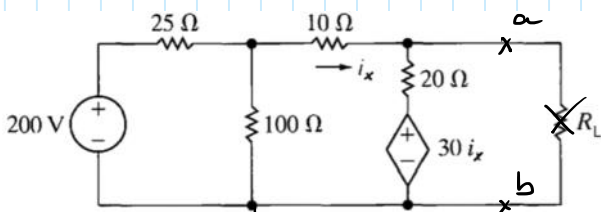

We find the Thevenin circuit + wrt. a and b.

$V_{o.c} = ?$

Source Transformation

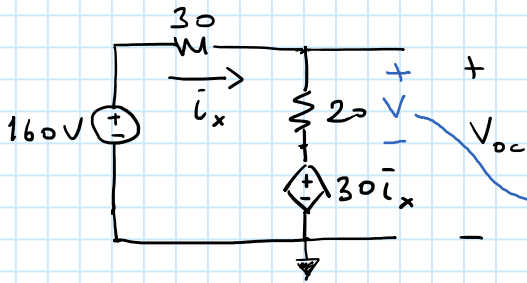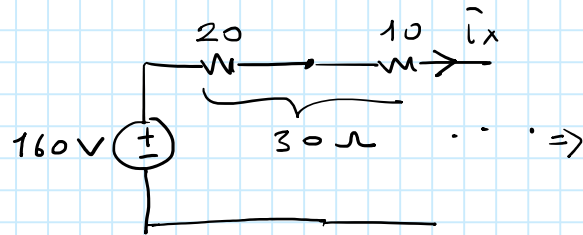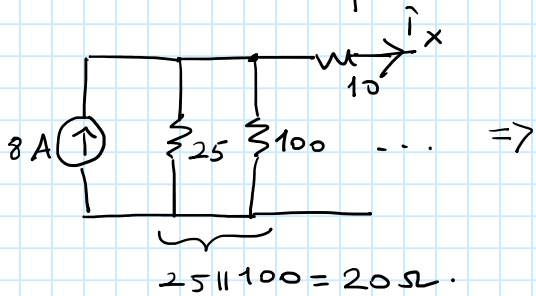

Mesh Equation (KVL) for mesh 1:

$$-160 + 30\hat{i}_x + V_{oc} = 0 \quad (1)$$

Ohm's law across 20Ω resistor:

$$V_{oc} - 30\hat{i}_x = 20\hat{i}_x \quad (2)$$

$$\hookrightarrow \hat{i}_x = \frac{V_{oc}}{50}$$

Substitute  $\hat{i}_x$  into (1),


$$30\left(\frac{V_{oc}}{50}\right) + V_{oc} = 160 \Rightarrow \frac{3V_{oc}}{5} + V_{oc} = 160 \Rightarrow \frac{8V_{oc}}{5} = 160$$

$$\Rightarrow V_{oc} = \frac{5 \cdot 160}{8} = 100 = V_{Th}$$

→ To find  $R_{Th}$ , we can use the test voltage,  $V_T$ , method:

# P36

Friday, November 6, 2020 9:16 AM

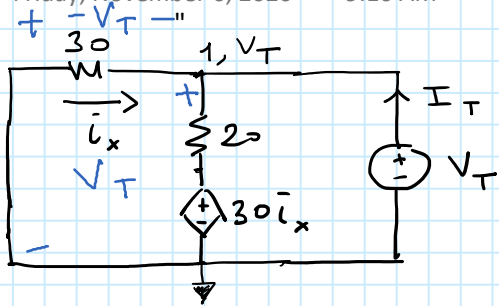

KCL at node 1:

$$-i_x + \frac{V_T - 30i_x}{20} - I_T = 0 \quad (1)$$

Ohm's law across 30 ohm resistor:

$$30i_x = -V_T \quad (2)$$

$$\Rightarrow i_x = \frac{-V_T}{30}$$

Substitute  $i_x$  in (1):

$$\frac{V_T}{30} + \frac{V_T - 30\left(\frac{-V_T}{30}\right)}{20} = I_T \Rightarrow \frac{V_T}{30} + \frac{V_T}{10} = I_T \Rightarrow$$


$$\frac{4V_T}{30} = I_T \Rightarrow R_{Th} = \frac{V_T}{I_T} = \frac{30}{4} = 7.5 \Omega.$$

To find  $P_{RL}$ :

$$P_{RL} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(100)^2}{4(7.5)} \approx 333 \text{ W.}$$


Ex:

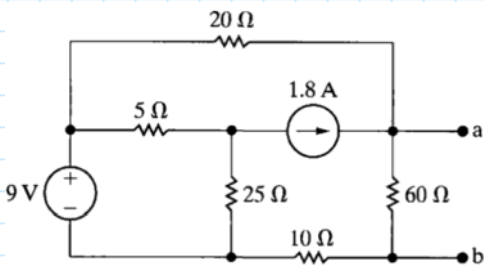For the circuit below, find the Thevenin circuit wrt. a-b.



Ans:

To find  $V_{Th}$ :

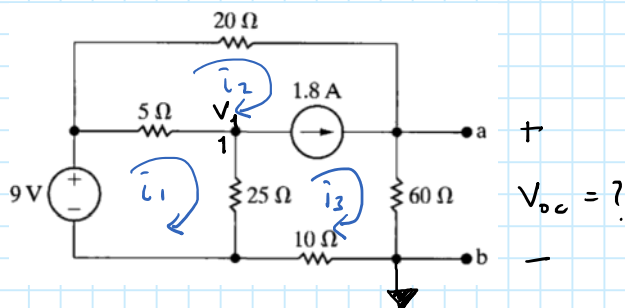


KVL for mesh 1:

$$-9 + 5(i_1 - i_2) + 25(i_1 - i_3) = 0 \quad (1)$$

KVL for mesh 2:

$$20i_2 + (V_{oc} - V_1) + 5(i_2 - i_1) = 0$$

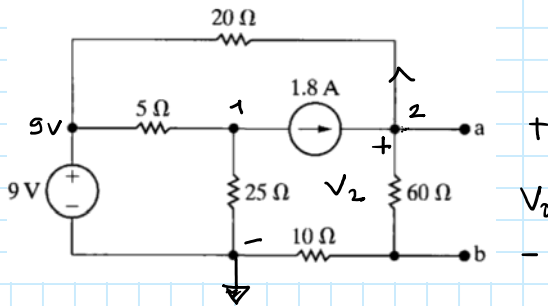$\Rightarrow$  5 unknown already  $\Rightarrow$  Let us not use "Mesh-current" method.



KCL at node 2:

$$\frac{V_2 - 9}{20} - 1.8 + \frac{V_2}{70} = 0$$


$$\frac{V_2 - 9}{20} + \frac{V_2}{70} = 1.8$$

$V_{o.c} = V_{Th}$

$$\Rightarrow V_2 = 35V.$$

$\Rightarrow V_{Th} = V_{o.c} = 35 \cdot \frac{60}{60 + 10}$  (Voltage division) = 30V.

To find  $R_{Th}$ :

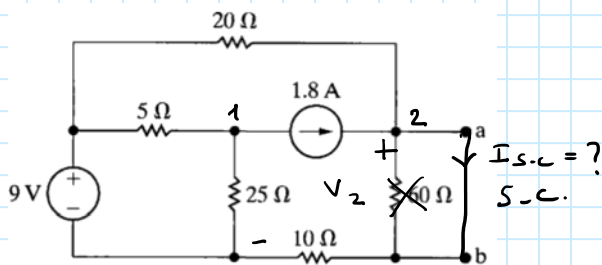

KCL at node 2:

$$\frac{V_2 - 9}{20} - 1.8 + \frac{V_2}{10} = 0$$



$$\Rightarrow V_2 = 15V.$$

Using Ohm's law across 10Ω:

$$\Rightarrow I_{sc} = \frac{V_2}{10} = 1.5A.$$

$\Rightarrow R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{30}{1.5} = 20\Omega.$

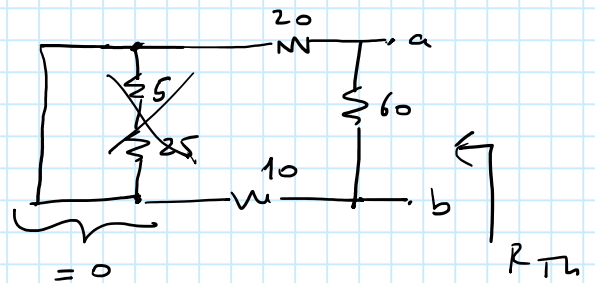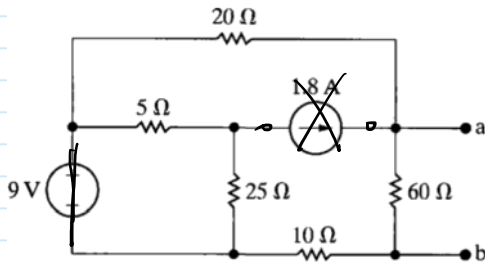Alternatively, we could use the de-activation technique:




$\Rightarrow R_{Th} = (20 + 10) \parallel 60 = 30 \parallel 60$


$$= \frac{30 \cdot 60}{90} = 20\Omega //$$

Ex:

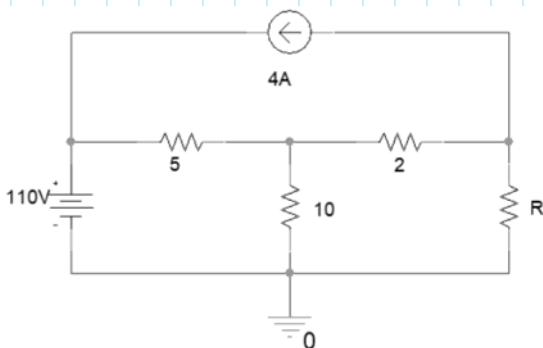For the circuit given below, find  $R$  for max. power transfer and  $P_{RL} = ?$




Ans:

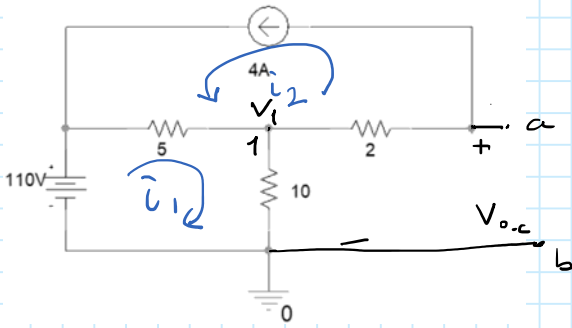

$$\Rightarrow V_{o.c} = 60 - 8 = 52V.$$

$$\Rightarrow V_{Th} = 52V.$$


To find  $R_{Th}$ :

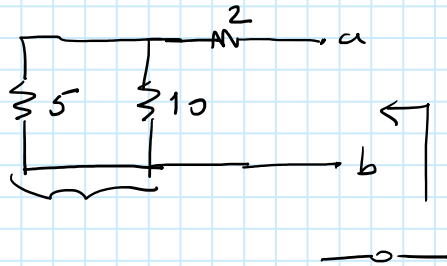

$$R_{Th} = 2 + (5 \parallel 10) \approx 5.3 \Omega.$$

Ex:

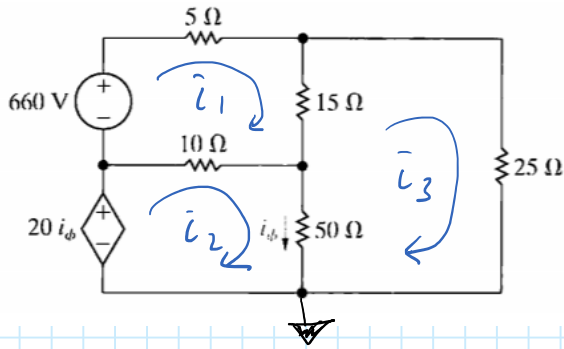Given the circuit below, find the power delivered by the dependent source:



Ans:

KVL in mesh 1:

$$-660 + 5\hat{i}_1 + 15(\hat{i}_1 - \hat{i}_3) + 10(\hat{i}_1 - \hat{i}_2) = 0$$

$$\Rightarrow 30\hat{i}_1 - 10\hat{i}_2 - 15\hat{i}_3 = 660 \quad (1)$$

KVL in mesh 2:

$$-20\hat{i}_\phi + 10(\hat{i}_2 - \hat{i}_1) + 50(\hat{i}_2 - \hat{i}_3) = 0$$

$$\text{Also, } \hat{i}_\phi = \hat{i}_2 - \hat{i}_3$$

$$\text{or } -10\hat{i}_1 + 60\hat{i}_2 - 50\hat{i}_3 = 20\hat{i}_\phi = 20\hat{i}_2 - 20\hat{i}_3$$

$$\text{or } -10\hat{i}_1 + 40\hat{i}_2 - 30\hat{i}_3 = 0 \quad (2)$$

KVL in mesh 3:

$$50(\hat{i}_3 - \hat{i}_2) + 15(\hat{i}_3 - \hat{i}_1) + 25\hat{i}_3 = 0$$

$$-15\hat{i}_1 - 50\hat{i}_2 + 50\hat{i}_3 = 0 \quad (3)$$

Let us solve (1), (2) and (3) simultaneously,

# P39

Friday, November 6, 2020 10:58 AM

$$30\hat{i}_1 - 10\hat{i}_2 - 15\hat{i}_3 = 660$$

or

$$6\hat{i}_1 - 2\hat{i}_2 - 3\hat{i}_3 = 132 \quad \text{--- (1)}$$

Similarly, eqn (2) also simplifies

$$-10\hat{i}_1 + 40\hat{i}_2 - 30\hat{i}_3 = 0$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\hat{i}_3 = 0 \quad \text{--- (2)}$$

Also, eqn (3) can be re-written as

$$-15\hat{i}_1 - 50\hat{i}_2 + 50\hat{i}_3 = 0$$

$$3\hat{i}_1 + 10\hat{i}_2 - 18\hat{i}_3 = 0 \quad \text{--- (3)}$$

$$6\hat{i}_1 - 2\hat{i}_2 - 3\hat{i}_3 = 132 \quad \text{--- (1)}$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\hat{i}_3 = 0 \quad \text{--- (2)}$$

$$3\hat{i}_1 + 10\hat{i}_2 - 18\hat{i}_3 = 0 \quad \text{--- (3)}$$

$$\left. \begin{array}{l} (1) \\ (2) \\ (3) \end{array} \right\} \begin{bmatrix} 6 & -2 & -3 \\ 1 & -4 & 3 \\ 3 & 10 & -18 \end{bmatrix} \begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \\ \hat{i}_3 \end{bmatrix} = \begin{bmatrix} 132 \\ 0 \\ 0 \end{bmatrix}$$

$$A \cdot \hat{i} = b$$

$$\hat{i} = A^{-1} \cdot b$$

Solve  $\hat{i}_1$  from (2)

$$\hat{i}_1 = 4\hat{i}_2 - 3\hat{i}_3 \quad \text{--- (4)}$$

Substitute (4) into (3):

$$3(4\hat{i}_2 - 3\hat{i}_3) + 10\hat{i}_2 - 18\hat{i}_3 = 0$$

or

$$12\hat{i}_2 - 9\hat{i}_3 + 10\hat{i}_2 - 18\hat{i}_3 = 0$$

or

$$22\hat{i}_2 = 27\hat{i}_3 \Rightarrow \hat{i}_3 = \frac{22}{27}\hat{i}_2 \quad \text{--- (5)}$$

Substitute (5) in (1) and (2)

$$6\hat{i}_1 - 2\hat{i}_2 - 3\left(\frac{22}{27}\hat{i}_2\right) = 132 \quad \text{--- (1)}$$

$$\hat{i}_1 - 4\hat{i}_2 + 3\left(\frac{22}{27}\hat{i}_2\right) = 0 \quad \text{--- (2)}$$

$$\Rightarrow 6\hat{i}_1 - 2\hat{i}_2 - \frac{22}{9}\hat{i}_2 = 132 \quad \text{--- (1)}$$

$$\Rightarrow \begin{pmatrix} \hat{i}_1 - 4\hat{i}_2 + \frac{22}{9}\hat{i}_2 \end{pmatrix} = \begin{pmatrix} 0 \end{pmatrix} \cdot (-6)$$

$$= -6\hat{i}_1 + 24\hat{i}_2 - \frac{6 \cdot 22}{9}\hat{i}_2 = 0 \quad \text{--- (7)}$$

Add (6) and (7)

$$22\hat{i}_2 - \frac{22}{9}\hat{i}_2 - \frac{6 \cdot 22}{9}\hat{i}_2 = 132$$

$$22\hat{i}_2 \left( \underset{(9)}{1} - \underset{(1)}{\frac{1}{9}} - \underset{(3)}{\frac{6}{9}} \right) = 132$$

$$\Rightarrow 22\hat{i}_2 \left( \frac{9-1-6}{9} \right) = 132 \Rightarrow \hat{i}_2 = \frac{132 \cdot 9}{22 \cdot 2} = 27 \text{ A} \Rightarrow \hat{i}_1 = 42 \text{ A}, \hat{i}_3 = 22 \text{ A}$$


$$\Rightarrow \hat{i}_\phi = 5 \text{ A} \Rightarrow 20 \hat{i}_\phi = 100 \text{ V}$$

$$P_{20\hat{i}_\phi} = -\hat{i} \cdot U = -100 \hat{i}_2 = -100 \cdot 27 = -2.7 \text{ kW}$$

or  
 $P_{20\hat{i}_\phi} = 2.7 \text{ kW}$  delivered power.  
 ↓  
 (- power)



Ex:

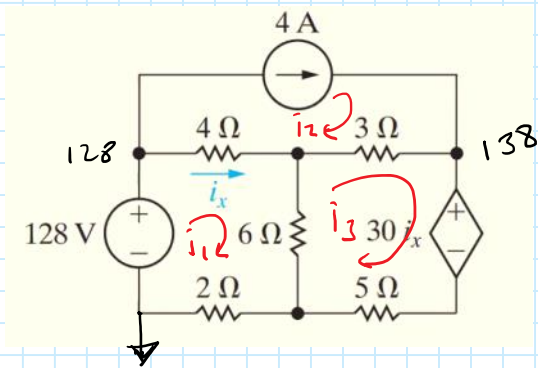

KVL for mesh 1:

$$-128 + 4i_x + 6(i_1 - i_3) + 2i_1 = 0 \quad (1)$$

KVL for mesh 2:

$$(128 - V_1) + 3(i_2 - i_3) + 4(i_2 - i_1) = 0 \quad (2)$$

KVL for mesh 3:

$$6(i_3 - i_1) + 3(i_3 - i_2) + 30i_x + 5i_3 = 0$$

$$i_2 = 4$$

$$i_x = i_1 - 4$$

$$4(i_1 - 4) + 6i_1 - 6i_3 + 2i_1 = 128$$

$$12i_1 - 6i_3 = 144 \quad (1)$$

$$128 - V_1 + 12 - 3i_3 + 16 - 4i_1 = 0$$

$$-4i_1 - 3i_3 - V_1 = -156 \quad (2)$$


$$6i_3 - 6i_1 + 3i_3 - 12 + 30(i_1 - 4) + 5i_3 = 0$$

$$24i_1 + 14i_3 = 132 \quad (3)$$

$$\begin{bmatrix} 12 & -6 & 0 \\ +4 & +3 & +1 \\ 24 & 14 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \\ V_1 \end{bmatrix} = \begin{bmatrix} 144 \\ 156 \\ 132 \end{bmatrix}$$

$$i_1 = 9, i_2 = -6, V_1 = 138$$

Ex!

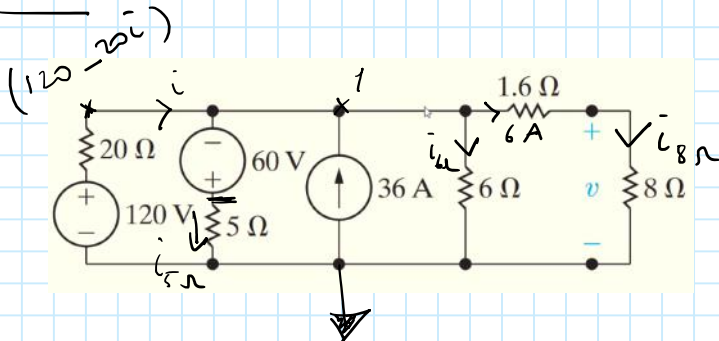

$$V = 48V$$


$$P_{120} = 374.4W$$

$$i_{8\Omega} = \frac{V}{R} = \frac{48}{8} = 6A \quad \checkmark$$

$$i_{5\Omega} = \frac{180 - 20i}{5} = 36 - 4i$$

$$i_{6A} = \frac{120 - 20i}{6} = 20 - \frac{10}{3}i \quad \checkmark$$

KCL at node 1:

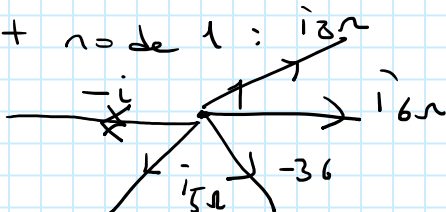

$$-i + i_{5\Omega} + i_{6A} + i_{8\Omega} - 36 = 0$$

$$-i + 36 - 4i + 20 - \frac{10}{3}i + 6 - 36 = 0$$

$$-5i - \frac{10}{3}i = -26$$

$$i(5 + \frac{10}{3}) = 26$$

$$i = \frac{26}{\frac{25}{3}} = \frac{26 \cdot 3}{25} A$$

$$P_{120V} = 120 \cdot \frac{26 \cdot 3}{25} = 374.4W$$

# Final Exam Starts from Here


## - RL & RC Circuits -

P41

Tuesday, November 10, 2020 4:35 PM

### Natural Response of an RL-Circuit: (Discharging the current of the inductor)

Consider the following circuit:

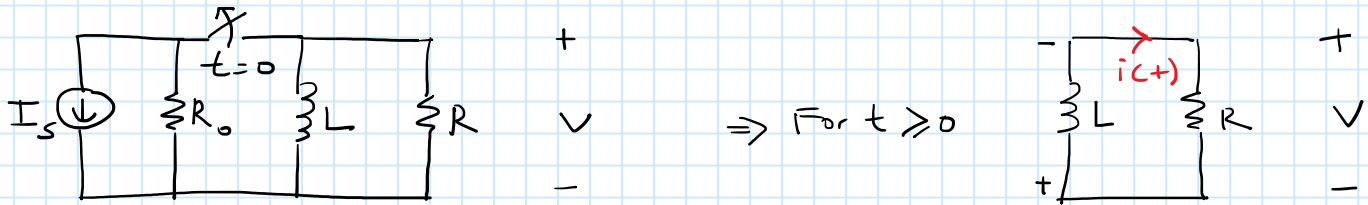

Norton circuit is used to charge L for  $t < 0$

charge L for  $t < 0$

Assume that  $L \frac{di}{dt} = 0$ ,  $t < 0$  (the inductor is a short circuit before the release of the switch.)

$\Rightarrow$  For  $t < 0$ , currents in  $R_0$  and  $R = 0$ .

All current flows through the L.

For  $t = 0$ , the inductor begins to release its energy.

For  $t \geq 0$ , the KVL equation for  $i(t)$  is:

$$\boxed{L \frac{di(t)}{dt} + Ri(t) = 0} \quad (1^{\text{st}} \text{ order ODE})$$

↳ Ordinary D.H. Eqn.

$$i(0^-) = i(0^+) = I_0$$

↳ just before 0      ↳ just after 0.


$$\Rightarrow i(0) = I_0 = I_s$$

$\Rightarrow$  The solution is:

$$\boxed{i(t) = I_0 \cdot e^{-\left(\frac{R}{L}\right)t}} \quad (A), \text{ and}$$

$v(t) = i(t)R$  gives
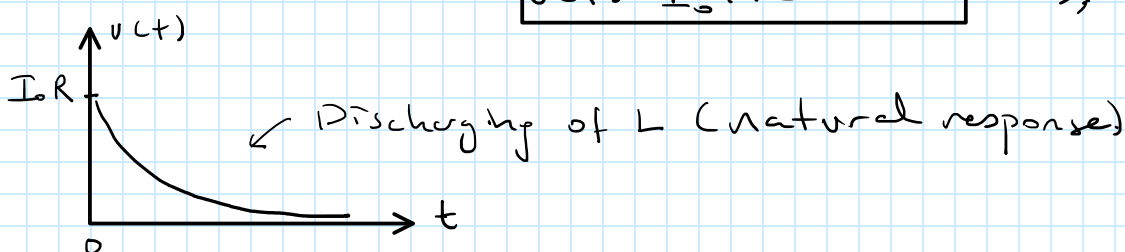
$$\boxed{v(t) = I_0 R e^{-\left(\frac{R}{L}\right)t}} \quad (V), \quad t \geq 0.$$



The power dissipation:  $p = v \cdot i = i^2 R = \frac{v^2}{R}$ . Thus,

$$p = i(t)^2 \cdot R = I_0^2 R e^{-2(R/L)t}, \quad t \geq 0.$$

The energy delivered to the resistor at any time  $t$ :

$$W = \int_0^t p \cdot dx = \int_0^t I_0^2 R \cdot e^{-2(R/L)x} dx = \frac{1}{2} L I_0^2 [1 - e^{-2(R/L)t}], \quad t \geq 0$$

Now,

$$\lim_{t \rightarrow \infty} W = \lim_{t \rightarrow \infty} \left\{ \frac{1}{2} L I_0^2 [1 - e^{-2(R/L)t}] \right\} = \frac{1}{2} L I_0^2 \text{ (J) is the initial energy stored in the inductor.}$$

Here, the constant  $(\frac{L}{R})$  is called the "time constant":

$$\text{Time constant} = \tau = \frac{L}{R}$$


At one  $\tau$  after  $t=0$ ,

$$i(\tau) = I_0 \cdot e^{-\left(\frac{R}{L}\right)\left(\frac{L}{R}\right)} = I_0 e^{-1} \Rightarrow \text{The current is reduced to } 0.37 \text{ } 37\% \text{ of its value at } t=0.$$

At  $2\tau$ ,  $i(2\tau) = 0.13 I_0 \Rightarrow$  Reduced to 13%.

At  $5\tau$ , it is conventional to assume that  $i(t)$  is reduced to zero, and all inductor energy is released.

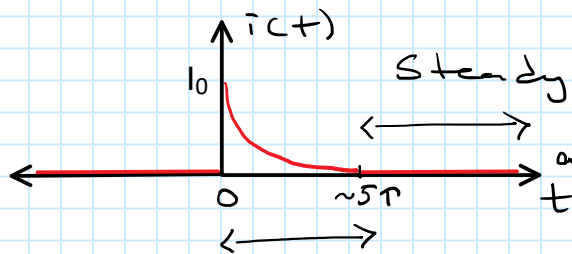**Remark:** Consider the overall response.




Steady State Response: The response that exists a long time after switching


Transient Response: (The response for momentary events)

## Natural Response of an RC-Circuit:

Consider the following circuit:

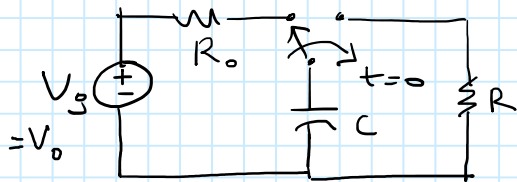

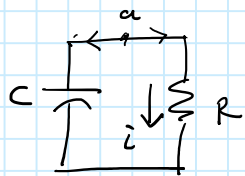For  $t \geq 0$ , the response is the "natural response":



KCL equation is:

$$C \frac{dV}{dt} + \frac{V}{R} = 0$$

$$V(0) = V_0 \text{ (initial capacitor voltage)}$$

The solution is:

$$V(t) = V_0 e^{-t/\tau}, \quad t \geq 0 \quad \text{where } \tau = RC \text{ (time constant)}$$

and

$$i(t) = \frac{V(t)}{R} = \frac{V_0}{R} e^{-t/\tau}, \quad t \geq 0.$$


$$P = \frac{V_0^2}{R} e^{-2t/\tau}, \quad t \geq 0.$$

$$W(t) = \frac{1}{2} C [V_0^2 (1 - e^{-2t/\tau})], \quad t \geq 0$$

$$\lim_{t \rightarrow \infty} W(t) = \frac{1}{2} C V_0^2 \text{ (initial energy stored in the capacitor)}$$

## Step Response of an RL-Circuit: (Charging the inductor)

Consider the following circuit:

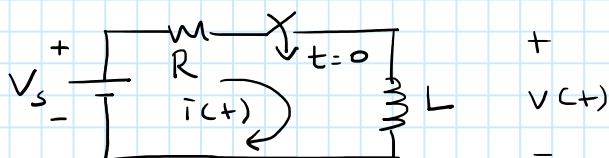

After the switch is closed, the KVL eqn is:

$$V_s = R i(t) + L \frac{di(t)}{dt}$$

$$\text{or } \frac{di(t)}{dt} = \frac{1}{L} [V_s - R i(t)]$$

# P44

Saturday, November 21, 2020 10:30 AM

$$\frac{d\bar{i}(t)}{dt} = \frac{1}{L} [V_s - R\bar{i}(t)]$$

or  $\frac{d\bar{i}(t)}{dt} + \frac{R}{L}\bar{i}(t) = \frac{V_s}{L}$  (1<sup>st</sup> order ODE, linear non-homogeneous)

The initial condition is  $\bar{i}(0) = I_0 = 0$


The solution is:

$$\bar{i}(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R}) e^{-\left(\frac{R}{L}\right)t}, \quad t \geq 0$$

For  $I_0 = 0$ :

(Step response of 1<sup>st</sup> order RL circuit)

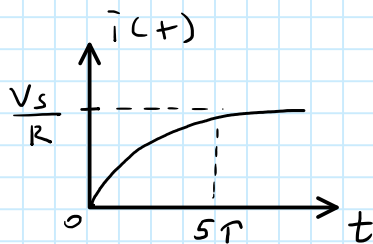
$$\bar{i}(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-\left(\frac{R}{L}\right)t}$$



The voltage can be obtained from:

$$v = L \frac{d\bar{i}(t)}{dt} = L \left(-\frac{R}{L}\right) \left(\underbrace{I_0 - \frac{V_s}{R}}_0\right) e^{-\left(\frac{R}{L}\right)t}$$
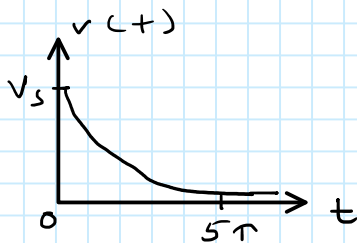
$$v(t) = V_s e^{-\left(\frac{R}{L}\right)t} \quad (v), \quad t \geq 0.$$



Ex:


For the following circuit

For  $t < 0$ , the circuit is already settled.


a-) Find  $i(t)$ ,  $t \geq 0$

b-) What is the initial voltage across the inductor just

after the switch is moved to position b.

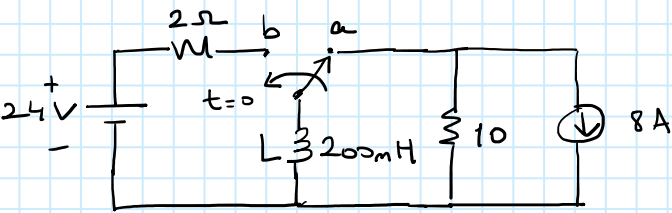

Ans:

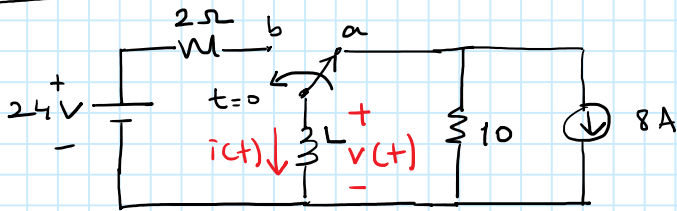

For  $t < 0$ ,  $i(0) = I_0 = -8 \text{ A}$ .

$$i(\infty) = I_{\text{final}} = \frac{24 \text{ V}}{2 \Omega} = 12 \text{ A}$$

$$\text{and } \tau = \frac{L}{R} = \frac{200 \text{ mH}}{2} = 100 \text{ ms}$$

a-) Using the step response for RL circuit:

$$i(t) = \frac{V_s}{R} + \left( I_0 - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}}, \quad V_s = 24, R = 2 \Omega$$

$\underbrace{\hspace{1.5cm}}_{I_{\text{final}}}$ 
 $\quad \underbrace{\hspace{1.5cm}}_{-8 \text{ A}}$ 
 $\quad \underbrace{\hspace{1.5cm}}_{I_{\text{final}}}$


$$\Rightarrow i(t) = 12 - 20 e^{-10t} \text{ A}$$

$$b-) v = L \cdot \frac{di(t)}{dt} = 0.2 (200 e^{-10t}) = 40 e^{-10t} \text{ (V)}, t \geq 0$$

$$\Rightarrow v(0^+) = 40 \text{ V} //$$

### Step Response of an RC-Circuit:

Consider the following circuit:

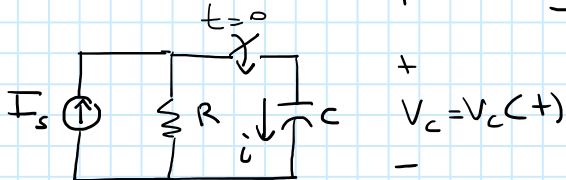

The KCL eqn is: for  $t \geq 0$

$$C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{R} = I_s$$

or

$$\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = \frac{I_s}{C} \quad (\text{1st order ODE})$$

The solution is:

$$V_c(t) = I_s R + [U_0 - I_s R] e^{-t/RC}, \quad t \geq 0$$

and

$$i(t) = \left[ I_s - \frac{U_0}{R} \right] e^{-t/RC}, \quad t \geq 0$$

$$\tau = 10$$

$$RC = 2$$

$$R = 2 \Omega$$

## General Response for Step & Natural Responses:

The general response is given as:

of 1<sup>st</sup> order diff. equations.

$$x(t) = X_f + [X(t_0) - X_f] e^{-(t-t_0)/\tau}$$

In another interpretation;

The Unknown variable = The final value of the variable +

$$\left[ \begin{array}{l} \text{The initial value} \\ \text{of the variable} \end{array} - \begin{array}{l} \text{The final} \\ \text{value of} \\ \text{the variable} \end{array} \right] e^{\frac{-(t-t_0)}{\tau}}$$

When computing the step and/or natural responses of an RL or RC circuits using this general formulation, the following steps are used:

1-) Identify the variable of interest:

For an RL circuit  $\rightarrow$  Inductor current.

For an RC circuit  $\rightarrow$  Capacitor voltage.

2-) Determine the initial value of the variable, which is its value at  $t_0$ . If chosen as capacitor voltage or inductor current as the variable of interest, then

$$V_C(t_0^-) = V_C(t_0^+) \text{ and } I_L(t_0^-) = I_L(t_0^+)$$

Otherwise, we must use the  $t_0^+$  value of the variable as initial value.


3-) Calculate the final value of the variable at  $t \rightarrow \infty$ .

4-) Calculate the time constant.

5-) Substitute all variables into the general formulation.

Ex:


For the following circuit

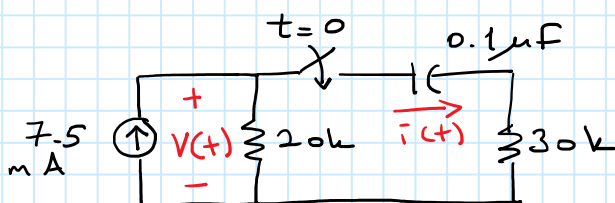

For  $t < 0$ , the circuit is already settled. Initial charge of the capacitor is 0.

Find, a-)  $i(t)$  for  $t \geq 0$   
b-)  $v(t)$ ,  $t \geq 0$ .

Ans:

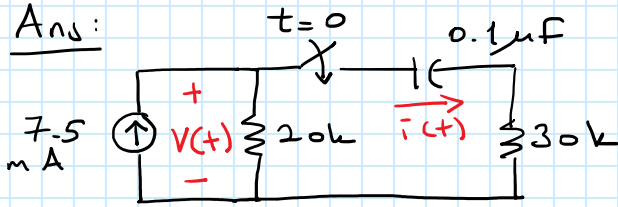


- a)
- 1) Variable of interest is  $i(t)$ .
  - 2) Variable of interest is the cap. current.

$t_0 = 0$

$i(0^+) = ?$

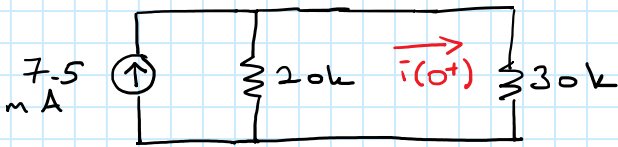At  $t = 0^+$  → At this instant, the rate of change in current is max.  $\nearrow$  max.



For the capacitor,  $i(t) = C \frac{dy_c(t)}{dt}$


When is  $i(t)$  max?  $\Rightarrow$  short circuit.

$i(0^+) = (7.5 \text{ mA}) \cdot \frac{20k}{50k} = 3 \text{ mA}$  (from current division.)

Note that  $i(0^-) = 0$   
 $i(0^+) = 3 \text{ mA}$  }  $i(0^-) \neq i(0^+)$

3-)  $i(t = \infty) = i_{\text{final}} = 0$  and

4-)  $\tau = RC = ?$

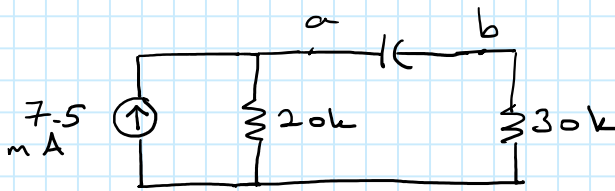

$R = R_{Th}$  wrt. point a-b.  
 To find  $R_{Th}$ : Deactivate the indep. sources:  
 $\Rightarrow R_{Th} = 20k + 30k = 50k \Omega$ .


$\Rightarrow \tau = RC = (50k)(0.1 \mu F) = 5 \text{ ms}$ .

5-)  $i(t) = 0 + (3 - 0)e^{-t/5 \times 10^{-3}}$  (mA),  $t \geq 0$ .

or  $i(t) = 3e^{-200t}$ , (mA),  $t \geq 0$ .

b-) Choose the unknown variable as the cap. voltage:  
 Then find  $V(t)$ .

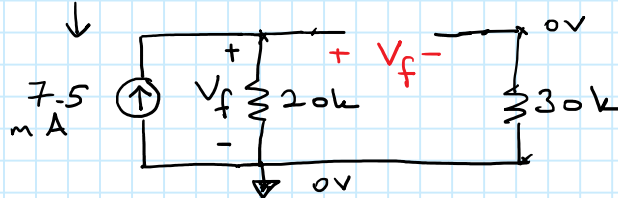$\Rightarrow V_c(0^+) = 0V$ ,  $V_f = (7.5)(20) = 150V$ ,  $\tau = 5 \text{ ms}$ .





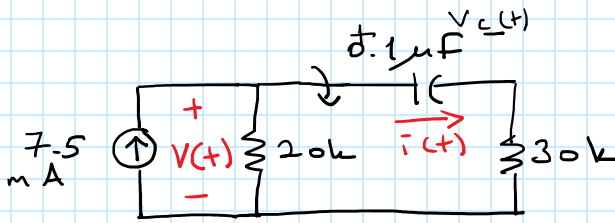
# P48

Saturday, November 21, 2020 11:47 AM

$$\Rightarrow v_C(t) = 150 - 150 e^{-200t}, \quad t \geq 0$$



$$\Rightarrow v(t) = v_C(t) + v_R(t), \quad t \geq 0$$


$\downarrow$                        $\downarrow$   
 $\checkmark$                        $i(t) \cdot R$

$$\Rightarrow v(t) = 150 - 150 e^{-200t} + (30)(3) e^{-200t}$$

$$\Rightarrow v(t) = 150 - 60 e^{-200t} \text{ (V)}, \quad t \geq 0. \quad //$$

Ex:

For the circuit

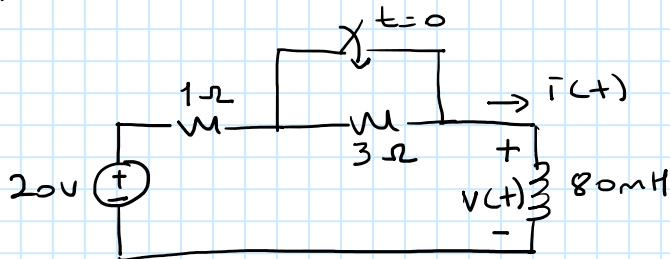

Find  $v(t)$  and  $i(t)$  for  $t \geq 0$ .

Ans:

Variable of interest  $\rightarrow$  inductor current  $i(t)$ .

$$I_0 = \frac{20V}{4\Omega} = 5A, \quad I_f = \frac{20V}{1\Omega} = 20A.$$


$$\tau = \frac{L}{R} = \frac{80mH}{1\Omega} = \frac{80mH}{1\Omega} = 80ms.$$

$$\Rightarrow i(t) = 20 + (5 - 20) e^{-t/80ms} = 20 - 15 e^{-12.5t} \text{ (A)}, \quad t \geq 0.$$

$$\Rightarrow v(t) = L \frac{di(t)}{dt} = 15 e^{-12.5t} \text{ (V)}, \quad t \geq 0.$$


Ex:

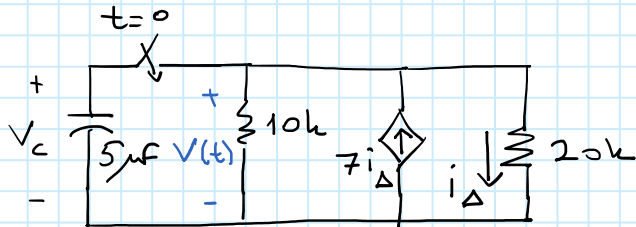For the given circuit, find  $V(t)$ . ( $V_c = 10V$  for  $t < 0$ )




Ans:

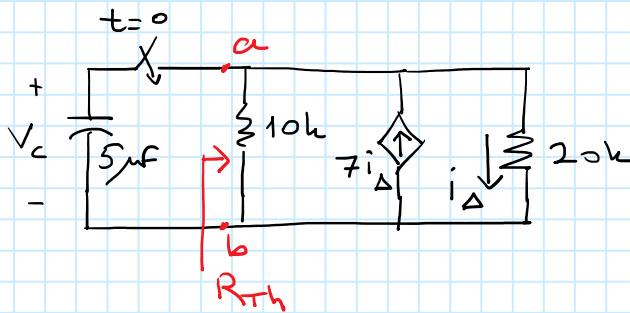- Variable of interest is the cap. voltage ( $V_c = V, t \geq 0$ )
- To determine  $V_o(0)$ , we can first replace the capacitor terminals by its Thevenin resistance.



To find  $R_{Th}$ :

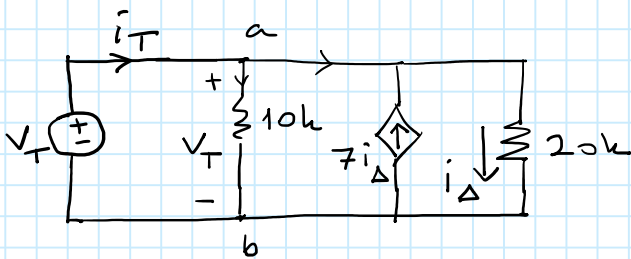

KCL at node a:


$$\Rightarrow \bar{i}_T = \left[ \frac{V_T}{10k} - 7i_\Delta + i_\Delta \right]$$

where  $i_\Delta = \frac{V_T}{20k}$  (Ohm's law across 20kΩ)

$$\Rightarrow \bar{i}_T = \left[ \frac{V_T}{10k} - 7 \frac{V_T}{20k} + \frac{V_T}{20k} \right]$$

$$\Rightarrow R_{Th} = \frac{V_T}{\bar{i}_T} = -5k\Omega$$

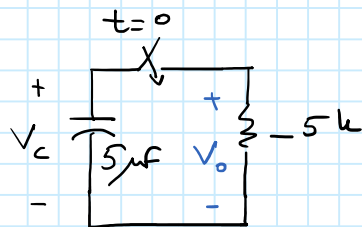Negative resistance indicates that signal grows.



$$- V_c(0^-) = V_c(0^+) = 10V$$

$$- V_c(\infty) = V_o(\infty) = 0V$$

$$- \tau = RC = (5\mu F)(-5k) = -25ms$$

$$- V(t) = V_f + [V(0) - V_f] e^{-[t/(-25ms)]}$$

$\downarrow$                        $\downarrow$                        $\downarrow$   
 $V_o$                       10V                       $V_o$

$$\Rightarrow V(t) = 10e^{40t}, t \geq 0 \text{ (Unbounded response)}$$


(not realistic!)

## RLC Circuits (Chapter 8)

### Natural & Step Response:

#### 1-) Natural Response of Parallel RLC Circuit:

The RLC circuit is given as: (parallel)

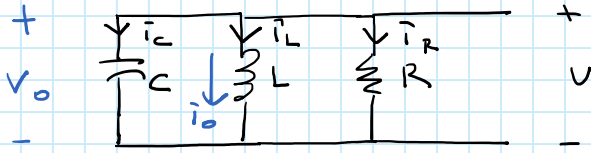

KCL at the top node:

$$\underbrace{\frac{V}{R}}_{i_R} + \underbrace{\frac{1}{L} \int v dt}_{i_L} + \underbrace{C \frac{dV}{dt}}_{i_C} = 0$$

Differentiate both sides wrt.  $t$ :

$$\frac{1}{R} \frac{dV}{dt} + \frac{V}{L} + C \frac{d^2 V}{dt^2} = 0$$

Re-arranging this equation,

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0 \quad (2^{\text{nd}} \text{ order differential equation})$$

The classical approach to solve this equation is to assume a solution in the form which is exponential.

Let  $v = Ae^{st}$  be the solution. Then, substitute this solution into the equation:

$$As^2 e^{st} + \frac{1}{RC} Ase^{st} + \frac{Ae^{st}}{LC} = 0$$

or

$$Ae^{st} \left( s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$$

$A=0$  is a trivial solution, it cannot be accepted.

$$\Rightarrow s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad \text{This equation is called the "characteristic equation".}$$

There are 2 roots:

$$s_{1,2} = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Thus,  $v = A_1 e^{s_1 t}$  and  $v = A_2 e^{s_2 t}$  are the 2 solutions.

Also,  $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$  is a solution.

Consider the roots of the characteristic equation in another notation:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where

$\alpha = \frac{1}{2RC}$  is called the "Neper frequency".

and

$\omega_0 = \frac{1}{\sqrt{LC}}$  is called the "Resonant radian frequency".

There are 3 possible outcomes:

1-) If  $\omega_0^2 < \alpha^2 \rightarrow$  Both roots are real. The response is called "overdamped".

2-) If  $\omega_0^2 > \alpha^2 \rightarrow$  Both roots are complex, and conjugate of each other. That is;  $s_1 = a_1 + jb_1$ , then  $s_2 = a_1 - jb_1$  or vice versa. The response is called "underdamped".

3-) If  $\omega_0^2 = \alpha^2 \rightarrow s_{1,2}$  are real and equal. The response is called "critically damped".

Ex:

For an RLC circuit, with  $R = 200 \Omega$ ,  $L = 50 \text{ mH}$ ,  $C = 0.2 \mu\text{F}$

a) Find the roots of the characteristic equation.

b) Determine the type of response?

c) Repeat part a and b for  $R = 312.5 \Omega$ .

d) What values of  $R$  causes the response to be critically damped?

Ans:

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(200)(0.2)} = 1.25 \times 10^4 \text{ rad/s}, \alpha^2 = 1.5625 \times 10^8$$

$$\omega_0^2 = \frac{1}{LC} = \frac{10^3 \cdot 10^6}{(50)(0.2)} = 10^8 \text{ rad}^2/\text{s}^2$$

$$a-) s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1.25 \times 10^4 \pm \sqrt{1.5625 \times 10^8 - 10^8}$$

$$\Rightarrow s_1 = -5000 \text{ rad/s}, s_2 = -20000 \text{ rad/s}$$

b-) Since  $\omega_0^2 < \alpha^2$ , it is overdamped.

c-) For  $R = 312.5 \Omega$ ,  $\alpha = 8000 \frac{\text{rad}}{\text{s}}$ ,  $\alpha^2 = 0.64 \times 10^8 \text{ rad}^2/\text{s}^2$   
and  $\omega_0^2 = 10^8 (\text{rad}/\text{s})^2$

$$s_1 = -8000 + j6000 \text{ (rad/s)}, \quad s_2 = -8000 - j6000 \text{ (rad/s)}$$

The response is underdamped since  $\omega_0^2 > \alpha^2$ .

d-) For critically damped response,  $\alpha^2 = \omega_0^2$

$$\Rightarrow \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = 10^8 \Rightarrow \frac{1}{2RC} = 10^4 \Rightarrow \boxed{R = 250 \Omega}$$

$\downarrow$   
0.2  $\mu\text{F}$ .

### The Overdamped Voltage Response:

The solution is in the form:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \text{where } s_1 \text{ and } s_2 \text{ are the}$$

roots of the characteristic equation.  $A_1$  and  $A_2$  are the constants to be determined by the initial conditions

$\Rightarrow$  Initial conditions:  $v(0^+)$  or  $\frac{dv(0^+)}{dt}$

Then,  $\boxed{v(0^+) = A_1 + A_2}$  and  $\boxed{\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2}$

— The  $v(0^+)$  is the initial voltage on the capacitor.

— The value of  $\frac{dv(0^+)}{dt}$  can be obtained by finding the current through the capacitor

$$\boxed{\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}}$$

Also, 
$$i_c(0^+) = \frac{-V_0}{R} - I_0.$$

Summary for Finding the "Overdamped" Response:

1-) Find  $s_1$  and  $s_2$

2-) Find  $v(0^+)$  and  $\frac{dv(0^+)}{dt}$


3-) Find  $A_1$  and  $A_2$  from 
$$v(0^+) = A_1 + A_2,$$
  
$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2.$$

4-) Substitute the values into the solution

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Ex:

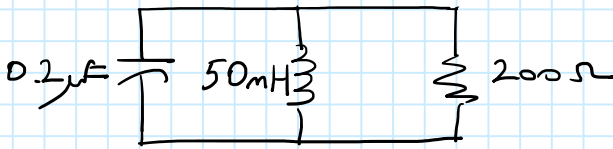For the circuit below, given that  $v(0^+) = 12V$ ,  $i_L(0^+) = 30mA$




a-) Find the initial current in each branch of the circuit.

b-) Find the initial value of  $\frac{dv}{dt}$ .

c-) Find the response for  $v(t)$ .

Ans:

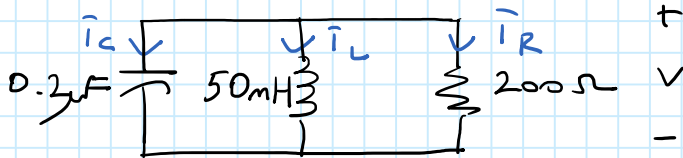

a-)  $i_L(0^+) = i_L(0^-) = i_L(0) = 30mA$

$i_R(0^+) = \frac{12V}{200} = 60mA$

Then, from the KCL at the top node:

top node:

$i_c(0^+) = -i_L(0^+) - i_R(0^+) = -90mA$ . (the real direction is opposite to our assumption.)

b-)  $\frac{dv(0^+)}{dt} = ?$ ,  $i_c(0^+) = C \frac{dv(0^+)}{dt}$

$\Rightarrow \frac{dv(0^+)}{dt} = \frac{1}{C} i_c(0^+) = \frac{-90 \times 10^{-3}}{0.2 \times 10^{-6}} = -450 \frac{kV}{s}$

c-) The roots of the characteristic equation are

$S_1 = -1.25 \times 10^4 + \sqrt{1.5625 \times 10^8 - 10^8} = -5000 \text{ rad/s}$


$S_2 = -1.25 \times 10^4 - \sqrt{1.5625 \times 10^8 - 10^8} = -20000 \text{ rad/s}$


To find the coefficients  $A_1$  and  $A_2$ :

$12 = A_1 + A_2$ ,  $-450 \times 10^3 = -5000 A_1 - 20000 A_2$

$\Rightarrow A_1 = -14V$ ,  $A_2 = 26V$

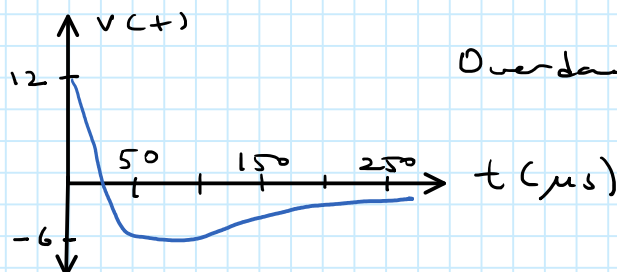$\Rightarrow v(t) = (-14e^{-5000t} + 26e^{-20000t}) (V), t \geq 0$



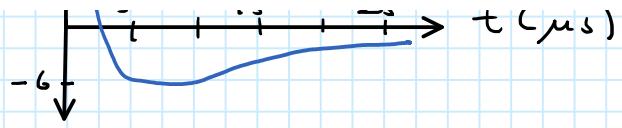

## Underdamped Voltage Response:

When  $\omega_0^2 > \alpha^2$ , the roots are

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \quad , \quad j = i = \sqrt{-1}$$

$$s_1 = -\alpha + j\omega_d \quad , \quad s_2 = -\alpha - j\omega_d$$

where

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  is called the "damped radian frequency".

The response is:

$$v(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

where the coefficients  $B_1$  and  $B_2$  can be obtained from:

$$v(0^+) = V_0 = B_1$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

( $\alpha$ : damping factor)

Ex!

For the given circuit

Given:

$$V_0 = 0V, \quad i_0 = -12.25mA$$

a-)  $s_1, s_2 = ?$

b-)  $v|_{t=0} = v(0), \quad \frac{dv}{dt}|_{t=0} = ?$

c-)  $v(t) = ? , t \geq 0$

Ans:

$$\alpha = \frac{1}{2RC} = 200 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^3 \text{ rad/s}$$


$$\Rightarrow \omega_0^2 > \alpha^2 \Rightarrow \text{Underdamped!}$$

Now,

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 100\sqrt{96} = 979.80 \text{ rad/s}$$

$$s_1 = -\alpha + j\omega_d = -200 + j979.8 \text{ rad/s}$$
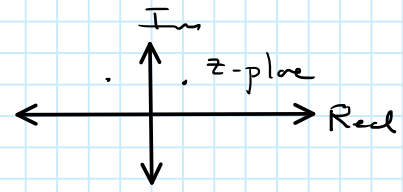
$$s_2 = -\alpha - j\omega_d = -200 - j979.8 \text{ rad/s}$$





$$b-) v(0^+) = ? , \frac{dv(0^+)}{dt} = ?$$

$$v(0) = v(0^+) = V_0 = 0V.$$

To find  $\frac{dv(0^+)}{dt}$ , we need  $i_C(0^+)$ .

$$\Rightarrow i_R(0^+) = 0 \text{ (since } V_0 = 0)$$

$$\Rightarrow i_C(0^+) = -i_L(0^+) - i_R(0^+) = -(-12.25 \text{ mA}) = 12.25 \text{ mA}.$$


Then,

$$\frac{dv(0^+)}{dt} = \frac{1}{C} i_C(0^+) = \frac{(12.25)(10^{-3})}{(0.125)(10^{-6})} = 98000 \frac{V}{s}.$$

c-) To find  $B_1$  and  $B_2$ :

$$v(0^+) = V_0 = B_1 = 0, \quad \frac{dv(0^+)}{dt} = 98000 = -\alpha B_1 + \omega_d B_2$$
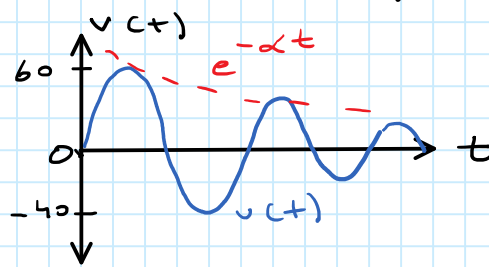
$$\Rightarrow v(t) = 100 e^{-200t} \sin(979.8t) \quad \Rightarrow B_2 = 100.$$



$\alpha$ : damping factor

$$\alpha = \frac{1}{2RC}$$

If  $R$  is  $\uparrow$

$\alpha$  is small

it takes longer to

damp.

- The oscillation frequency is  $\omega_d$ .

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}, \quad \text{for a large } R \uparrow, \alpha \text{ is small } \downarrow$$

$$\Rightarrow \omega_d \approx \omega_0 \text{ (resonant radian frequency.)}$$

- Note that oscillators or sine wave generators are based on RLC circuit underdamped response.

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L, C \text{ determines the freq. of oscillation}$$

### Critically Damped Voltage Response:


$$S_1 = S_2 = -\alpha = -\frac{1}{2RC}$$

The response is  $v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

I.C.'s:  $v(0^+) = D_2, \quad \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$

Ex:

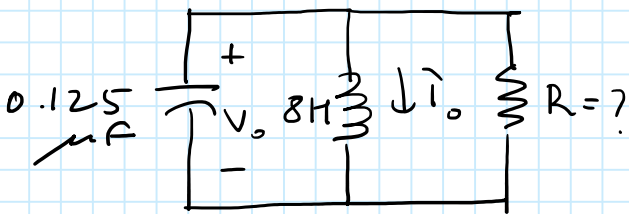For the circuit given below,  $V_0 = 0$ ,  $I_0 = -12.25 \text{ mA}$



- + a-) Find the value for  
 V R such that the response  
 is critically damped.  
 - b-) Find  $v(t)$ .

Ans:

$$a-) \omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\frac{10^6}{8(0.125)}} = 10^3 \text{ rad/s.}$$


In critically damped response,  $\alpha^2 = \omega_0^2$ ,  $\alpha = \omega$

$$\alpha = 10^3 = \frac{1}{2RC} \Rightarrow R = \frac{10^6}{(2000)(0.125)} = 4 \text{ k}\Omega.$$

$$b-) v(0^+) = 0 = D_2$$


$$\frac{dv(0^+)}{dt} = 98000 \frac{\text{V}}{\text{s}} \Rightarrow D_1 = 98000 \frac{\text{V}}{\text{s}}.$$
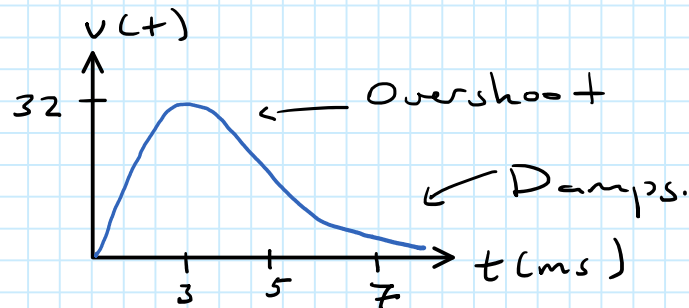
$$\Rightarrow v(t) = 98000 t e^{-1000t} \text{ (V), } t \geq 0$$



## Step Response of Parallel RLC-Circuit: (Charging)

→ Consider the following circuit:

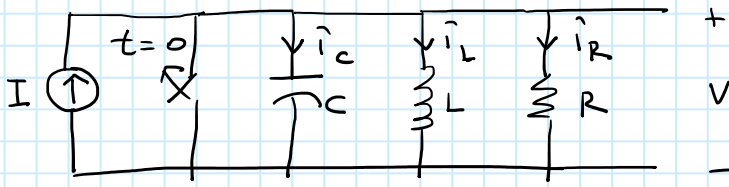

The governing equation for this circuit is:

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

- The solution can be expressed as  $i_L$  as a function of  $t$ .  
Then, we have from  $V = L \frac{di_L}{dt}$ , differentiating both sides,

$$\frac{dV}{dt} = L \cdot \frac{d^2 i_L}{dt^2}$$

- Thus, the circuit equation is:

$$\frac{1}{L} \frac{dV}{dt} + \frac{1}{RC} \frac{V}{L} + \frac{1}{L^2 C} \int_0^t V d\tau = \frac{I}{LC}$$

- Multiply both sides by  $LC$ ,

$$\frac{1}{L} \int_0^t V d\tau + \frac{V}{R} + C \frac{dV}{dt} = I,$$

- Differentiate both sides wrt.  $t$ :

$$\frac{V}{L} + \frac{1}{R} \frac{dV}{dt} + C \frac{d^2 V}{dt^2} = 0$$

or

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0 \quad (\text{Circuit eqn. in terms of } V)$$

→ The solution is:

$$V = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$V = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad (\text{Underdamped})$$

$$V = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad \text{depending on the roots}$$

$s_1$  and  $s_2$  of the characteristic equation.

→ The solution for  $i_L$  is:

$$i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t} \quad (\text{Over damped})$$

$$\text{or } i_L = I + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t) \quad (\text{Under damped})$$

$$\text{or } i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t} \quad (\text{Critically damped})$$

Ex:

The initial energy stored in the circuit is zero. At  $t=0$  a DC current source of  $24 \text{ mA}$  is applied to the circuit.


The value of the resistor is  $400 \Omega$ .

a-) What is the initial value of  $i_L$ ?

b-) " " " " " "  $\frac{di_L}{dt}$ ?

c-) Find  $s_1, s_2$ .

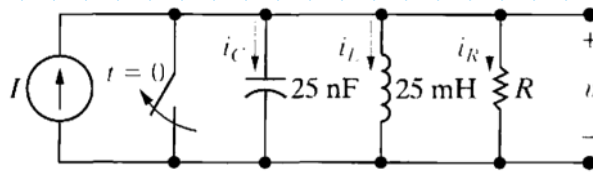d-) Find the expression for  $i_L(t)$  for  $t \geq 0$ .



Ans:

$$a-) i_L(0) = 0 \Rightarrow i_L(0^+) = 0$$

$$b-) v = L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = \frac{v}{L} \quad \text{and } v(0) = v(0^+) = 0 \text{ from the cap. voltage.}$$

$$\Rightarrow \frac{di_L(0^+)}{dt} = 0.$$

$$c-) \omega_0^2 = \frac{1}{LC} = \frac{10^{12}}{(25)(25)} = 16 \times 10^8$$

and

$$\alpha = \frac{1}{2RC} = \frac{10^9}{2(400)25} = 5 \times 10^4 \text{ rad/s.}$$

$$\text{or } \alpha^2 = 25 \times 10^8$$

Because,  $\omega_0^2 < \alpha^2$ , the roots of the characteristic equation are real and distinct. Thus,

$$s_1 = -5 \times 10^4 + 3 \times 10^4 = -20000 \text{ rad/s.}$$

$$s_2 = -5 \times 10^4 - 3 \times 10^4 = -80000 \text{ rad/s.}$$

d-) The inductor current response is overdamped. Thus,

$$i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

To find  $A_1'$  and  $A_2'$ :

$$i_L(0) = I + A_1' + A_2' = 0$$


and

$$\frac{d i_L(0)}{dt} = s_1 A_1' + s_2 A_2' = 0$$

Solving these equations yields  $A_1' = -32 \text{ mA}$ ,  $A_2' = 8 \text{ mA}$ .

→ Then, the solution for  $i_L(t)$  is:

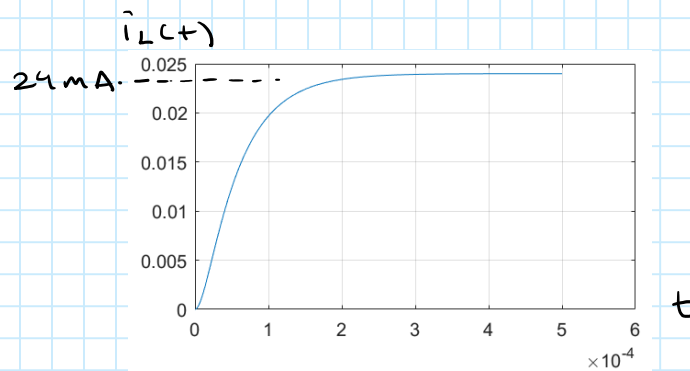
$$i_L(t) = (24 - 32 e^{-20000t} + 8 e^{-80000t}) \text{ mA}, t \geq 0.$$



— 0 —

If  $R$  was  $625 \Omega$ , then

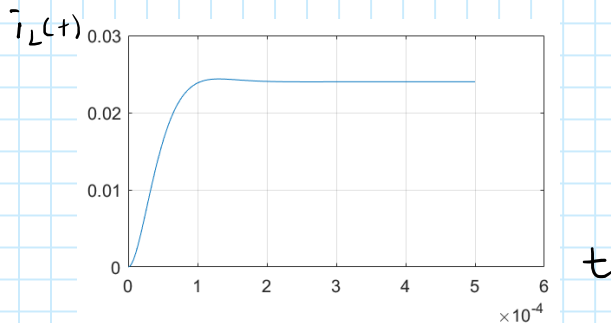
$$i_L(t) = \left[ 24 - 24 e^{-32000t} \cos(24000t) - 32 e^{-32000t} \sin(24000t) \right] \text{ mA}.$$



— 0 —

## Natural and Step Response of Series RLC-Circuit:

Consider the circuit,

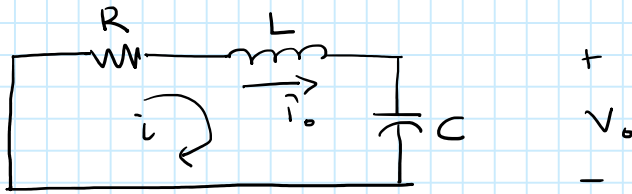

- The governing equation is:  $Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0$
- Differentiate both sides:

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

- Re-arranging,

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} = 0$$

→ The characteristic eqn is:  $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

where

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{where} \quad \alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

and the solution of the natural response is:


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad \text{over-damped.}$$

$$\text{or } i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t), \quad \text{under-damped.}$$

$$\text{or } i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad \text{critically damped responses.}$$


The initial conditions can be obtained as before

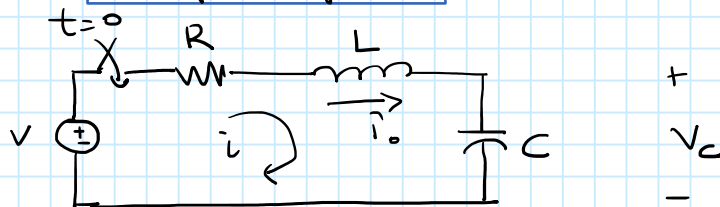To find the step response, we consider the following circuit:



- The governing eqn is:
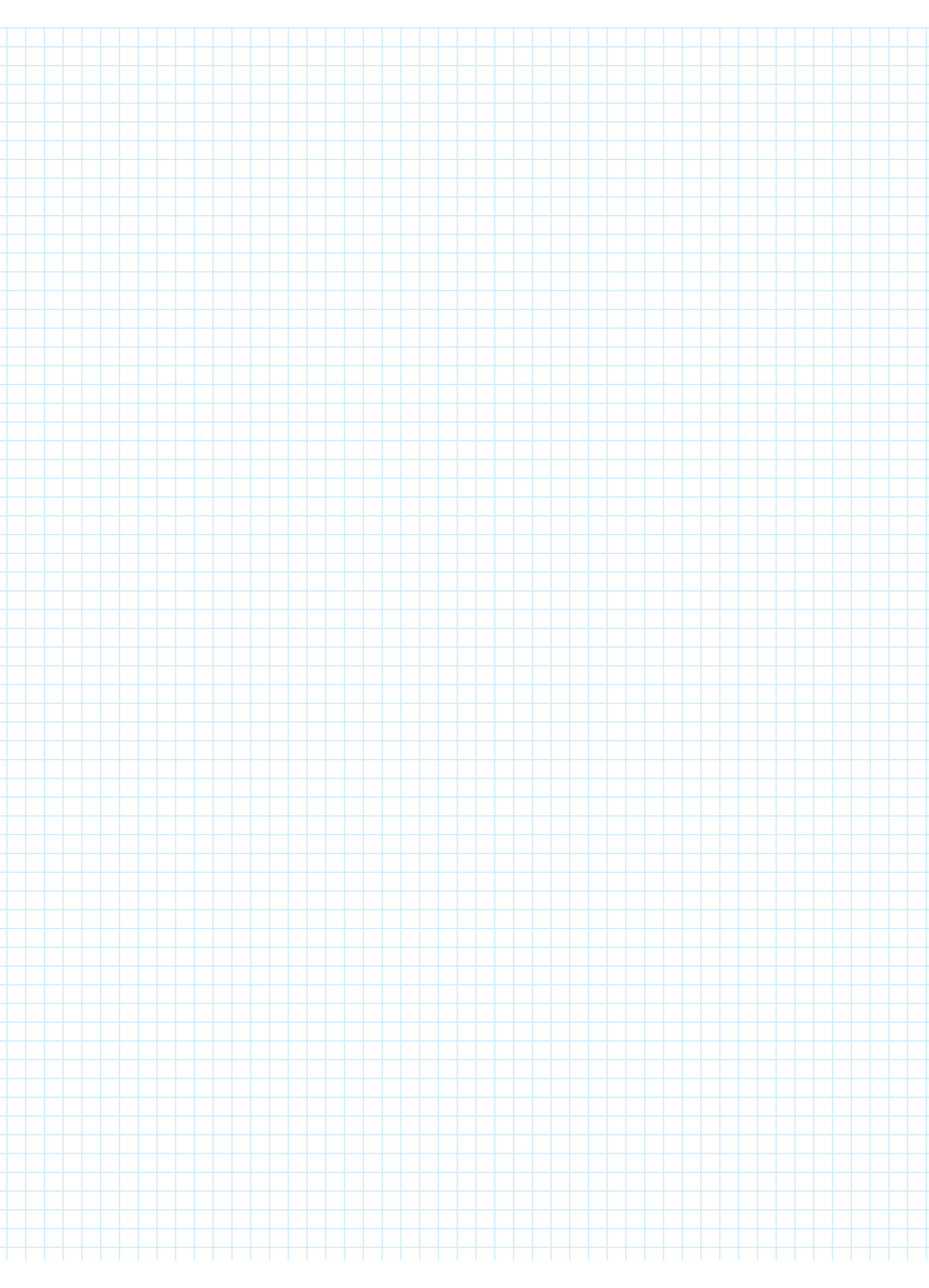
$$\frac{d^2V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{V_c}{LC} = \frac{V}{LC}$$



The solution is:


$$V_c = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$\text{or } V_c = V_f + B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \quad (\text{Under-damped})$$

Ex: or

$$V_c = V_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \quad (\text{critically damped.})$$

For the given circuit,

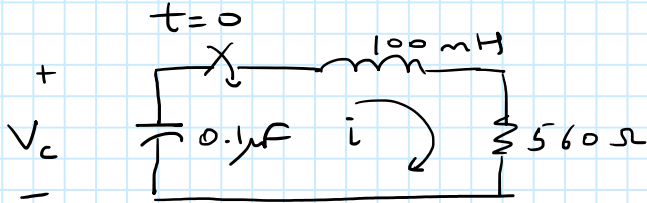

a-) Find  $i(t)$ ,  $t \geq 0$

b-) Find  $V_c(t)$ ,  $t \geq 0$ .

$$V_c(0) = 100 \text{ V.}$$

Ans:

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(0.1)(0.1) \times 10^{-6}} = 10^8 \text{ rad/s.}$$

and

$$\alpha = \frac{R}{2L} = \frac{560}{2(0.1)} = 2800 \text{ rad/s.}$$

$$\Rightarrow \omega_0^2 > \alpha^2 \Rightarrow \text{Underdamped!}$$

$\Rightarrow$  The solution is:

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2} = [10^8 - (2800)^2]^{\frac{1}{2}} = 9600 \text{ rad/s.}$$

and  $B_1$  and  $B_2$  can be obtained from:

$$i(0) = 0 = B_1.$$

For  $B_2$ , we need  $\frac{di(t)}{dt}$ , so  $L \frac{di(0^+)}{dt} = V_0$

$$\text{or } \frac{di(0^+)}{dt} = \frac{V_0}{L} = \frac{100}{0.1} = 1000 \frac{\text{A}}{\text{s}}. \quad \frac{di(0^+)}{dt} = B_1(-\alpha) + B_2 \omega_d$$


$$\Rightarrow \frac{di(t)}{dt} = B_2 (-\alpha) e^{-\alpha t} \sin(\omega_d t) + B_2 e^{-\alpha t} \omega_d \cos(\omega_d t) \quad (\text{with } B_1 = 0)$$

Now,

$$\frac{di(0^+)}{dt} = 1000 = B_2 \omega_d \Rightarrow B_2 = \frac{1000}{\omega_d} = \frac{1000}{9600} \approx 0.1042 \text{ A}$$

Thus,
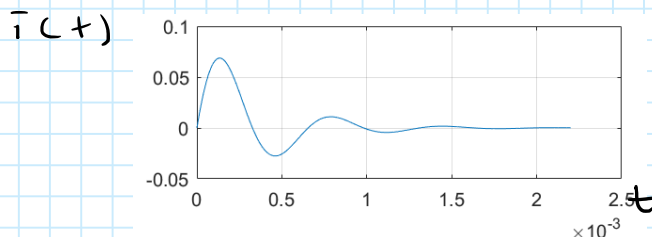
$$i(t) = 0.1042 e^{-2800 t} \sin(9600 t), \quad t \geq 0.$$



(Underdamped)



To find  $V_c(t)$ , we use the KVL in the circuit:

$$V_c = iR + L \frac{di}{dt} \quad \text{or} \quad V_c = -\frac{1}{C} \int_0^t i(\tau) d\tau + 100$$

$\uparrow$   
C

Then,

$$\begin{aligned} V_c(t) &= R i(t) + L \frac{di(t)}{dt} \\ &= 560 \left[ 0.1042 e^{-2800t} \sin(5600t) \right] \\ &\quad + 0.1 \left[ (0.1042)(-2800) e^{-2800t} \sin(5600t) + \right. \\ &\quad \left. (0.1042) e^{-2800t} (5600) \cos(5600t) \right] \end{aligned}$$


Re-arranging this expression gives us:

$$V_c(t) = \left[ 100 \cos(5600t) + 25.17 \sin(5600t) \right] e^{-2800t}, \quad t \geq 0.$$

Complex Numbers:


We show real numbers on the horizontal axis:

by addition, translate on real axis.

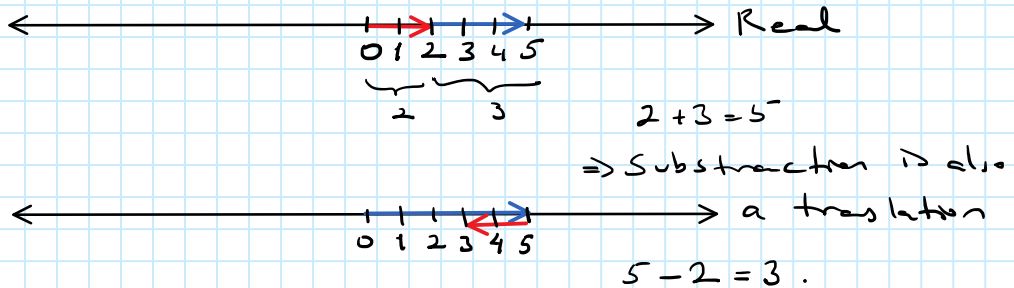


on the opposite direction.

Multiplication = scaling the number.

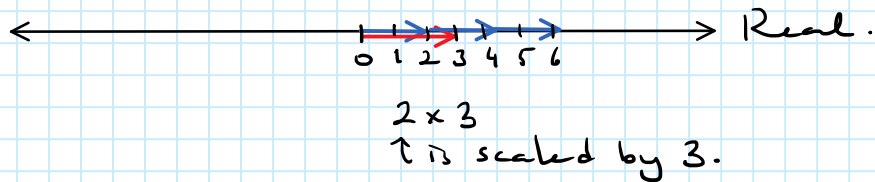


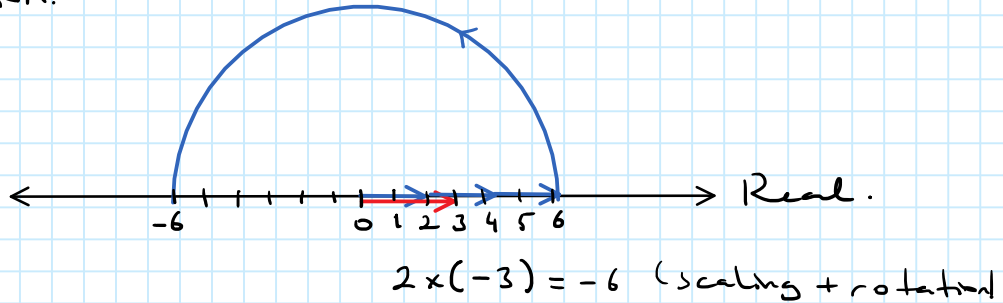Multiplication by a "-" number: yields scaling + rotation.



Similarly,  $(-6) \times (-1)$  means scaling + rotation.


$$(-6) \times (-1) = 6$$

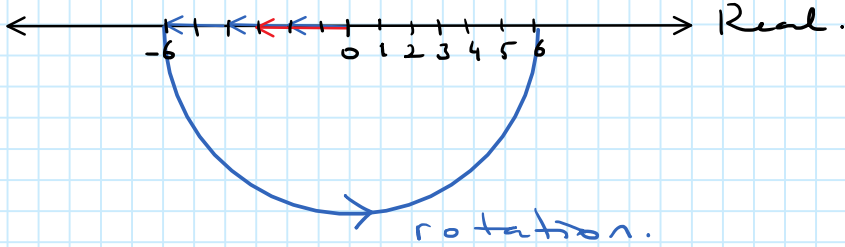


Division = Multyp:

$$6 \div (-3) = -2$$

$\Rightarrow$  Scaling + rotation.

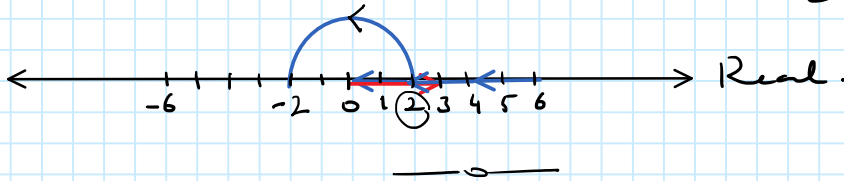

Let us consider the following case:

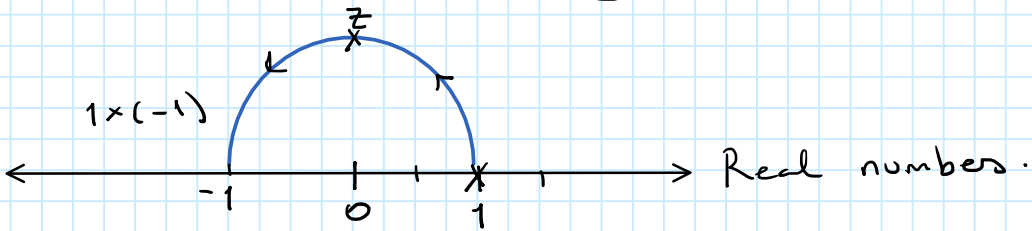


$$1 \times z \times z = -1, \quad i = \text{the number that makes a quarter turn.}$$

$$z^2 = -1$$


$$z = \sqrt{-1} = i \text{ (Mathematicians)}$$

$$= j \text{ (Engineers)}$$

For example,

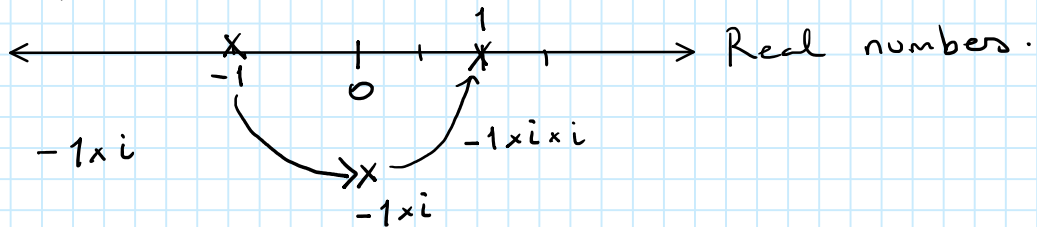

Now,

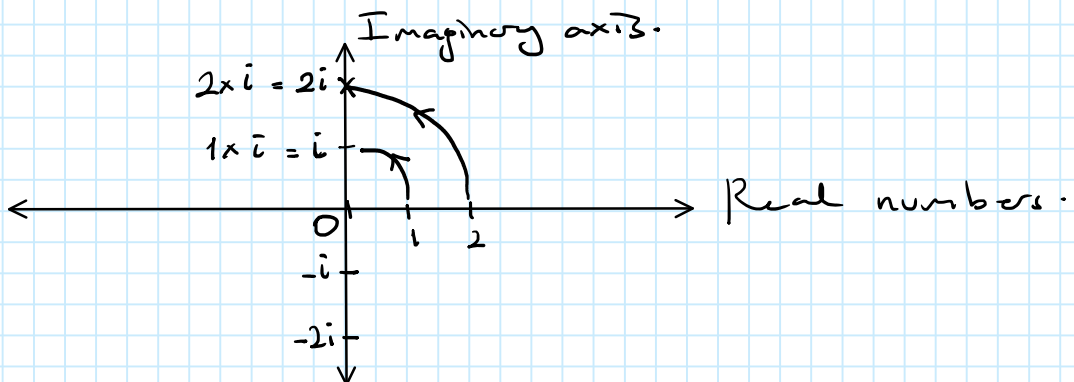


# P65

Monday, March 1, 2021 10:31 AM


$\Rightarrow z = j = \sqrt{-1}$ , where is this number on the number line

$1 \times \sqrt{-1} = \sqrt{-1}$

$2 \times \sqrt{-1} = 2\sqrt{-1}$

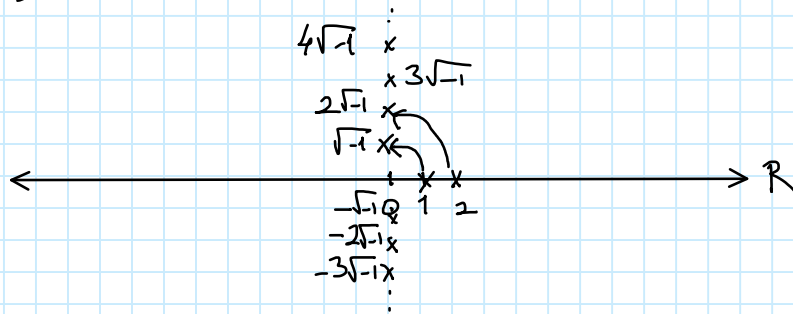

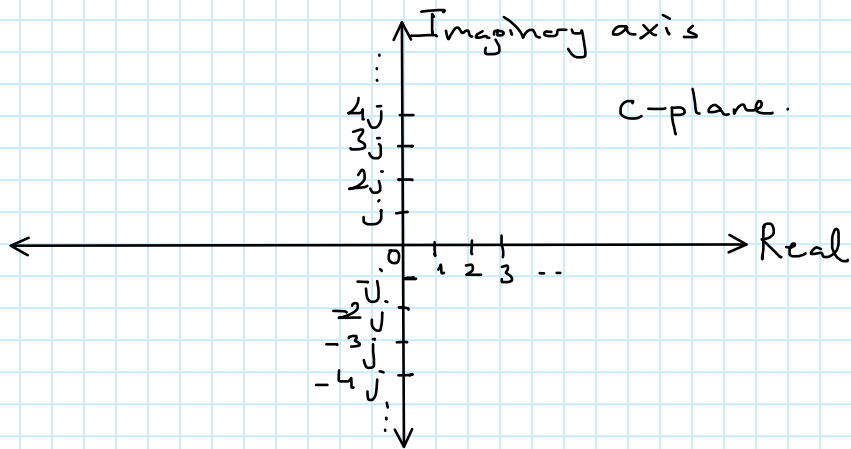$\Rightarrow$  We can draw a vertical line.




- This plane is called "complex plane" (C-plane) and any number on this plane is called a "complex number"

## Ex

Suppose  $z = -3$ , what should be done to rotate this number  $\frac{1}{4}$  of a turn cw and ccw?

## Ans

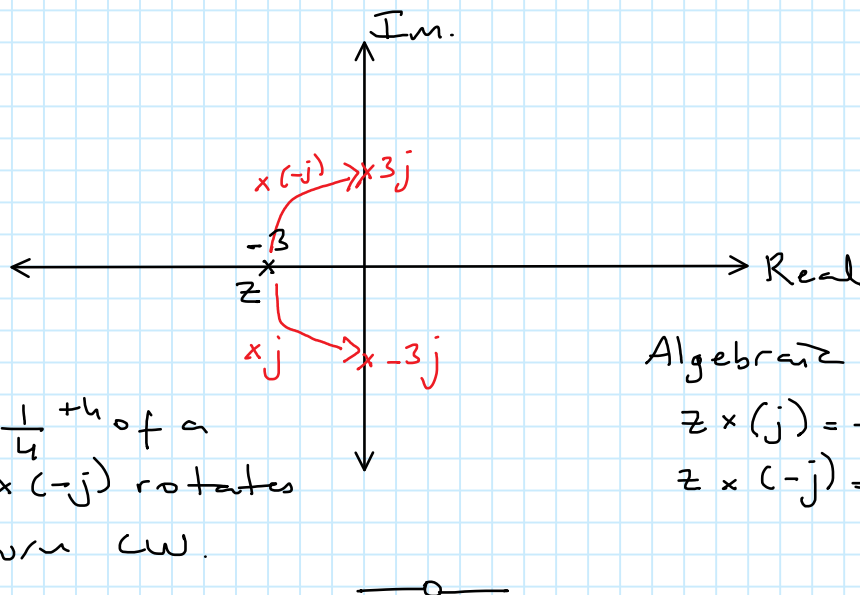


multiply  
 $\Rightarrow$   $\times (j)$  rotates  $\frac{1}{4}$  of a turn ccw.  $\times (-j)$  rotates  $\frac{1}{4}$  of a turn cw.

Algebraic Calculations:

$z \times (j) = -3j$

$z \times (-j) = 3j$

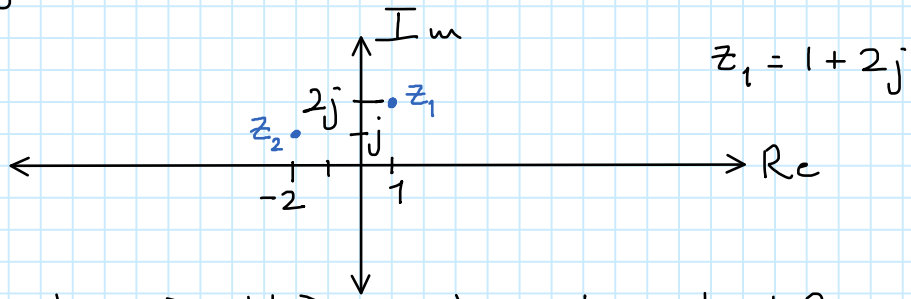Writing a Complex Number in terms of its Real and imaginary parts (components).




$z_2 = z_1 \times j = ?$  where is this number located?

$j = \sqrt{-1}$   
 $j^2 = -1$

Ans

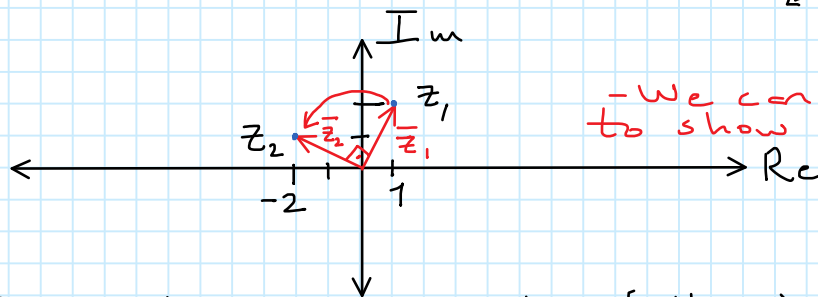Algebraic solution:  $z_1 \times j = (1 + 2j) \times (j) = j + 2j^2 = -2 + j$




⇒ Up to this point, we have the following notations:

$z = a + jb$  (component notation)  
 Real Imaginary.

$\vec{z} = \vec{a} + j\vec{b}$  (vector notation, used in geometric analysis)

What if we multiply  $z_1$  by  $2j$ .

$z_3 = z_1 \times (2j) = ?$

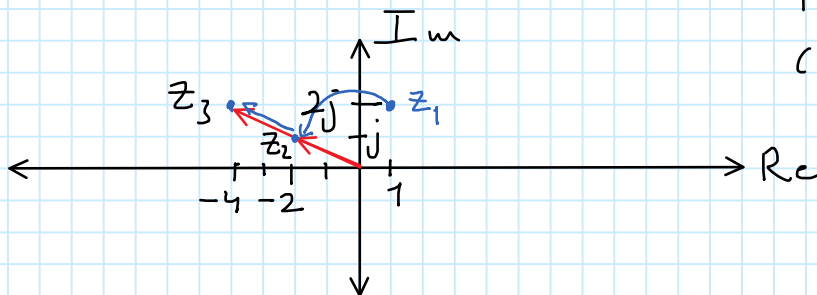


Algebraic Sol:  
 $(1 + 2j) \cdot (2j)$   
 $= 2j + 4j^2$   
 $z_3 = -4 + 2j$

⇒  $z_1 \times (2j) =$  (rotation + scaling by 2.)

# Exponentiation with Complex Numbers (Power of a Complex Number):


$$j^n = ?$$

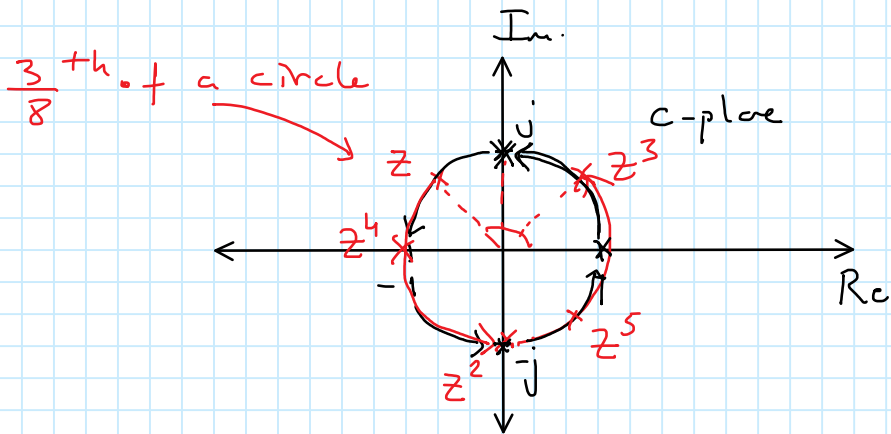


$1 \times j = j$	$(j^1)$
$j \times j = -1$	$(j^2)$
$-1 \times j = -j$	$(j^3)$
$-j \times j = 1$	$(j^4)$
$1 \times j = j$	$(j^5)$

=> Taking the power of  $(j)$  rotates ccw on the unit circle

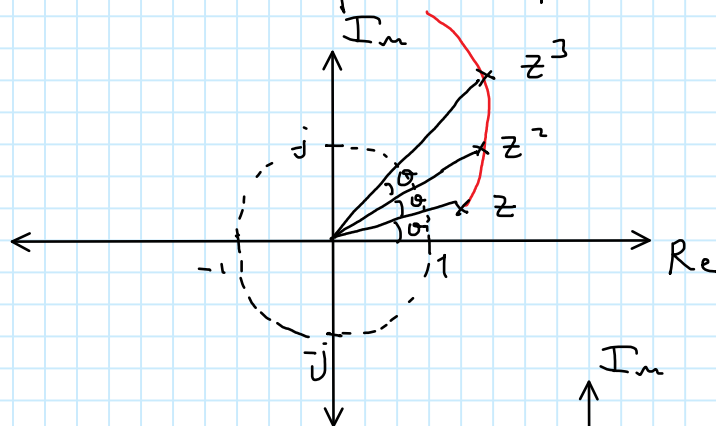- Taking the power of any complex number  $z$  which is on the unit circle rotates ccw by the same angle that  $z$  makes with the real axis
- What if  $z$  is outside the unit circle? Then, what happens when we take the power of  $z$




- If  $z$  is inside the unit circle.

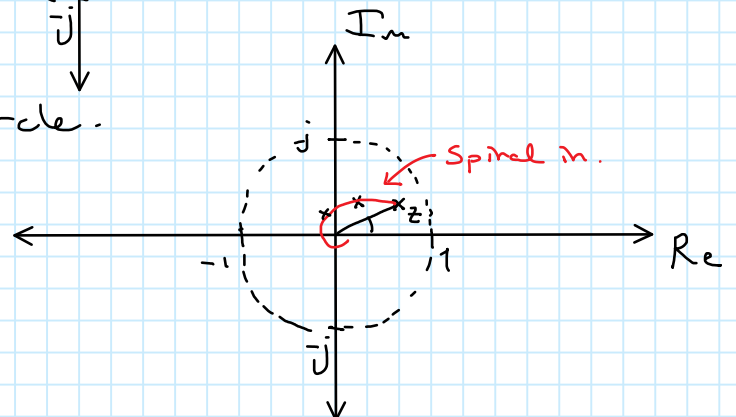


Time Variable:

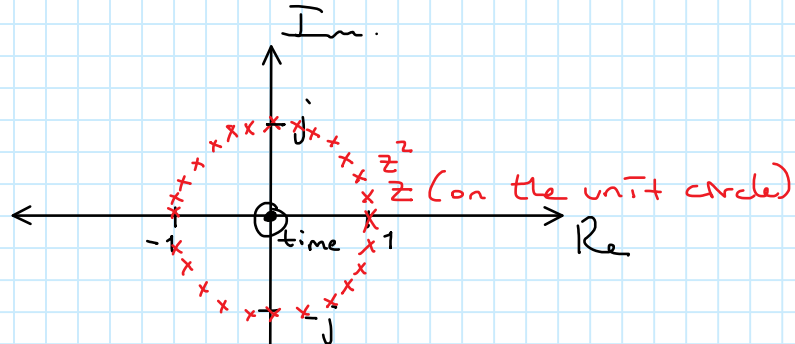Let us introduce the variable in complex domain.  
 Let us assume that we increase the exponent over time.




In 3D view:

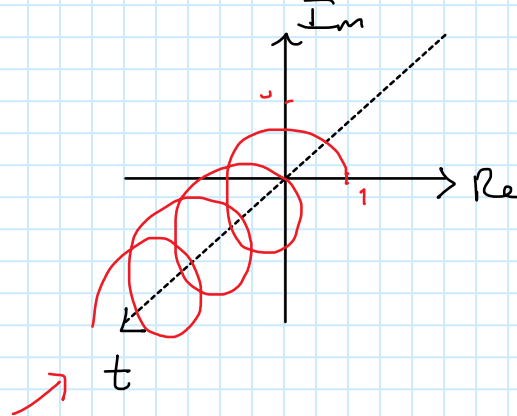


- In 3D, with the time axis, we get a helix shape.

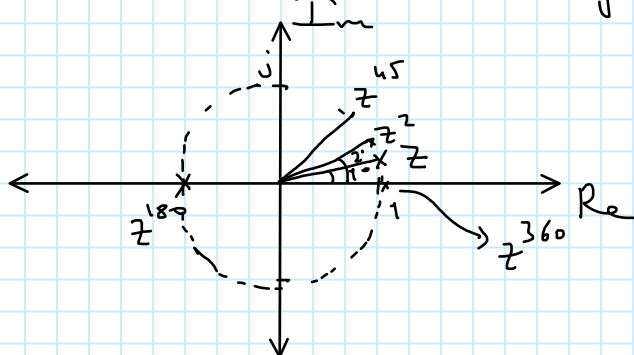If  $z$  is on the unit circle with  $1^\circ$  angle.




$z$  with  $1^\circ$  is not a base or a standard

The base  $i$

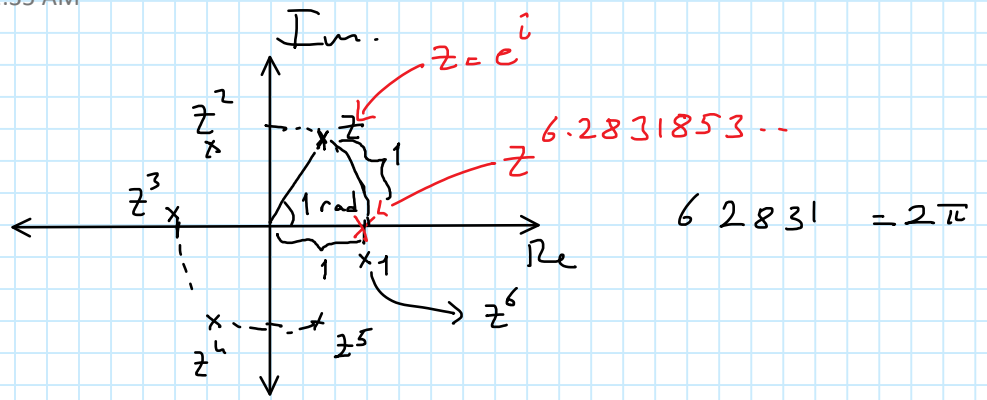


The  $z$  is also equal to  $z = e^j$ ,  $e = 2.71828...$  (Euler's number)

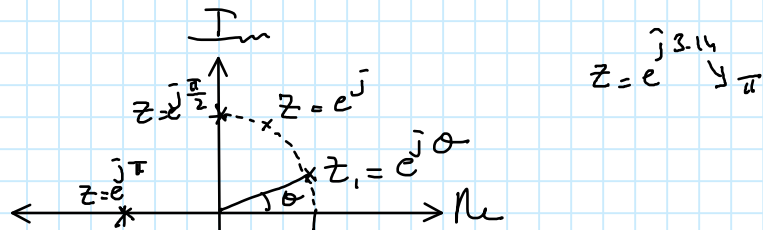Also,  $z_1 = e^{j\theta}$  is on the unit circle with angle  $\theta$  in radians



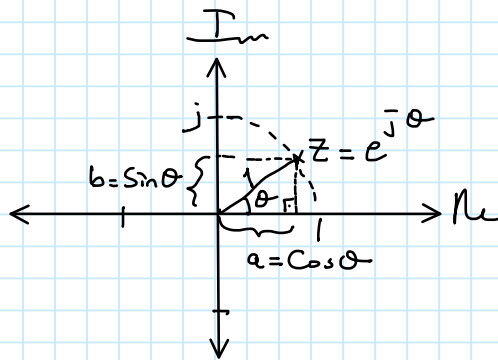Let us observe  $z = e^{j\theta}$  closely: (Complex exponential)



$\Rightarrow z = e^{j\theta} = a + jb = \cos\theta + j\sin\theta$  (Euler's formula)

Exponential notation      Rectangular notation

$z = re^{j\theta} = r\cos\theta + jr\sin\theta$

Ex:


Find a  $\frac{1}{4}$ th turn of a complex number  $z=1$  on the unit circle in terms of exponential notation.



# P70

Monday, March 1, 2021 11:48 AM

Ans

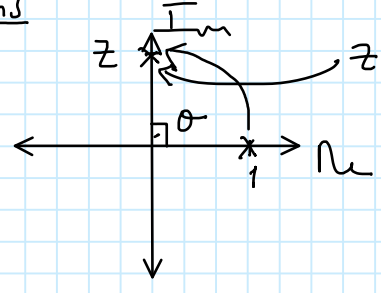

$$z = e^{j\theta} \quad (\theta = \frac{\pi}{2}) \Rightarrow z = e^{j\frac{\pi}{2}} = j.$$

Proof.

$$e^{j\frac{\pi}{2}} = \cos\frac{\pi}{2} + j\sin\frac{\pi}{2} = j$$

Ex:

Draw  $z = e^{j2\pi ft}$  (Exponential notation)  
 where  $f = \text{frequency} = \text{constant}$ ,  $t = \text{time} = \text{variable}$ .


Ans

Analysis

- $e = \text{constant} = 2.7$
- $j = \text{constant}$
- $2\pi = \text{constant}$
- $f = \text{constant}$

$$\Rightarrow z = e^{j\theta}$$


$$\theta = 2\pi ft$$

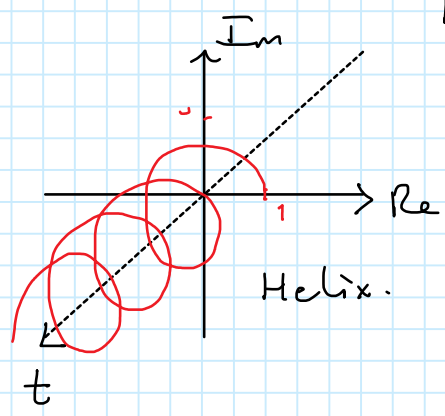

- Until now: The formats for complex numbers.

$z = a + jb = \text{rectangular}$ ,  $\bar{z} = \text{vectorial}$ ,  
 3<sup>rd</sup> format. Polar form (exponential form)

$\theta = \text{Argument, Angle, Phase}$

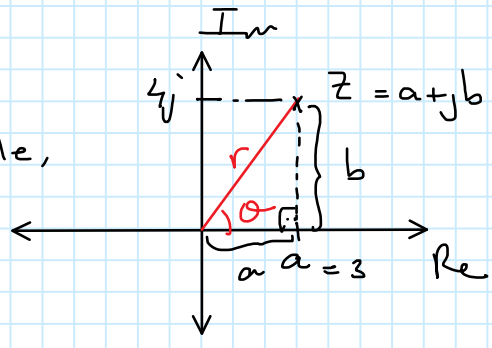

$$z = a + jb = 3 + 4j = r e^{j\theta} = r \angle \theta$$

where  
 $r = \text{Magnitude, amplitude, radius, modulus.}$   
 $r = \text{distance from origin}$

$r = |z|$  ( $r$  is found by taking the absolute value of  $z$ )

$$\|\vec{z}\| = |\vec{z}| = \text{Magnitude} = r$$

### Transformations

A complex number given in rectangular form

$$z = a + jb, \quad z = r e^{j\theta}$$

Rect. to polar  $\Rightarrow r^2 = a^2 + b^2, \quad \theta = \tan^{-1}\left(\frac{b}{a}\right)$

Polar to Rect  $\Rightarrow a = r \cos \theta, \quad b = r \sin \theta.$

—o—

### Addition & Subtraction of Complex Numbers:

- Using rectangular notation is easier

Ex:

$$z_1 = 3 + 4i$$

$$z_2 = 2 - 2i$$

a)  $z_1 + z_2 = ?$

b)  $z_1 - z_2 = ?$

Ans

$$z_1 + z_2 = (3 + 4i) + (2 - 2i)$$

$$= (3 + 2) + (4i - 2i)$$

$$= 5 + (4 - 2)i = 5 + 2i$$

$$z_1 - z_2 = (3 + 4i) - (2 - 2i)$$

$$= (3 + 4i) - 2 + 2i$$

$$= (3 - 2) + (4i + 2i)$$

$$= 1 + 6i$$

### Multiplication & Division

Polar form is easier.

Ex

$$z_1 = 3 + 4j, \quad z_2 = 8 - 6j$$

a)  $z_1 \cdot z_2 = ?$

b)  $\frac{z_2}{z_1} = ?$

Ans

$$z_1 \cdot z_2 = (3 + 4j) \cdot (8 - 6j)$$

$$= 24 - 18j + 32j - 24j^2$$

$$= 24 - 18j + 32j + 24$$

$$= 48 + 14j$$



$$z_1 = 3 + 4j, \quad z_2 = 8 - 6j$$

$$z_1 = 5e^{j\arctan\frac{4}{3}}, \quad z_2 = 10e^{j\arctan\left(-\frac{6}{8}\right)}$$

$$z_1 \cdot z_2 = 5e^{j0.93} \cdot 10e^{-j0.64} = 50e^{j(0.93-0.64)} = 50e^{j0.29}$$


$$= 50 \cos(0.29) + j50 \sin(0.29) = 48 + j14 \quad \checkmark$$

$$b-) \frac{z_2}{z_1} = \frac{8-6j}{3+4j} \cdot \frac{(3-4j)}{(3-4j)} = \frac{24-32j-18j-24}{9+16} = \frac{-50j}{25} = -2j$$

conjugate (reverse the sign of the imaginary part)

$$\frac{z_2}{z_1} = \frac{10e^{j(-0.64)}}{5e^{j0.93}} = \frac{10}{5} \cdot e^{j(-0.64-0.93)}$$
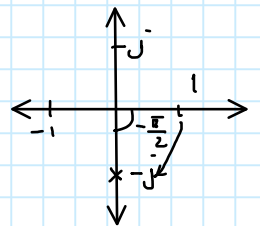
$$= 2e^{j(-1.57)} = 2e^{j\left(-\frac{\pi}{2}\right)} = 2e^{-j} = -2j \quad \checkmark$$



## - Sinusoidal Steady State Analysis - (C.p.s)

### - Sinusoidal Source:

Consider the following voltage source:

$$v = V_m \cos(\omega t + \phi) + V_{\text{off}}$$

where

$t$  = time variable (s)

$v$  = Voltage (V)

$\omega$  = Radian frequency (rad/s)

$V_m$  = Maximum amplitude (V)

$\phi$  = Phase angle (rad)

and  $V_{\text{off}}$  = DC voltage added to  $v$ . (offset)

$\omega = 2\pi f$ ,  $f$  = frequency (Hz)

and  $T = \frac{1}{f}$  = Period (s)


- The phasor is a complex number that carries the amplitude and phase information of a sinusoidal function.

- It is based on the Euler's identity

$$e^{\mp j\theta} = \cos\theta \mp j \sin\theta.$$

- Before moving further, let us study complex numbers:

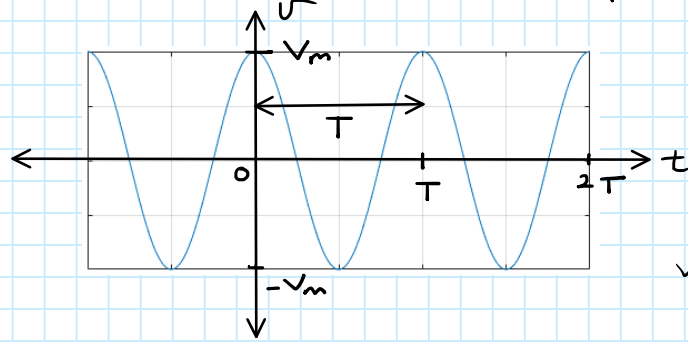
If we plot a sinusoidal source wave form wrt. time:




$v(t) = v(t + T)$   
(Periodic)

Thus,

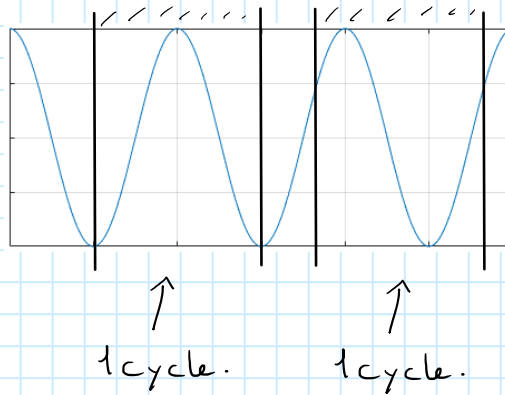Cycle: The smallest non-repeatable portion of the periodic waveform.




Frequency: # of cycles in 1 sec.

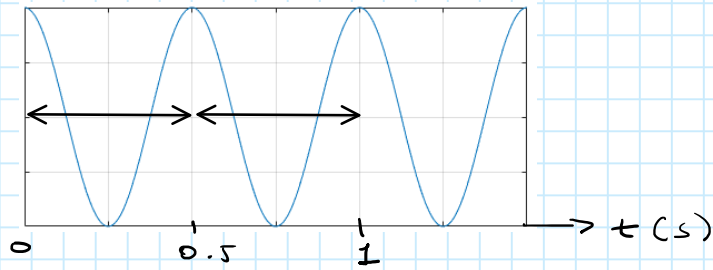


There are 2 cycles  $\Rightarrow f = 2 \text{ Hz}$ .

or

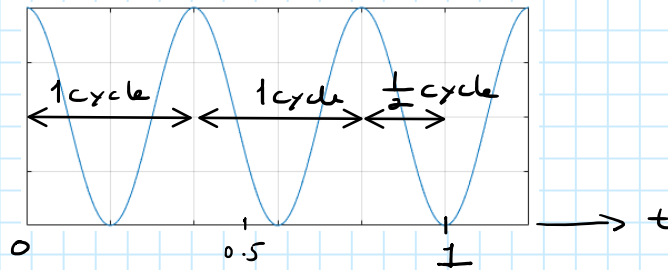

$f = 1 + 1 + \frac{1}{2} = 2 + \frac{1}{2} = \frac{5}{2} \text{ Hz} = 2.5 \text{ Hz}$ .


Period  $= T =$  Time for 1 cycle.

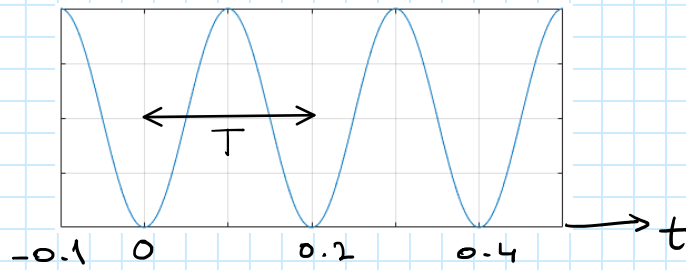

$$\Rightarrow T = 0.2 \text{ sec.} \Rightarrow f = \frac{1}{T} = \frac{1}{0.2} = 5 \text{ Hz.}$$

Phase Angle  $= \phi$

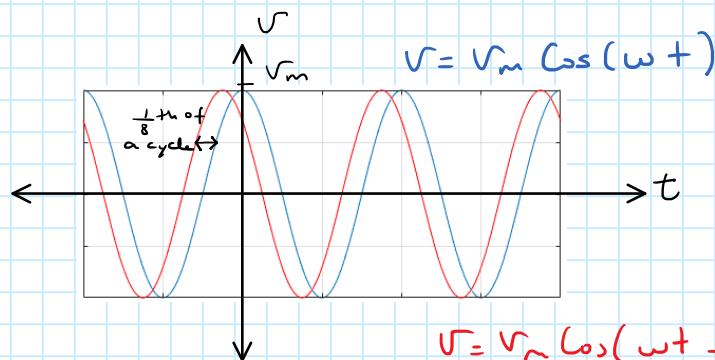It shifts the graph left or right for  $+$  or  $- \phi$  respectively.



$$v = V_m \cos\left(\omega t + \frac{\pi}{4}\right)$$

$$\phi = \frac{\pi}{4}$$

- 1 cycle is from  $0$  to  $2\pi$ .

$\Rightarrow \frac{\pi}{4}$  is  $\frac{1}{8}$  th of a cycle.

That's why we shift the graph of  $v = V_m \cos(\omega t)$  by a  $\frac{1}{8}$  th of a cycle to the left.

## The Radian Frequency, $\omega$ :

Consider

$$v(t) = V_m \cos(\omega t + \phi) \quad v.$$

For  $\phi = 0$  for simplicity


$$v(t) = V_m \cos(\underbrace{\omega t}_{\text{Angle (radian)}})$$

Put  $\omega = 0$ :

$$v(t) = V_m \quad (\text{DC signal})$$

for  $\omega = 2\pi$ :

$$v(t) = V_m \cos(2\pi t)$$

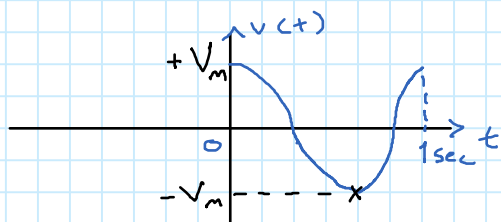

$$\uparrow t=0 \rightarrow v(0) = V_m$$

$$t=0.5 \rightarrow v(0.5) = -V_m$$


$$t=1 \text{ sec} \rightarrow v(1) = V_m$$

$$\Rightarrow f = 1 \text{ Hz.}$$

$$\text{For } t=0 \rightarrow 1 \quad \text{Angle} = \omega t \rightarrow 0 - 2\pi.$$

for  $\omega = 4\pi$ :
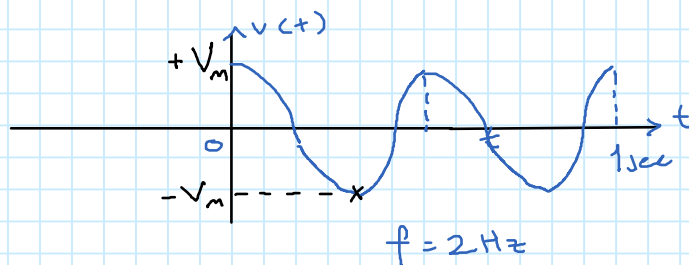
$$t=0 \rightarrow 1 \quad \text{Angle} = \omega t \rightarrow 0 - 4\pi$$



$$f = 2 \text{ Hz}$$

- Therefore,  $\omega = \text{radian freq.}$  gives the number of cycles in 1 sec in terms of radians (# of  $2\pi$ 's).



Another important property of a sinusoidal voltage (or current) is the "rms value".

rms: Root Mean Square.

Thus, if  $v(t) = V_m \cos(\omega t + \phi)$

$$V_{rms} = \left[ \frac{1}{T} \int_{t_0}^{t_0+T} v^2 dt \right]^{\frac{1}{2}} = \text{Root of the mean value (average) of the squared voltage.}$$


$$\Rightarrow V_{rms} = \left[ \frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt \right]^{\frac{1}{2}} =$$

Using the identity  $\cos^2 x = \frac{1}{2} (1 + \cos 2x)$

$$V_{rms} = \left[ \frac{1}{T} V_m^2 \int_{t_0}^{t_0+T} \frac{1}{2} [1 + \cos(2\omega t + 2\phi)] dt \right]^{\frac{1}{2}}$$

$$= \left[ \frac{1}{T} V_m^2 \left( \int_{t_0}^{t_0+T} \frac{1}{2} dt + \int_{t_0}^{t_0+T} \cos(2\omega t + 2\phi) dt \right) \right]^{\frac{1}{2}}$$
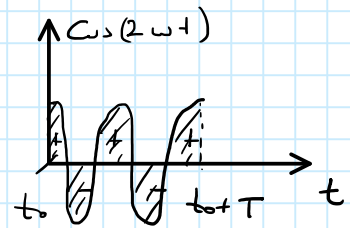
$$= \left[ \frac{1}{T} V_m^2 \left( \frac{1}{2} \int_{t_0}^{t_0+T} dt + 0 \right) \right]^{\frac{1}{2}} = \left[ \frac{1}{T} V_m^2 \frac{T}{2} \right]^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} \quad (V)$$



$$V_{rms} = \left[ \frac{1}{T} V_m^2 \frac{T}{2} \right]^{\frac{1}{2}} = \left( \frac{V_m^2}{2} \right)^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} \quad (V)$$

or

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad (V) \quad (\text{rms value of a sinusoidal voltage signal } v(t))$$



The use of rms value for sinusoidal voltage and/or current:

$$U = U_m \cos(\omega t + \phi) \quad P_R = ? \quad P_R = U \cdot i = \frac{U^2}{R} = i^2 \cdot R \quad (\text{W})$$


$$\Rightarrow P_R = \frac{U_m^2}{R} \cos^2(\omega t + \phi) \quad (\text{W})$$

Using the identity  $\cos^2 x = \frac{1}{2} (1 + \cos 2x)$

$$P_R = \frac{U_m^2}{R} \frac{1}{2} [1 + \cos(2\omega t + 2\phi)] = \frac{U_m^2}{2R} + \frac{U_m^2}{2R} \cos(2\omega t + 2\phi)$$

Let's say  $\phi = 0$  for simplicity.
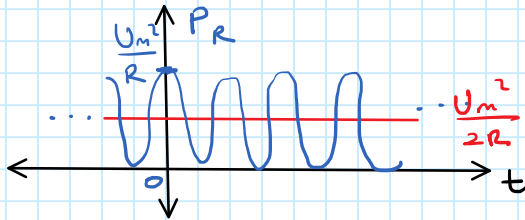
$$P_R = \frac{U_m^2}{2R} + \frac{U_m^2}{2R} \cos(2\omega t)$$



- This power keeps changing.

Thus, it is not useful.

- Thus, we use the average of this power.

$$P_{\text{avg}} = \frac{1}{T} \int_0^T P_R dt = \frac{1}{T} \left[ \int_0^T \frac{U_m^2}{2R} dt + \underbrace{\int_0^T \frac{U_m^2}{2R} \cos(2\omega t + 2\phi) dt}_{=0} \right]$$

$$\Rightarrow P_{\text{avg}} = \frac{1}{T} \frac{U_m^2}{2R} T = \frac{U_m^2}{2R} \quad (\text{W})$$

$$\frac{V_{\text{rms}}^2}{R} = \frac{V_m^2}{2R}$$

Ex:

A light bulb is connected to  $v = 311 \cos(\omega t)$  (V) where  $\omega = 2\pi f = 2\pi(50) = 100\pi$ . Find the average power consumed by  $R = 100 \Omega$  when connected to this voltage source.

Ans:

The power consumed means the average power  $P_{\text{avg}}$ .

$$\Rightarrow P_{\text{avg}} = \frac{V_m^2}{2R} = \frac{(311)^2}{2(100)} = 484 \text{ W.}$$

- We could also use the relation  $V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$ . Thus,

$$P_{\text{avg}} = \frac{(\sqrt{2} V_{\text{rms}})^2}{2R} = \frac{2 V_{\text{rms}}^2}{2R} = \frac{V_{\text{rms}}^2}{R} \quad (\text{W})$$

Thus, the same problem could be solved by finding the rms voltage first,

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{311}{\sqrt{2}} = 220 \text{ V.}$$


Then, for finding the average power, use

$$P_{avg} = \frac{V_{rms}^2}{R} = \frac{220^2}{100} = 484 \text{ W.}$$

Ex:

Find the resistance of a 60 W light bulb?

Ans:

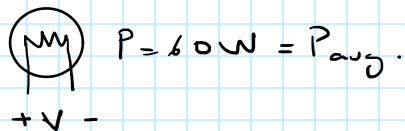


$$P_{avg} = \frac{V_m^2}{2R}$$

or


$$P_{avg} = \frac{V_{rms}^2}{R} \checkmark$$

$$\Rightarrow 60 = \frac{(220)^2}{R} \Rightarrow R = 806 \Omega.$$

Ex:

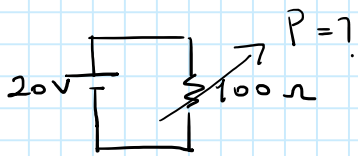
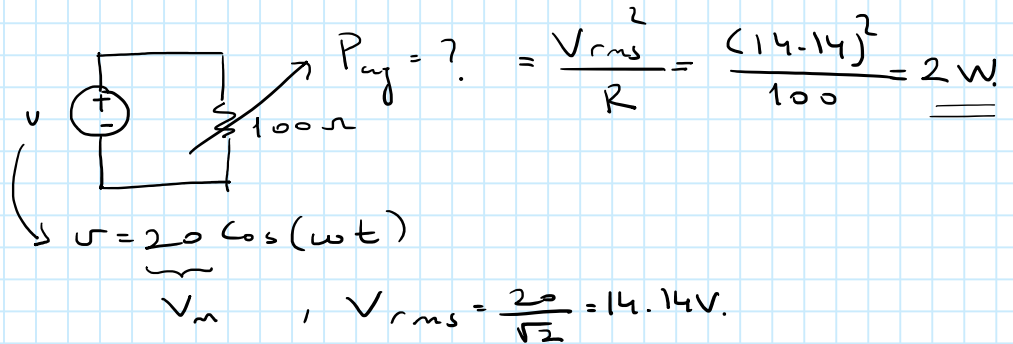
$$P = \frac{20^2}{100} = \frac{20 \cdot 20}{100} = 4 \text{ W.}$$




$$v = 20 \cos(\omega t)$$

$$V_m, \quad V_{rms} = \frac{20}{\sqrt{2}} = 14.14 \text{ V.}$$

### Sinusoidal Response:

Consider the following circuit:

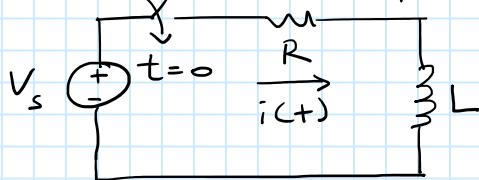

$$\text{where } V_s = V_m \cos(\omega t + \phi)$$

$$i(0) = 0$$

$$i(t) = ?, \quad t \geq 0.$$

→ This is the step response of an RL-circuit as we've known before. The difference is that we have a sinusoidal source,  $V_s$ .

Writing the mesh equation (KVL):

$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$

The solution is:

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi + \theta) e^{-\left(\frac{R}{L}t\right)} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$


where  $\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$ .

- The first term of this solution is called the "transient response".
  - The 2<sup>nd</sup> term of this solution is called the "Steady State Response".
  - Because for  $t \geq 0$ , the 1<sup>st</sup> term decreases rapidly, and the 2<sup>nd</sup> term starts to dominate.
  - So, the 1<sup>st</sup> term disappears after a while, and the 2<sup>nd</sup> term remains.
  - We can make the following conclusions for the steady state response:
    - 1-) It is also sinusoidal.
    - 2-) It has the same frequency as the source.
    - 3-) Amplitude and phase change.
    - 4-) The solution of the differential equation is rather long and complicated.
  - The remedy for conclusion 4 is to use "Phasors".
- Phasor = Complex number representation of the sinusoidal expressions to make mathematized computations easier.


Let's start to use complex numbers:

Consider a complex exponential:

$$\bar{z} = e^{j\theta}$$

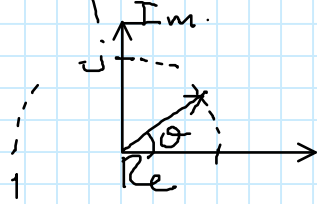

$$\bar{z} = r e^{j\theta}$$

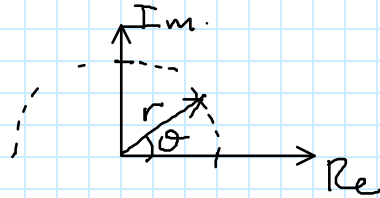

$$z = r e^{j\theta} = r \cos \theta + j r \sin \theta$$

Polar form
Rectangular

$$\Rightarrow r \cos \theta = \text{Re}[r e^{j\theta}] \quad , \quad r \sin \theta = \text{Im}[r e^{j\theta}]$$

Then, we can write the sinusoidal source

$$V = V_m \cos(\omega t + \phi) \text{ as } V = \text{Re}[V_m e^{j(\omega t + \phi)}]$$

or in the sine case:

$$V = \text{Im}[V_m e^{j(\omega t + \phi)}]$$

Considering the cosine notation

$$V = \text{Re}[V_m e^{j(\omega t + \phi)}] = \text{Re}[V_m e^{j\omega t} \cdot e^{j\phi}] \quad (\text{Inverse formula})$$

Phasor

Since the frequency ( $\omega$ ) does not change in the solution for voltages and/or currents, we don't need "wt" term in the computations, it can be neglected. Then, we will only use

$$V = \text{Re}[V_m e^{j\phi} e^{j\omega t}] \quad \text{where } z = V_m e^{j\phi} \text{ is called the "phasor" of } V. \quad \text{or } z = V_m \angle \phi$$

The phasor is a complex exponential having the amplitude and phase information of the source.

# P83


Monday, March 8, 2021 11:38 AM

Ex: For  $V = 10 \cos(2000\pi t + \frac{\pi}{4})$ , write its phasor?

Ans:

$$\bar{V} = 10 e^{j\frac{\pi}{4}}$$
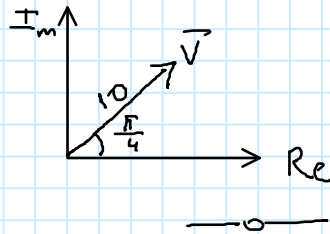
$$\text{or } \bar{V} = 10 \angle \frac{\pi}{4}$$




In calculations, using phasors instead of sinusoids makes the solution easier.

Ex.

If  $y_1 = 20 \cos(\omega t - 30^\circ)$  and  $y_2 = 40 \cos(\omega t + 60^\circ)$

a-)  $y_1 + y_2 = ?$  using sinusoids

b-) Find  $y_1 + y_2$  using phasors.

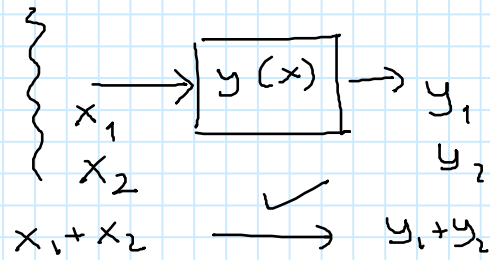

Ans:


a-)  $y_1 = 20 \cos(\omega t) \cos(30^\circ) + 20 \sin(\omega t) \sin(30^\circ)$  Linear.

$$y_2 = 40 \cos(\omega t) \cos(60^\circ) - 40 \sin(\omega t) \sin(60^\circ)$$

$$y_1 + y_2 = \cos(\omega t) (20 \cos 30^\circ + 40 \cos 60^\circ) + \sin(\omega t) (20 \sin 30^\circ - 40 \sin 60^\circ)$$

$$= 37.32 \cos(\omega t) - 24.64 \sin(\omega t)$$
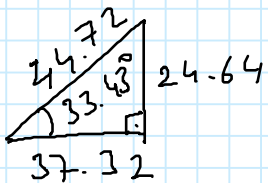
$$\Rightarrow y_1 + y_2 = 44.72 \left[ \underbrace{\frac{37.32}{44.72}}_{\cos(33.43^\circ)} \cos(\omega t) - \underbrace{\frac{24.64}{44.72}}_{\sin(33.43^\circ)} \sin(\omega t) \right]$$



From  $\cos A \cos B - \sin A \sin B = \cos(A+B)$

b-)  $\bar{y}_1 = 20 e^{j\frac{\pi}{6}}$ ,  $\bar{y}_2 = 40 e^{j\frac{\pi}{3}}$

$$\Rightarrow y_1 + y_2 = 44.72 \cos(\omega t + 33.43^\circ)$$

$$\bar{y}_1 + \bar{y}_2 = \left[ 20 \cos\left(-\frac{\pi}{6}\right) + j 20 \sin\left(-\frac{\pi}{6}\right) \right] + \left[ 40 \cos\left(\frac{\pi}{3}\right) + j 40 \sin\left(\frac{\pi}{3}\right) \right]$$

# P84

Monday, March 8, 2021 12:04 PM

$$= (17.32 - j10) + (20 + j34.64) = 37.32 + j24.64 = 44.72 e^{j0.5835}$$

$$\bar{y}_1 + \bar{y}_2 = 44.72 e^{j33.43^\circ} \text{ (Phasor)}$$

Time expression of  $\bar{y}_1 + \bar{y}_2$  is

$$y_1 + y_2 = \text{Re}[(\bar{y}_1 + \bar{y}_2) \cdot e^{j\omega t}] = \text{Re}[44.72 e^{j33.43^\circ} \cdot e^{j\omega t}]$$

$$= \text{Re}[44.72 e^{j(\omega t + 33.43^\circ)}]$$

$$y_1 + y_2 = 44.72 \cos(\omega t + 33.43^\circ) \checkmark$$

Passive Circuit Elements (R, L, C) in Frequency Domain -  
 1) V-I Relation for a Resistor: Phasor domain



$$V = R [I_m \cos(\omega t + \phi)]$$

$$= R I_m \cos(\omega t + \phi) \text{ (V)}$$

$$\Rightarrow \bar{V} = R I_m e^{j\phi} = R \underbrace{I_m \angle \phi}_{\bar{I}}$$

$$\text{or } \boxed{\bar{V} = R \bar{I}}$$

2) V-I Relation for an Inductor.

$$V = L \frac{di}{dt} \text{ assuming that } i = i(t) = I_m \cos(\omega t + \phi)$$


or

$$V = L (-\omega) I_m \sin(\omega t + \phi)$$

$$= -\omega L I_m \sin(\omega t + \phi)$$

or
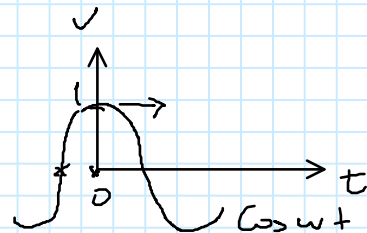
$$V = -\omega L I_m \cos(\omega t + \phi - \frac{\pi}{2})$$



Thus,

$$\bar{V} = -\omega L I_m e^{j(\phi - \frac{\pi}{2})}$$

$$\text{and } \bar{V} = -\omega L I_m e^{j\phi} \underbrace{e^{-j\frac{\pi}{2}}}_{-j} = j\omega L I_m e^{j\phi} = j\omega L \bar{I}$$





- Kirchoff's Laws in Frequency Domain -

1-) KVL in Phasor domain:


$$\bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n = 0$$

2-) KCL in Phasor domain:

$$\bar{I}_1 + \bar{I}_2 + \dots + \bar{I}_n = 0$$


3-) Series and Parallel Connections:

a-) Series Connection

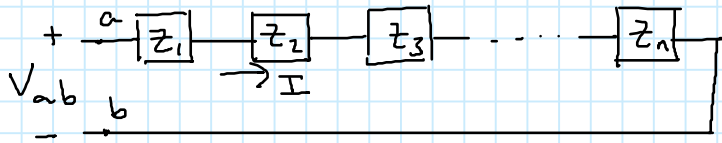

$$Z_{ab} = \frac{\bar{V}_{ab}}{\bar{I}} = z_1 + z_2 + \dots + z_n$$

b-) Parallel Connection:

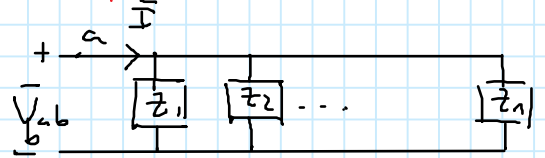

$$Z = \frac{\bar{V}_{ab}}{\bar{I}} \Rightarrow$$


$$\frac{1}{Z_{ab}} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_n}$$

However,


$$Y_{ab} = \text{Admittance} = G + jB$$

$$Y_{ab} = Y_1 + Y_2 + \dots + Y_n$$

Source Transformation in Freq. Domain:

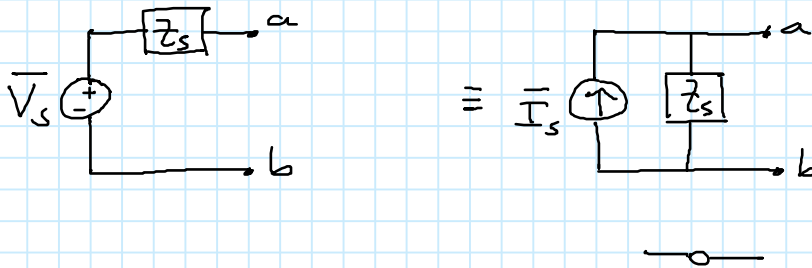

Ex:  $V_c$

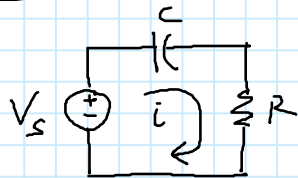

$$V_s = V_s(t) = V_m \cos(\omega t + \phi), \quad V_c(0) = 0$$

$V_R = ?$  (steady state)

Time domain solution.

$$\text{KVL equation: } -V_s + V_c + iR = 0$$



$$\text{or } V_c + iR = V_s \Rightarrow V_c + RC \frac{dV_c}{dt} = V_m \cos(\omega t + \phi)$$

$$\Rightarrow \text{Find } V_c \Rightarrow V_R = V_s - V_c$$

# P87

Monday, March 15, 2021 10:36 AM

## Phasor Analysis:

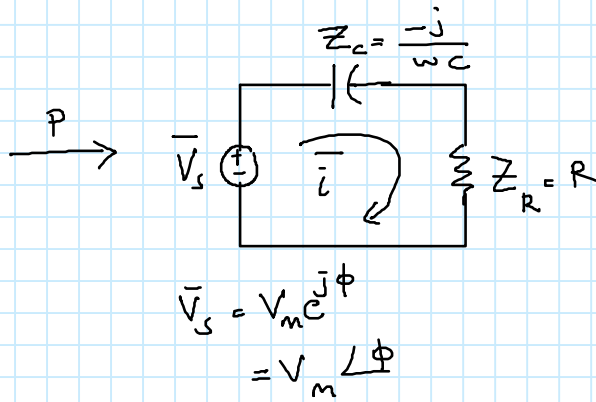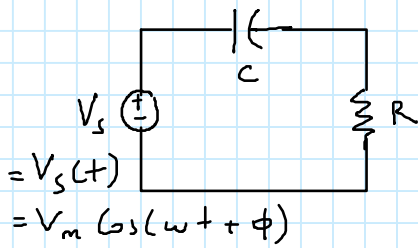

KVL:

$$-\bar{V}_s + Z_c \bar{i} + Z_R \bar{i} = 0$$

$$V_c + R C \frac{dV_c}{dt} = V_m \cos(\omega t + \phi) \xrightarrow{P} \frac{-j}{\omega C} \cdot \bar{i} + R \bar{i} = V_m e^{j\phi}$$

$$\Rightarrow \bar{i} = \frac{V_m e^{j\phi}}{R - j \frac{1}{\omega C}}$$



$$\text{or } \bar{i} = \frac{V_m e^{j\phi}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}} \cdot e^{j \tan^{-1}(-\frac{1}{\omega R C})}}$$

Find  $\bar{i}$ .

Then,  $\bar{V}_R = R \cdot \bar{i}$ .

Then,  $V_R(t) = \text{Re}[\bar{V}_R \cdot e^{j\omega t}]$ .

## Ex:

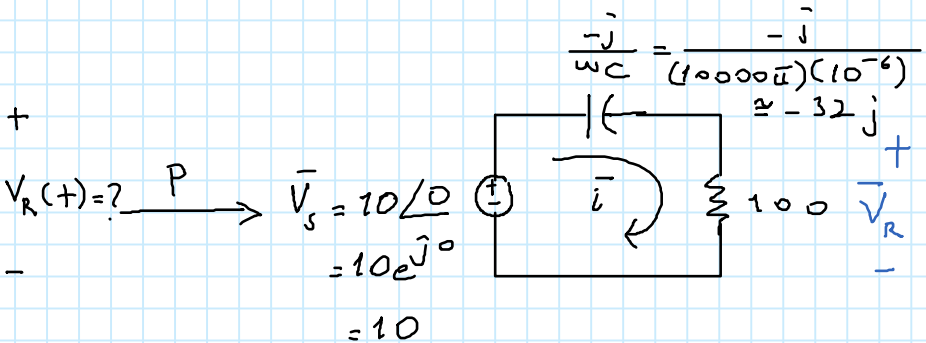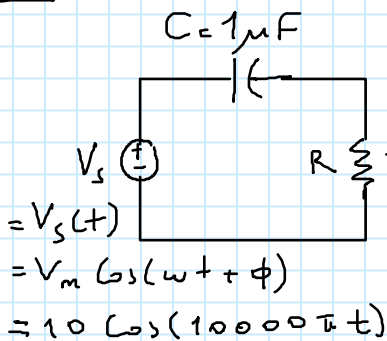

# P88

Monday, March 15, 2021 10:55 AM

$$\bar{i} = \frac{\bar{V}_s}{100 - 32j} \quad (\text{Ohm's law})$$

$$= \frac{10}{100 - 32j} \cong 0.1 + 0.03j$$


$$= 0.095 e^{j \tan^{-1}\left(\frac{0.03}{0.1}\right)}$$


$$= 0.095 e^{j 0.3}$$

$$\bar{i} = 0.095 e^{j 17.73^\circ} \quad (\text{A})$$

$$\Rightarrow \bar{V}_R = R \cdot \bar{i} = 9.5 e^{j 17.73^\circ} \quad (\text{V})$$

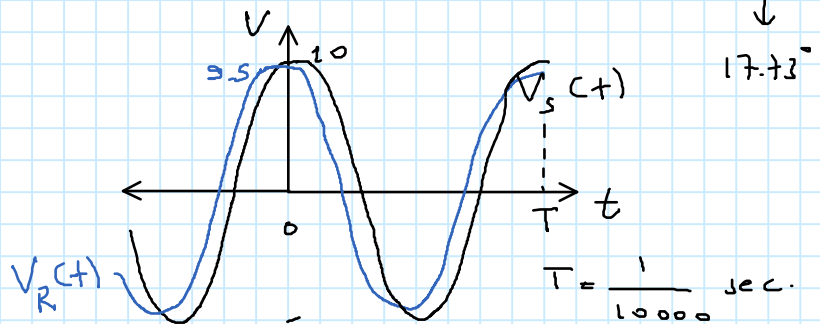Time expression:  $V_R(t) = \text{Re}[\bar{V}_R \cdot e^{j\omega t}] = 9.5 \cos(10000\pi t + 0.3)$



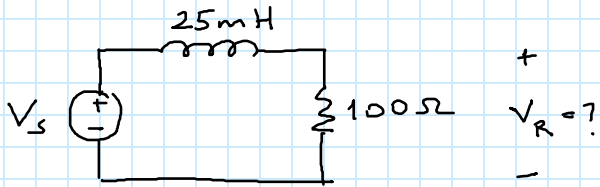
Ex:

where  $V_s = 10 \cos(6000t)$

Find the current and the voltage across the resistor.

Ans.

Phasor circuit is:

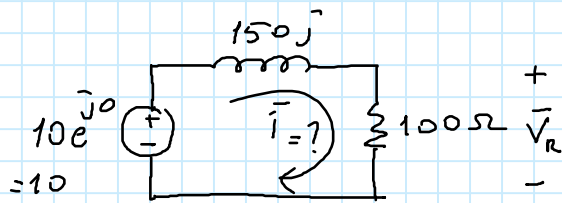

$$\bar{i} = \frac{10}{100 + 150j}$$

$$= \frac{10(100 - 150j)}{100^2 + 150^2} = 0.03 - 0.046j \text{ A.}$$

$$\text{or } \bar{i} = \sqrt{(0.03)^2 + (-0.046)^2} e^{j \tan^{-1}\left(\frac{-0.046}{0.03}\right)}$$

$$= 0.055 e^{j(-56.8^\circ)}$$

$$\Rightarrow i(t) = \text{Re}[\bar{i} \cdot e^{j\omega t}] = \text{Re}\left[0.055 e^{j(-56.8^\circ)} \cdot e^{j6000t}\right]$$

$$= \text{Re}\left[0.055 e^{j(6000t - 56.8^\circ)}\right]$$

$$= 0.055 \cos(6000t - 56.8^\circ)$$


$$\Rightarrow V_R(t) = \bar{i}(t) \cdot R = 5.5 \cos\left(6000t - 56.8^\circ \times \frac{\pi}{180}\right)$$

$$= 5.5 \cos(6000t - 1) \text{ V.}$$

# P90

Friday, December 17, 2021 12:07 PM


Ex:

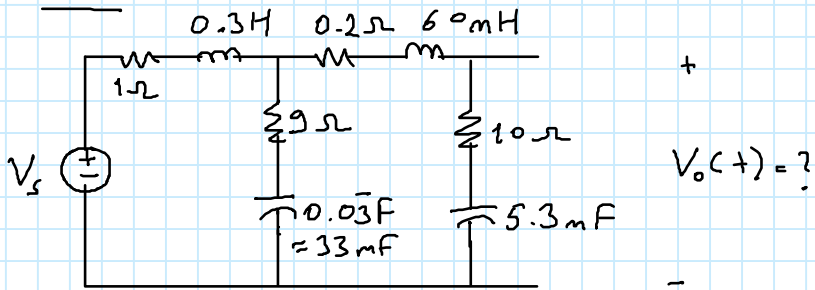

$$V_s = 40 \cos(10t) \text{ (V)}$$

Ans:

Phasor domain equivalent circuit is:

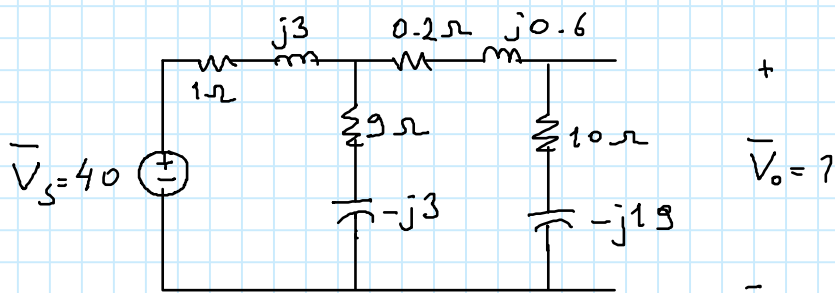

$$Z_{0.3H} = j\omega L = j(10)(0.3) = j3(\Omega)$$


$$Z_{33mF} = \frac{-j}{\omega C} = \frac{-j}{10(0.03)} = -j3(\Omega)$$

$$Z_{60mH} = j\omega L = j(10)(60 \times 10^{-3}) = j0.6(\Omega)$$

$$Z_{5.3mF} = \frac{-j}{\omega C} = \frac{-j}{(10)(5.3 \times 10^{-3})} = -j1.9(\Omega)$$


# P91

Monday, March 15, 2021 11:35 AM

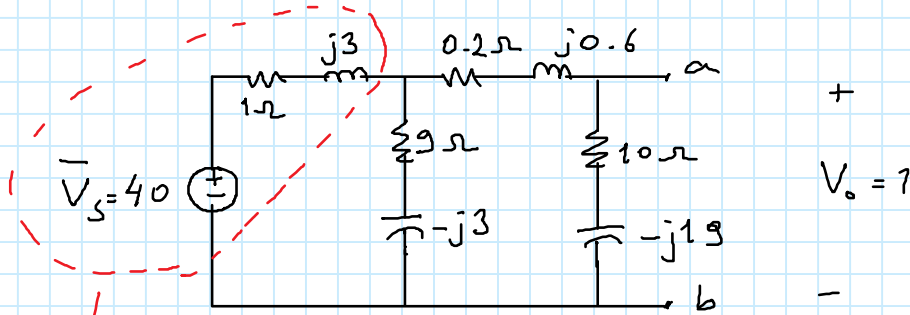

Replace by its Norton equivalent  $\Rightarrow \bar{I} = \frac{40}{1+j3} = \frac{40(1-j3)}{10}$   
 $\bar{I} = 4 - j12 \text{ (A)}$

Then, we have

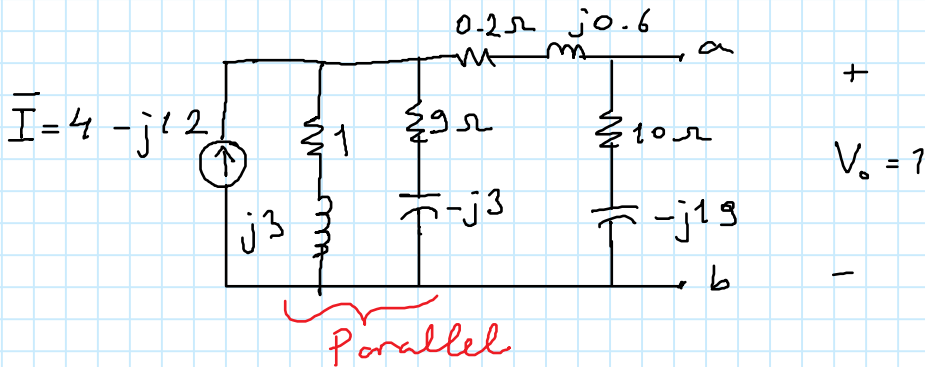


Parallel

$$\Rightarrow Z_1 || Z_2 = Z_t \Rightarrow \frac{1}{Z_t} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\Rightarrow Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(1+j3)(9-j3)}{10}$$

$$Z_T = 1.8 + j2.4 \Omega$$

Now, we have:

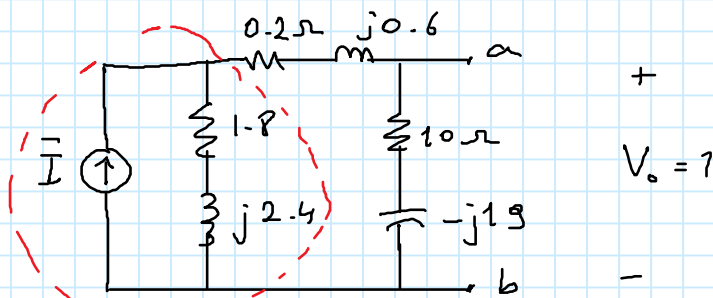


Transfer to Thevenin equivalent

$$\bar{V}_{Th} = (4 - j12)(1.8 + j2.4) = 36 - j12 \text{ (V)}$$

Then,

# P92

Monday, March 15, 2021 11:45 AM

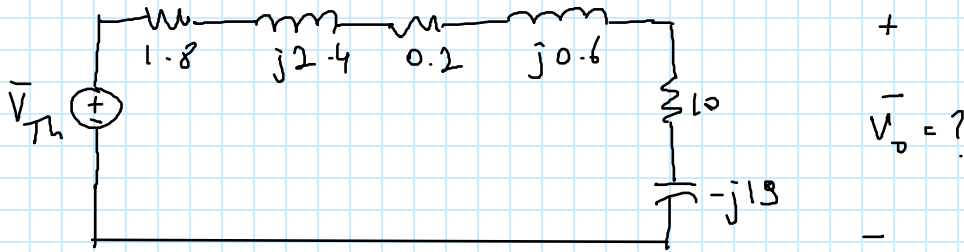

Using the voltage divider:

$$\begin{aligned} \bar{V}_o &= \bar{V}_{Th} \cdot \frac{(10 - j13)}{12 - j16} \\ &= (36 - j12) \cdot \frac{(10 - j13)}{12 - j16} = (36 - j12) \cdot \frac{(10 - j13)(12 + j16)}{12^2 + 16^2} = \\ &= \frac{1}{400} \cdot \underbrace{(36 - j12)}_{r e^{j\theta}} (10 - j13)(12 + j16) \\ &= \frac{1}{400} \cdot \underbrace{(37.95 e^{-j18.4^\circ})}_{r e^{j\theta}} (21.5 e^{-j62.2^\circ}) (20 e^{j53^\circ}) \\ &= \frac{(37.95)(21.5)(20)}{400} \cdot e^{j(53^\circ - 18.4^\circ - 62.2^\circ)} \\ &= 40.8 e^{-j27.6^\circ} = 40.8 e^{j \underbrace{(-27.6^\circ) \times \frac{\pi}{180}}_{-0.48 \text{ rad}}} \end{aligned}$$

Time expression of  $\bar{V}_o$  is

$$\begin{aligned} v_o(t) &= \text{Re} \left[ \bar{V}_o \cdot e^{j\omega t} \right] = \text{Re} \left[ 40.8 \underbrace{e^{-j0.48}}_{e^{j(10t - 0.48)}} \cdot e^{j10t} \right] \\ &= \text{Re} \left[ 40.8 \cos(10t - 0.48) + j40.8 \sin(10t - 0.48) \right] \\ &= 40.8 \cos(10t - 0.48) \text{ (V)} \end{aligned}$$



Examples -

1-)

For the circuit below,

- a) Draw the phasor domain circuit.
- b) Find the current in the circuit in phasor notation and in time notation.
- c) Find the voltage across the capacitor in phasor notation.


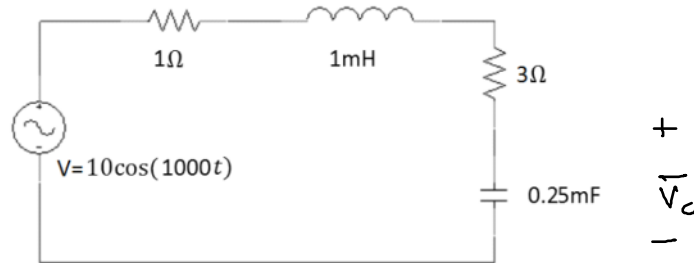


Figure 4: Circuit for question 4.

Ans:

a-)  $\omega = 1000 \text{ rad/s}$
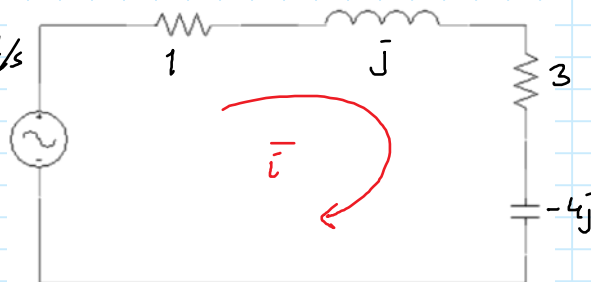
$$\bar{V} = 10 e^{j0} = 10 \angle 0^\circ$$



$$Z_{1mH} = j\omega L = j(1000)(10^{-3}) = j$$

$$Z_{0.25mF} = \frac{-j}{\omega C} = \frac{-j}{(1000)(\frac{1}{4} \times 10^{-6})} = -4j$$

$$b-) \bar{i} = \frac{\bar{V}}{Z_{total}} = \frac{10}{4 - 3j} = \frac{10(4 + 3j)}{16 + 9} = \frac{10}{25} (4 + 3j) = \frac{40}{25} + \frac{30}{25}j$$

$$= 1.6 + 1.2j \text{ (A)}$$

$$= \sqrt{1.6^2 + 1.2^2} e^{j \tan^{-1} \frac{1.2}{1.6}}$$

$$= 2 e^{j 36.87^\circ}$$


$$\Rightarrow i(t) = \text{Re}[\bar{i} \cdot e^{j\omega t}] = 2 \cos(1000t + 36.87^\circ \times \frac{\pi}{180}) = 2 \cos(1000t + 0.6435)$$

$$c-) \bar{V}_c = \bar{V} \times \frac{(-4j)}{4 - 3j} = 10 \cdot \frac{-4j}{4 - 3j} = \frac{10}{25} \frac{(-4j)(4 + 3j)}{(4 + 3j)(4 - 3j)}$$

$-12j^2 = 12$

$$= \frac{10}{25} (-16j + 12) = \frac{120}{25} - \frac{160}{25}j = 4.8 - 6.4j \text{ (V)}$$

2-7

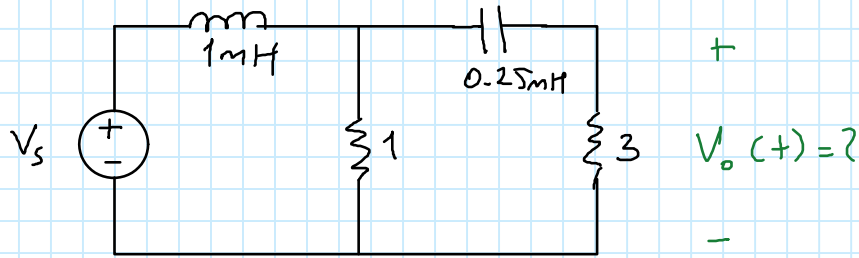


$V_s = 10 \cos(1000t) \text{ V.}$

Find  $V_o(t)$ .  $\omega = 2\pi f \Rightarrow f = \frac{1000}{2\pi} \approx 160 \text{ Hz}$

Ans:

Phasor domain circuit:

$\omega = 1000$

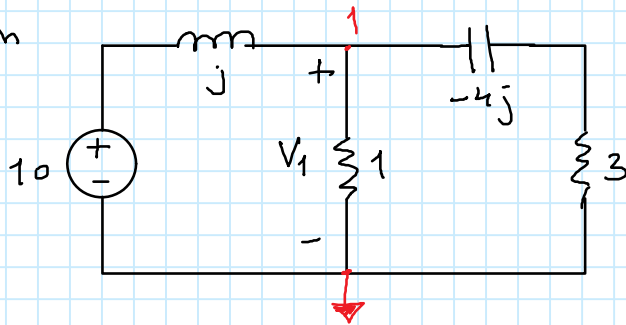

Using the Node-Voltage method.

$$\frac{\bar{V}_1 - 10}{j} + \frac{\bar{V}_1}{1} + \frac{\bar{V}_1}{3 - 4j} = 0$$

$$(3 - 4j)(\bar{V}_1 - 10) + \bar{V}_1 j(3 - 4j) + \bar{V}_1 j = 0$$

$$3\bar{V}_1 - 30 - 4j\bar{V}_1 + 40j + 3j\bar{V}_1 + 4\bar{V}_1 + \bar{V}_1 j = 0$$

$$7\bar{V}_1 - 30 + 40j = 0$$

$$\therefore \bar{V}_1 = \frac{1}{7} (30 - 40j) = 4.3 - 5.7j \text{ (V)}$$

From Voltage Division:

$$\bar{V}_o = \bar{V}_1 \cdot \frac{3}{3 - 4j} = (4.3 - 5.7j) \frac{3}{3 - 4j} = \frac{3(3 + 4j)(4.3 - 5.7j)}{25}$$

$$= \frac{3}{25} \cdot (12.9 - 17.1j + 17.2j + 22.8)$$


(approx.)

$$= \frac{3}{25} (35.7) = 4.28 \text{ V}$$

$$\Rightarrow V_o(t) = 4.28 \cos(1000t)$$

3-

For the circuit given below

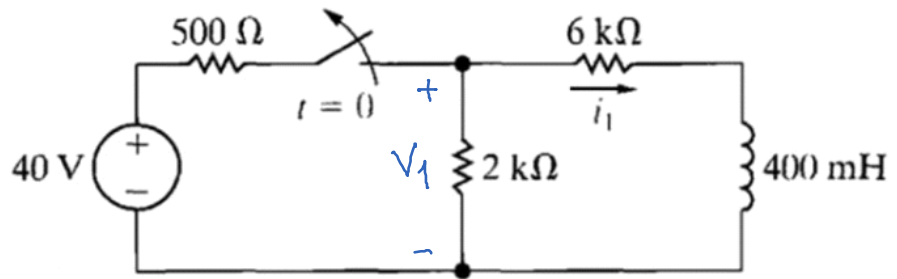Find  $i_1(t)$  for  $t \geq 0$ . (20 points)

Ans: Variable of interest = Inductor current.

Initial values:  $i_1(0^-) = ?$

For  $t < 0$ :

$$V_1 = (40V) \frac{(2k \parallel 6k)}{500 + (2k \parallel 6k)} = 40 \cdot \frac{3}{\frac{2000}{4}} = 30V.$$

$$\Rightarrow \bar{i}_1(0^-) = \frac{30}{6k} = 5mA = \bar{i}_1(0^+)$$

$\bar{i}_1(\infty) = 0$  final value.

$$\tau = \frac{L}{R} = \frac{400 \times 10^{-3}}{8000} = \frac{4 \times 10^{-3}}{2^8 \times 10^1} = 0.5 \times 10^{-4} = 50 \mu\text{sec}.$$

$$\bar{i}_1(t) = \bar{i}_{1f} + [\bar{i}_1(0) - \bar{i}_{1f}] e^{-(t-t_0)/\tau}$$

$$\text{or } \bar{i}_1(t) = 5 e^{-t/\tau} \text{ mA} = 5 e^{-\frac{t}{\frac{1}{2} \times 10^{-4}}} = 5 e^{-20000t} \text{ mA}.$$

4-)

For  $t < 0$ , the current is already settled. Initial charge of the capacitor is 0V. For the circuit below, find  
 a)  $i(t)$  for  $t \geq 0$ ,  
 b)  $v(t)$  for  $t \geq 0$ .


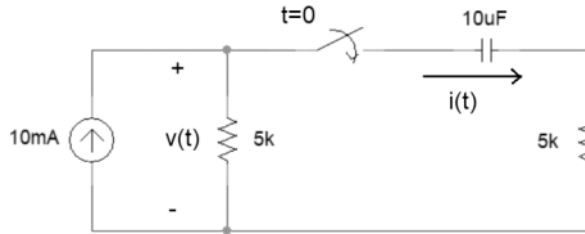


Figure 1: Circuit for question 1.

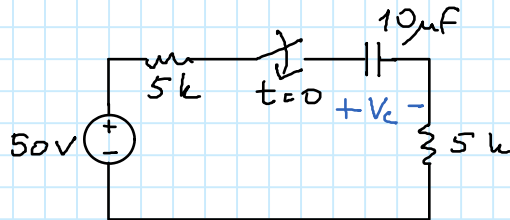Ans This is the step response of an RC-circuit.  
 The equivalent circuit is.





Variable of interest is the capacitor voltage (standard)

$$V_c(0^-) = 0 = V_c(0^+) = V_c(0)$$


$$V_c(\infty) = 50V.$$

$$\tau = RC$$

$R_{Th}$ :

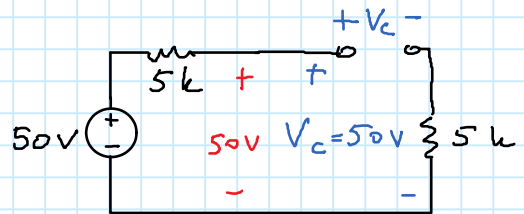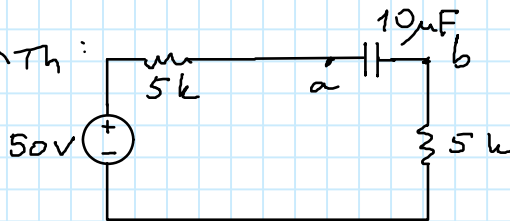

De-activate the indep sources

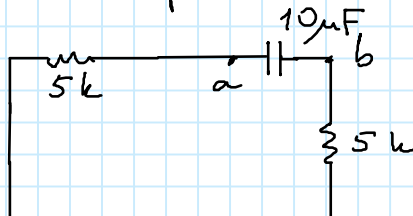

$$\Rightarrow R_{Th} = 10k.$$


$$\Rightarrow \tau = (10k)(10\mu F) = 10^5 \times 10^{-6} = 0.1 \text{ sec}$$

$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-(t-0)/0.1}$$


$$= 50 - 50 e^{-10t} \quad (V)$$

Thus,
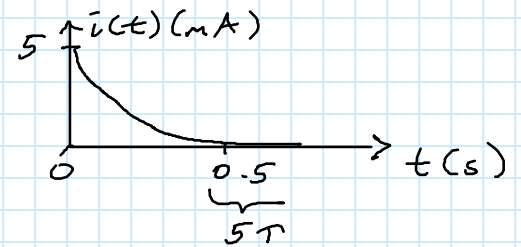
$$\begin{aligned}
 i(t) &= C \frac{dV_C(t)}{dt} = (10 \times 10^{-6}) \times \frac{d}{dt} (50 - 50e^{-10t}) \\
 &= (10^{-5}) \times 500 e^{-10t} \\
 &= 5 \times 10^{-3} e^{-10t} = 5e^{-10t} \text{ mA}
 \end{aligned}$$



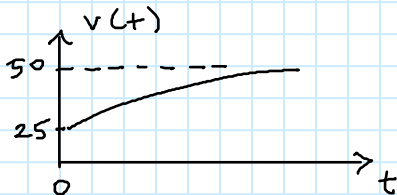
$$\begin{aligned}
 b-) \quad v(t) &= (5k) [10 \text{ mA} - i(t)] \\
 &= 5000 (10 - 5e^{-10t}) \text{ mA} \\
 &= 50 - 25e^{-10t} \text{ V.}
 \end{aligned}$$



5-)

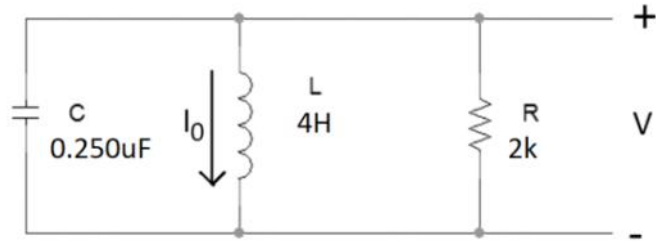For the circuit given below, it is given that  $V_0=0V$ ,  $I_0=-30mA$ .



a-) Determine the type of the response. Show your work.

b-) Find  $v(t)$ ,  $t \geq 0$ .

Ans: This is a parallel RLC circuit natural response.

$$\alpha = \frac{1}{2RC} = \frac{1}{2(2000)(\frac{1}{4} \times 10^{-6})} = 1000$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times \frac{1}{4} \times 10^{-6}}} = \frac{1}{10^{-3}} = 1000$$

$\alpha^2 = \omega_0^2 \Rightarrow$  critically damped!

b-)  $S_1 = S_2 = -\alpha = -1000$

The response is  $v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

I.C.'s:  $v(0^+) = D_2 = 0$ ,  $\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = D_1 - \alpha D_2$

$$\Rightarrow D_1 = \frac{1}{C} i_c(0^+) = \frac{1}{C} [-i_0(0^+)]$$


$$= \frac{1}{\frac{1}{4} \times 10^{-6}} \cdot (30mA)$$

$$= \frac{4 \times 30 \times 10^{-3}}{10^{-6}}$$

$$= 4 \times 30 \times 10^3$$

$$= 120000$$
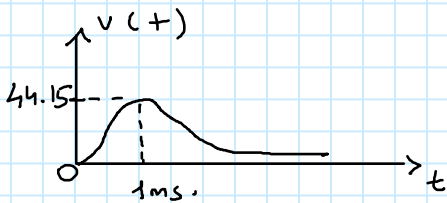
$$\Rightarrow v(t) = 120000 t e^{-1000 t} \text{ V.}$$




$$\frac{dv(t)}{dt} = 0 \text{ gives } 120000 e^{-1000t} - 120000 t (1000) e^{-1000t} = 0$$

$$t = 1 \text{ ms.}$$

$$v(1ms) = 120000 (10^{-3}) e^{-1} = 120 \times \frac{1}{e} = \frac{120}{2.718...} = 44.15$$

6-

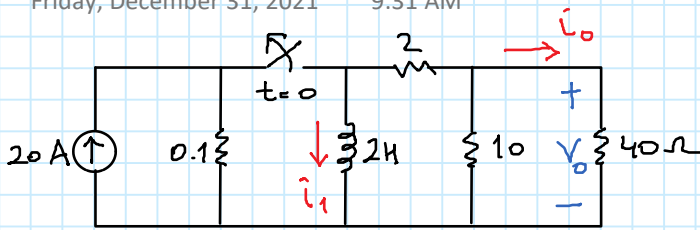


Find


- a-)  $i_1(t)$  for  $t \geq 0$
- b-)  $i_0(t)$  for  $t \geq 0$
- c-)  $V_0(t)$  for  $t \geq 0$

Ans.

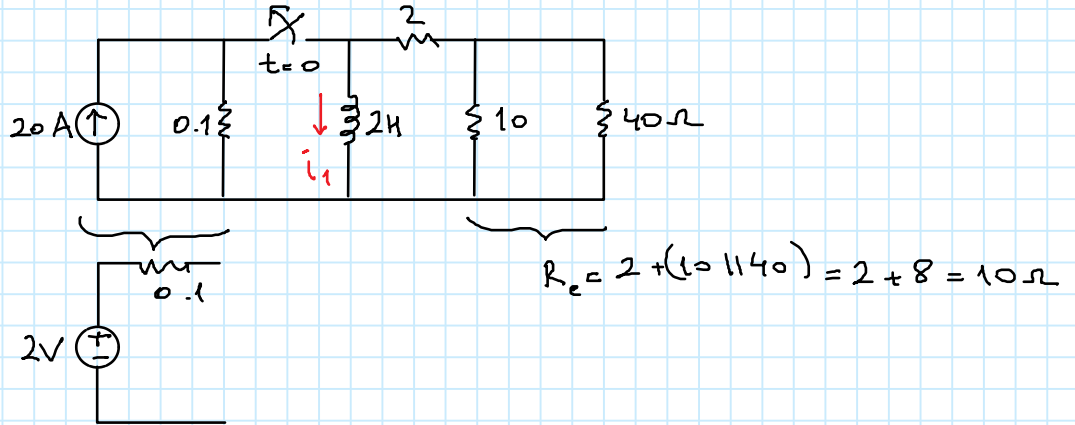a-) The variable of interest is the inductor current



Then, we have

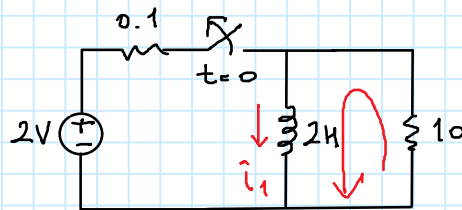

This is the natural response of an RL-circuit.

The general solution is

$$i_1(t) = i_{1f} + [i_1(0) - i_{1f}] e^{-t/\tau}$$


$$i_1(0^-) = i_1(0^+) = i_1(0) = \frac{2}{0.1} = 20 \text{ A}$$

$$i_{1f} = i_1(\infty) = 0$$

$$\tau = \frac{L}{R} = \frac{2}{10} = 0.2$$

Substitute the values into the formula

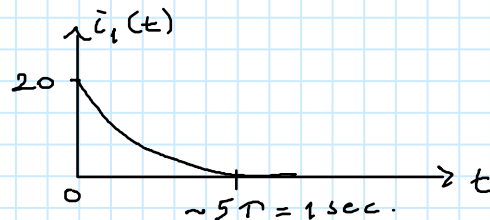
$$\Rightarrow i_1(t) = 20 e^{-\frac{t}{0.2}} = 20 e^{-5t} \text{ (A)}$$



# P100

Friday, December 31, 2021 10:00 AM

b-)

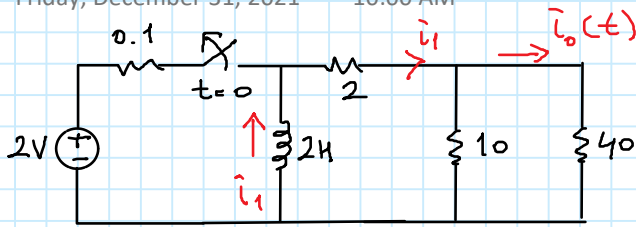


$$\bar{i}_0(t) = ? , t \geq 0$$

Using the current division

$$\bar{i}_0(t) = \bar{i}_1(t) \cdot \frac{10}{50} = \frac{1}{5} \bar{i}_1(t) = -4e^{-5t} , t \geq 0$$

c-)  $V_o(t) = 40 \bar{i}_0(t) = -160e^{-5t} , t \geq 0$

7-)

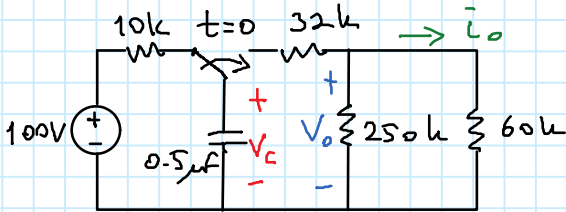

Find

- a-)  $V_c(t) , t \geq 0$  , d-)  $E_{60k} = ?$
- b-)  $V_o(t) , t \geq 0$
- c-)  $\bar{i}_o(t) , t \geq 0$

Ans:

a-) The variable of interest is the capacitor voltage  $V_c(t)$

$$V_c(t) = V_{cf} + [V_c(0) - V_{cf}] e^{-t/\tau}$$

where

$$V_c(0) = V_c(0^-) = 100V$$

$$V_{cf} = 0V$$

$$\tau = RC \Rightarrow R_{Th} = 32k + (250k \parallel 60k) = 80k$$

$$\text{Then, } \tau = (80k) \left(\frac{1}{2}\right) (10^{-6}) = (8)(10^4) \left(\frac{1}{2}\right) (10^{-6}) = 4 \times 10^{-2} = 0.04$$

Thus,

$$V_c(t) = 100 e^{-t \left(\frac{1}{4 \times 10^{-2}}\right)} = 100 e^{-t(0.25 \times 100)} = 100 e^{-25t} V$$

b-)  $V_o(t) = V_c(t) \frac{(250k \parallel 60k)}{(250k \parallel 60k) + 32k} = V_c(t) \cdot \frac{48k}{80k} = \frac{3}{5} V_c(t) = 60 e^{-25t} V$

c-)  $\bar{i}_o(t) = \frac{V_o(t)}{60k} = e^{-25t} mA$

d-)  $P_{60k} = \bar{i}_o^2(t) R = (e^{-50t} \times 10^{-6}) (60k) = 6 \times 10^{-2} e^{-50t} = 0.06 e^{-50t} W = 60 e^{-50t} mW$

$$E_{60k} = \int_0^{\infty} P_{60k} \cdot dt = \int_0^{\infty} 60 e^{-50t} dt = 60 \int_0^{\infty} e^{-50t} dt = 60 \left( \frac{-1}{50} e^{-50t} \Big|_0^{\infty} \right) = \frac{6}{5} (e^0 - e^{\infty}) = \frac{6}{5} J = 1.2 J$$




# P101

Friday, December 31, 2021 11:21 AM

8-)

In the circuit in Fig. P7.10, the switch has been closed for a long time before opening at  $t = 0$ .

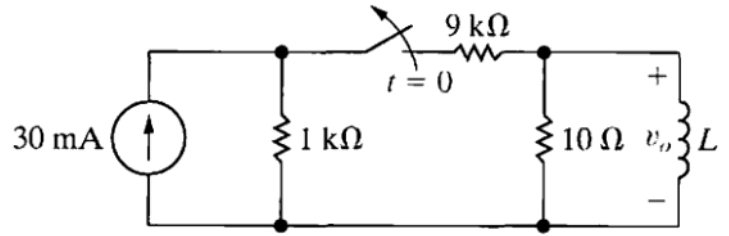a) Find the value of  $L$  so that  $v_o(t)$  equals  $0.5 v_o(0^+)$  when  $t = 1 \text{ ms}$ .




Ans:

This is the natural response of an RL-circuit

The variable of interest is the inductor voltage

$$i_o(t) = i_{of} + [i_o(0) - i_{of}] e^{-t/\tau} \quad , \quad i_o(t) = \text{Inductor current}$$
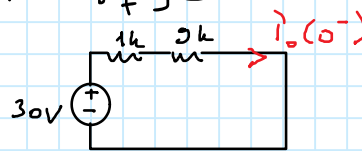
$$\begin{aligned} i_o(0) &= i_o(0^+) = i_o(0^-) = ? \\ &= \frac{30}{10k} = 3 \text{ mA} \end{aligned}$$



$$i_o(\infty) = 0$$

$$\tau = \frac{L}{R} = \frac{L}{10}$$

Thus,

$$i_o(t) = 3 e^{-\frac{10t}{L}} \text{ mA}$$

$$\text{Then, } v_o(t) = L \frac{di_o(t)}{dt} = L \cdot \frac{d}{dt} (3 e^{-\frac{10t}{L}} \times 10^{-3}) = L (3 \times 10^{-3}) \cdot \left( -\frac{10}{L} e^{-\frac{10}{L} t} \right)$$

$$\text{Given that } v_o(1 \text{ ms}) = 0.5 v_o(0^+)$$

$\Rightarrow$

$$\cancel{L} (3 \times 10^{-3}) \left[ \frac{-10}{\cancel{L}} e^{-\frac{10}{L} (10^{-3})} \right] = \frac{1}{2} \cancel{L} (3 \times 10^{-3}) \left( \frac{-10}{\cancel{L}} \right)$$

$$e^{-\frac{10^{-2}}{L}} = \frac{1}{2} \Rightarrow e^{\frac{10^{-2}}{L}} = 2$$

$$\frac{10^{-2}}{L} = \ln 2$$

$$\frac{-10^{-2}}{L} = \ln \frac{1}{2}$$

$$L = \frac{10^{-2}}{\ln 2} = \frac{0.01}{\ln 2}$$


$$L = \frac{10^{-2}}{0.69} = \frac{0.01}{0.7}$$

$$= 14.28 \text{ mH}$$

# P102

Monday, January 3, 2022 1:40 PM

9-)

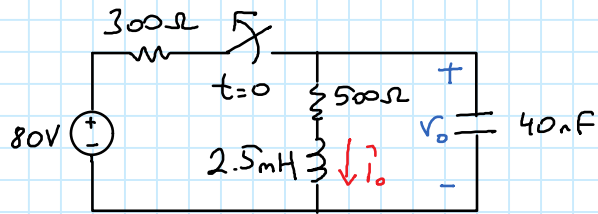

The switch in the circuit has been closed for a long time.

The switch opens at  $t=0$

Find a-)  $i_o(t)$ ,  $t \geq 0$

b-)  $v_o(t)$ ,  $t \geq 0$ .

Ans.

a-) For  $t \geq 0$ , this is a series RLC circuit natural response

Thus, for  $t < 0$

$$\hat{i}_o(0) = \hat{i}_o(0^+) = \hat{i}_o(0^-) = \frac{80}{500+300} = \frac{80}{800} = 0.1 \text{ A} = 100 \text{ mA}$$

Also,

$$v_o(0) = v_o(0^+) = v_o(0^-) = 80 \cdot \frac{500}{500+300} = 80 \cdot \frac{5}{8} = 50 \text{ V}$$

Now that we have the initial conditions, we need to find the type of the response: (Look at pg-63)

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

or

$$\alpha = \frac{500}{2(2.5 \times 10^{-3})} = 10^5 \text{ rad/s}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(2.5 \times 10^{-3})(40 \times 10^{-5})} = 100 \times 10^8 = 10^{10}$$

$$\Rightarrow \omega_0 = 10^5$$

Then,  $\alpha = \omega \Rightarrow$  Critically damped!

$$\begin{aligned} \hat{i}(t) &= D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \\ &= D_1 t e^{-10^5 t} + D_2 e^{-10^5 t} \end{aligned}$$

$$\Rightarrow \hat{i}_o(0) = D_2 = 100 \text{ mA}$$

$$\frac{d\hat{i}_o(0)}{dt} = \frac{v_L(0^+)}{L} = -\alpha D_2 + D_1 = 0 \Rightarrow D_1 = 10^5 (100 \times 10^{-3}) = 10000$$

Thus,

$$\hat{i}_o(t) = 10000 t e^{-10^5 t} + 0.1 e^{-10^5 t} \text{ A}$$

$$b-) v_o(t) = D_3 t e^{-10^5 t} + D_4 e^{-10^5 t} \text{ V.}$$

$$v_o(0) = D_4 = 50, \quad c \frac{dv_o(0)}{dt} = -0.1$$

# P103

Monday, January 3, 2022 2:06 PM

$$\frac{dV_o(t)}{dt} = \frac{-0.1}{40 \times 10^{-9}} = -25 \times 10^5 \frac{V}{s} = -(D_4 + D_3)$$

$$\Rightarrow D_3 = 10^5 (50) - 25 \times 10^5 = 25 \times 10^5$$

$$\Rightarrow V_o(t) = 25 \times 10^5 t e^{-10^5 t} + 50 e^{-10^5 t} \quad V., t \geq 0.$$